 


Q1 Draw the logic circuit using the input (A, B, C, D) & out put (X) waveforms in figure 01.

Ans Solution

The output expression for the circuit is develop in SOP form. The SOP form indicates that the output is HIGH when A is low & C is HIGH or when B is low & C is HIGH or when C is low & D is HIGH.



$$X = \overline{(A+B)}C + \overline{C}D = \overline{A+B}C + \overline{C}D = \overline{A}C + \overline{B}C + \overline{C}D$$

Q₂ For the 4-input multiplexer, data inputs are given as.

Ans

In multiplexer, the output Y takes the value of the input corresponding to the select bits. Select bits are S_1S_0 .

Using this we can find the value of Y given the select inputs.

a) - $S_0 = 1, S_1 = 0$
 $S_1S_0 = 01$ (1 in decimal).
Thus, $Y = D_1 = 1$.

b) - $S_0 = 0, S_1 = 1$
 $S_1S_0 = 10$ (2 in decimal).
Thus, $Y = D_2 = 0$.

c) - $S_0 = 1, S_1 = 1$
 $S_1S_0 = 11$ (3 in decimal).
Thus, $Y = D_3 = 1$.

d) - $S_0 = 0, S_1 = 0$
 $S_1S_0 = 00$ (0 in decimal).
Thus, $Y = D_0 = 0$.

Q₃ For the circuit in figure 02, assume the inputs are $\overline{\text{Add/subt.}} = 1$, $A = 1010$, $C_0 = 1$, $B = 1101$.
What is the output?

Answer.

Let us say ADD/SUB as K .

If $K = 1$ it work as 4 bit subtractor.

If $K = 0$ it works as 4 bit adder.

We know $A - B = A + B'$ so first find B' and then add.

Given

$$\overline{\text{Add/subt.}} = 1$$

$$A = 1010 \text{ } C_0$$

$$B = 1101$$

as adder & subtractor

If $\overline{\text{Add/subt.}} = 0 \Rightarrow$ it work as adder

say $K \Rightarrow \overline{\text{Add/subt.}} = 1 \Rightarrow$ it work as subtractor

for $\overline{\text{Add/subt.}} = 1 \Rightarrow K$

⊕ for first full adder

$$A_3 \ A_2 \ A_1 \ A_0$$

$$1 \ 0 \ 1 \ 0$$

$$B_3 \ B_2 \ B_1 \ B_0$$

$$1 \ 1 \ 0 \ 1$$

$$B \oplus K = B_0$$

$$\Rightarrow B_0 = 1 \oplus 1$$

$$= 0$$

$$A_0 + B_0 + C_0 = 0 + 0 + 1$$

$$S_0 = 1$$

$$C_1 = 0$$

P.T.O

② for second full adder.

$$B_1 \oplus K = B_1 \quad \& \quad C_1 = 0$$

$$B_1 = 0 \oplus 1 \\ = 1$$

$$\Sigma_1 = A_1 + B_1 + C_1 = 1 + 1 + 0.$$

$$C_2 = 1 \quad = 0.$$

Simplify other two adders.

$$A + \bar{B} = A - B \quad (\text{when } K=1)$$

$$A = 1010.$$

$$B = 1101 \Rightarrow \bar{B} = 0010.$$

$$A + \bar{B} = 1010$$

$$\underline{0010}$$

$$1100$$

$$\Sigma_0 = 0$$

$$\Sigma_1 = 0$$

$$\Sigma_2 = 1$$

$$\Sigma_3 = 1$$

$$C_{out} = 0.$$

Q4 Determine the $A=B$, $A>B$ & $A<B$ outputs for the inputs numbers show on the Comparator in figure 3.

Answer

A comparator first compares the MSB (Most Significant Bit) to the two numbers A & B .
If the bit of $A=1$ & bit of $B=0$, then $A>B$.
Similarly if the bit of $A=0$ & Bit of $B=1$, the ~~$A>B$~~
 $A<B$.

If both have their MSBs as 0 or 1, then the comparator compares the next significant bit & so on till all the pairs of bits are compared.

Here $A=0110$ & $B=0011$.

First we compare the MSB (bit 3) of A & B .

Bit 3 of $A=0$ & Bit 3 of $B=0$.

As we both bits are 0, so we move to the next significant bits.

Now we compare the Bit 2 of A & B .

Bit 2 of $A=1$ & Bit 2 of $B=0$.

So $A>B$, output is HIGH & other outputs are Low.

Q5 show the logic required to convert 4-bit Gray code to binary & use the logic to convert the following Gray code words to binary: 1011.

Solution

Gray Code to Binary.

$$b_3 = g_3 = 1$$

$$b_2 = b_3 \oplus g_2 = 1 \oplus 0 = 1$$

$$b_1 = b_2 \oplus g_1 = 1 \oplus 1 = 0$$

$$b_0 = b_1 \oplus g_0 = 0 \oplus 1 = 1$$



\therefore Binary: 1101.

Q6 Draw & explain the logic diagram for 4-bit active low decoder.

Ans The simple example below of a 2-to-4 line binary decoder consists of an array of four AND gates. The 2 binary inputs labelled A & B are decoded into one of 4 outputs, hence the description of 2-to-4 binary decoder. Each output represents one of the minterms of the 2 input variables. (each output = a minterm).


The binary inputs A & B determine which output line from Q₀ to Q₃ is "HIGH" at logic level "1" while the remaining outputs are held 'low' at logic "0" so only one output can be active (HIGH) at any one time. Therefore, whichever output line is "HIGH" identifies the binary code present at the input, in other words it "de-codes" the binary input.

P.T.O.

  

Q7 Draw & explain the logic diagram for frequency divider (use 3 J-k flip-flops and assume 16 kHz frequency of the initial wave-form).

Ans

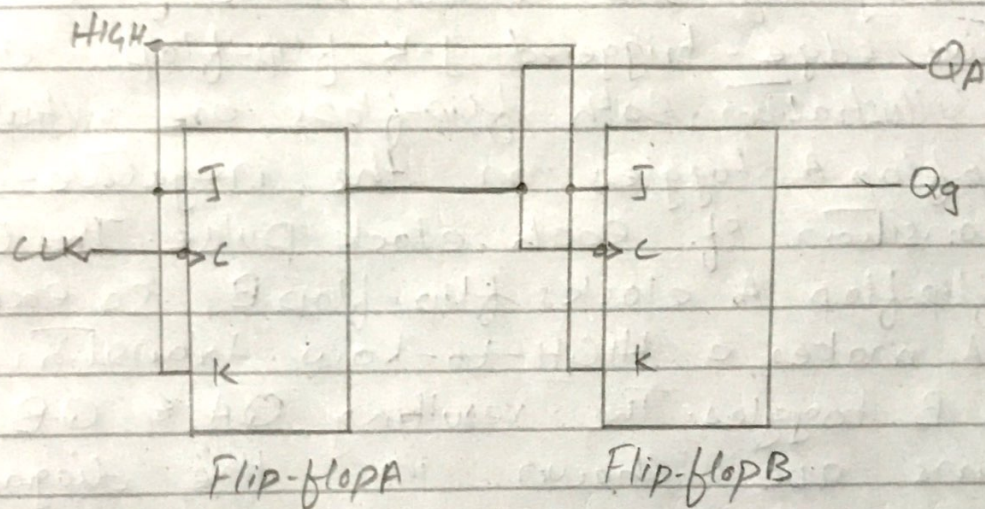

	1	2	3	4	5	6	7	8
CLK	[Pulse sequence]							
QA	0	1	0	1	0	1	0	1
QB	0	0	1	1	0	0	1	1
	0	1	2	3	0	1	2	3
	Binary Sequence.				Binary Sequence.			


P.T.O

Explanation:

In logic diagram for frequency divider using 3 J-K flip-flops & assume 16 kHz frequency of the initial wave-form. The negative edge-triggered J-K flip-flops are used for illustration. Both flip-flops are initially Reset. Flip-flop A toggles on the negative-going transition of each clock pulse. The Q output flip-flop A clocks flip-flop B, so each time Q_A makes a HIGH-to-LOW transition, flip-flop B toggles. The resulting Q_A & Q_B wave forms are shown in the diagrams.

Q8 Determine the Q wave form relative to the clock if the signals shown in figure 4 are applied to the inputs of the J-K flip-flop. Assume that Q is initially Low.

Ans.

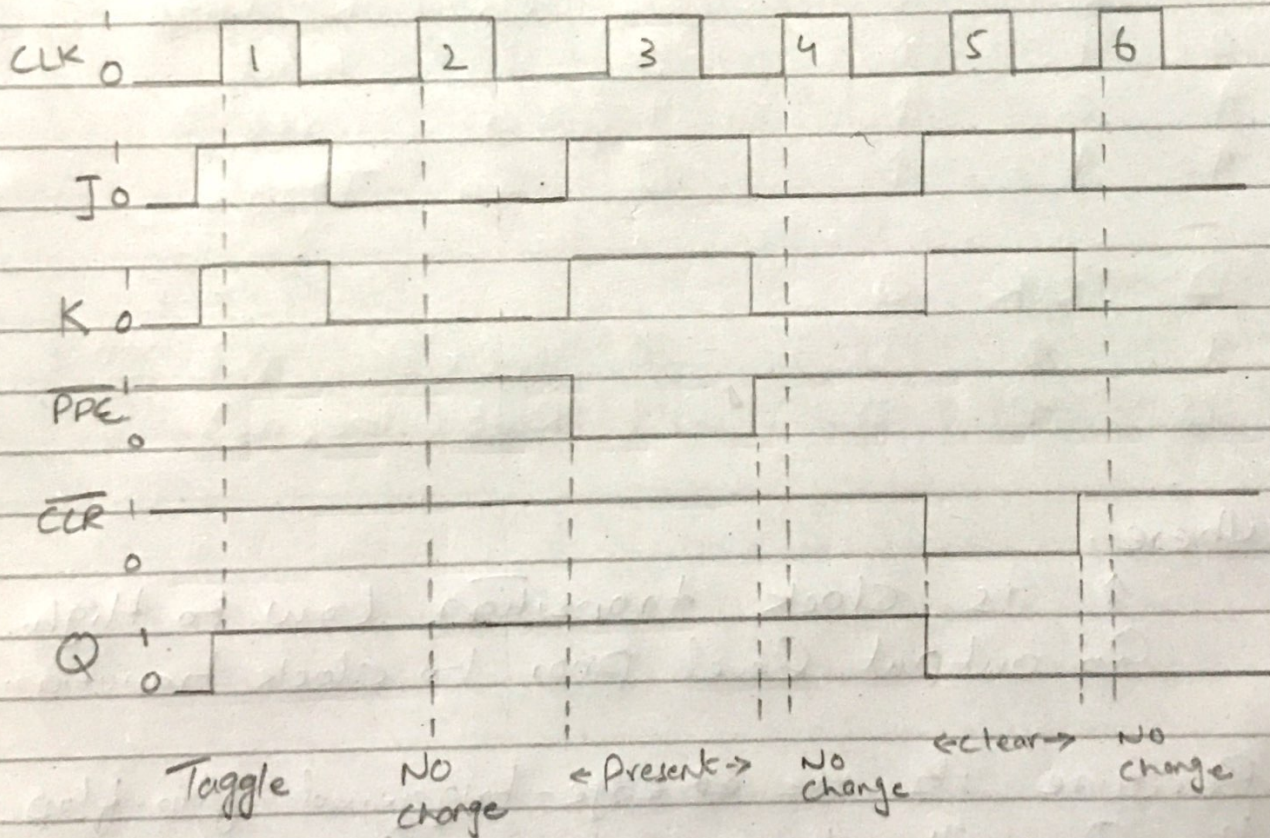

P.T.O.

Solution.

Truth table for +ve edge-triggered J-K flip flop.

Inputs			Outputs		Comments.
J	K	CLK	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change.
0	1	↑	0	1	Reset
1	0	↑	1	0	Set
1	1	↑	\bar{Q}_0	Q_0	Toggle
D	CLK	Q			
1	↑	1	0		Set (stores 1)
0	↑	0	1		Reset (stores 0)

Where,


↑ is clock transition Low to High.
 Q_0 output level prior to clock transition.

Because its +ve edge-triggered flip-flop, the Q will change only on the +ve-going edge of clock pulse.

Q9 Draw the logic diagram & timing diagram for the 4-stage synchronous binary counter. verify that the waveforms of the Q outputs represent the proper binary number after each clock pulse.

Ans

Binary 4-bit Synchronous Up counter.

 

clock Pulse.

Second counting cycle.

clock	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
A																		
B																		
C																		
D																		

In the above image, clock input cross flip-flops & the output timing diagram is shown. on each clock pulse, synchronous counter counts sequentially. The counting output across four output pin is P.T.O.

Muhammad Hamza.

Page 14.

13136.

incremental from 0 to 15, in binary 0000 to 1111 for 4-bit synchronous up counter. After 15 or 1111, the counter reset to 0 or 0000 & count once again with a new counting cycle.