

Department of Electrical Engineering

Assignment

Date: 24/06/2020

Course Details

Course Title: Electronic Circuit Design

Module: 04

Instructor: Eng Mujtaba Ihsan

Total Marks: 50

Student Details


Name: M.Salman shahid

Student ID: 15006


Q1.	(a)	Discuss the darlington connection for multistage amplifiers.	Marks 05+10
	(b)	The input of a certain regulator increases by 4.5 V. As a result, the output voltage increases by 0.062 V. The nominal output is 40 V. Evaluate the line regulation in both % and in %/V	CLO 2
Q2.		Explain Colpitts and Hartley oscillators.	Marks 10
			CLO 2
Q3.	(a)	Describe the idea behind class B amplifiers.	Marks 06+06
	(b)	Explain the types of voltage regulators and their purposes.	CLO 2
Q4.		Explain the working of Flash ADC.	Marks 05
			CLO 2
Q5.	(a)	Differentiate between the following: Low pass & high pass filters	Marks 04+04
	(b)	Active and passive filters	CLO 2

Darlington Pair

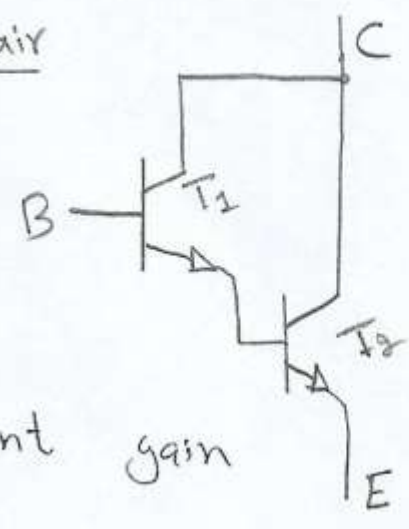- Darlington Pair is a cascading of two Biopolar Transistor.
- Used for High current gain & low resistance.



Multi stage Darlington Pair Amplifier

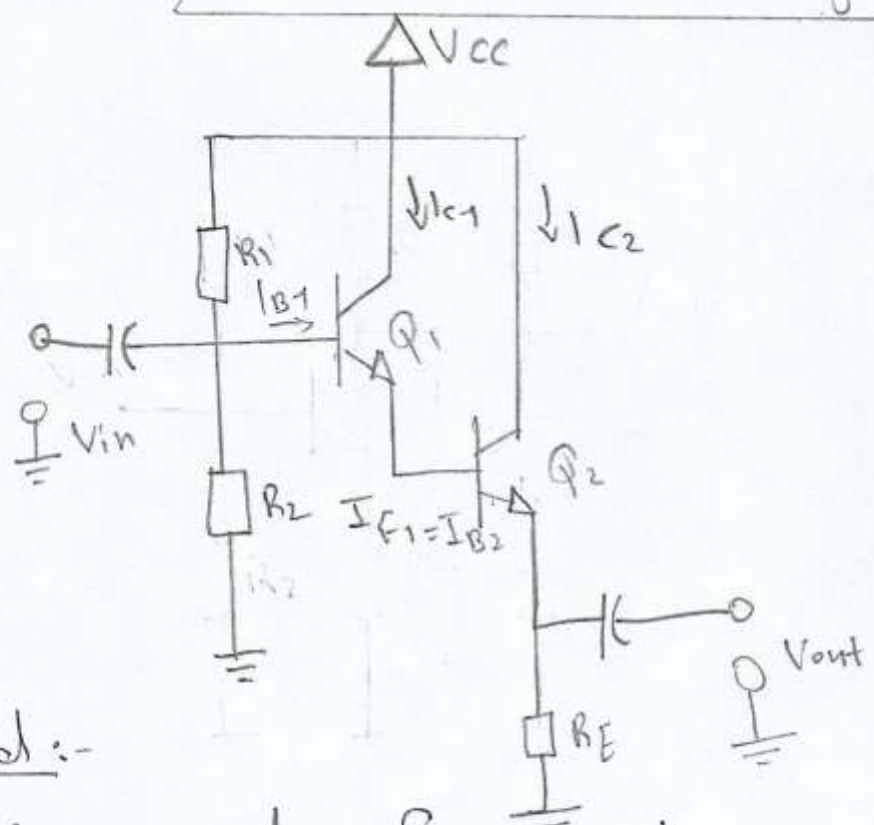

Explained :-

It is used for interconnecting common-emitter stages with other emitter follower stages.

The above circuit shows the darlington pair multistage amplifier which was just discussed to meet the requirement of

of current gain (A_i) & input impedance

- It have high input impedance (MΩ)
- High current gain
- low output impedance.

(b) The input of a certain regulator increases by 4.5 V. As a result, the output voltage increases by 0.062 V. The nominal output is 40 V. **Evaluate** the line regulation in both % and in %/V

CLO 2

b)

Given data:-

$$\text{Input Voltage} = V_{IN} = 4.5$$

$$\text{Output voltage} = \Delta V_{out} = 0.062 \text{ V}$$

$$\text{Nominal output} = 40 \text{ V}$$

By using Line Regulation equation

$$\text{Line regulation} = \left(\frac{\Delta V_{out}}{\Delta V_{IN}} \right) \times 100\%$$

$$= \frac{0.062}{4.5} \times 100\%$$

$$= 1.3777\%$$

$$\text{Line regulation} = \frac{(\Delta V_{out} / V_{out}) \times 100\%}{\Delta V_{IN}}$$



$$= \frac{0.062 / 40}{4.5} \times 100\%$$

$$= 0.0344\% / \text{V}$$

Q2 :-
Intro to Colpitts Oscillator:-

The Colpitts Oscillator uses two Centre-tapped Capacitor in series with a Parallel inductor to form its resonance tank circuit Producing sinusoidal oscillation

Basic Colpitts Circuit:-

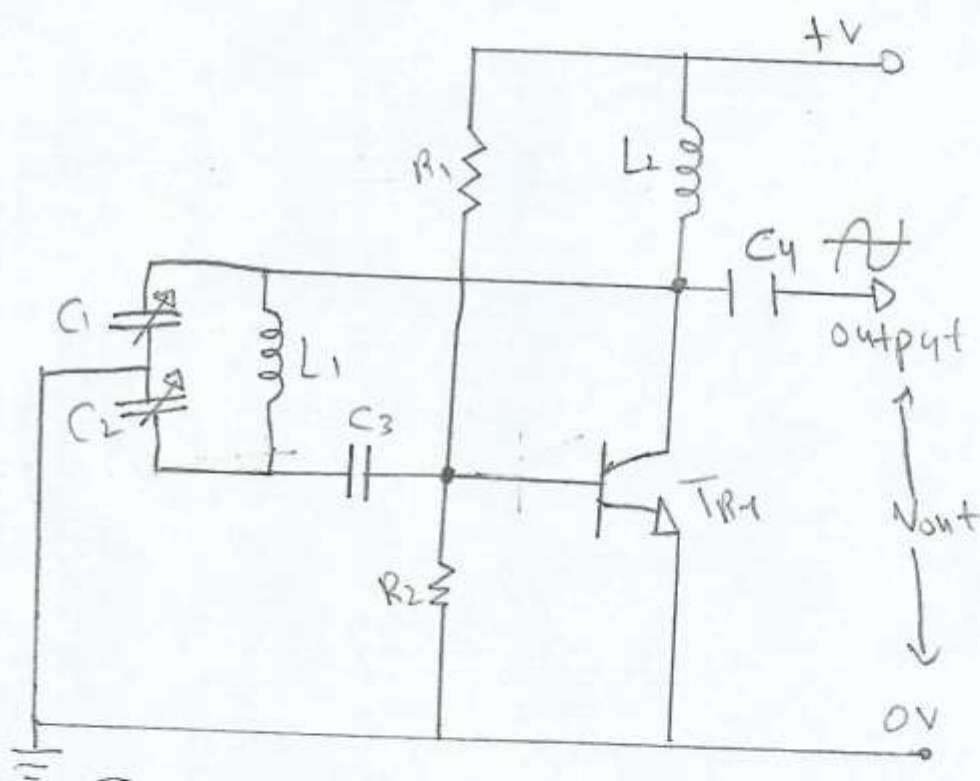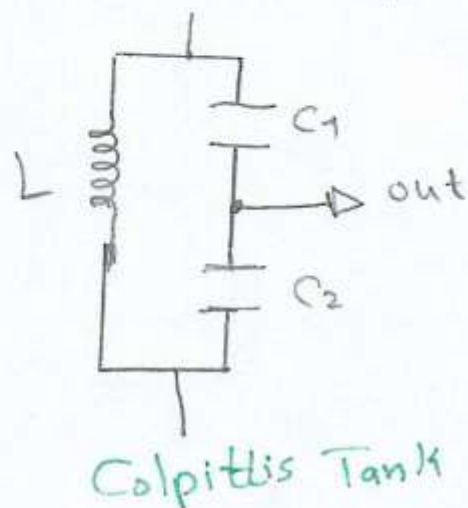

Circuit Explanation:-

The emitter terminal is connected to the junction of the two Capacitor C_1 & C_2 which are connected in series and act as a voltage divider

When power supply (V_s) applied C_1 & C_2 charges up & discharge through the coil L .



The oscillation across the capacitor are applied to the base-emitter junction and appear in the amplified at collector output

- R_1 & R_2 provide DC stabilizing DC bias for transistor in the normal manner while blocking additional capacitor act as a DC
- RFC is used in the collector circuit to provide high reactance at the frequency oscillation.
- The required +ive feedback obtained for sustained undamped oscillation.

The Hartley Oscillator:-

Oscillator uses two inductive coils in series with parallel capacitor to form tank circuit producing sinusoidal oscillation

Basic Circuit:-

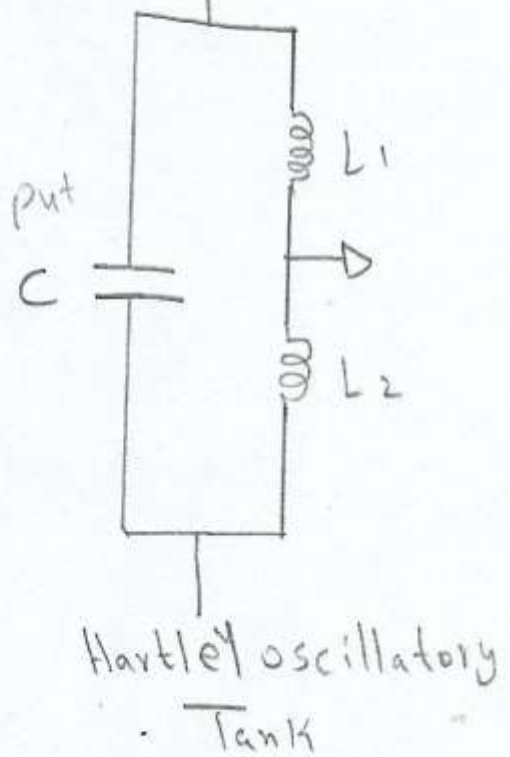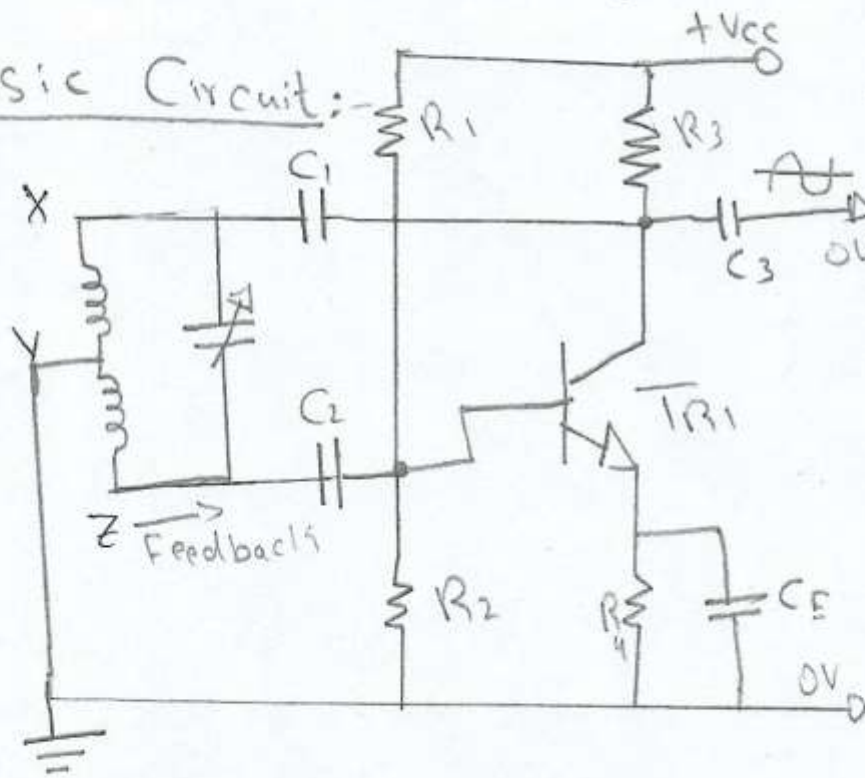

Explanation:-

Hartley's Oscillator circuit can be made from any configuration that uses either a single tapped coil or a pair of series connected coils in parallel

When the circuit is oscillating the voltage at point X (collector) relative to point Y (emitter) is 180° out of phase with the voltage at point Z (base) relative to point Y

Thus there is 180° phase change in the voltage b/w base & collector and this shift along with the original 180° phase correct in the feedback loop provide the phase relation.

The amount of feedback depend upon the position of the tapping point of the inductor. If this is moved nearer to the collector the amount of feedback increased.


The frequency of oscillation increased or decreased by tuning capacitor.

Q3:-

Idea behind class B amplifier:-

Class B amplifier is a type of power amplifier where the active device (transistor) conducts only for one half cycle of the input signal.

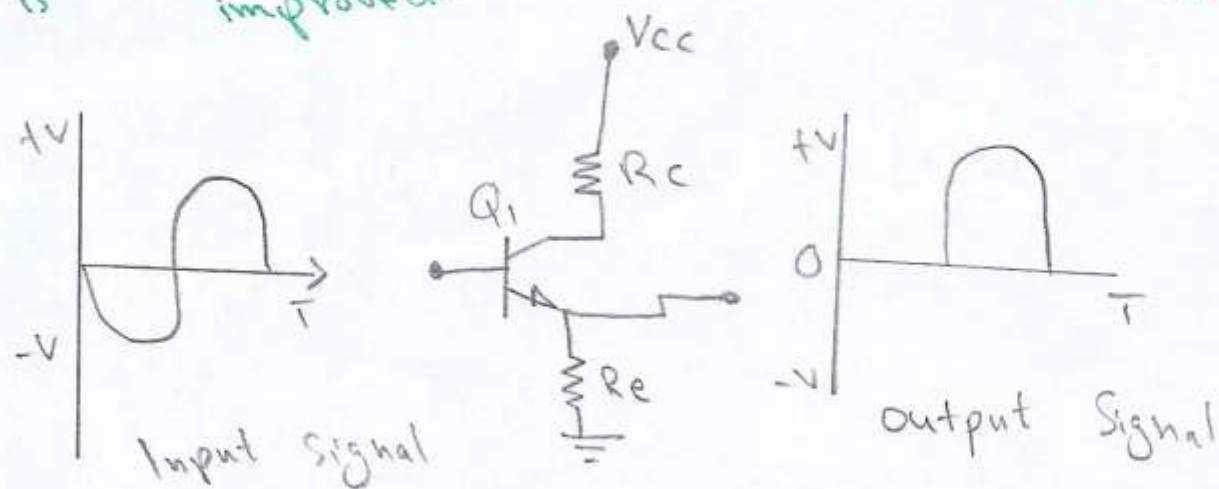Since the transistor is switched off for half the input cycle, the active device dissipates less power & hence the efficiency is improved.



It is clear from the circuit that the base of the transistor Q1 is not biased and the -ive half cycle of waveform is missing in output. It improves power efficiency but it creates a lot of distortion.

input will be available in the output and that is bad thing.

(b) Explain the types of voltage regulators and their purposes.

CLO 2

b) Types of Voltage Regulators:-

- Linear Voltage Regulator
- Switching Voltage Regulator

Linear Voltage Regulator:- If the transistor stays in active region or ohmic region or linear region during voltage regulation then the regulator is called Linear voltage regulator.

When a load is connected, the changes in either input or load will result in a variation in current through the transistor so that the output is maintained constant for the transistor to be able to vary its current (collector-emitter current) in case of BJT. it must be operated in ohmic region.

During this process the regulator wastes a lot of power as the net voltage


Classified into five categories

Positive Adjustable Regulator
Negative Adjustable Regulator
fixed output Regulator
Tracking Regulator
floating Regulator

Switching Voltage regulator:- When the transistor operates in cut off state & saturation state i.e it switches b/w off state & saturation state, then the regulator is called switching voltage regulator.

Switching regulator operates different than the Linear Regulator in the sense that the Pass transistor acts as a switch it stays in on state & off state.

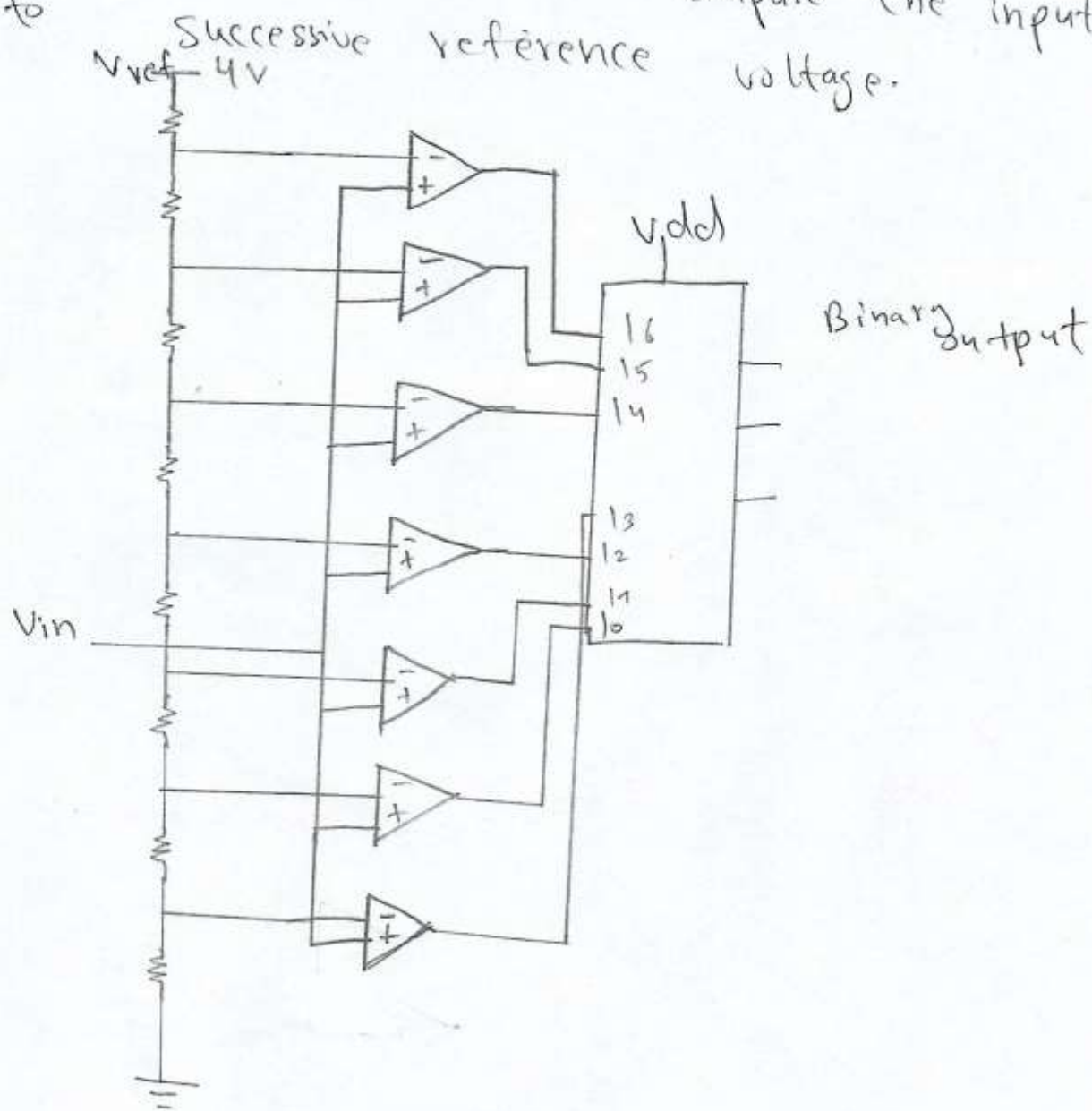Flash ADC :- A flash ADC is a type of linear Analog-to-digital converter that uses a voltage ladder with a comparator at each "rung" of the ladder to compare the input voltage to successive reference voltage.



Flash ADC (Analog to Digital converter)

The comparator output connected to the input of a priority encoder which then produce a binary output


V_{ref} is a steady reference voltage provided by a precision voltage regulator

As the analog input voltage exceeds the reference voltage at each comparator the comparator state sequentially saturate to a high

Analog input



Digital output

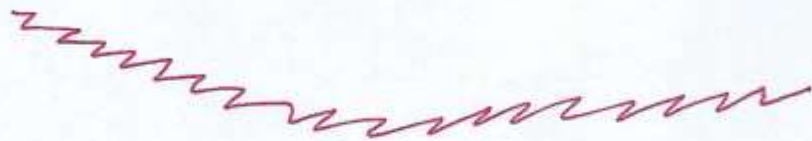

Q5. Differentiate between the following:

(a) Low pass & high pass filters

(b) Active and passive filters


Marks

04+04

CLO 2


Difference b/w Low Pass & High Pass filters

High Pass filter:-

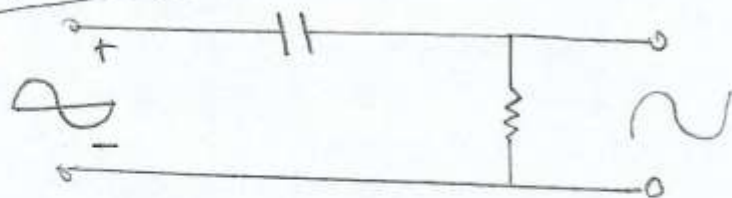

It allows only high frequencies to pass through it while blocking low frequencies.

Low Pass Filter:-

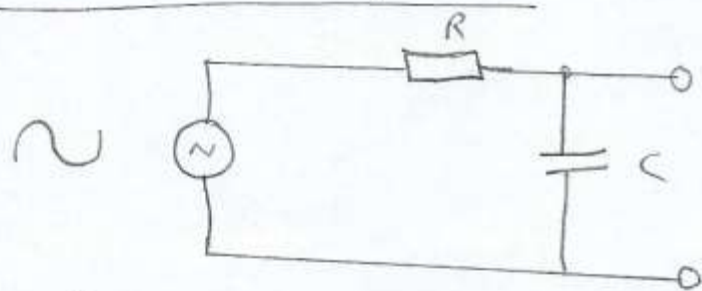

It allows only low frequencies to pass through it and blocks high frequencies.

Passive & active filters:-

Passive filter :- It include only passive components such as resistors, capacitors, inductors

Passive filters are most responsive to a frequency range from roughly 100Hz to 300MHz

The limitation on the lower end is a result of the fact that at low frequencies the inductance or capacitance would have to be quite large.

Active filter :- Active filter's deals with very low frequencies (0 Hz) and they can provide voltage gain (Passive filter cannot)

Active filters are used to design high order filters with out the use of inductors
Active filters are less suitable for high frequencies.