

**Department of Electrical Engineering**

**Assignment**

**Date: 14/04/2020**



---

**Course detail**

**Instructor:** Dr .sohail imran

**Course title** Leaner circuit analysis

**Module** 02





**Total marks** 30

**Student Details**

**Name:** amjad ali

**Student ID :** 16012

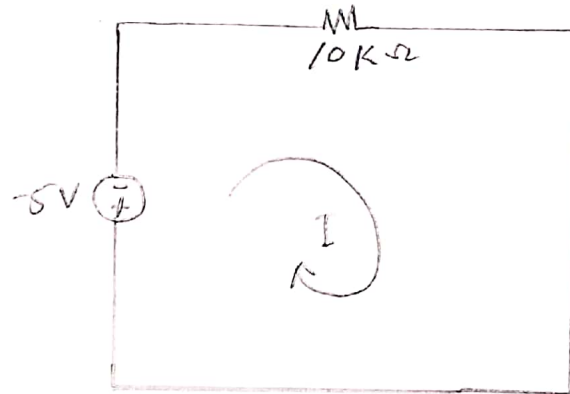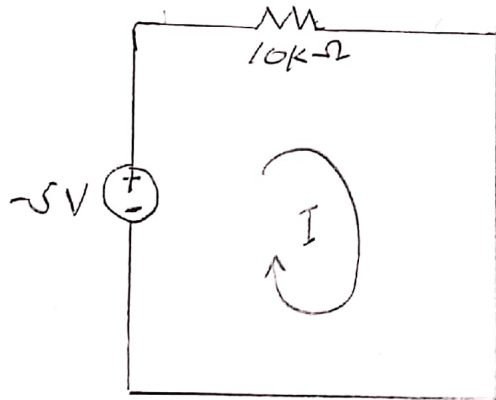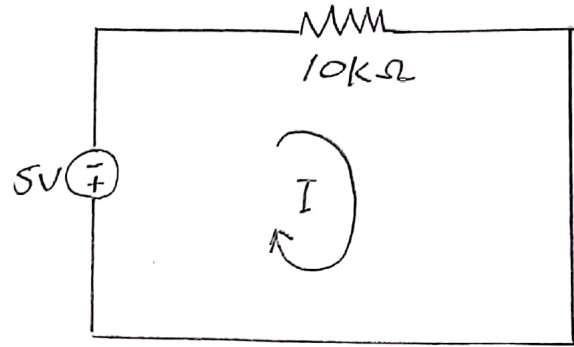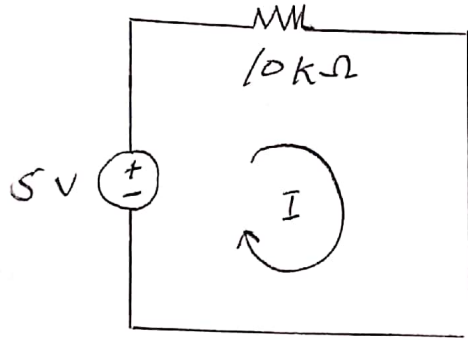Q1(a): For each of the following circuits in figure, Find the current  $I$  and compute the power absorbed by the resistor.



Ans 1(a):

We use ohm's Law  
Find circuit

$$V = IR$$

$$I = V/R$$

For power is:

$$P = VI$$

To obtain result so we need to substitute a given values for each circuit. so if current is succeeding from negative side to positive of voltage generator. so we practice current voltage with negative sign.

For first circuit:

$$V = IR$$

$$I = V/R$$

$$I = 5V/10000\Omega$$

$$I = 0.0005A$$

$$I = 0.5mA$$

$$P = VI$$

$$P = 5 \times 0.5 \times 10^{-3}$$

$$P = 2.5 \times 10^{-3}$$

$$P = 0.25mW$$

For 2nd circuit:

$$V = IR$$

$$I = V/R$$

$$I = -5V/10000\Omega$$

$$I = -0.0005A$$

$$I = -0.5mA$$

2nd Circuit:

power = ?

$$P = VI$$

$$P = 5 \times (-0.5) \cdot 10^{-3}$$

$$P = -2.5 \times 10^{-3}$$

$$P = -0.0025 \text{ W}$$

$$P = -0.25 \text{ mW}$$

For circuit 3rd :

$$V = IR$$

$$I = V/R$$

$$I = -5V / 10000 \Omega$$

$$I = -0.0005 \text{ A}$$

$$I = -0.5 \text{ mA}$$

power = ?

$$P = VI$$

$$P = 5 \times (-0.5) \times 10^{-3}$$

$$P = -2.5 \times 10^{-3}$$

$$P = -0.25 \text{ mW}$$

Circuit 4th :

$$V = IR$$

$$I = V/R$$

$$I = 5V / 10000 \Omega$$

$$I = 0.0005 A$$

$$\boxed{I = 0.5 mA}$$

Power = ?

$$P = VI$$

$$P = 5V \times 0.5 \times 10^{-3}$$


$$P = 2.5 \times 10^{-3}$$

$$\boxed{P = 0.25 mW}$$

Name A-mjad Ali  
ID 16012  
paper LCA

5

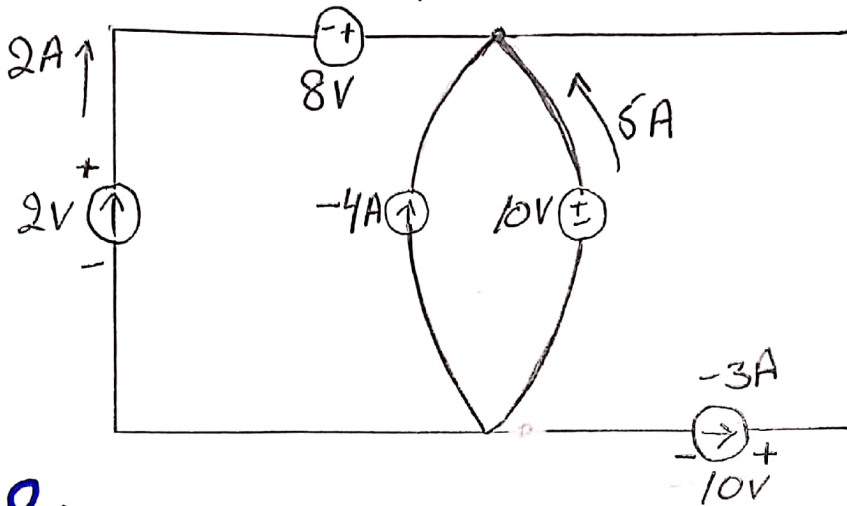Q1(b): Determine the power supplied by the leftmost element in the circuit of following figure:



Ans

$$P = VI$$

$$P = 2V \times 2A$$


$$P = 4W$$

Now we could simplify this circuit but as the voltage and current are given we can find the power by multiplying in this two vectors.


$$(2V)(2A) = 4W \text{ supplied}$$

Remember that this 4W is supplied power as the current direction conflicts with passive sign convention.

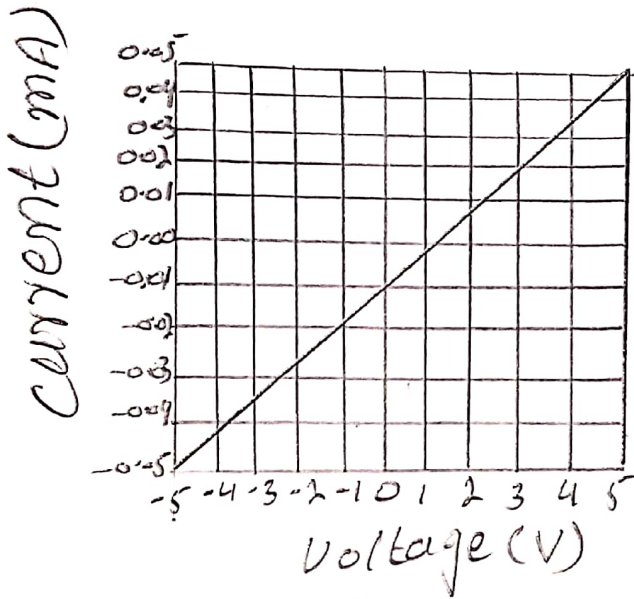
Q1(c) :: Following figure depicts the current-voltage characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in according with the passive sign convention.



(a)

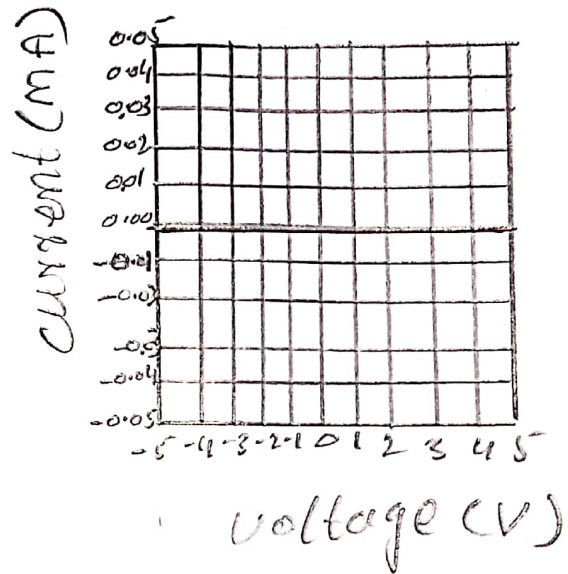

(b)

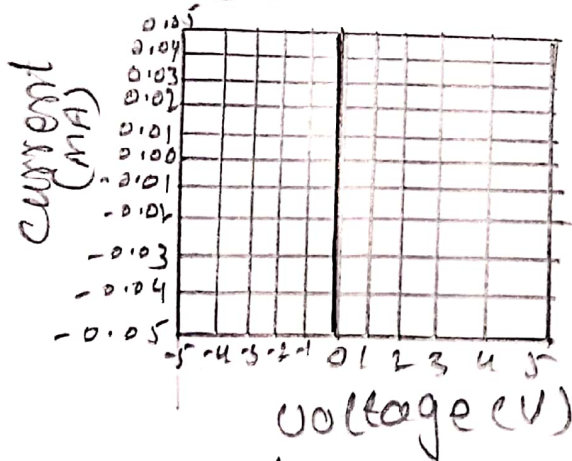

(c)

ANS ::

Use ohm's Law :

$$V = IR$$

(OR)

$$R = V/I$$

So we can calculate  $R$  from the slope on the graph.

We can take any point on the line to get the values of "I" and "V".

Calculate (a):

$$I = 0.01 \text{ mA}$$

$$V = 1 \text{ V}$$

$$R = ?$$

use ohm's Law

$$V = IR$$

$$R = V/I \Rightarrow \frac{0.5 \text{ A}}{5 \text{ V}} \Rightarrow 10 \mu\text{S}$$

$$R = 1 \text{ V} / 0.01 \times 10^{-3}$$

$$\boxed{R = 100 \text{ k}\Omega}$$

Calculate (b): Through difficult to see, the current is zero as slope is zero (S)

$$V = IR \Rightarrow R = V/I$$

$$R = \frac{1 \text{ V}}{0} \Rightarrow \boxed{R = \infty}$$



Calculate (C) ∞

Through difficult to see  
the current is infinite.

as slope is ∞ (S)

$$R = \frac{1}{\infty}$$

OR

$$R = 0$$



Thus we have zero resistance

$$\boxed{R = 0}$$

Q2a): Refer to the circuit of following figures and answer the following:

- (1) How many distinct nodes are contained in the circuit?
- (2) How many elements are contained in the circuit?
- (3) How many branch does the circuit have?
- (4) Determine if each of the following represents a path, a loop, both, or neither:

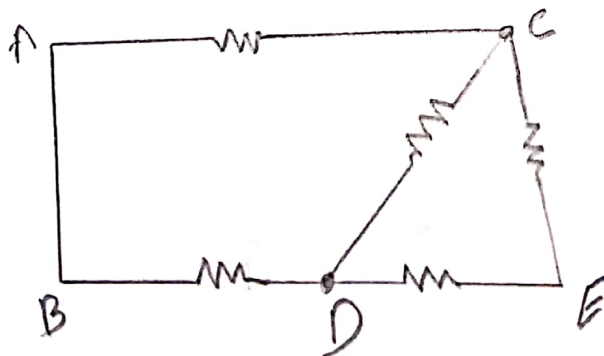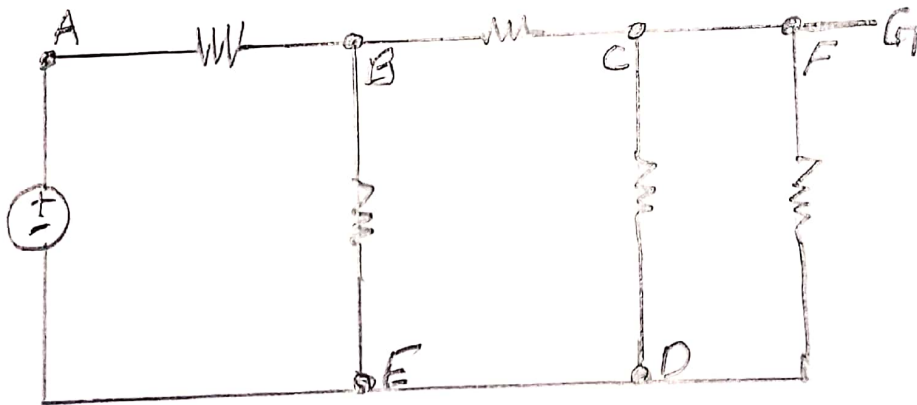- (i) A to B, (ii) B to D to C to E
- (iii) C to E to D to B to A to C
- (iv) C to D to B to A to C to E




Ans: Next page

Ans 2(a):

- (1) We get that the number of nodes in the circuit is (4)
- (2) Number of element (5)  
(The 5 resistor)
- (3) A branch is a section between two nodes. So the number of branch in the circuit is (5).  
(The same as the number of active elements).
- (4)
- (i) Neither, we're still in the same nodes.
  - (ii) only path, where moved by 3 node and visited each only once.
  - (iii) path and loop, where moved by 4 nodes and closed the loop in node c.
  - (iv) Neither, where visited node c twice, but didn't finish in it.

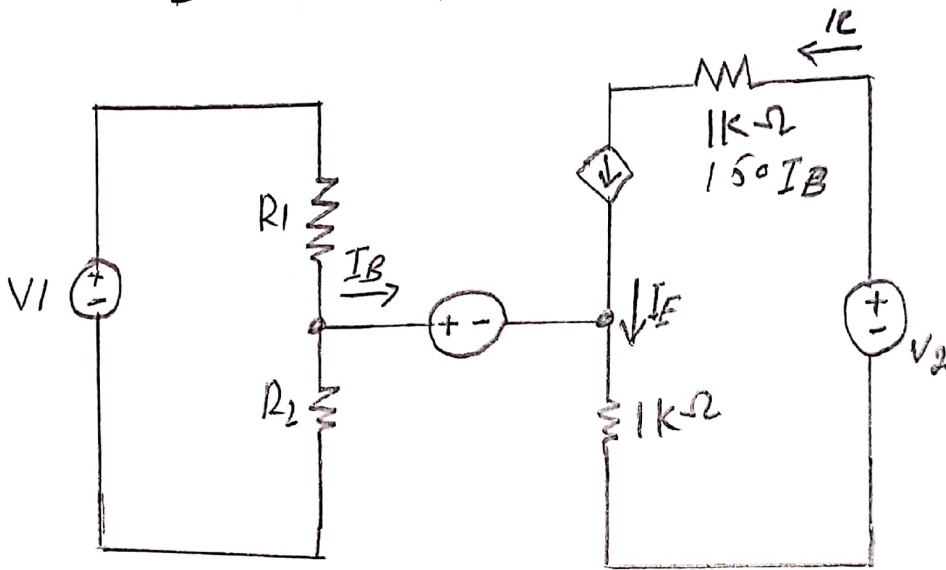Q2(b): For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region),  $I_B$  is measured to be 200  $\mu\text{A}$ . Determine  $I_C$  and  $I_E$ .



ANS 2(b)

KCL, total <sup>current</sup> entering a node = Total current leaving a node.

$$I_B + I_C = I_E \quad (\text{WR})$$

$$I_E = I_B + I_C \Rightarrow I_C = 150 \cdot I_B$$

$$I_E = 200 \mu\text{A}$$

$$I_C = 15 \text{ mA}$$


calculate  $I_E$  as:

$$I_E = 15 \cdot 10^{-3} + 100 \cdot 10^{-6}$$

$$I_E = 15.1 \text{ mA}$$


Q 3(a) Although drawn so that it may not appear obvious at first glance, the circuit of the following figure is in fact a single-node-pair circuit.

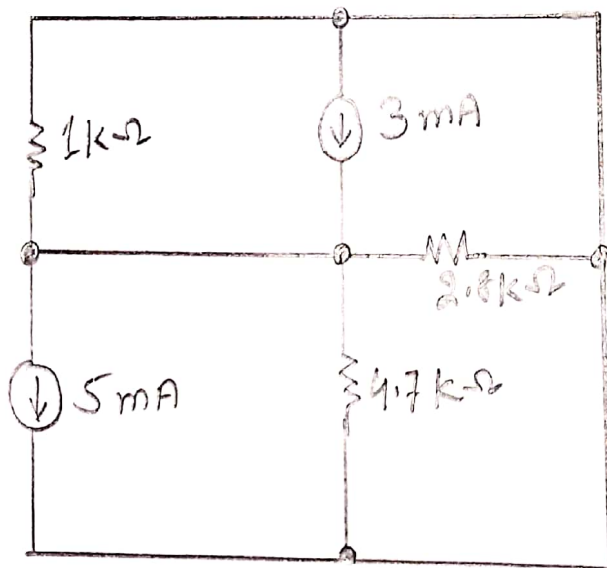- (a) Determine the ~~following~~ <sup>minimum</sup> power absorbed by each resistor.
- (b) Determine the power supplied by each current source.
- (c) Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).



ANS:  
 Find  $P(2.8k\Omega)$ ,  $P(4.7k\Omega)$ ,  $P(1k\Omega)$ ,  $P(5mA)$ ,  
 $P(3mA)$

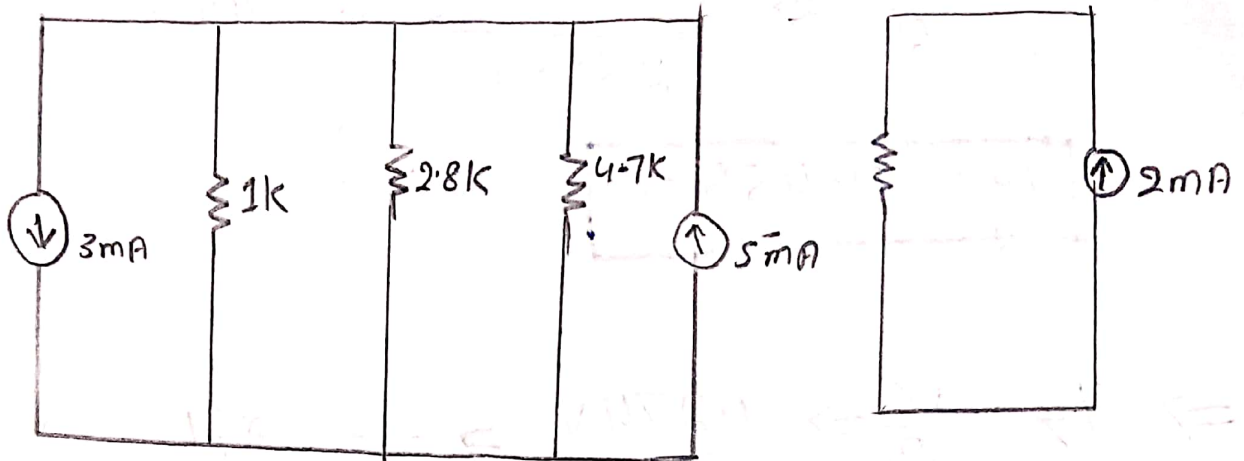Find  $v$  value in a better force  
 Find  $v$  by combining similar element.




use ohm's law

$$U = IV$$

$$U = 2 \times 10^{-3} \times 637 = \boxed{1.274V}$$

No its the I of each

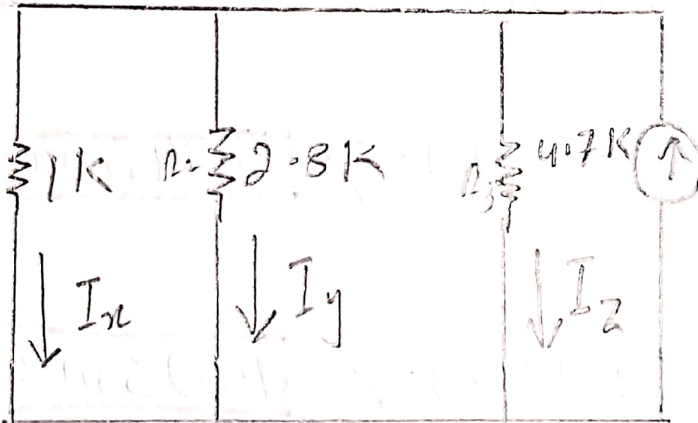

$$V = IR$$

$$I = \frac{V}{R}$$

$$I_x = \frac{V}{R_1} \Rightarrow \frac{1.274V}{1000 \Omega} \Rightarrow \boxed{1.274mA}$$

$$\boxed{1.274mA}$$

next page

$$\Rightarrow I_y = \frac{V}{R_2} \Rightarrow \frac{1.274V}{2800\Omega} \Rightarrow 0.000455$$

$$I_y = 0.455 \text{ mA}$$

$$\Rightarrow I_z = \frac{V}{R_3} \Rightarrow \frac{1.274V}{4700} \Rightarrow 0.000271$$

$$I_z = 0.271 \text{ mA}$$

Power:  
 $P = VI$

$$\Rightarrow P(2.8k) = (1.274)(0.271) \Rightarrow 0.5797 \text{ m watts}$$


$$\Rightarrow P(4.7k) = (1.274)(0.271) \Rightarrow 0.345 \text{ m watts}$$

$$\Rightarrow P(1k) = (1.274)(1.274) \Rightarrow 1.623 \text{ m watts}$$

$$\Rightarrow P(5 \text{ mA}) = (1.274)(-5) \Rightarrow -6.37 \text{ m watts}$$

$$\Rightarrow P(3 \text{ mA}) = (1.274)(3) \Rightarrow 3.822 \text{ m watts}$$

Q36) Determine the power absorbed by the  $15\Omega$  resistor in the circuit of the following figure.

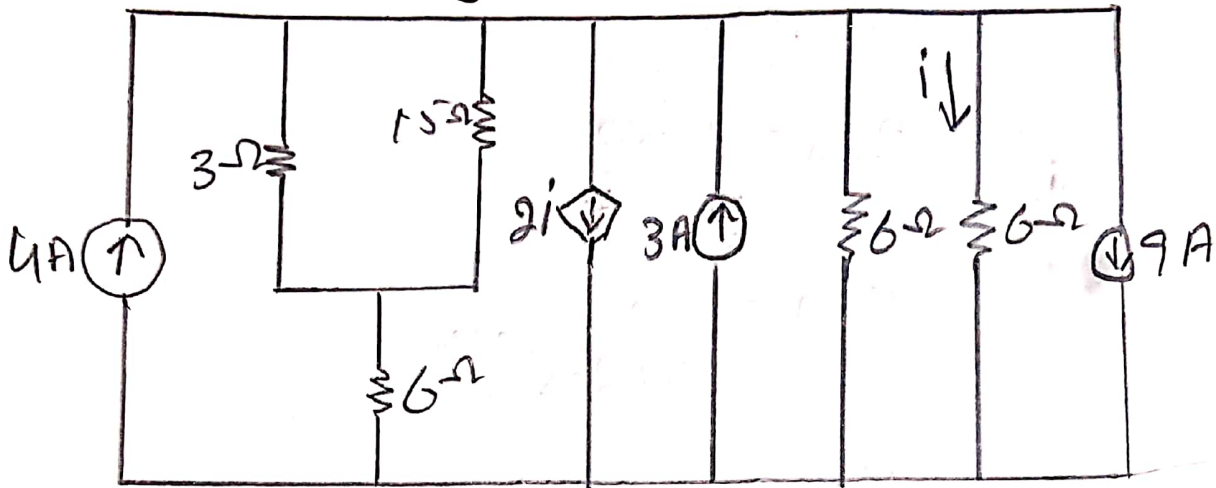

ANS 36):

First simplify the circuit by calculation source and resistance equalance.

$$I_{eq} = 4 - 2i + 3 - 9 = -2 - 2i$$

$$R_{eq} = (6 + 3 \parallel 15) \parallel 6 \parallel 6$$

$$R_{eq} = 8.5 \parallel 3 = 2.2174 \Omega$$

Now we can calculate voltage:

$$V = I_{eq} \times R_{eq}$$

$$V = (-2 - 2i) \times (2.2174 \Omega)$$

and from the diagram we can see that

$$V = 6i$$

$$= 6i = (-2 - 2i) \times 2.2174$$

$$= 10.4348i = -4.4348$$

Next page



$$j = -0.425 \text{ A}$$

$$V = -2.55 \text{ V}$$

power consumed by the  $15\text{-}\Omega$  resistor will need the voltage on that resistor that

$$P = V^2/R$$

$$P_{15\text{-}\Omega} = \frac{V_{15\text{-}\Omega}^2}{15\text{-}\Omega}$$

$$V_{15\text{-}\Omega} = \frac{6}{6+2.5} \text{ V}$$

$$V_{15\text{-}\Omega} = 1.8 \text{ V}$$

and power is:

$$P_{15\text{-}\Omega} = \frac{1.8^2}{15\text{-}\Omega}$$

$$P_{15\text{-}\Omega} = 0.216 \text{ W}$$