

①



②

③

Name: Mohsin Ali
ID = 13746

Paper: EDCI

instructor name: Dr. Shagar Shafiqe:

Q2:

The IN 4747 zener diode used
The regulation current in figure 20V
Given Data.

$$V_Z = 20V \quad I_Z = 17.5mA$$

$$I_{ZK} = 0.25mA \quad Z_Z = 22\Omega$$

(a) for I_{ZK}

$$V_{out} = V_Z - I_Z Z_Z$$

$$20V - (17.5mA - 0.25mA) 22\Omega$$

$$20V - 0.267V$$

$$V_{out} = 19.73V$$

P. 10

Calculate the Zener diode maximum current. The power dissipation is 1W

$$I_{Zm} = \frac{P_D(\text{max})}{V_Z} = \frac{1W}{20V} = 50mA$$

for I_{Zm}

$$\begin{aligned} V_{out} &= V_Z + 4I_Z Z_Z \\ &= 20V + (I_{Zm} - I_Z) Z_Z \\ &= 20V + (50mA - 12.5mA) 22\Omega \\ &= 20V + (37.5mA) 22\Omega \\ &= 20V + 0.825V \\ V_{out} &= \boxed{20.825V} \end{aligned}$$

(b) Calculate the value of R for Max Zener current when there is no load as shown in figure.



(3)

$$R = \frac{V_{in} - V_{out}}{I_{Zm}}$$

$$= \frac{24V - 20.825V}{50mA}$$

$$R = 63.5\Omega$$

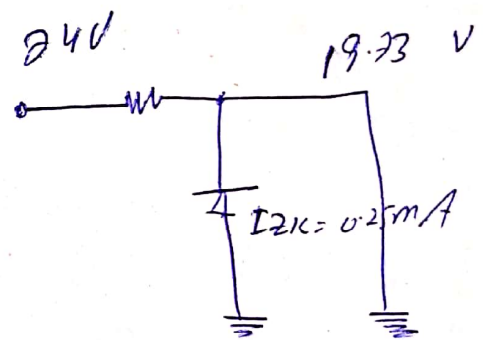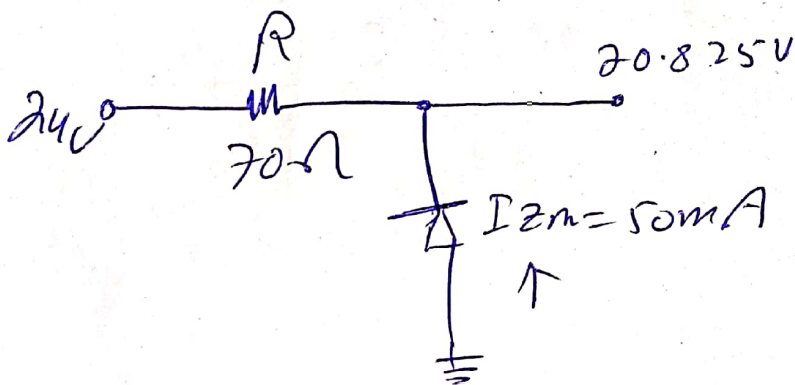$R = 70\Omega$ (nearest largest standard)



c) for maximum load resistance (maximum current) The zero diode current ~~is~~ minimum ($I_{Zk} = 0.25$)

$$I_T = \frac{V_{in} - V_{out}}{R} = \frac{24 - 19.73V}{70\Omega} = 0.061A$$

Question 2

(4)

Soll:

$$V_{BE} = 0.7V$$

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$= \frac{5V - 0.7V}{3.9k\Omega} = \boxed{1102\mu A}$$

$$\Rightarrow I_C = \beta_{DC} \cdot I_B$$

$$= (50)(1102\mu A) = \boxed{165.3mA}$$

$$= I_E = I_C + I_B \Rightarrow (165.3mA) + (1102\mu A)$$

$$= 165.3mA + 1102\mu A$$

$$= 166.4mA$$

$$\boxed{166.4mA}$$

$$\boxed{166.4mA}$$

Solve for V_{CE} and V_{CS}

$$V_{CE} = V_{CC} - I_C R_C = 15V - (165.3mA)(180\Omega)$$

$$= 15V - 29.7V = \boxed{-14.7V}$$

P.T.O

$$\begin{aligned} V_{CB} &= V_{CE} - V_{BE} = -14.7V - 0.7 \\ &= -15.4V \end{aligned}$$

Since the collector is at a lower voltage than the base, the collector base junction is forward biased.

Q3:

Ans:

Bipolar Junction Transistor:


BJT:

Transistors:

→ Invented in Dec 1947 at bell labs at USA

* BJT is a Three Terminal device and it is used in amplification of weak signal ~~and it is~~ in Switching operation.

Physical structure:

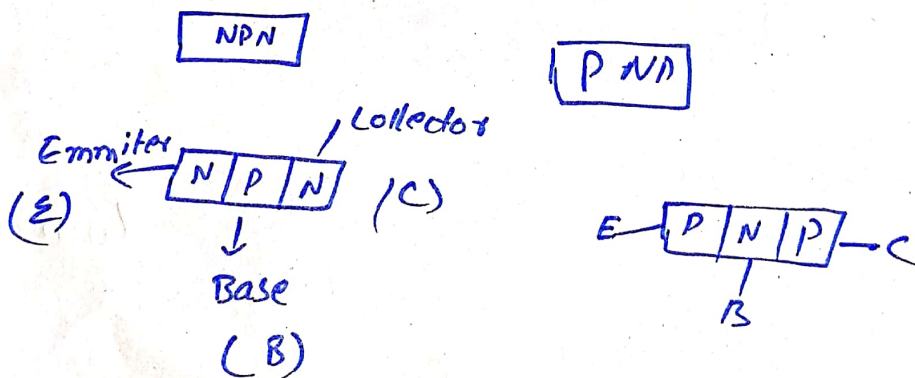

* 2 Junction (N)

* 1 Junction (P)

* $J_1 \rightarrow$ emitter-base

* $J_2 \rightarrow$ collector-base

* There is depletion region at J_1



width $C > E > B$

doping $E > C > B$

Q-40

⑦



• There is depletion region T_2

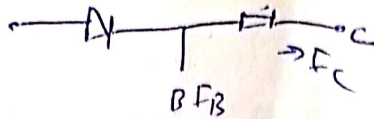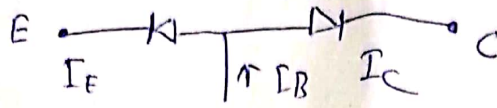



~~Symbol~~

Cross Section view

NPN

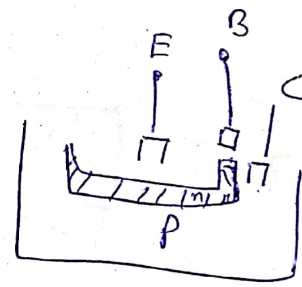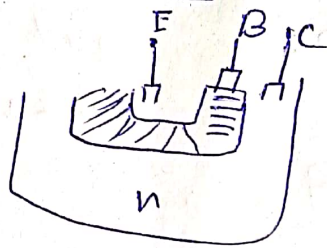

Symbol

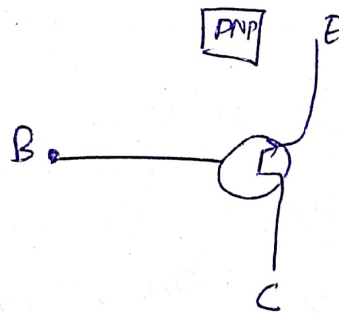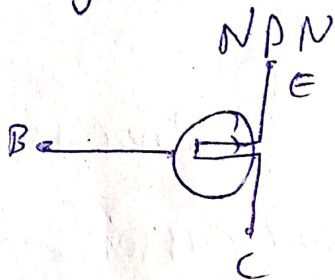


increas of NPN there will more from B → E

Q6

① ② ③

⑧

What is V_{CE} where $V_{in} = 0V$

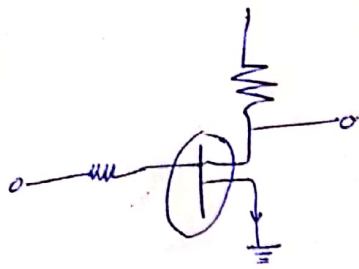

@

$V_{CE} = ?$ $V_{in} = 0V$

When $V_{in} = 0V$ so Transmitter is cut off mode.

$V_{CE} = V_{CC} = 10V$

(b)

$\min I_B = ?$ $\beta_{DC} = 125$

$V_{CE(sat)} = 0.4V$

$I_C(sat) = \frac{V_{CC}}{R_C} = \frac{10V}{1.0k\Omega} = 10mA$

$I_B = (\min) \frac{I_C(sat)}{\beta_{DC}} = \frac{10mA}{125}$


$I_B(\min) = 0.08\mu A$

Q5


Ans

②①⑨

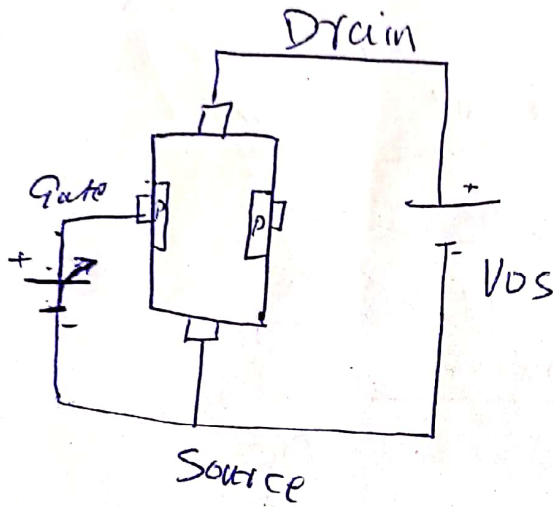JFET is a type of Junction field effect Transistor which is voltage controlled device as differ from BJT which is current controlled




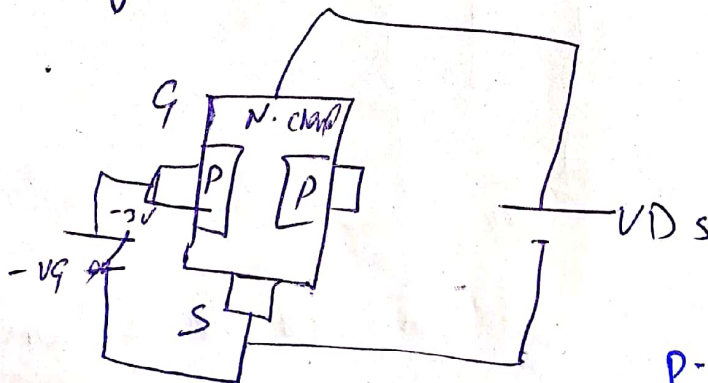Actually in FET the Drain to source current is controlled by the width of the channel the electric field \rightarrow produced by the gate to source voltage




p-t-d

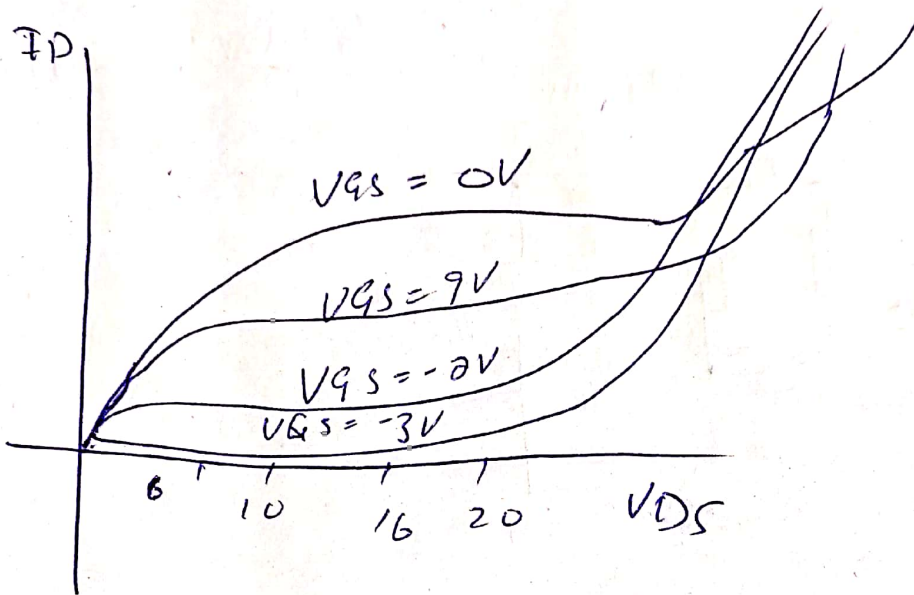So V_{GS} is more negative than this effect is called Pinch off region no current or less current flows.



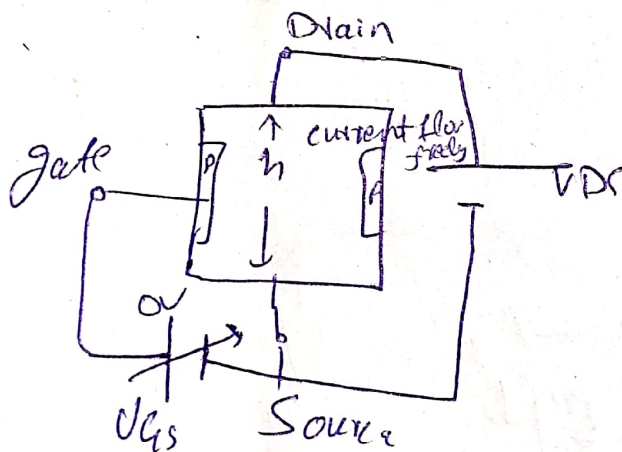So if we see to the graph with the no voltage applied to the gate the current flows



The channel is under wider and Drain $P. + 0$

current moves freely

(11)

(12)

(13)

(14)

if we ~~not~~ move f_0 decreases
and current cannot move \perp

Q4:

- Transmitter Fully ON

- Transmitter Fully OFF

- input and base at least 0V

- Collector current $I_C = 0$

- $V_{CE} = V_{CC}$

~~BE~~ - BE Junction in R-B

- BC Junction in R-B

- Max of Saturation current I_C flows

- BE Junction in F-B

- BC Junction in F-B

- $V_{CE} = 0$

- BE Junction is less than 0.7V

(B)

(11)

ON

OFF