

IQRA NATIONAL UNIVERSITY

Department of Electrical Engineering



Power Electronics

Name: Kaleem Ullah

ID: 13170


Submitted to: Engr Shayan Tariq Jan

Semester: 8th

Kaleem


13170

Question No (1):-

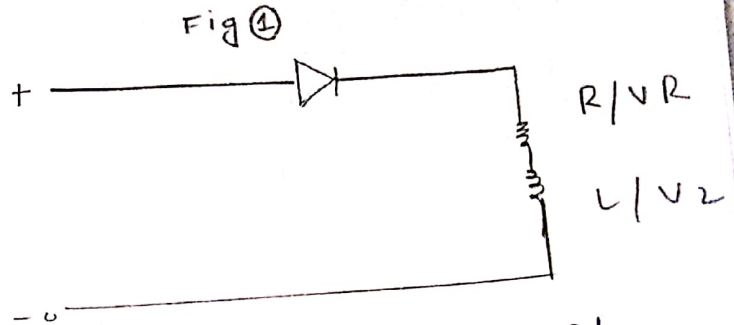

Answer: when diode is connected in RL

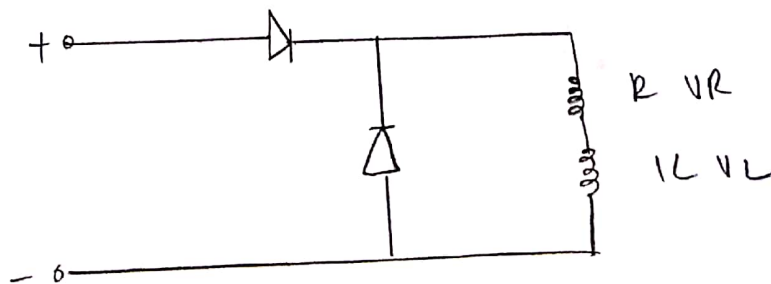
Circuit during positive the inductor become energize the its function is that inductor will store energy when the positive cycle is start the inductor become deenergize and creation of the decay current and high voltage take place



When the Free wheeling diode is connected in parallel will RL circuit during negative diode the

the inductor become deenergize and Free wheeling diode will provide path to decay current to avoid from any damage



=> waveForm

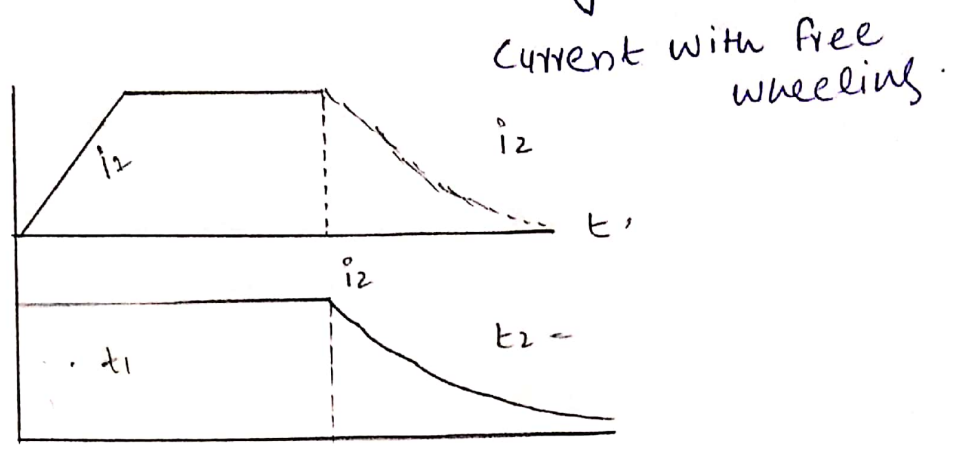

=> where RL circuit there is no need of the free wheeling diode and have no impact on the circuit.

Method # 02

=> RL connected in Series with diode.

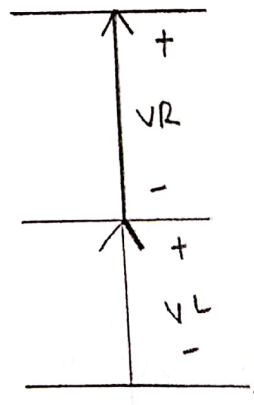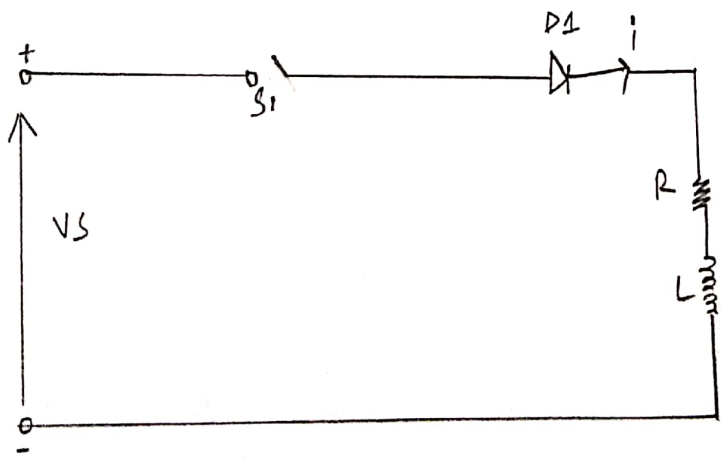

=> when S1 is closed at t=0, the current through the inductor increase

⇒ and is expressed as

$$V_S = V_L + V_R = L \frac{di}{dt} + Ri$$

⇒ with the initial condition $i(t=0)=0$

$i(t)$ is expressed as

$$i(t) = \frac{V_S}{V_R} (1 - e^{-tR/L})$$

$$i(t) = \frac{V_S}{V_R} (1 - e^{-tR/L})$$

⇒ The rate of change of this circuit can be obtained from.

$$\frac{di}{dt} = \frac{V_S}{L} e^{-tR/L}$$


⇒ The initial rate of rise of the current (at $t=0$) is obtained

$$\left. \frac{di}{dt} \right|_{t=0} = \frac{V_S}{L}$$


The voltages across the inductor

is
$$V_L(t) = L \frac{di}{dt} = V_S e^{-tR/L}$$

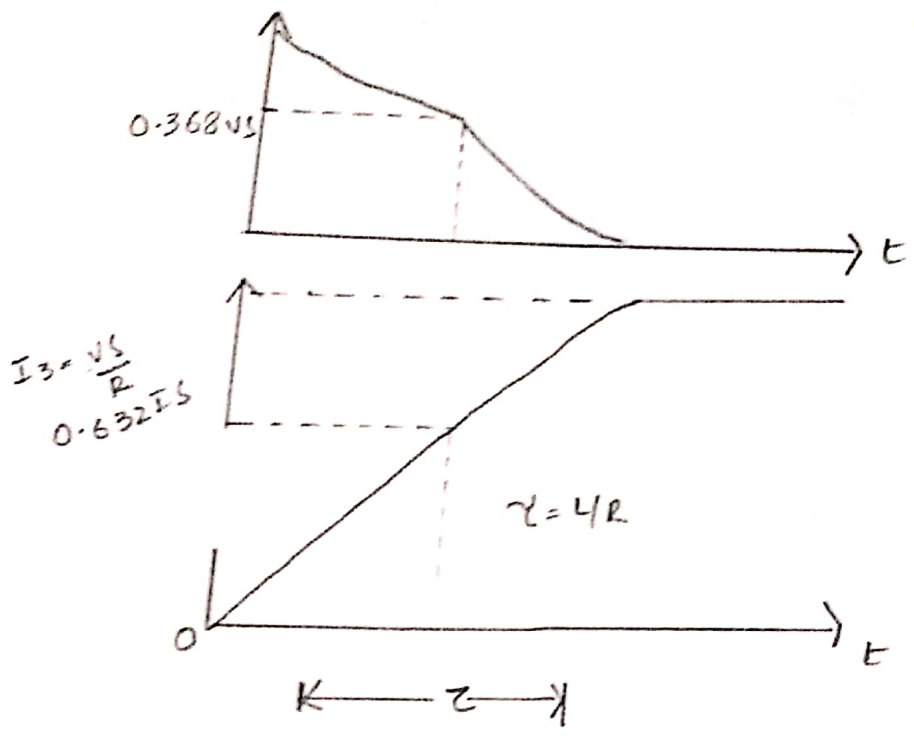
=> where $L/R = \tau$ is the time constant of RL load the waveforms for the voltage and current are shown.



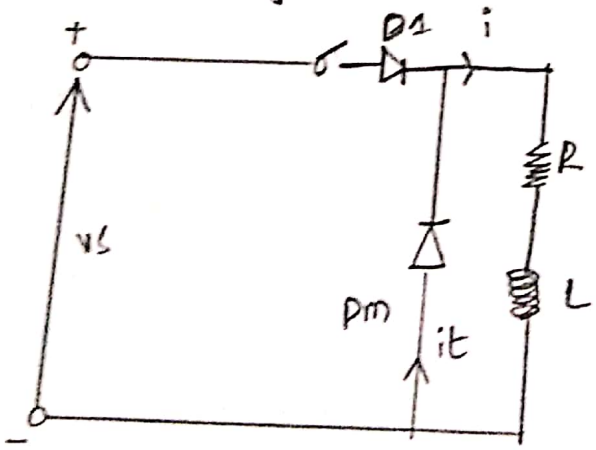
=> RL circuit connected in parallel with wheeling diode



(Circuit diagram)

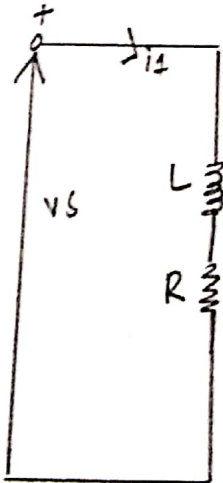


Model (1)

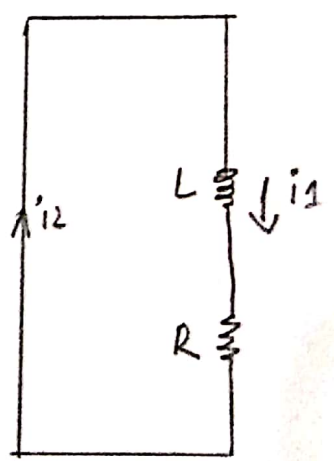

Model (2)

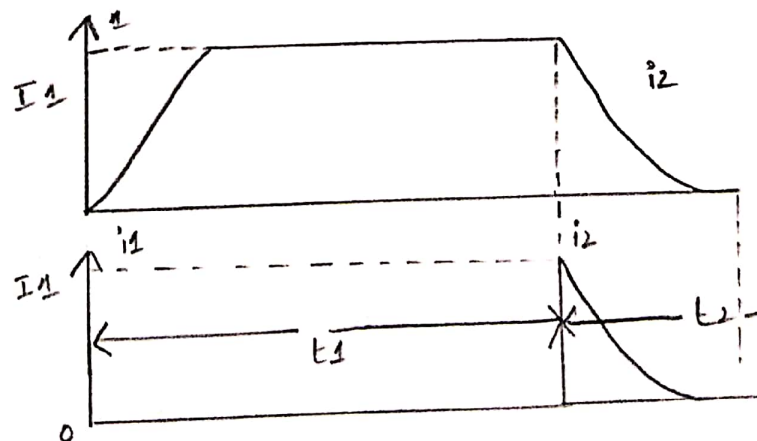- => The inductor has property to store energy
- => In AC current during positive half cycle the inductor stores energy
- => At negative half cycle the inductor de-energises
- => This may cause reverse damage to circuit
- => To avoid energy discription free wheeling diode is used
- => In negative half cycle the free wheeling diode is becomes forward bias so the current will flow through diode.



=> waveform

Question No #01 (part B)

=> Data

Answer :-

$$V_T = 1V$$

$$V_{DS} = 70V$$

$$V_{GS} = ?$$

For Saturation mode

$$V_{DS} = V_{GS} - V_T$$

$$V_{GS} = V_{DS} + V_T$$

$$V_{GS} = 70 + 1$$

$$\boxed{V_{GS} = 71V} \text{ Ans.}$$

(IP#13170)

Question No # 02

=> Part (A)

Answer :- ① The Switch Rate of the appliance will be low because BJT have lower switching rate than MOSFET (Performance Base)

② Losses will be low because losses in BJT is less than MOSFET and is an important advantage of BJT in appliance.

③ ON high frequency BJT are less efficient and it also effect the performance

④ Switching losses will increase because of the BJT in a Ppliance.

⑤ BJT operate on high frequency also have an impact on performance

- ⑥ ON state voltage low for BJT so the efficiency of the appliance decrease
- ⑦ Conduction losses decrease in BJT performance improve.

⇒ (B) Question (2)

- (i) SCR have no capabilities to handle high frequency that is the one of the impact on its performance.
- (iii) SCR can handle more power, voltage current which increase the efficiency of the appliance
- (iv) SCR can be protected and become one of the fuse which can decrease losses used as switch the performance will be improve.

- page (9)
- (V) The cost of the SCR is less than MOSFET is the one of advantage
- (VI) And another problem is that simultaneously one the SCR is the one of the disadvantage
- (VII) And it is very easy to operate.

Question # 03

(a) Given Data

$$V_{CC} = 170V$$

$$V_B = 10V$$

$$V_{CE} = 1V$$

$$V_{BE} = 1.5V$$

$$R_C = 70V$$

=> To Find

(a) Mode = ?

(b) $R_B = ?$

(c) $\beta_{Force} = ?$

(d) $P_T = ?$

⇒ (Solution)

(a) Transistor as switch

(b) $R_B = ?$

⇒ we know that

$$I_{CS} = \frac{V_{CC} - V_{CE}(\text{Sat})}{R_C}$$

$$\frac{170 - 1}{70}$$

$$I_{CS} \Rightarrow 2.4 \text{ A}$$

we know that

$$I_{BS} = \frac{I_{CS}}{\beta F(\text{min})}$$

$$\Rightarrow \frac{2.4}{8}$$

$$= 0.3 \text{ A}$$

we know that

$$I_B = 0.05 * I_{BS}$$

$$\Rightarrow 5 * 0.3$$

$$\Rightarrow 0.5 A$$

we know that

$$R_B = \frac{V_B - V_{BE}}{I_B}$$

$$\Rightarrow \frac{10 - 1.5}{1.5 A}$$

$$\Rightarrow 5.6 \Omega$$

(c)
$$I_{C \text{ force}} = \frac{I_C}{I_B}$$

$$\Rightarrow \frac{2.4}{1.5}$$

$$\Rightarrow 1.6 A$$

(d)
$$P_T = ?$$

we know that

$$P_T = V_{BE} I_B + V_{CE} I_C$$

$$\Rightarrow (1.5)(1.5) + (1)(2.4)$$

$$\Rightarrow 2.25 + 2.4$$

$$\Rightarrow 4.65 \text{ watt}$$

Answer: