

P.No 1

Department of Electrical Engineering
Assignment

Course Detail

Course title:- Electrical Networks
Analysis

Module: 4th


Total Marks :- 20

Instructor :- Dr Engz Shehryar
Shafique

Student detail

Name :- MaaZ Khan

Student ID: 14569

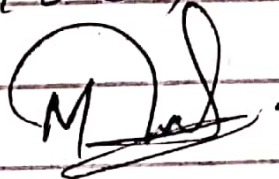Student sign: 

Question no 7

ANS:-

$$(a) |V_{ab}| = \sqrt{3} V_p = 240$$

Here Now

$$V_p = \frac{240}{\sqrt{3}} = 138.56$$

$$V_{ab} = V_p \angle -30^\circ$$

$$P_f = 0.5 = \cos \theta$$

$$\theta = 60^\circ$$

$$P = S \cos \theta$$

$$S = \frac{P}{\cos \theta}$$

$$= \frac{5}{0.5}$$

$$= 10 \text{ KVA}$$

$$Q = S \sin \theta$$

$$= 10 \sin 60$$

$$= 8.66$$

$$S_p = 5 + j 8.66 \text{ KVA}$$

But

$$S_p = \frac{V_p^2}{Z_p}$$

$$Z_p = \frac{V_p^2}{S_p}$$

$$Z_p = \frac{(138.56)^2}{(5 + j8.66) \times 10^3}$$

$$Z_p = 0.96 - j1.663$$

$$Z_p = 0.96 + j1.663 \Omega$$

(b)

$$I_a = \frac{V_{ab}}{Z_p} = \frac{138.56 \angle -30^\circ}{0.96 + j1.6627}$$


$$I_a = 72.17 \angle -90^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ$$

$$I_b = 72.17 \angle -210^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ$$

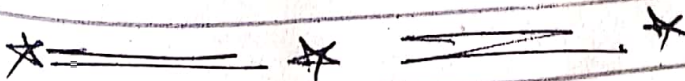
$$I_c = 72.17 \angle 30^\circ \text{ A}$$



P.No 4

Question No 6

ANS:- The given circuit is:

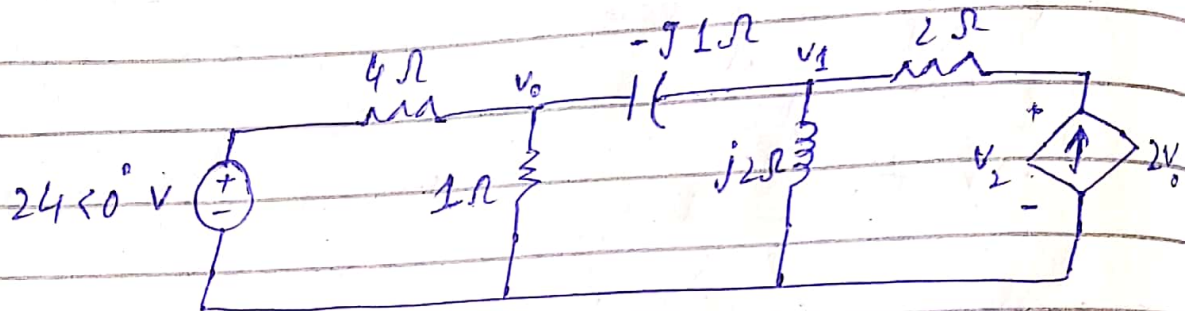

At Node 0,

$$\frac{24 - V_0}{4} = \frac{V_0}{1} + \frac{V_0 - V_1}{-j}$$

$$24 = (5 + j4)V_0 - j4V_1 \rightarrow \textcircled{1}$$

At Node 1,

$$\frac{V_0 - V_1}{-j} + 2V_0 = \frac{V_1}{j2}$$

$$V_1 = (2 - j4)V_0 \rightarrow \textcircled{2}$$

Now substituting $\textcircled{2}$ into $\textcircled{1}$,

$$24 = (5 + j4 - j8 - 16)V_0$$

$$V_0 = \frac{-24}{11 + j4}$$

$$V_1 = \frac{(-24)(6 - j4)}{11 + j4}$$

P. No 5

The voltage across the dependent source is:

$$V_2 = V_1 + (2)(2V_0) \\ = V_1 + 4V_0$$

$$V_2 = \frac{-24}{11+j4} \cdot (2-j4+4)$$

$$V_2 = \frac{(-24)(6-j4)}{11+j4}$$

$$S = \frac{1}{2} V_2 I^* = \frac{1}{2} V_2 (2V_0^*)$$

$$S = \frac{(-24)(6-j4)}{11+j4} \cdot \frac{-24}{11-j4}$$

$$S = \left(\frac{576}{137} \right) (6-j4)$$

$$S = 25.23 - j16.82 \text{ VA}$$

* \Rightarrow * \Rightarrow * \Rightarrow *

Question No 5

ANS:-

Given data:

$$\text{Source voltage} = V_s = 115 \angle 0^\circ \text{ V}$$

$$\text{Source Impedance} = Z_s = 1 + j0.5 \Omega$$

$$\text{Line Impedance} = Z_l = 0.4 + j0.3 \Omega$$

$$\text{Load Impedance} = Z_L = 23.2 + j18.9 \Omega$$

So Find the load current I_L .

$$Z = Z_a + 2Z_l + Z_b$$

$$Z = (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$Z = 25 + j20$$

$$I_L = \frac{V_s}{Z} = \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = 3.592 \angle -38.66^\circ \text{ A.}$$

* ≡ * ≡ * ≡ *

Question No 3

Solution:

Given that $s_1 = -10$ and $s_2 = -20$,
we recall that

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -10, -20$$

Clearly,

$$s_1 + s_2 = -2\alpha = -30 \quad \text{or}$$

$$\alpha = 15 = R/(2L) \quad \text{or}$$

$$R = 60L \rightarrow \textcircled{1}$$

$$s_1 = -15 + \sqrt{15^2 - \omega_0^2} = -10$$

which lead to

$$15^2 - \omega_0^2 = 25 \quad \text{or}$$

$$\omega_0 = \sqrt{225 - 25}$$

$$= \sqrt{200} = \frac{1}{\sqrt{LC}},$$

$$\text{thus } LC = \frac{1}{200} \rightarrow \textcircled{2}$$

Since we have a series
RLC circuit, $i_L = i_C = C dv_C/dt$

which gives,

P. No 8

$$i_L/c = \frac{dv_L}{dt} = \left[200e^{-20t} - 300e^{-30t} \right]$$

$$\text{or } i_L = 100c \left[2e^{-20t} - 3e^{-30t} \right]$$

But,

$$i \text{ is also } = 20 \left\{ \left[2e^{-20t} - 3e^{-30t} \right] \times 10 \right\}$$
$$= 100c \left[2e^{-20t} - 3e^{-30t} \right]$$

therefore,

$$c = \left(\frac{0.02}{10^2} \right)$$

$$= 200 \mu\text{F}$$

$$L = \frac{1}{(200c)}$$

$$= 25 \text{ H}$$

$$R = 30L$$

$$= 750 \text{ ohms}$$



Question No 1

Solution:

$$(a) \quad \tau = R_c = \frac{1}{4}$$

$$\Rightarrow -1 = C \frac{dv}{dt}$$

$$\Rightarrow -0.2 e^{-4t} = C(10)(-4) e^{-4t}$$

$$\Rightarrow C = 5 \text{ mF}$$

$$R = \frac{1}{4C} = 50 \Omega$$

$$(b) \quad \tau = R_c = \frac{1}{4} = 0.250$$

$$(c) \quad W_c(t) = \frac{1}{2} C V^2$$

$$\Rightarrow \frac{1}{2} (5 \times 10^{-3}) (100)^2$$

$$\Rightarrow 250 \text{ mJ}$$

(d)

$$W_p = \frac{1}{2} \times \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{1}{2} C V_0^2 (1 - e^{-2t_0})$$

$$0.5 = 1 \cdot e^{-8t}$$

$$\Rightarrow e^{-8t_0} = \frac{1}{2}$$

OR

$$e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2)$$

$$= 86.6 \text{ ms}$$



Question NO 2

Solution:

Step 1

Let the inductor current,
for $t < 0$

$$i(0) = \frac{120}{100} = \frac{12^6}{10^5} = 1.2 \text{ A}$$

For $t > 0$ we have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100+400}$$

$$= \frac{50}{500} = \frac{81}{50 \cdot 10} = 0.1$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 1.2 e^{-10t}$$

$$\text{At } t = 100 \text{ ms} = 0.1 \text{ s}$$

$$i(0.1) = 1.2 e^{-1}$$

$$= 0.441 \text{ A}$$

which is the same as the current through the resistor
step 2

$$\tau = R_{\text{eq}} C = 60 \mu\text{s}$$

An integrator

$$T < 0.1 \quad \tau = 6 \mu\text{s}$$


$$T_{\text{min}} = 6 \mu\text{s}$$



Question No 4


Solution:

The given circuit is:

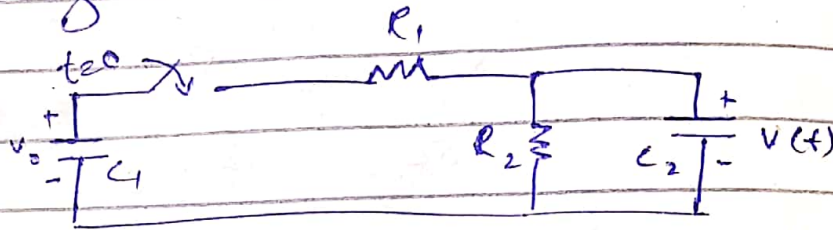

For $t = 0$, $v(0) = 0$

For $t > 0$ the circuit is:

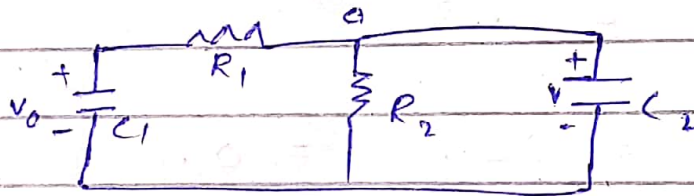

$$v_0 = \frac{v}{R_1} = \left(\frac{v}{R_2} \right) + C_2 \frac{dv}{dt}$$

$$v_0 = v \left(1 + \frac{R_1}{R_2} \right) + R_1 C_2 \frac{dv}{dt}$$

$$60 = \left(1 + \frac{5}{2 \cdot 5} \right) + (5 \times 10^6 \times 5 \times 10^{-6}) \frac{dv}{dt}$$

$$60 = 3V + 25 \frac{dv}{dt}$$

$$v(t) = v_s + [A e^{-3t/25}]$$

where

$$3v_s = 60 \text{ yields } v_s = 20$$

$$v(0) = 0 = 20 + A \text{ or } A = -20$$

$$v(t) = -20 (1 - e^{-3t/25}) V$$

