

Department of Electrical Engineering

Midterm Exam

Date: 29/09/2020

Course Details

Course Title: Electronic Devices and Circuits
 Instructor: _____


Module: _____
 Total Marks: 50

Student Details

Name: _____

Student ID: _____

Student Signature: _____

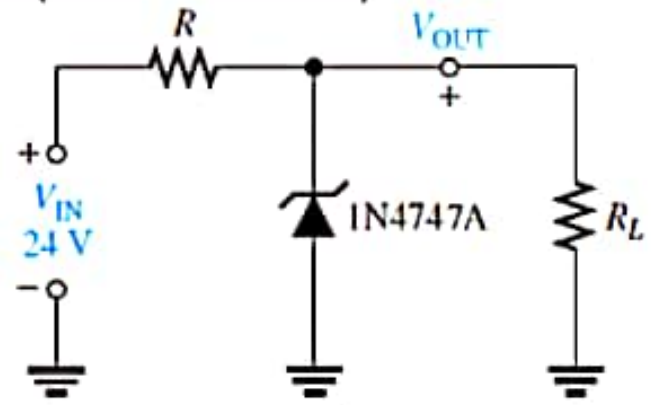Q1.	<p>The 1N4747A zener used in the regulator circuit of Figure 1 is a 15 V diode, determine the following:</p> <p>(a) Determine V_{OUT} at I_{ZK} and at I_{ZM}. (b) Calculate the value of R that should be used. (c) Determine the minimum value of R_L that can be used.</p> <p>The electrical characteristics and values of V_Z, I_Z, I_{ZK}, Z_Z can be found in diode datasheet Fig 3-7 (in course reference book) and online.</p>  <p align="center">Figure 1</p>	<p>Marks 10 CLO 02</p>
Q2.	<p>Determine I_B, I_C, I_E, V_{BE}, V_{CE} and V_{CB} in the circuit shown in Figure 2.</p>	<p>Marks 05 CLO 02</p>

Yasir Ahmad 13788

13788 Yasir Ahmad

Q1

Ans

The 1N4747 Zener Diode used
The regulation ckt in figure is 20V.

$$V_z = 20V \quad I_{z2} = 12.5mA$$

$$I_{zK} = 0.25mA \quad z_z = 22\Omega$$

(a) for I_{zK}

$$V_{out} = V_z - \Delta I_z \cdot z_z$$

$$= 20V - (I_z - I_{zK}) z_z$$

$$= 20V - (12.5mA - 0.25mA) \cdot 22\Omega$$

$$= 20V - (12.25mA) \cdot 22\Omega$$

$$= 20V - 0.267V$$

$$V_{out} = 19.73V$$

Calculate the Zener Diode Maximum
current the power dissipation in μW

P#1

$$I_{ZM} = \frac{P_{D \max}}{V_Z} = \frac{1W}{20V} = 50mA$$

For I_{ZM}

$$V_{out} = V_Z + \Delta I_Z Z_Z$$

$$= 20V + (I_{Z01} - I_Z) Z_Z$$

$$= 20V + (50mA - 12.5mA) 22\Omega$$

$$= 20V + (37.5mA) 22$$

$$= 20V + 0.825V$$

$$V_{out} = 20.825V$$

(b) Calculate the value of R For maximum Zener Current when there is no load as shown in figure



$$R = \frac{V_{in} - V_{out}}{I_{ZM}}$$

$$= \frac{24V - 20.825V}{50mA}$$

$$= 63.5\Omega$$

PAD

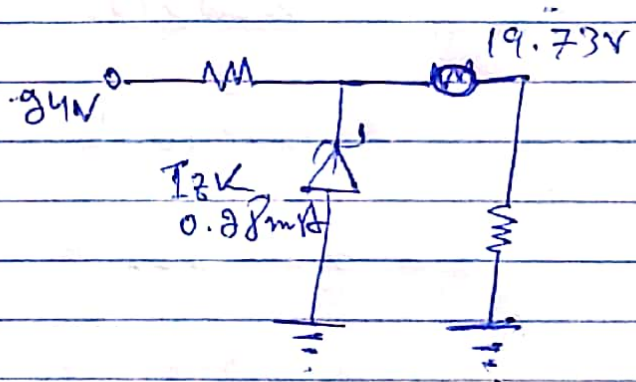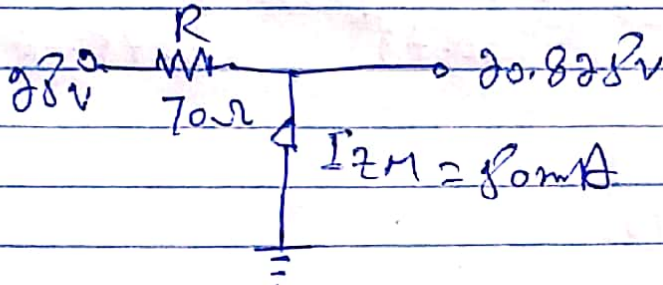$R = 70 \Omega$ (nearest largest standard)



(c) for maximum load Resistance
(maximum current)

The Zener diode Current minimum

$$(I_{ZK} = 0.28)$$

$$I_T = \frac{V_{in} - V_{out}}{R} = \frac{24V - 19.73V}{70 \Omega}$$

$$= 0.061A$$

$$I_T = 61mA$$

$$I_L = I_T - I_{ZK}$$

$$= 61 - 0.28mA$$

P#3

$$I_L = 60.78 \text{ mA}$$

$$R_L = \frac{V_{out}}{I_L} = \frac{19.3}{60.78} = \frac{19.3}{60.78 \text{ mA}}$$

$$= \frac{19.3}{0.0678}$$

$$= 285.92 \Omega$$

$$R_L = 286 \Omega$$

P#4

Q9

VA

$$I_B = ?$$

$$I_C = ?$$

$$I_E = ?$$

$$V_{BE} = ?$$

$$V_{CE} = ?$$

$$V_{CB} = ?$$

Solution.

$$V_{BE} = 0.7 \text{ V.}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{8 \text{ V} - 0.7 \text{ V}}{3.9 \text{ k}\Omega} = \boxed{1102 \mu\text{A}}$$

$$I_C = \beta_{DC} \cdot I_B = (110) (1102) = \boxed{165.3 \text{ mA}}$$

$$I_E = I_C + I_B = 165.3 \text{ mA} + 1102 \mu\text{A}$$

$$I_E = \boxed{166.4 \text{ mA}}$$

P#4

10

Solve for V_{CE} and V_{CB}

$$\begin{aligned}V_{CE} &= V_{CC} - I_C R_C = 18V - (165.3mA)(180\Omega) \\ &= 18V - 29.7V \\ &= -11.7V \quad \underline{\text{Ans}}\end{aligned}$$

$$\begin{aligned}V_{CB} &= V_{CE} - V_{BE} = -11.7V - 0.7V \\ &= -12.4V \quad \underline{\text{Ans}}\end{aligned}$$

Since the collector is at ^{Lower} ~~Higher~~ voltage than the base, collector-base junction is ~~reverse~~ biased Forward.



P#N#P

Q3

Bipolar Junction Transistor.

Ans

BJT

BJT Transistor was invented in Dec 1947 at bell labs at USA.


⇒ BJT is a three terminal device and it is used in Amplification

of weak signal used in switching operation.

⇒ physical structure

NPN

PNP

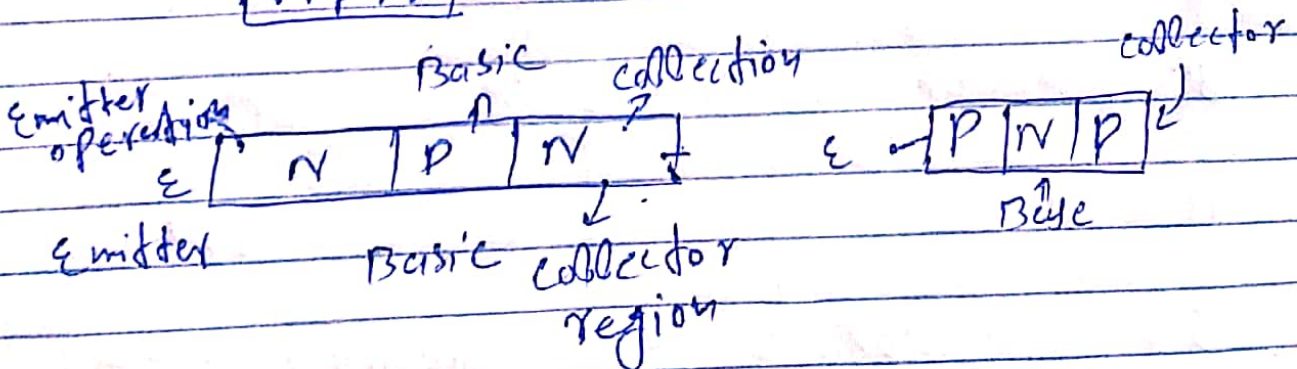

PNP

④

⇒ 2 Junction (N)



⇒ 1 Junction (P)

⇒ J_1 → emitter-base

⇒ J_2 → collector-base

⇒ There is depletion region at J_1

⇒ There is depletion region at J_2

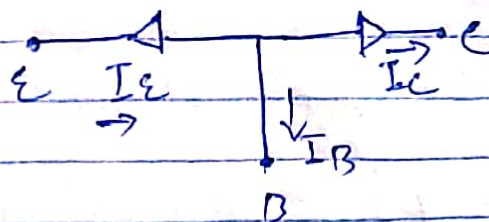
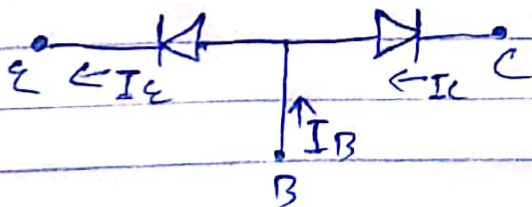


P#9

2

Cross Section view



NPN

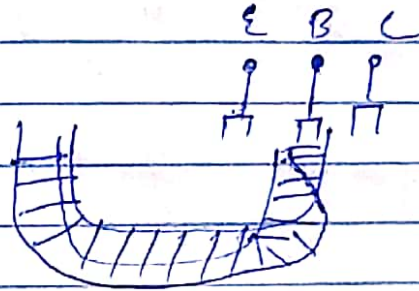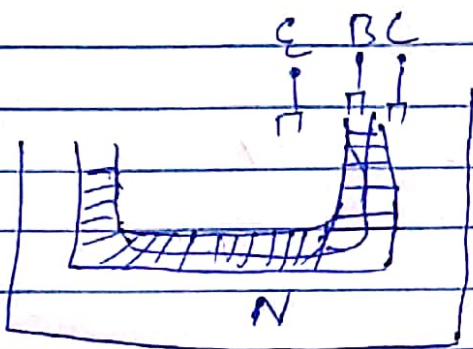

Symbols

NPN

PNP

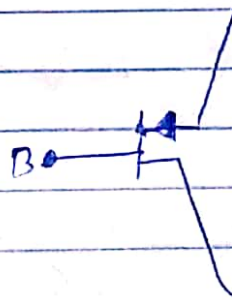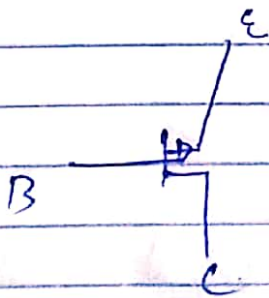

increased of NPN the
will more from B → E

⊙

P#9

~~P#9~~

Now using the following relationship.


$$I_c = \beta_{DC} \cdot I_B$$

Value of the I_c are calculated and tabulated in below Table

The resulting curves are

Table

I_B	I_c
0.8 mA	0.8 mA
1.0 mA	1.0 mA
1.8 mA	1.8 mA

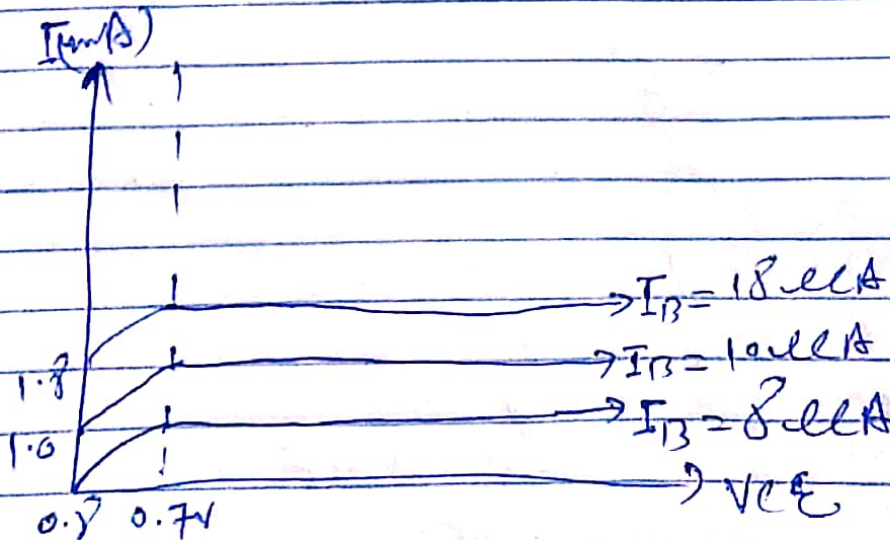

P#10

Q4

Ans

Transistor Fully ON (ON)

Transistor Fully OFF (OFF)

Input and base are at 0V (OFF)

Collector current $I_c = 0$ (OFF)

$V_{ce} = V_{cc}$ (OFF)

BE Junction is reverse bias (OFF)

BC Junction is forward bias (OFF)

Maximum of saturation current flows

BE Junction is forward bias (ON)

BC Junction is forward bias (ON)

$V_{ce} = 0V$ (ON)


BE Junction is less than 0.7V (OFF)

(ON)

Q.P
Ans


JFET is a Type of Junction field Effect Transistor.

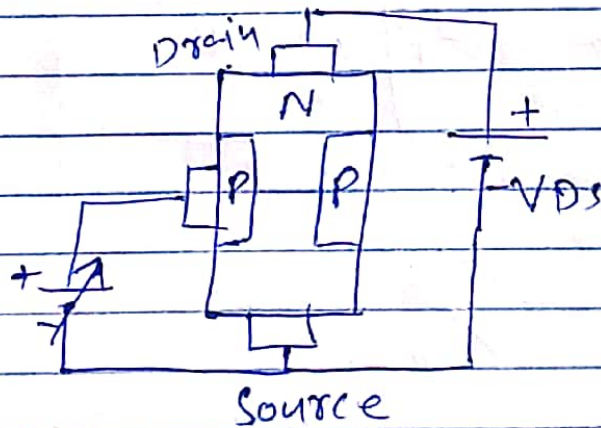which is voltage controlled device as differ from ~~controlled~~ BJT which is ~~current~~ current controlled




Actually in EFT the Drain to source current is controlled by the width of the channel the electric field is produced by the

~~electric~~ gate to source voltage.

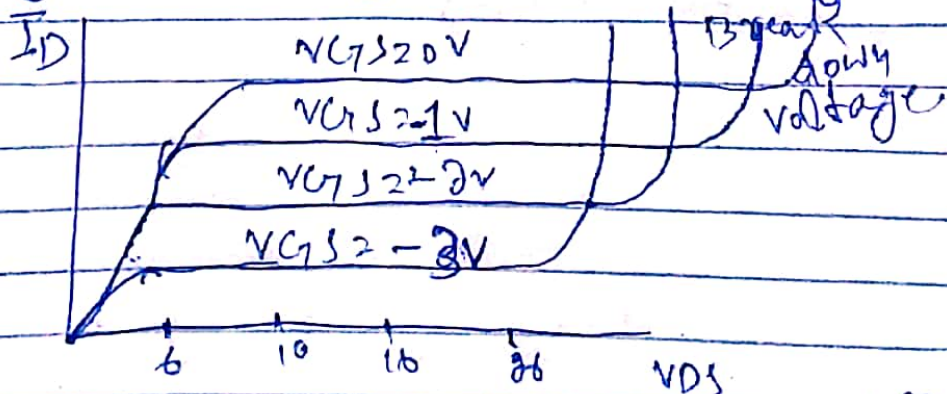


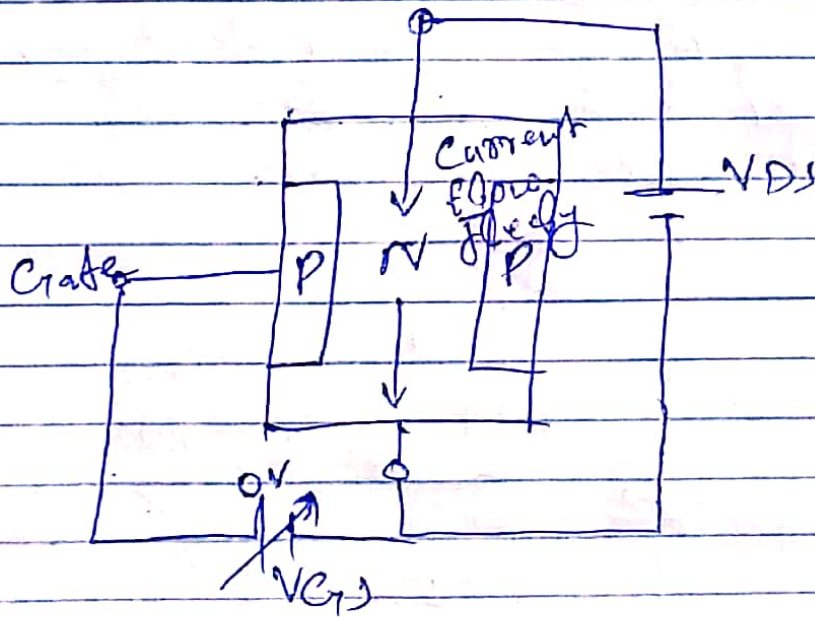So if we see to the graph with the no voltage Applied to the gate the current flows freely.



The channel are under and Drain current move freely

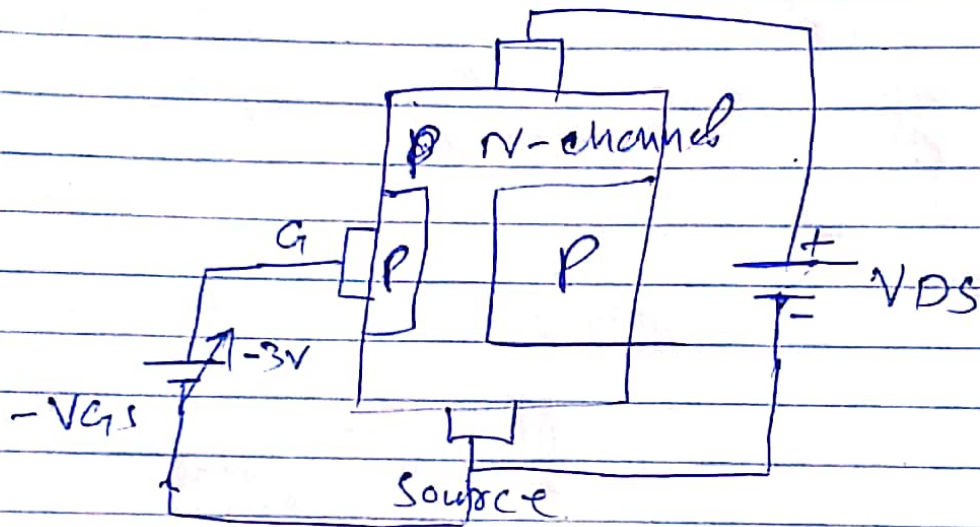if we move V_{GS} to negative value the channel width start to decreases and current cannot move.



So V_{GS} is more negative so
 no current flows and
 this effects is called pinch

off region no current or less
 current flows.

Q6

Ans(a) Find $V_{CE} = ?$ When $V_{in} = 0V$ (b) $I_B = ?$ $\beta_{DC} = 125$, $V_{CE} = 0.4V$ Solution.

When $V_{in} = 0V$ so Transistor is in Cutt OFF mode and

$$V_{CE} = V_{CC} = 10V$$

So $V_{CE} = 10V$.

$$(b) I_C(\text{sat}) = \frac{V_{CC}}{R_C} = \frac{10V}{1k\Omega} = 0.01A = 10mA$$

$$I_B(\text{min}) = \frac{I_{CC}(\text{sat})}{\beta_{DC}} = \frac{10mA}{125} = \frac{10 \times 10^{-3}}{125}$$

$$= 0.00008$$

$$I_B(\text{min}) = 80.0\mu A$$

P#

Ans