

Basic Electro Mechanics 1

7493
Bilal Hussain

Answer # 2 (a)

Ans For Two Resistance :-


$$R_{eq} = \frac{R_1 + R_2}{R_2 + 1}$$

For "n" Number of Resistance :-

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$

Answer # 2 (b)

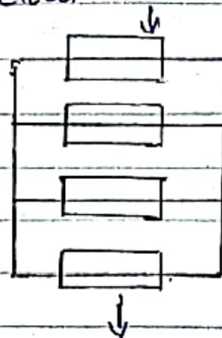Ans In a Parallel circuit resistance decrease and conductance increase with addition of more resistors



Adding successive Resistance is parallel

R increase with more Resistor.
G Decrease with more Resistor.

(2)

Answer # (2)

Given Data:-

Voltage, $V = 24$ volts
Resistance, $R_1 = 1 \Omega$
Resistance, $R_2 = 2 \Omega$
Resistance, $R_3 = 3 \Omega$

Required:-

Current = $I_1, I_2, I_3 = ?$

Power = $P_1, P_2, P_3 = ?$

Solution:-

By Ohm's law

$$I = V/R$$

For $I_1 = V = 24$ volts, $R_1 = 1 \Omega$

$$I_1 = \frac{V}{R_1} = \frac{24}{1}$$

$$I_1 = 24 \text{ (amperes) A}$$

For $I_2 = V = 24$ volts, $R_2 = 2 \Omega$

$$I_2 = 24/2$$

$$I_2 = 12 \text{ Amperes}$$

③

$$I_3 = V = 24 \text{ volts}, R_3 = 3 \Omega$$

$$I_3 = 24/3$$

$$I_3 = 8 \text{ Amperes}$$

Power \Rightarrow

$$P = I \times V$$

$$\text{For } P_1 = I_1 = 24 \text{ A}, V = 24 \text{ volts}$$

$$P_1 = 24 \times 24$$

$$P_1 = 576 \text{ watts}$$

$$\text{For } P_2 = I_2 = 12 \text{ A}, V = 24 \text{ volts}$$

$$P_2 = 12 \times 24$$

$$P_2 = 288 \text{ watts}$$

$$\text{For } P_3 = I_3 = 8 \text{ A}, V = 24 \text{ V}$$

$$P_3 = 8 \times 24$$

$$P_3 = 192 \text{ watts}$$

(4)

Answer # (3)

Q Differentiate between the following

(a)	Voltage	Current
(1)	Voltage also called electromotive force is simply the energy per unit charge. In other words voltage is the difference in electric potential b/w two points	(1) Current is just rate of flow of electric charge. In simple words the current is the rate at which electric charge flows in a circuit at a particular points.
(2)	The SI unit of voltage = (V)	(2) The SI unit is Ampere (A)
(3)	Denoted by 'V'	(3) Denoted by 'I'
(4)	Measured by voltmeter	(4) Measured by using an Ammeter.
(5)	Voltage create an electrostatic field	(5) Current create a magnetic field.

(B)

Resistance

Conductance

→ The length of conductor is similar to the length of a hallway. A shorter hallway would allow people to move through at a higher rate than a longer one.

→ So a shorter would allow electrons to move through at a higher rate than longer one.

→ Symbol OHMS Ω

→ Conductance is reciprocal of resistance

Conductance is a term is not used much in wired circuits but it is used extensively in circuits involving solution

Symbol G .

(C)

Power

→ Power is the rate at which work is done or energy transmitted.

→ ^{unit} Watt = Joules/second

→ Symbol = P

→ Power is the rate at which energy is transferred.

→ Power cannot be transferred from one to another

Energy

→ Energy is the capacity to do work. Energy is Power integrated over time.

→ Unit = watt-second or joule = Newton meter.

W

→ Energy is what makes changes happen and can be transferred from one object to another.

Energy change from one to another.

(D)

Inductance

→ The electrical component associated with inductance is known as inductor which usually coils with a core or without.

→ Inductance is measured by Henry (H) symbol is L.

Capacitance.

Capacitance is associated with capacitors. There are several types of capacitor used in circuits.

Capacitance is measured by Farad in symbol is C.

(e)

Synchronous Motor

Asynchronous Motor

(i) Synchronous motor is a machine whose rotor speed and speed of the stator magnetic field is equal
 $N = N_s = 120 \frac{F}{p}$

(ii) Brushless motor variable reluctance motor

(iii) The value of slip is zero

(iv) It requires an additional DC power source to initially rotate to get or near at the synchronous speed

(v) Synchronous motor is costly

(vi) Efficiency is greater than asynchronous motor

(vii) Not self starting

(i) Asynchronous motor is a machine whose rotor rotates at speed less than synchronous speed $N < N_s$

(ii) AC induction motor is known as asynchronous

(iii) The value of slip is not equal to zero

(iv) It doesn't require any additional starting source.

(v) Less costly

(vi) Less efficient.

(vii) self starting