

# Department of Electrical Engineering

## Assignment

Date: 13/04/2020

### Course Details

Course Title: Linear Circuit Analysis

Module: 2

Instructor: \_\_\_\_\_

Total Marks: 30

### Student Details

Name: Saheeb Ul Hassan




Student ID: 16318

Q1	(a)	<p>For each of the circuits in figure, find the current <math>I</math> and compute the power absorbed by the resistor</p> <div style="text-align: center;"> </div>	Marks 3 PLO1
	(b)	Determine the power supplied by the leftmost element in the circuit of following	Marks 4

	figure		PLO1
(c)	Following figure depicts the current-voltage characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.	Marks 3	PLO1


--	--	--	--

Q2	(a)	Refer to the circuits of following figures, and answer the following: 1. How many distinct nodes are contained in the circuit?	Marks 4
----	-----	---	------------

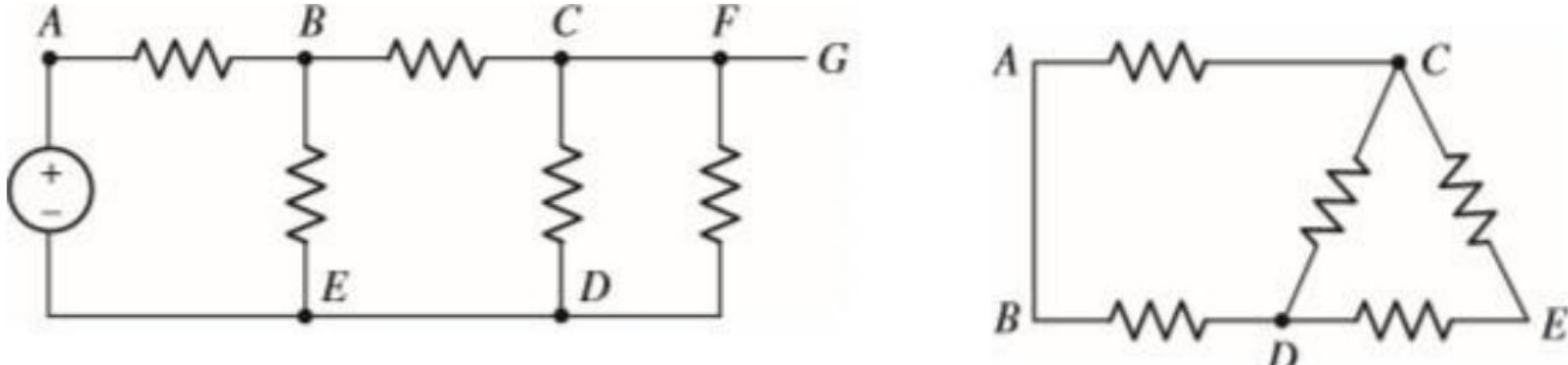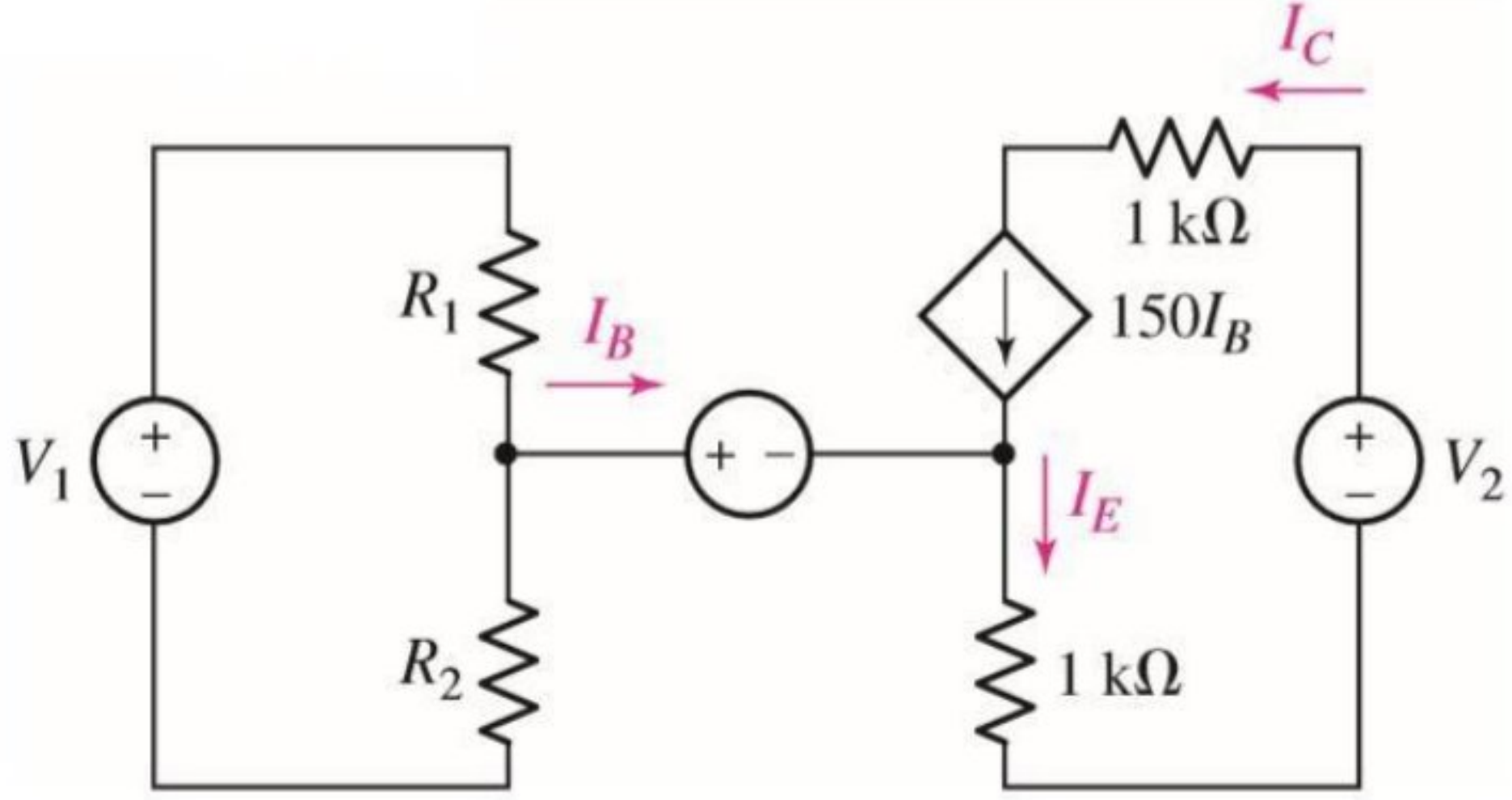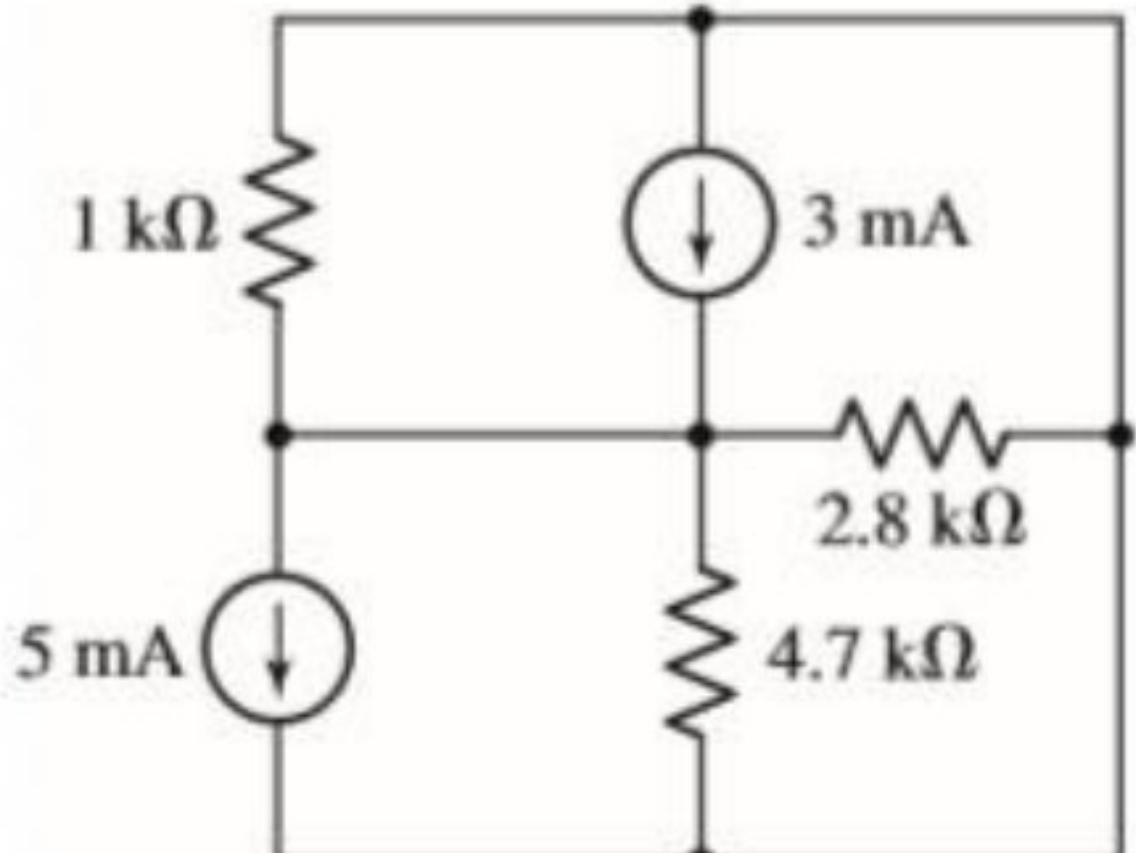	<p>2. How many elements are contained in the circuit?  3. How many branches does the circuit have?  4. Determine if each of the following represents a path, a loop, both, or neither:</p> <p>i. A to B  ii. B to D to C to E  iii. C to E to D to B to A to C  iv. C to D to B to A to C to E</p> 	PLO2
(b)	<p>For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region), <math>I_B</math> is measured to be <math>100 \mu\text{A}</math>. Determine <math>I_C</math> and <math>I_E</math></p>	Marks 6 PLO2
		
Q3	<p>(a) Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.</p> <p>a. Determine the power absorbed by each resistor.  b. Determine the power supplied by each current source.  c. Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).</p> 	Marks 5 PLO1
(b)	<p>Determine the power absorbed by the <math>15 \square</math> resistor in the circuit of following</p>	Marks 5

figure

PLO1

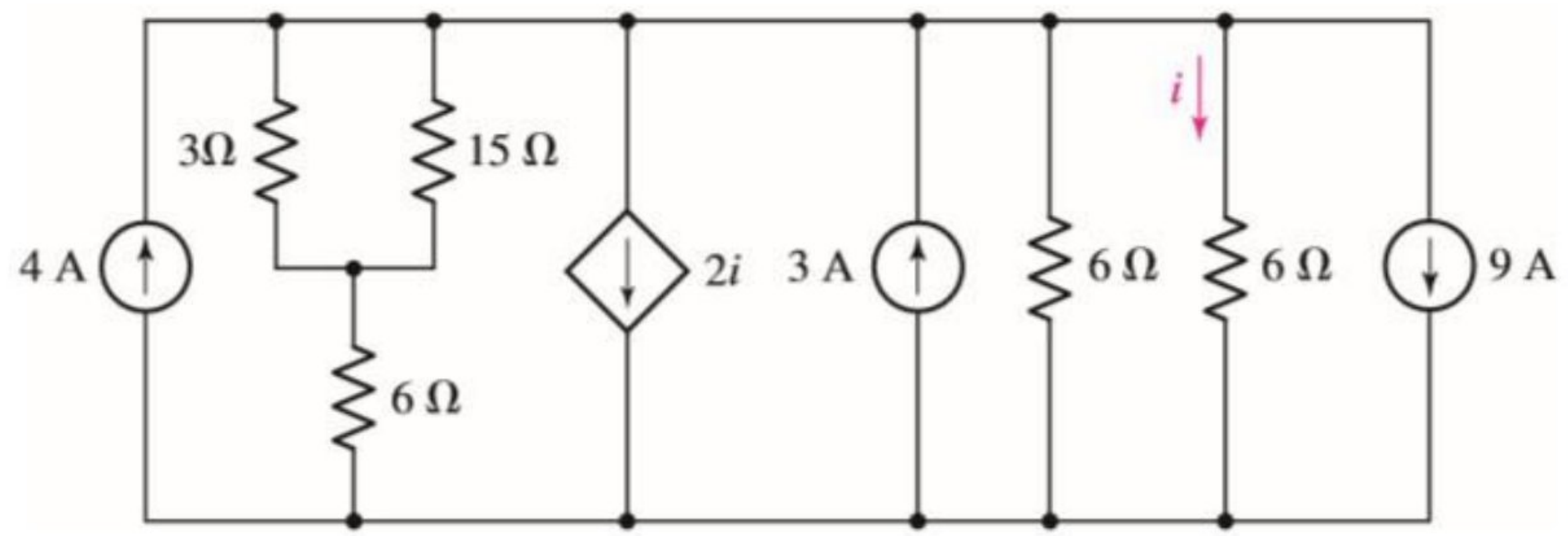

Date \_\_\_\_\_

①


ID #16318

Saheeb ul Hassan



Answer:

Q1 (a)

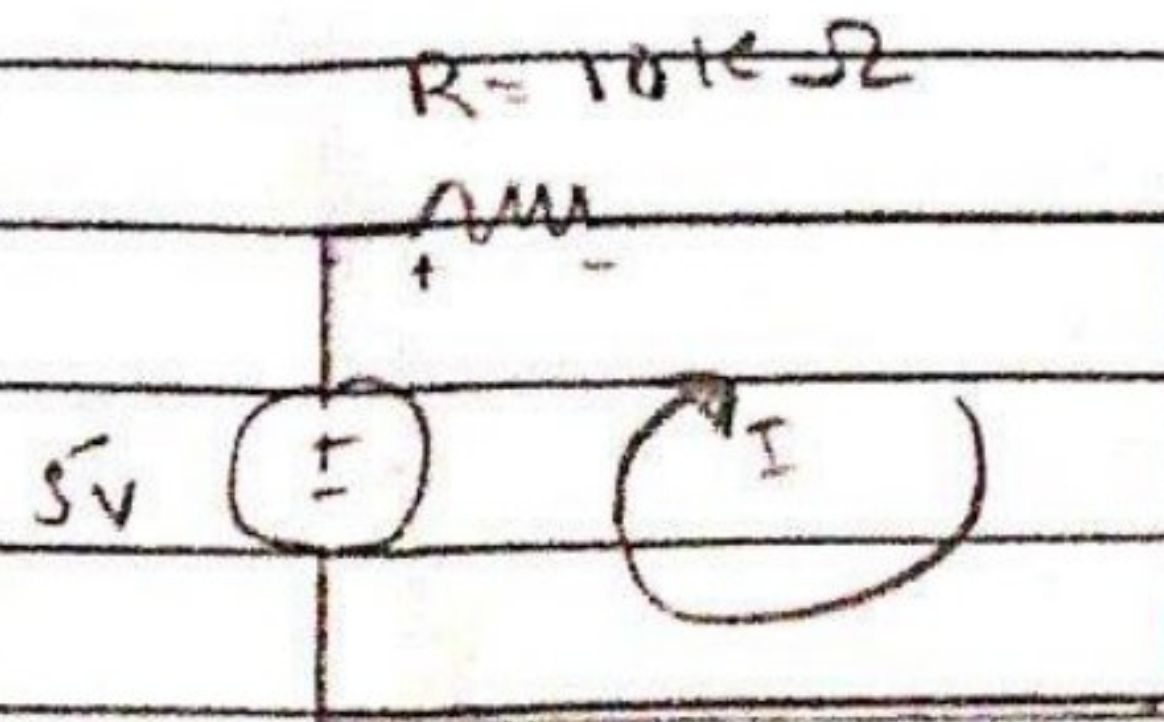

$$P = IV$$


$$I = \frac{5}{10} = \frac{1}{2} = 0.5 \text{ mA}$$

Both V & I Ad here to passive sign convention

$$P = IV$$

$$\Rightarrow (0.5)(5)$$

$$2.5 \text{ watt}$$

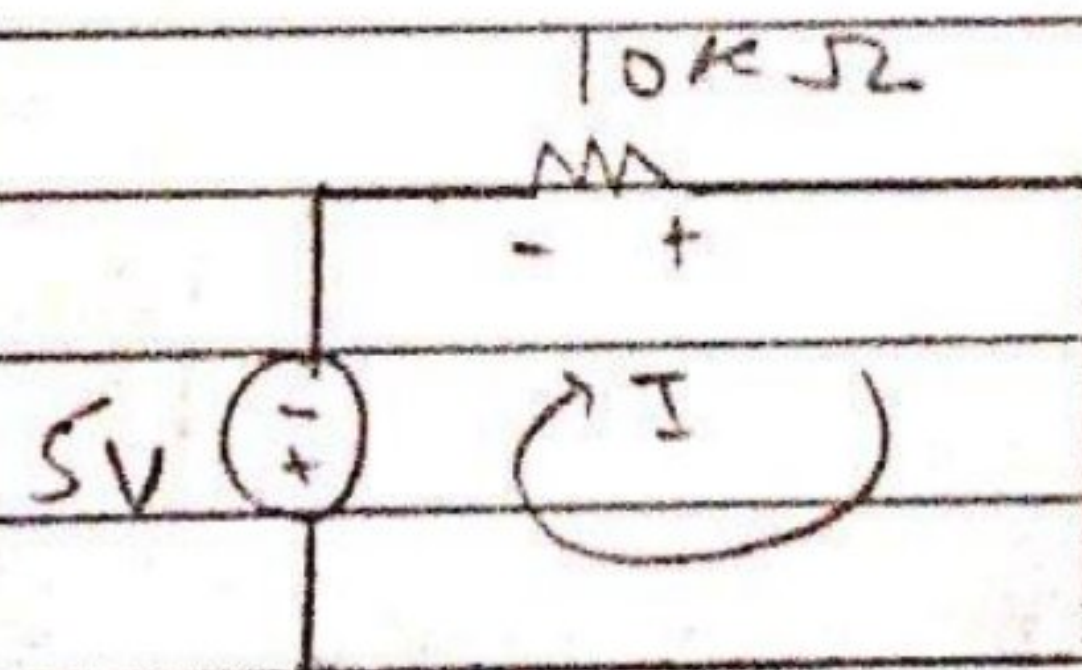

$$P = IV$$

$$I = \frac{-5}{10} = -0.5 \text{ mA}$$

V & I doesnot adhere to passive sign convention

The power  $P = (-I)(-V)$


absorbed by  $\uparrow = (-0.5)(-5) = -2.5 \text{ watt}$

Date \_\_\_\_\_

(2)


Q1  
(a)

Answer

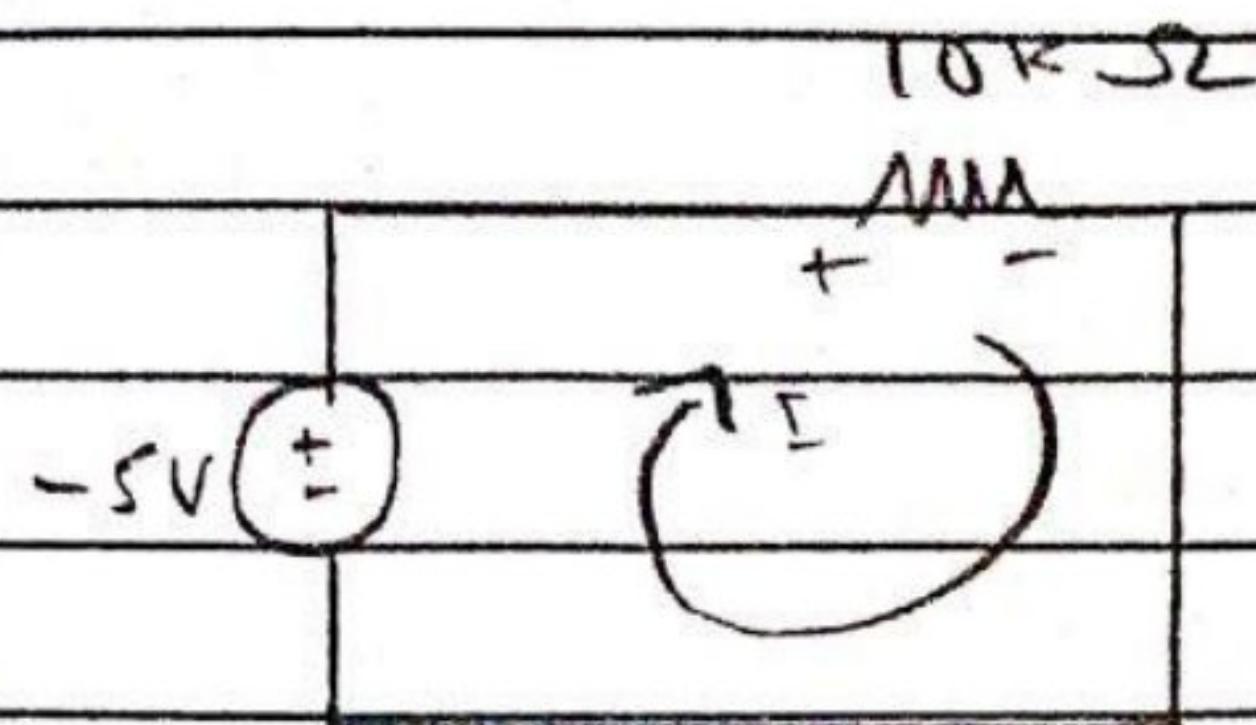

$$\begin{aligned} \text{Current} = I &= V/R \\ &= -5/10 = -0.5 \text{ mA} \end{aligned}$$
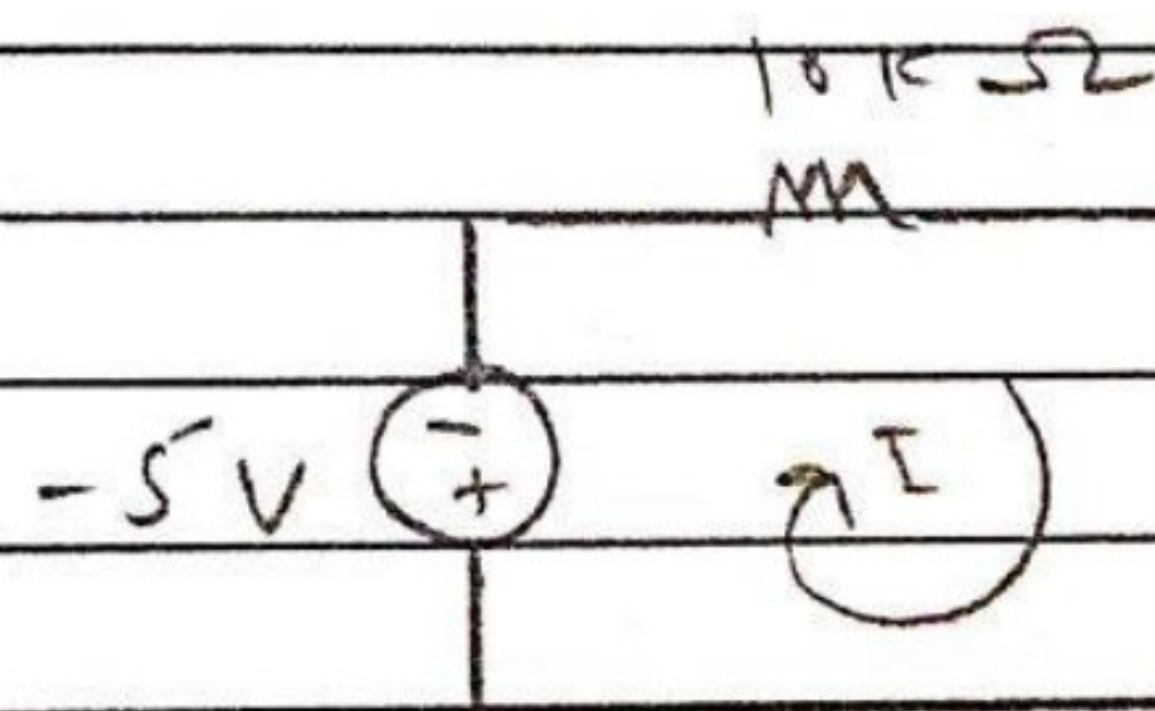
$$\begin{aligned} P &= (V)(I) \\ &= (-5)(-0.5) \\ &= 2.5 \text{ m watt} \quad \text{Power absorbed} \end{aligned}$$



$$\begin{aligned} \text{Current} = I &= V/R \\ &= -5/10 = -0.5 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{Power absorbed by Resistor} \\ P &= (I)(V) \\ &= (0.5)(5) \\ &= 2.5 \text{ m watt} \end{aligned}$$


Date \_\_\_\_\_

3



Answer:

Q1 (b)

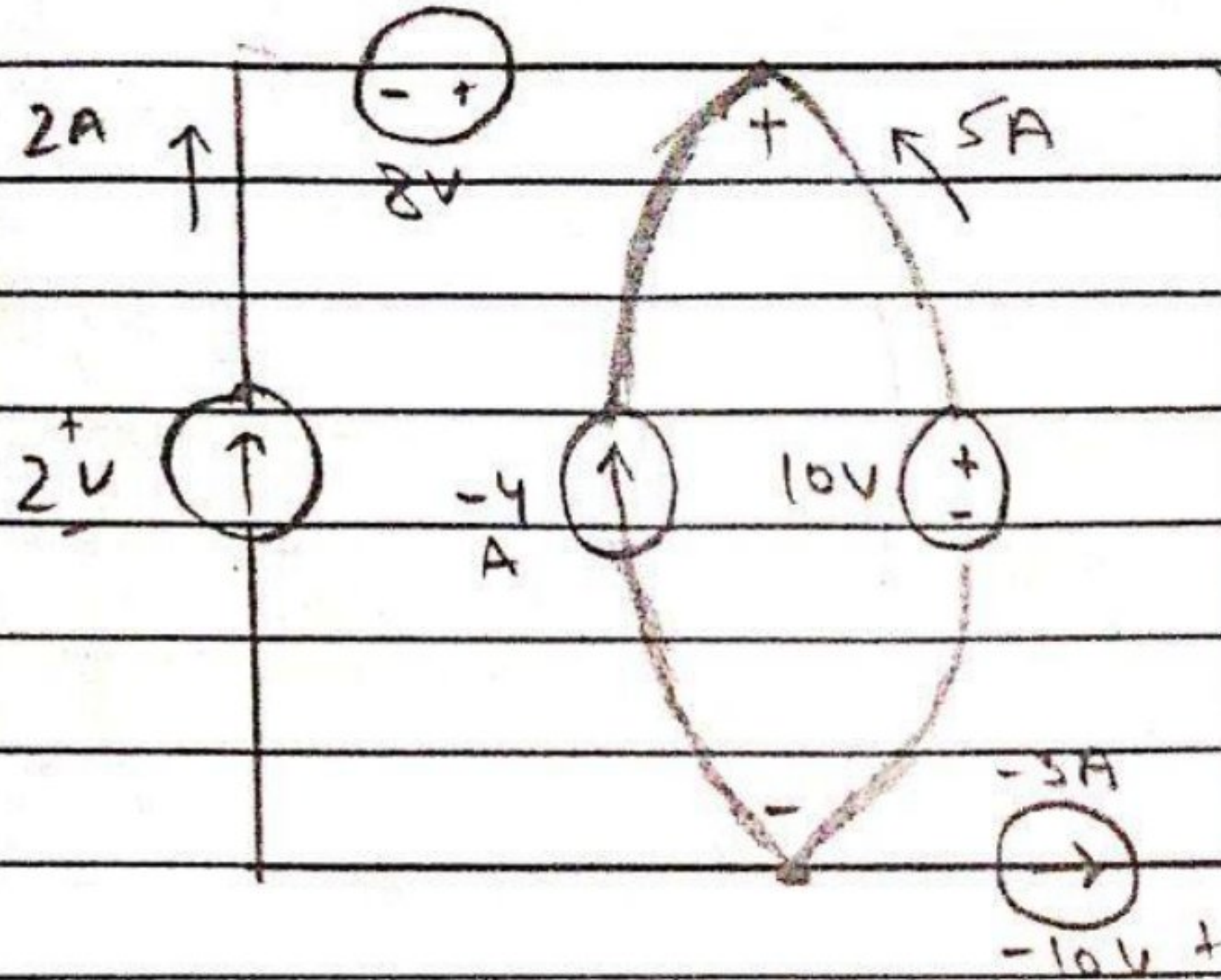

$$P = VI$$

$$= (2)(2)$$

$$= 4 \text{ watt Power is}$$

supplied to the circuit.

Date \_\_\_\_\_

(4)



Q1(c)

Linear Graph

Answer:-

(i)  $R = V/I$

$R = -5/0.5 \Rightarrow$  ~~100~~ 100 ohm's

(ii) As circuit is "0 Amp" and voltage is being increased the  $\downarrow$  Resist must be infinity ( $\infty$ )

(iii)  $V = IR$

$R = V/I$

$R = 0$



Date \_\_\_\_\_

(5)



Answers:

Q2 (a)

1) As we know that

Node :- Point between two or more than two element is known is node. So count the nodes.

There are 9 nodes in the circuit.

2) There are 5 resistors so the number of elements in circuit is 5

3) Branch which is a section between two nodes. So the number of branches in circuit is 5

4) (i) neither (ii) path only (iii) path and loop (iv) neither

Date \_\_\_\_\_

(6)

Answer :-

Q2 (b)

"KLC"

$$I_B + I_C = I_E$$

else

$$I_C = 150 \cdot I_B$$

$$I_C = 15 \text{ mA}$$

Now calculate  $I_E$  :-

$$I_E = 15 \cdot 10^{-3} + 100 \cdot 10^{-6}$$


$$I_E = 15.1 \text{ mA}$$

$$I_C = 15 \text{ mA}$$

$$I_E = 15.1 \text{ mA}$$

Answer :-

Q3 (a)

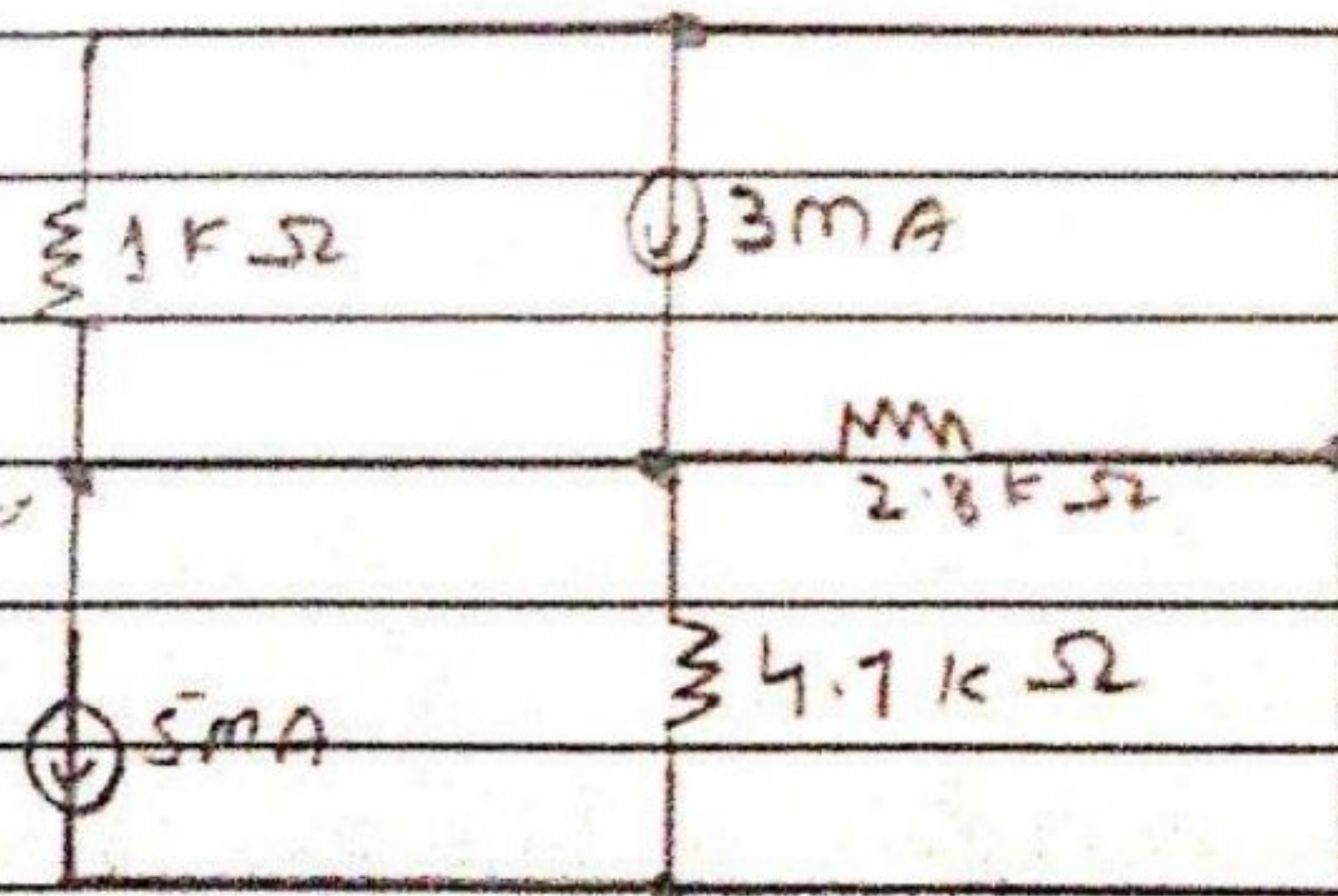

Finding  $P(2.8 \text{ k}\Omega)$ ,  $P(4.7 \text{ k}\Omega)$ ,  $P(1 \text{ k}\Omega)$   
 $P(5 \text{ mA})$ ,  $P(3 \text{ mA})$

Find  $v$  in a better force

Find  $v$  by combine similar element SM Notes

Date \_\_\_\_\_


(7)



Answer :-

Q3 (a)


Continue

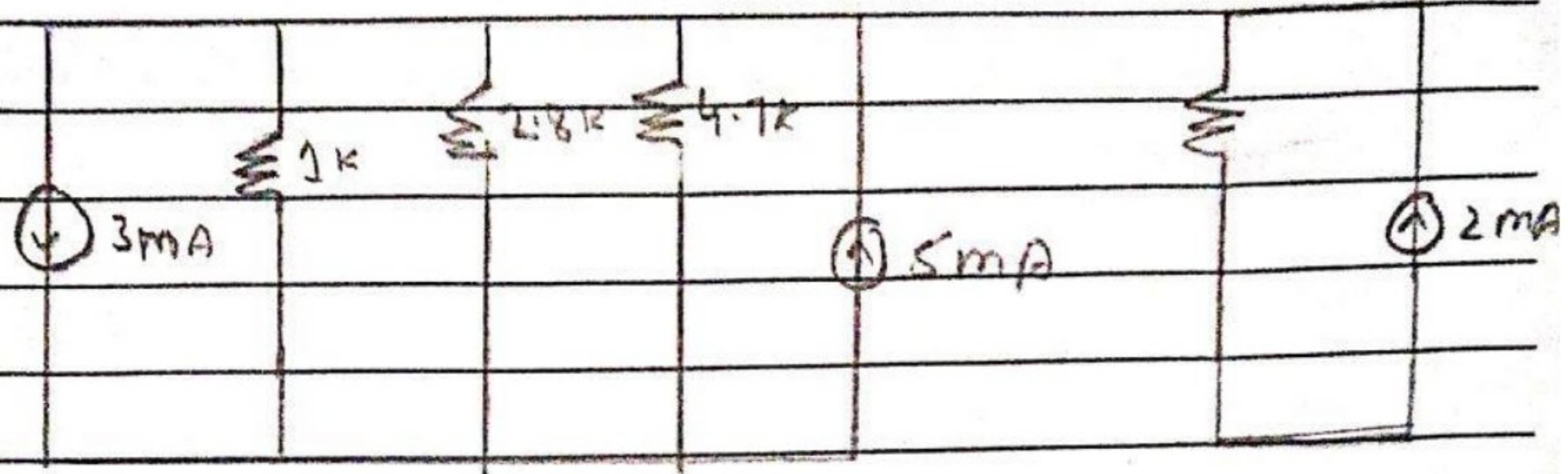

By using ohm's law

$$V = IR$$
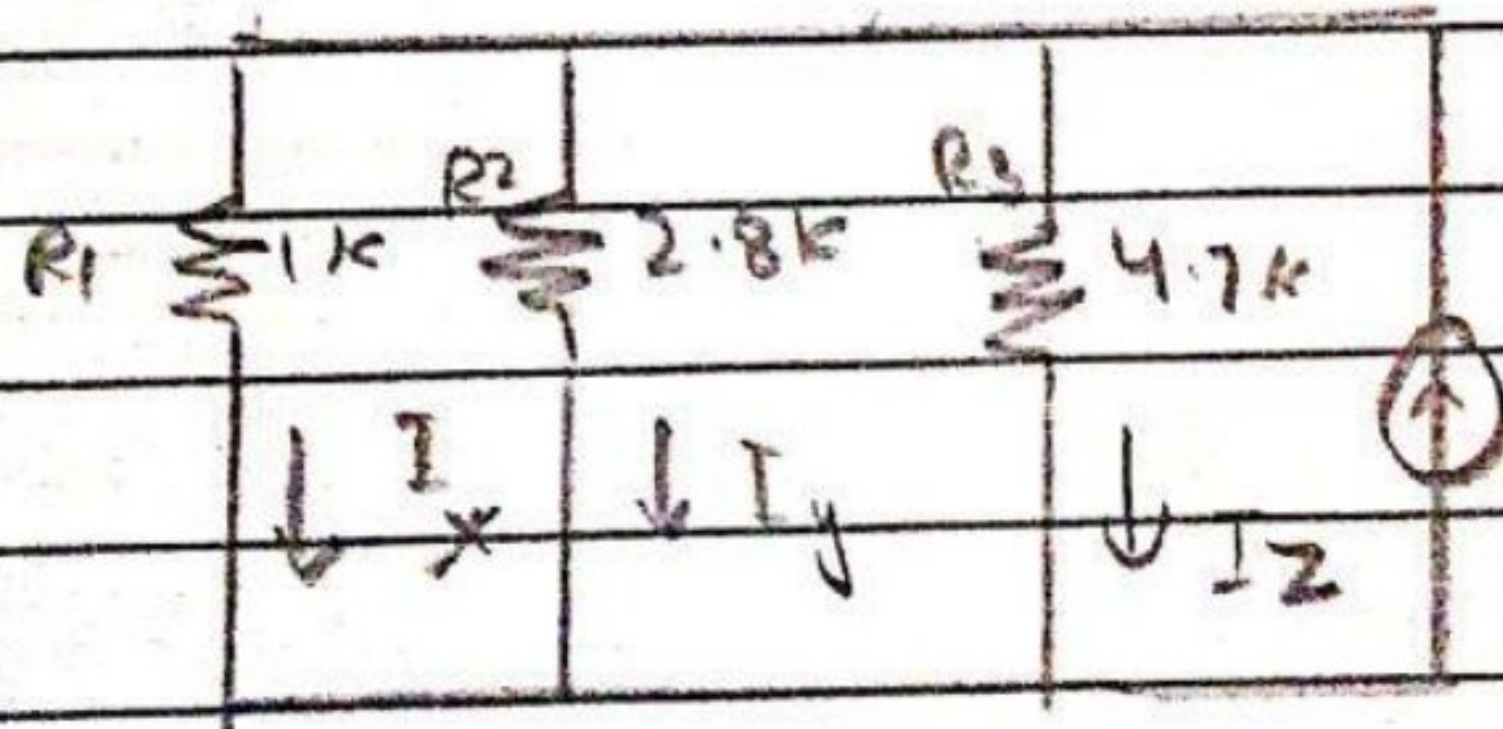
$$V = 2 \times 10^{-3} \times 637 = \boxed{1.274V}$$



$$V = IR$$

$$V = 2 \times 10^{-3} \times 637 =$$

$$I = V/R$$

$$I_x = V/R_1 \Rightarrow \frac{1.274V}{1000\Omega} = 1.274mA$$

$$I_y = V/R_2 = \frac{1.274V}{2800\Omega} \Rightarrow 0.00455$$

$$I_y = 0.455mA$$

Date \_\_\_\_\_

(8)



Answer

Q3 (a)

Continue

$$I_z = \frac{V}{R_3} = \frac{1.274V}{4700} = 0.000271$$

$$I_z = 0.271 \text{ mA}$$

$$P = VI$$

$$P(2.8k) = (1.274)(0.271) = 0.346 \text{ mWatts}$$

$$P(4.7k) = (1.274)(0.271) = 0.346 \text{ mWatts}$$

$$P(1k) = (1.274)(1.274) = 1.623 \text{ mWatts}$$

$$P(5mA) = (1.274)(-5) = -6.37 \text{ mWatts}$$

$$P(3mA) = (1.274)(3) = 3.822 \text{ mWatts}$$

~ ~ ~ ~ ~

Answer

Q3 b

'Calculation'

$$i_{eq} = 4 - 2i + 3 - 9 = -2 - 2i$$

$$R_{eq} = (6+3 || 15) || 6 || 6$$

$$R_{eq} = 8.5 || 3 = 2.2174 \Omega$$

'Calculation of voltage'

$$V = i_{eq} \cdot R_{eq}$$

Date \_\_\_\_\_

(9)



Answer  
Q3 b  
Continue

$$V = i_{eq} \cdot R_{eq}$$

$$V = (-2 - 2i) \cdot 2.2174 \text{ k}\Omega$$

From diagram  
we know that

$$V = 6i$$

$$6i = (-2 - 2i) \cdot 2.2174$$

$$10.4318 \cdot i = -4.4318$$

$$i = -0.425 \text{ A}$$

$$V = -2.55 \text{ V}$$

Now

$$P = \frac{V^2}{R}$$

$$P_{15\Omega} = \frac{V_{15\Omega}^2}{15\Omega}$$

$$V_{15\Omega} = \frac{6}{6+25} \cdot V$$

$$V_{15\Omega} = 1.8 \text{ V}$$

and

$$P_{15\Omega} = \frac{1.8^2}{15\Omega}$$

$$P_{15\Omega} = 0.216 \text{ W}$$