

Q: Solve following question
from text book

(i) Chapter 4: 2, 12, 13, 19, 29,
32, 35, 46, 47

(ii) Chapter 5: 10, 11, 13, 25,
27.

Chapter 4

(2) Evaluate the following
determinants.

$$(a) \begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}, (b) \begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

Solution (a)

The first determinant is
simply evaluated as

$$\begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix} = (2 \times 3) - (1 \times (-4))$$

$$= 6 - (-4)$$

$$= 6 + 4$$

$$\boxed{\det(A) = 10}$$

Apply KCL to node v_3 gives


$$5 - 2 = \frac{v_3 - v_2}{1050} + \frac{v_3}{200} \quad (4)$$

Solving the four equations

(1), (2), (3) and (4), Thus

$$v_p = 171.639 \text{ V}$$

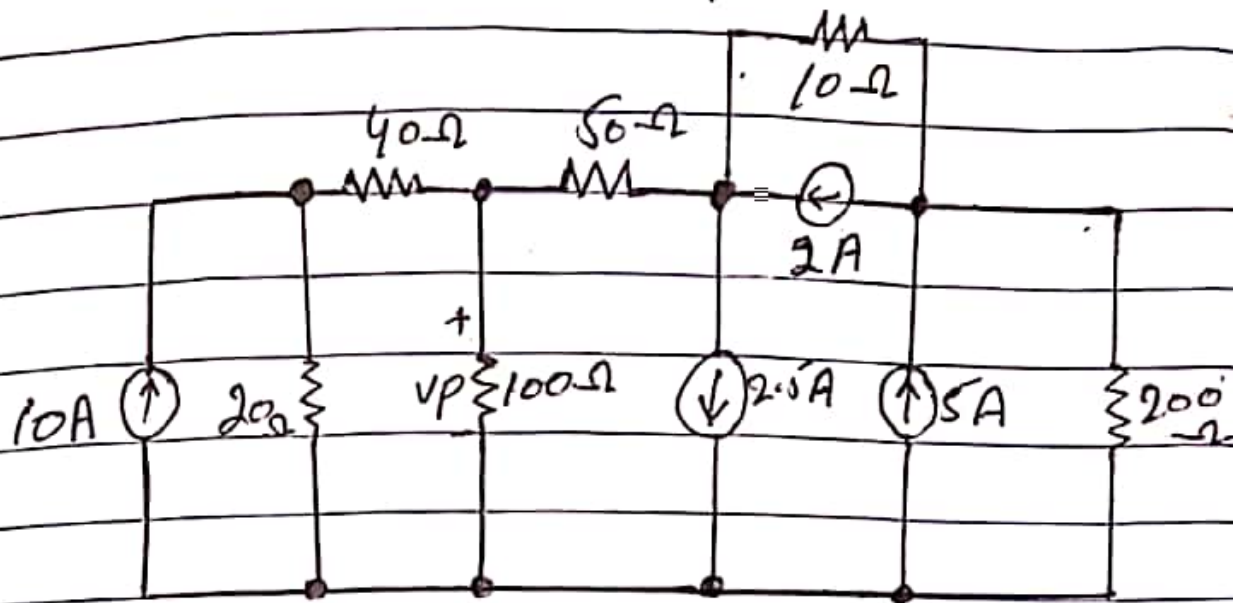(12) use nodal analysis to find v_p in the circuit.



Solution:

we redraw the given circuit and specify the nodal voltage as shown below.

Apply KCL to node v_1 gives

$$10 = \frac{v_1}{20} + \frac{v_1 - v_p}{40} \quad \text{--- (1)}$$


Apply KCL to node v_p gives

$$0 = \frac{v_p - v_1}{40} + \frac{v_p}{100} + \frac{v_p - v_2}{50} \quad \text{--- (2)}$$

Apply KCL to node v_2 gives

$$2 - 2.5 = \frac{v_2 - v_p}{50} + \frac{v_2 - v_3}{10} \quad \text{--- (3)}$$

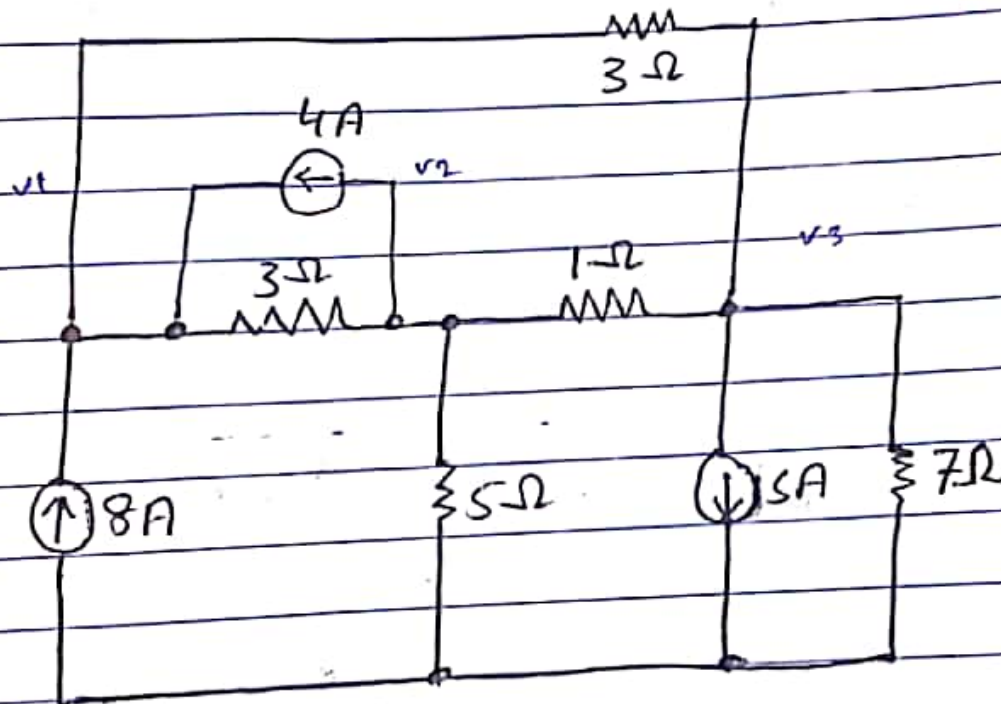(13): Using the bottom node as reference, determine the voltage across the 5Ω resistor in the circuit of Fig. 4.39, and calculate the power dissipated by the 7Ω resistor.



Solution:

Start with labeling the nodes of the circuit.

Let the voltage across the $8A$ current source to be v_1 , while v_2 denote the voltage across the 5Ω resistor. Finally, let the voltage across the $5A$ current source is labeled v_3 .

For the node v_1 .

$$-8 - 4 + \frac{v_1 - v_2}{3} + \frac{v_1 - v_3}{3} = 0$$

$$\left(\frac{1}{3} + \frac{1}{3}\right)v_1 - \left(\frac{1}{3}\right)v_2 - \left(\frac{1}{3}\right)v_3 = 12$$

$$2v_1 - v_2 - v_3 = 36 \quad \text{--- (1)}$$

For the node v_2

$$4 + \frac{v_2 - v_1}{3} + \frac{v_2}{5} + \frac{v_2 - v_3}{1} = 0$$

$$-\left(\frac{1}{3}\right)v_1 + \left(\frac{1}{3} + \frac{1}{3}\right)v_2 - v_3 = -4$$

$$-5v_1 + 23v_2 - 15v_3 = -60 \quad \text{--- (2)}$$

For node v_3

$$5 + \frac{v_3 - v_2}{1} + \frac{v_3 - v_1}{3} + \frac{v_3}{7} = 0$$

$$-\left(\frac{1}{3}\right)v_1 - v_2 + \left(1 + \frac{1}{3} + \frac{1}{7}\right)v_3 = -5$$

$$-7v_1 - 21v_2 + 31v_3 = -105 \quad \text{--- (3)}$$

Solves the three equations

(1), (2) and (3)

$$V_1 = 26.733 \text{ V}$$

$$V_2 = 8.833 \text{ V}$$

$$V_3 = 8.633 \text{ V}$$

Thus, $V_{5\Omega} = V_2$

$$V_{5\Omega} = 8.833 \text{ V}$$

Since the voltage across the 7Ω resistor is V_3 , therefore


$$P_{7\Omega} = \frac{V_3^2}{7}$$

$$= \frac{8.633^2}{7}$$

$$= \frac{74.528689}{7}$$

$$P_{7\Omega} = 10.646 \text{ W}$$

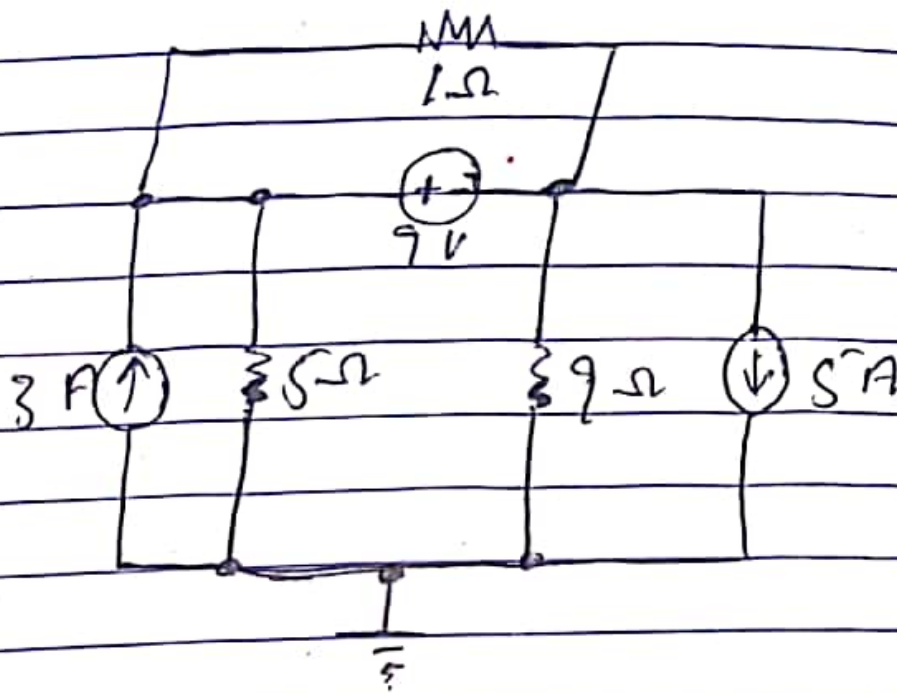19) determine a numerical values for the voltage labeled v_1



Solution: consider v_1 and v_2 as a supernode

Apply KCL on supernode

$$\frac{v_1 - v_2}{1} + \frac{v_1}{5} + \frac{v_2 - v_1}{1} + \frac{v_2}{9} = 3 - 5$$

$$\frac{4.5v_1 - 4.5v_2 + 9v_1 + 4.5v_2 - 4.5v_1 + 9v_2}{4.5} = -2$$

$$9v_1 + 9v_2 = 135 \quad \text{--- (1)}$$

$$\text{So } v_1 - v_2 = 9 \quad \text{--- (2)}$$

Combining eq (1) and (2)

$$\begin{aligned} 9v_1 + 9v_2 &= 135 \\ 9v_1 - 9v_2 &= 81 \\ \hline 18v_1 &= 216 \end{aligned}$$

$$v_1 = \frac{216}{18}$$

$$v_1 = 12 \text{ V}$$


putting in eq (2)

$$v_2 = v_1 - 9$$

$$v_2 = 12 - 9$$


$$v_2 = 3$$

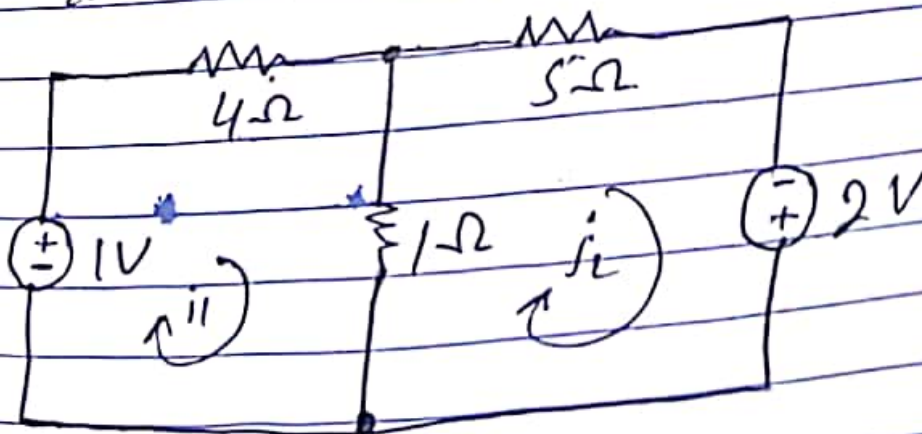29: Determine the current flowing out of the positive terminal of each voltage source in the circuit.



Result:
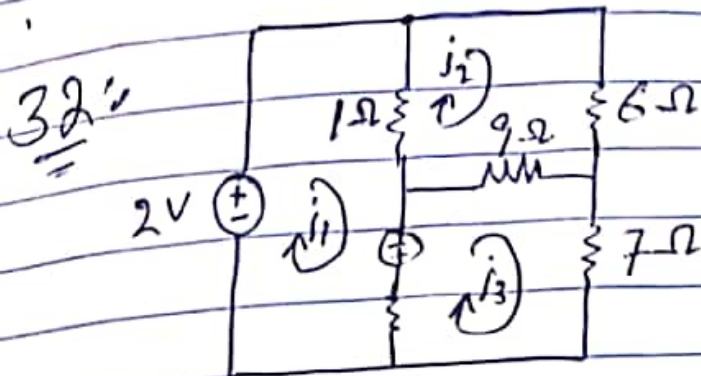
$$i_1 = 0.275 \text{ A}$$
$$i_2 = 0.379 \text{ A}$$



Solution:

write the first mesh equation,

$$-2 + 1(i_1 - i_2) - 3 + 5(i_1 - i_3) = 0$$

$$6i_1 - i_2 - 5i_3 = 5 \quad \text{--- (1)}$$

write the 2nd mesh equation

$$1(i_2 - i_1) + 6i_2 + 9(i_2 - i_3) = 0$$

$$-i_1 + 16i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

write 3rd mesh equation


~~$5(i_3 - i_1) + 3 + 9(i_3 - i_2) + 7i_3 = 0$~~

$$5(i_3 - i_1) + 3 + 9(i_3 - i_2) + 7i_3 = 0$$

Result:

$$i_1 = 0.275 \text{ A}$$

$$i_2 = 0.379 \text{ A}$$

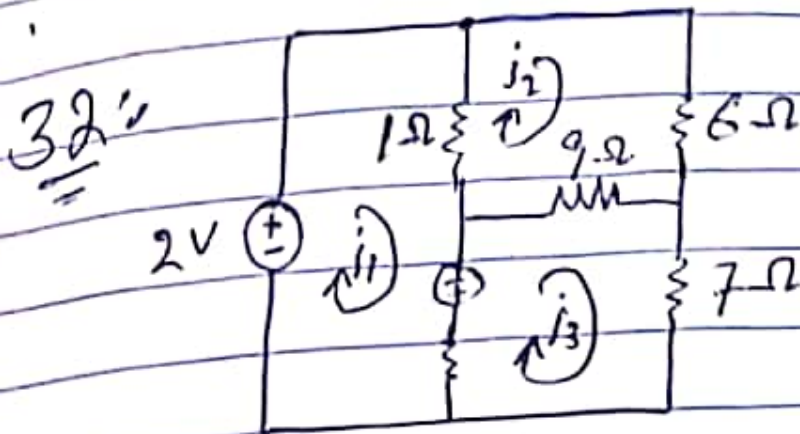

Solution:

write the first mesh equation,

$$-2 + 1(i_1 - i_2) - 3 + 5(i_1 - i_3) = 0$$

$$6i_1 - i_2 - 5i_3 = 5 \quad \text{--- (1)}$$

write the 2nd mesh equation

$$1(i_2 - i_1) + 6i_2 + 9(i_2 - i_3) = 0$$

$$-i_1 + 16i_2 - 9i_3 = 0 \quad \text{--- (2)}$$

write 3rd mesh equation

$$-5i_1 - 9i_2 + 2i_3 = -3 \quad (3)$$


Solves the three equations (1), (2) and (3). Thus,

$$i_1 = 989.205 \text{ mA}$$

$$i_2 = 150.147 \text{ mA}$$

$$i_3 = 157.017 \text{ mA}$$

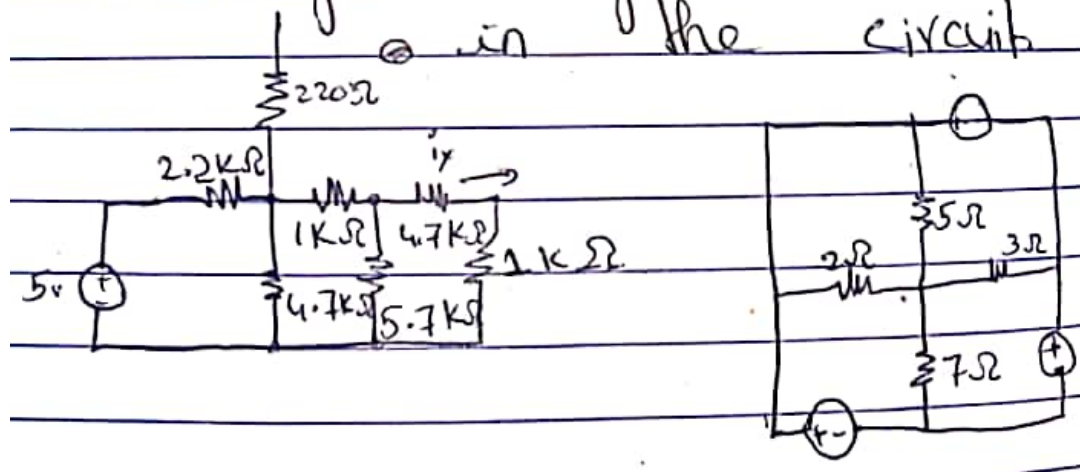35. Choose nonzero value of the three voltage source of figure so that no current flows through any resistor in the circuit



Solution: Let's name the sources V_1 , V_2 and V_3 from top to bottom.

and the current i_1, i_2, i_3
and i_4

For the currents in resistors
to be equal to
zero, we need.

$$i_1 - i_2 = 0$$

$$i_3 - i_4 = 0$$

$$i_1 - i_3 = 0$$

$$i_2 - i_4 = 0$$

Now we'll apply KVL
on each of the
your loops.


$$2 \cdot (i_1 - i_3) + 5 \cdot (i_1 - i_2) = 0$$

$$3 \cdot (i_2 - i_4) + 5 \cdot (i_2 - i_1) = -V_2$$

$$7 \cdot (i_3 - i_4) + 2 \cdot (i_3 - i_2) = V_1$$

$$3 \cdot (i_4 - i_2) + 7 \cdot (i_4 - i_3) = V_3$$

$$V_1 = V_2 = V_3 = 0$$

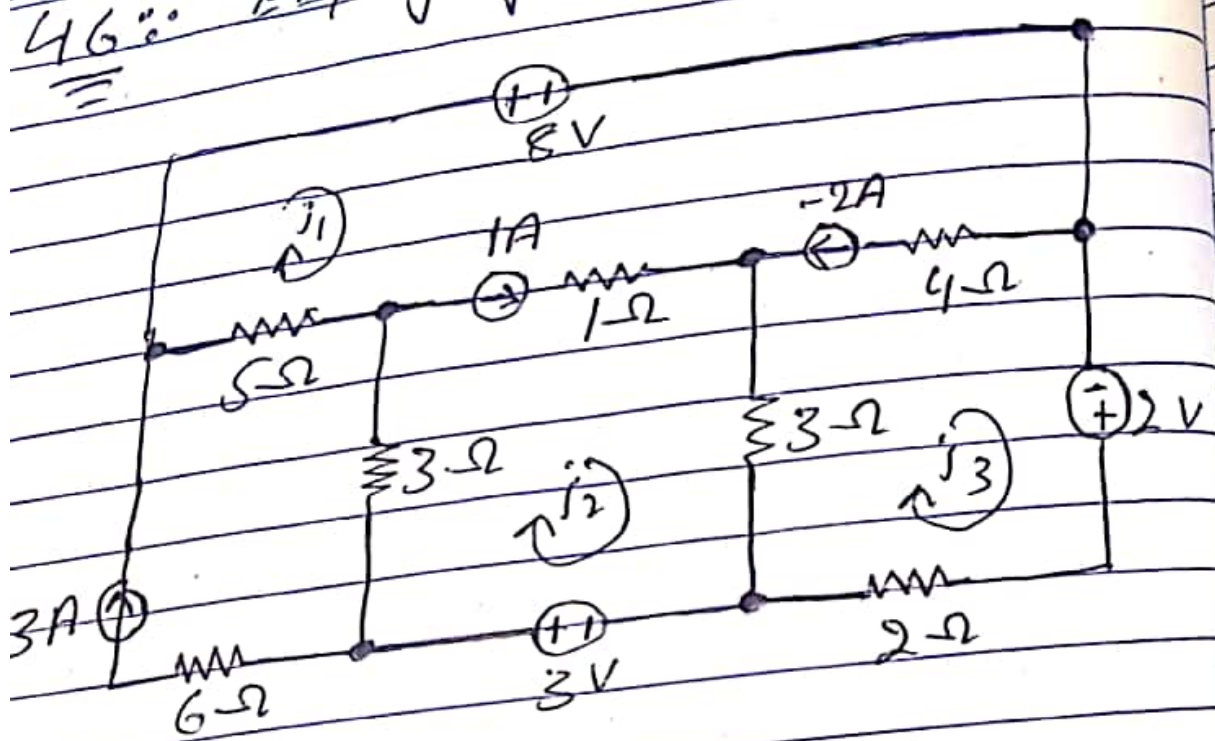

Solution: We call the unlabeled mesh current i_4 , we can immediately see that:

$$i_4 = 3A$$

mesh analysis of i_1, i_2, i_3 supermesh gives us:

$$8 + 6(i_1 - 3) + 3(i_2 - 3) = 0$$

$$-3 + 2i_3 - 2 = 0$$

By apply KVL on the lower left supermode

and the upper right node
we get:

$$i_2 - i_1 - 1 = 0$$

$$2 + i_1 - i_3 = 0$$

After solving these three
equations we get


$$i_1 = 1.4 \text{ A}$$

$$i_2 = 2.4 \text{ A}$$

$$i_3 = 3.4 \text{ A}$$

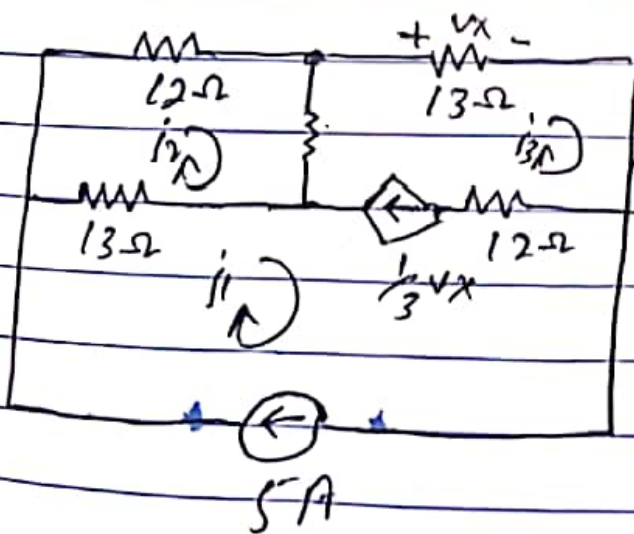47: Figure

Through careful application
of the supermesh technique,
obtain values for all three
mesh currents as labeled.



Solution:

We are given in the
problem that $I_1 = 5 \text{ A}$

The equation for the second mesh can be write as:

$$I_3 - I_1 = \frac{V_x}{3}$$

$$3I_3 - 5(3) = V_x = 13I_3$$

$$3I_3 - 15 = 13I_3$$

$$-15 = 10I_3$$

$$I_3 = -1.5 \text{ A}$$

The equation of the 3rd mesh:

$$-13I_1 + 36I_2 - 11I_3 = 0$$

$$-13(5) + 36I_2 - 11(-1.5) = 0$$

$$-65 + 36I_2 + 16.5 = 0$$

$$36I_2 = 48.5$$

$$I_2 = 1.3 \text{ A}$$


Result: $I_1 = 5 \text{ A}$

$$I_2 = 1.3 \text{ A}$$

$$I_3 = 1.5 \text{ A}$$

Chapter No 5

(10) Figure

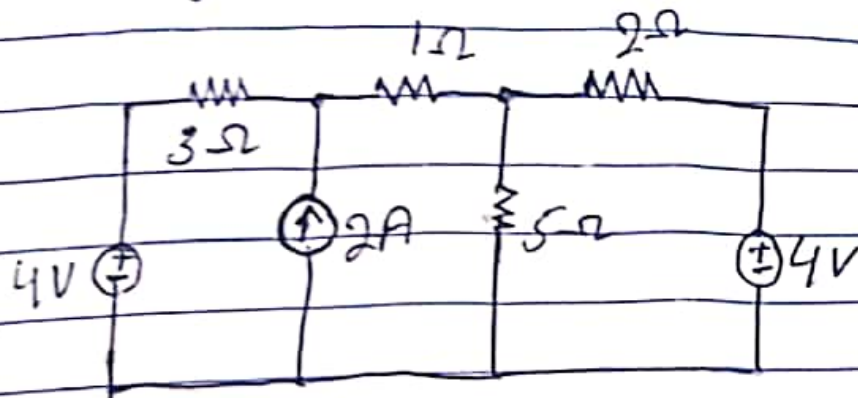

Solution:

Since there are three sources, as

$$V_x = V_1 + V_2 + V_3$$

where V_1 , V_2 and V_3 are the contribution due to the left 4V voltage source, 2A current source

and the right 4 voltage source, respectively

To obtain V_1 we set the 2A and the right 4V source to zero as shown below
Apply mesh analysis to the

Two meshes 1 and 2, we obtain the following matrix equation.


$$\begin{bmatrix} 3+1+5 & -5 \\ -5 & 5+2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix}$$

we find

$$i_1 = \frac{14}{19} \text{ A}$$

For $1\text{-}\Omega$ resistor, ohm's law gives
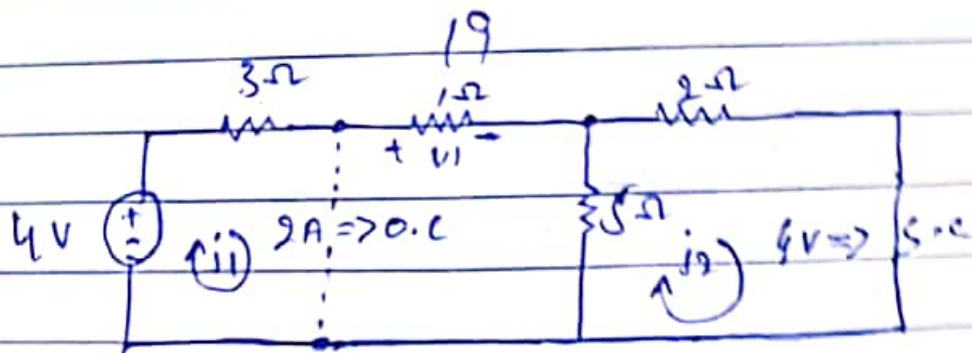
$$v_1 = 1 \cdot i_1 = \frac{14}{19} \text{ V} \approx 736.84 \text{ mV}$$



To obtain v_2 we set the two 4V source to zero as shown below.

Apply nodal analysis to the two nodes v_a and v_b we obtain the following matrix equation

$$\begin{bmatrix} \frac{1}{3} + 1 & -1 \\ -1 & 1 + \frac{1}{3} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$


matrix equation we find:

$$v_a = \frac{51}{19} \text{ V and } v_b = \frac{21}{19} \text{ V}$$

By inspection, it is clear that

$$v_2 = v_a - v_b = \frac{51}{19} - \frac{30}{19} = \frac{21}{19}$$

$$v_2 = 1.105 \text{ V}$$

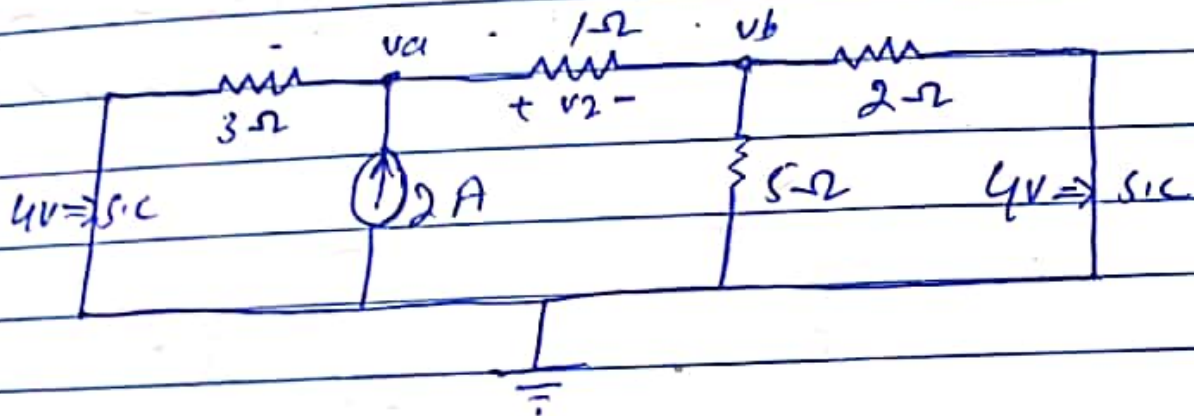

To obtain v_3 we set the 2A and the left 4V source to zero as shown below

Apply mesh analysis to the two meshes 1 and 2 we obtain the following matrix equation.

$$\begin{bmatrix} 3+1+5 & -5 \\ -5 & 5+2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -4 \end{bmatrix}$$

The matrix equation we find:

$$i_1 = -\frac{10}{19} \text{ A}$$

For the $1\text{-}\Omega$ resistor, ohm's law gives

$$V_3 = I \cdot R = \frac{10}{19} \text{ V}$$


$$V_3 = -526.32 \text{ mV}$$

Therefore

$$V_x = V_1 + V_2 + V_3$$

$$V_x = 736.84 \text{ mV} + 1.105 \text{ V} - 526.32 \text{ mV}$$

$$V_x = 1.316 \text{ V}$$

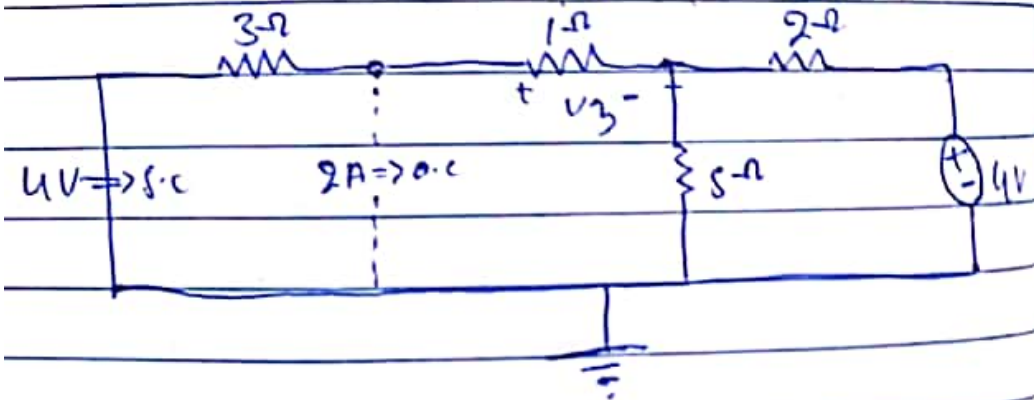

It is required to evaluate the values of the current source that results in reducing the V_x values by 10%.

Let the new values of V_x is V_x' the current source values affects only its contribution which is V_2 . Let the new values

v_2 is v_2 . Thus

$$v'_x = 0.9 \cdot v_x = 0.9 \cdot 1.316 \text{ V}$$

$$v'_x = 1.1844 \text{ V}$$

and

$$v'_2 = v'_x - (v_1 + v_3) = 1.1844 \text{ V} - (736.84 \text{ mV} - 526.32 \text{ mV}) = 973.88 \text{ mV}$$

Apply nodal analysis to the two nodes v_a and v_b in the circuit shown below gives.

$$i_{cs} = \left(1 + \frac{1}{3}\right) v_a - v_b \quad \text{--- (1)}$$

$$0 = -v_a + \left(1 + \frac{1}{5} + \frac{1}{2}\right) v_b \quad \text{--- (2)}$$


we have

$$v_a - v_b = v'_2 = 973.88 \text{ mV} \quad \text{--- (3)}$$

Solving the three equations

(1), (2) and (3) we


$$i_{cs} = 1.7623 \text{ A}$$

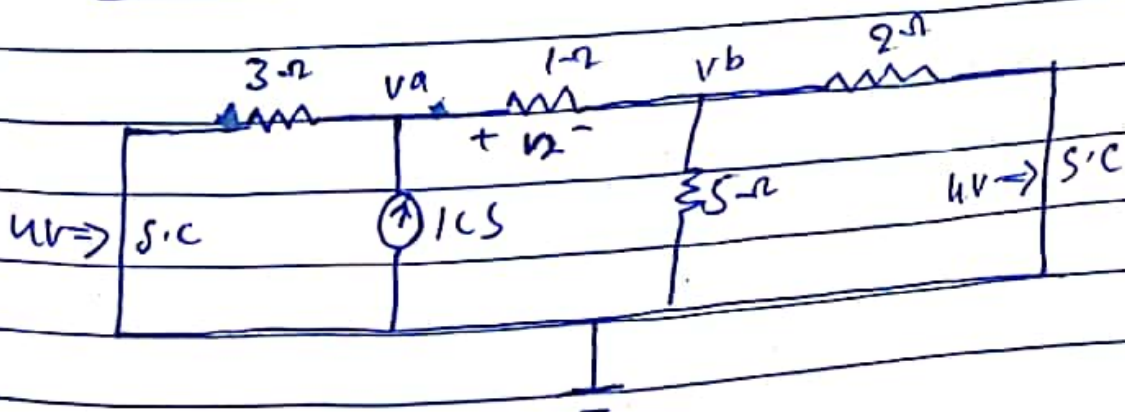

we verify our result in part
 (a) using Pspice as shown below
 we obtain.

$$V_x = 6.053 - 4.737 = 1.316V$$

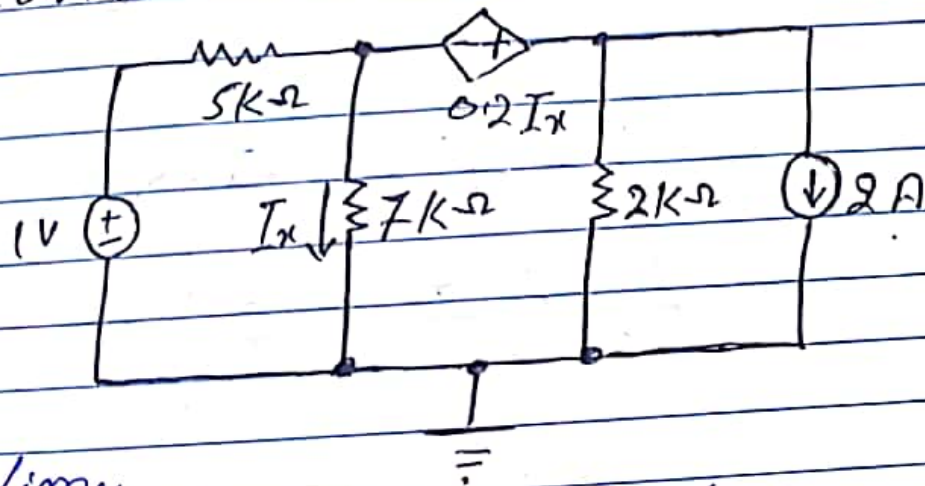(ii) Employ superposition principles
 to obtain a value for the
 current I_x as labeled.



Solution:

Since there are two independent sources, let

where I_{x1} and I_{x2} are the contributions due to the 1V voltage source and 2A current source, respectively.

To obtain I_{x1} , we set the 2A current source to zero (replacing it with an open circuit) as shown below.

Apply KCL to the supernode
 $\sum I = 0$ gives

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{v_2}{2000} = 0$$

But $v_2 = v_1 + 0.2 I_{x1}$; hence

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{v_1 + 0.2 I_{x1}}{2000} = 0$$


But $v_1 = 7000 I_{x1}$; hence,

$$\frac{7000 I_{x1} - 1}{5000} + \frac{7000 I_{x1}}{7000}$$

$$+ \frac{7000 I_{x1} + 0.2 I_{x1}}{2000} = 0$$

Then

$$I_{x1} = 33.9 \mu A$$

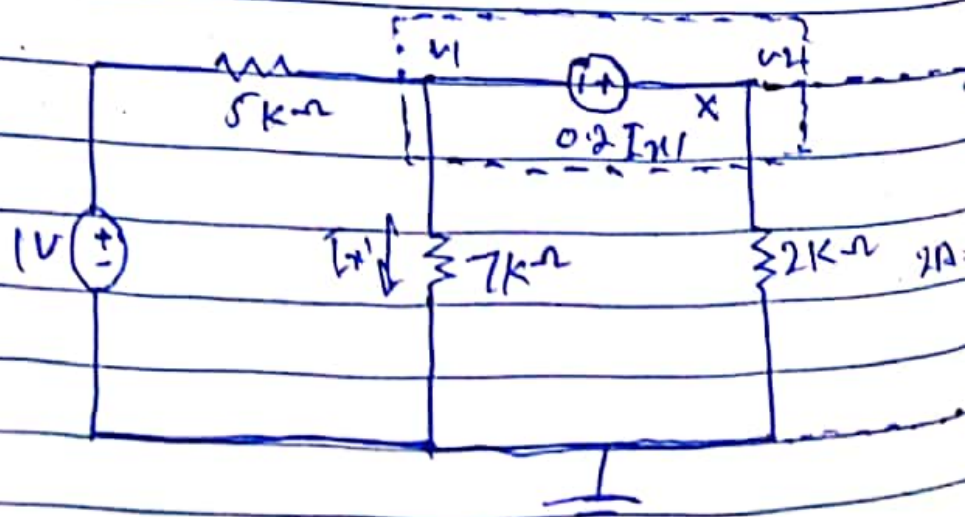

Apply KCL to the supernode
X gives

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{v_2}{2000} = 0$$

But $v_2 = v_1 + 0.2 I_{x1}$; here

$$\frac{v_1 - 1}{5000} + \frac{v_1}{7000} + \frac{v_1 + 0.2 I_{x1}}{2000} = 0$$


But $v_1 = 7000 I_{x1}$; hence,

$$\frac{7000 I_{x1} - 1}{5000} + \frac{7000 I_{x1}}{7000}$$

$$+ \frac{7000 I_{x1} + 0.2 I_{x1}}{2000} = 0$$

Then

$$I_{x1} = 33.9 \mu A$$

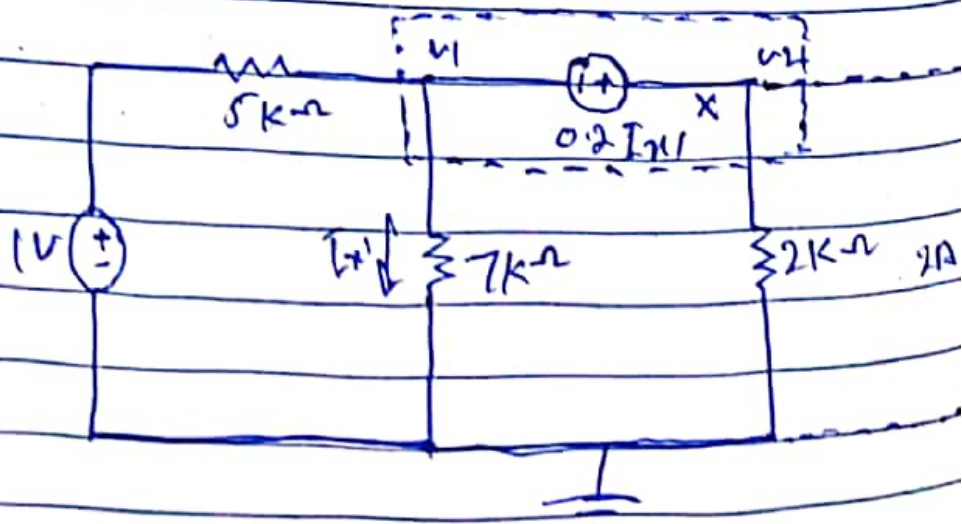

To obtain I_{x2} we set the 1V voltage source to zero (replacing it with a short circuit) as shown below.

Apply KCL to the supernode y given

$$\frac{V_1}{5000} + \frac{V_1}{7000} + \frac{V_2}{2000} = -2$$

But $V_1 = 7000 I_{x2}$; hence


$$\frac{7000 I_{x2}}{5000} + \frac{7000 I_{x2}}{7000} + \frac{7000 I_{x2} + 0.2 I_{x2}}{2000} = -2$$

Thus

$$I_{x2} = -338.98 \text{ mA}$$

Thus for e ; $I_x = I_{x1} + I_{x2}$
 $= 33.9 \mu\text{A} + (-338.98 \text{ mA})$



$$I_x = -338.95 \text{ mA}$$

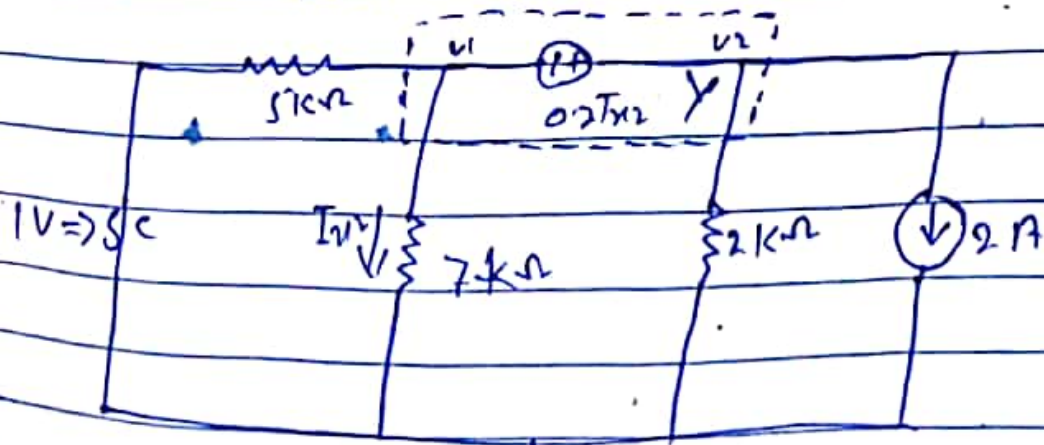

Result:

$$I_x = -338.95 \text{ mA}$$

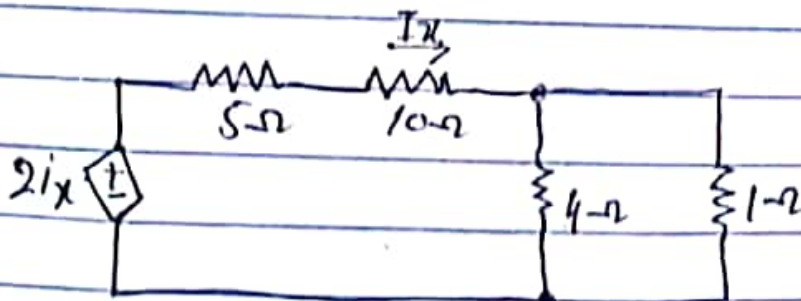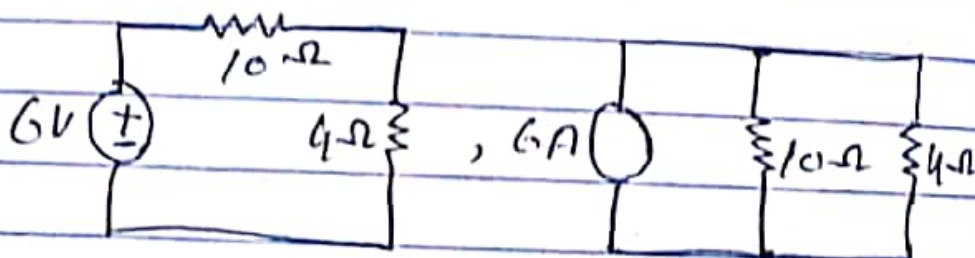3: perform an appropriate source transformation on each of the circuit depicted in 5.58, taking care to retain the $4\text{-}\Omega$ resistor in each final circuit.



Solution:


To get the values of the new source we use:

$$I = 4/R$$

$$I = 6/10$$

$$I = 0.6 \text{ A}$$

And we can draw the circuit as:

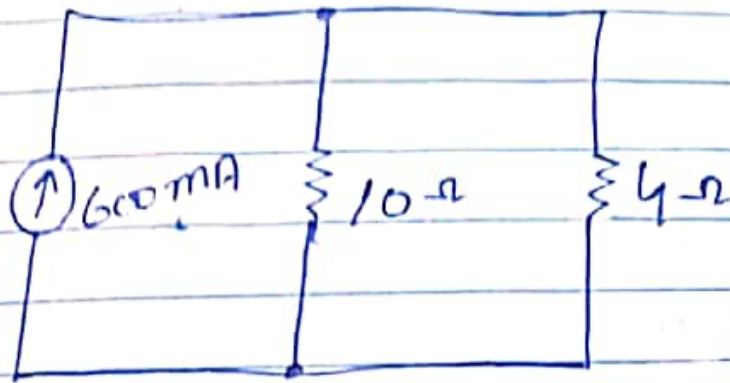


The new voltage source will have the value of:

$$V = 10 \times 6$$

$$V = 60V$$

And we draw it as

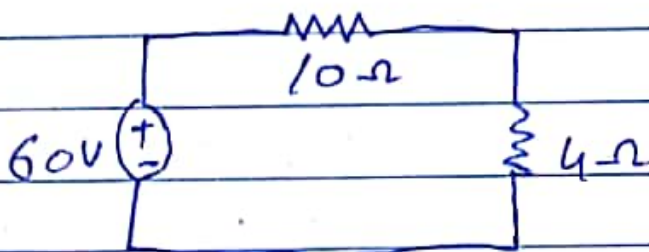


To get the value of the new current source we use

$$I = \frac{2ix}{5}$$

$$I = 0.4ix$$

And we draw it as -

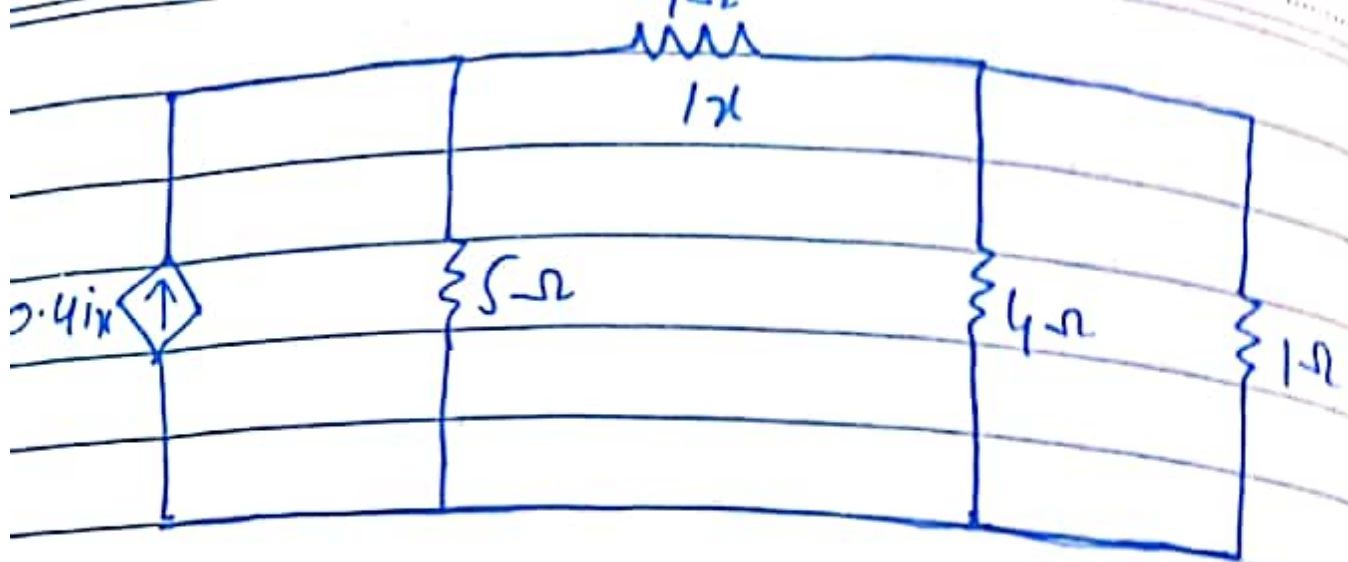


Result ::

(a) we replace the 10Ω resistor and the voltage source with a 600 mA current source in parallel with a 10Ω resistor.

b) we replace the 10Ω resistor and the current source with a 60 V voltage source in series with a 10Ω resistor.

(c) we replace the 5Ω resistor and the dependent voltage source with a dependent current source labeled $0.4i_x$ in parallel with a 5Ω resistor.

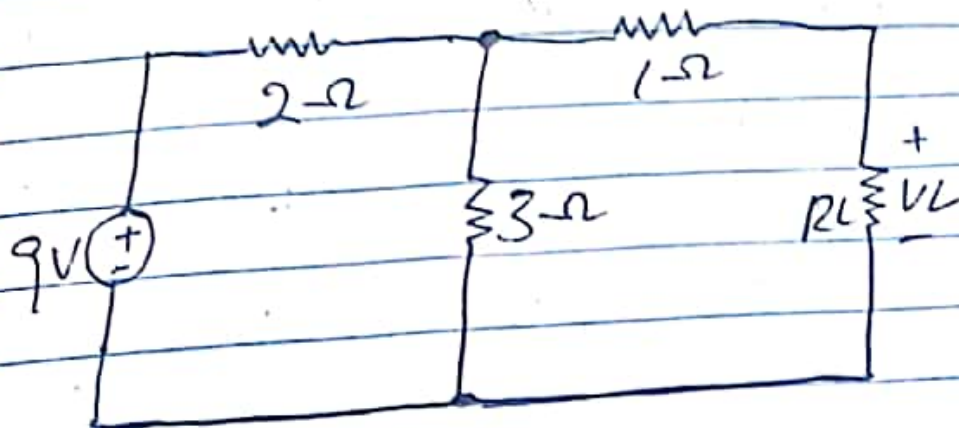25: determine the Thevenin equivalent of the network connected to R_L . b). Determine V_L for $R_L = 1\ \Omega, 3.5\ \Omega, 6.257\ \Omega$ and $9.8\ \Omega$



Solution:

To get V_{TH} we disconnect R_L and find the voltage between the two disconnected points. As we can see this voltage is the one on the $3\ \Omega$ resistor.

$$V_{TH} = 9V \cdot \frac{3}{5}$$

$$V_{TH} = 5.4V$$

we can calculate R_{TH} as:

$$R_{TH} = 1 + 3 \parallel 2$$

$$R_{TH} = 2.2\ \Omega$$

then we calculate V_L as:

$$V_L = V_{Th} \cdot \frac{R_L}{R_L + R_{Th}}$$

For each value of R_L we get:

$$R_L = 1\Omega \Rightarrow V_L = 1.688V$$

$$R_L = 3.5\Omega \Rightarrow V_L = 3.316V$$

$$R_L = 6.257\Omega \Rightarrow V_L = 3.995V$$

$$R_L = 9.8\Omega \Rightarrow V_L = 4.41V$$

Result:

$$V_{Th} = 5.4V, R_{Th} = 2.2\Omega$$


$$V_L = 1.688V, 3.316V, 3.995V, 4.41V$$

27: (a) obtain the norton equivalent of the network connected to R_L .

(b) obtain the Thevenin equivalent of the same network.

(c) use either to calculate it for $R_L = 0\Omega, 1\Omega, 4.923\Omega$

cmd 8.107Ω

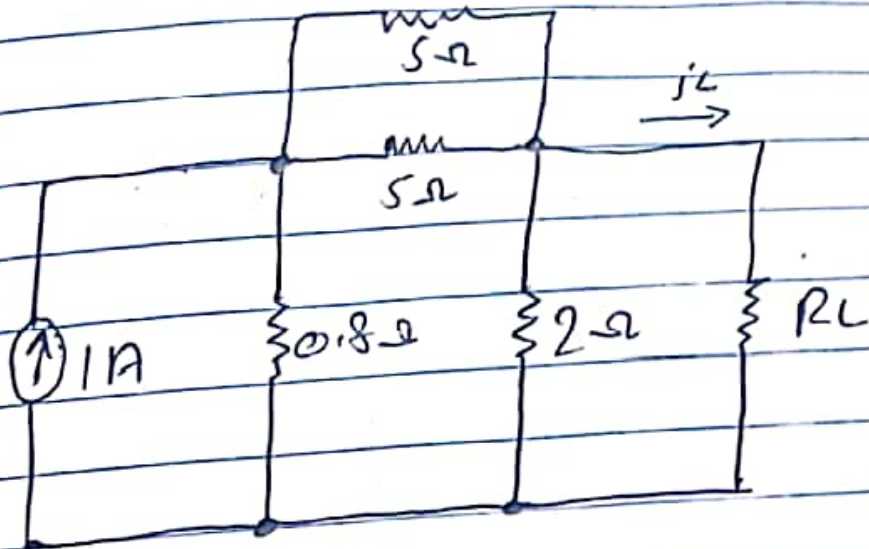

Solution:

(a) we calculate R_N as:

$$R_N = (0.8 + 5 \parallel 5) \parallel 2$$

$$R_N = 3.3 \parallel 2$$

$$R_N = 1.245 \Omega$$

For i_N we have:

$$i_N = \frac{0.8}{0.8 + 2.5}$$

$$i_N = 0.242 A$$

(b) now we can V_{TH} as:

$$* V_{TH} = i_N \cdot R_N$$

$$V_{Th} = 0.302 V$$

ind

using Thevenin equivalent we get:

$$i_L = \frac{V_{Th}}{R_{Th} + R_L}$$

for each value of R_L giving us:

(1) $R_L = 0 \Omega \Rightarrow i_L = 0.243 A$

(2) $R_L = 1 \Omega \Rightarrow i_L = 0.135 A$

(3) $R_L = 4.923 \Omega \Rightarrow i_L = 0.049 A$

(4) $R_L = 8.107 \Omega \Rightarrow i_L = 0.032 A$

Result :



(a) $i_N = 0.242 A, R_N = 1.245 \Omega$

(b) $V_{Th} = 0.302 V, R_{Th} = 1.245 \Omega$

(c) $i_L = 0.243 A, 0.135 A, 0.049 A, 0.032 A.$

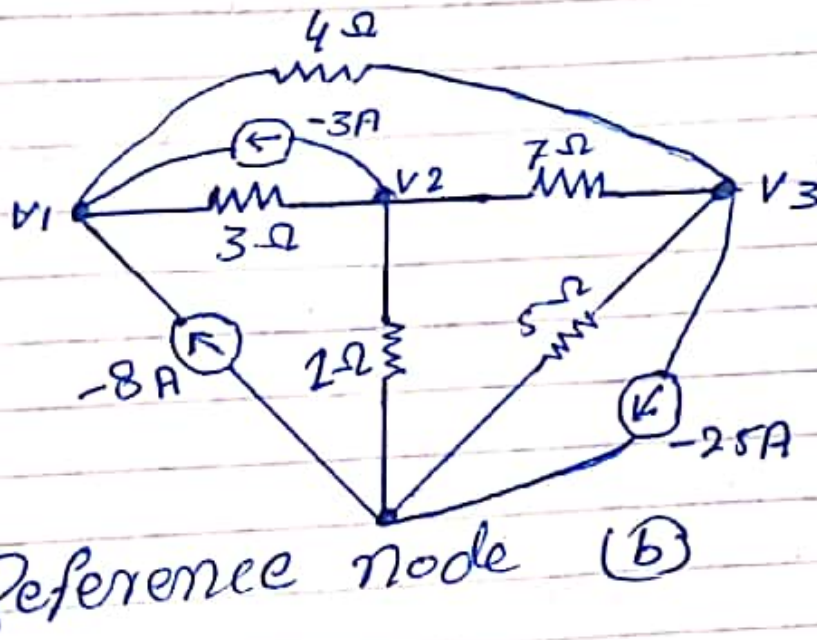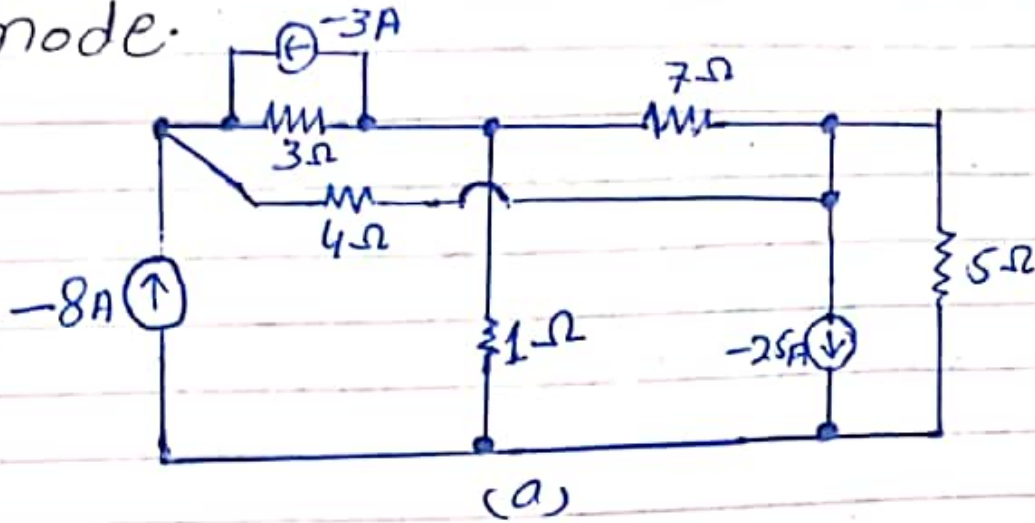Example 4.2

Determine the nodal voltages for the circuit of 4.4a, as reference to the bottom node.



Solution:

We have three nodes in the circuit V_1 , V_2 and V_3 .

Applying KCL on node 1

$$-8 - 3 = \frac{V_1 - V_2}{3} + \frac{V_2 - V_3}{4}$$

Taking L.C.M

$$-11 = \frac{4V_1 - 4V_2 + 3V_2 - 3V_3}{12}$$

$$-11 = \frac{4V_1}{12} - \frac{V_2}{12} - \frac{3V_3}{12}$$

$$-11 = 0.3333V_1 - 0.0833V_2 - 0.25V_3$$

Applying KCL At node 2

$$3 = \frac{V_2 - V_1}{3} + \frac{V_1}{1} + \frac{V_2 - V_3}{7}$$

$$3 = \frac{7V_2 - 7V_1 + 21V_2 + 3V_2 - 3V_3}{21}$$

$$3 = \frac{-7V_1 + 31V_2 - 3V_3}{21}$$

$$3 = -0.3333V_1 + 1.4762V_2 - 0.1429V_3$$

Applying KCL At node 3

$$25 = \frac{V_3}{5} + \frac{V_2 - V_3}{7} + \frac{V_3 - V_1}{4}$$

$$\Delta x = 0.49868 - 0.0777 + 0.079$$

$$\Delta x = 0.316$$

Now

$$V_1 = \frac{1}{\Delta x} \begin{bmatrix} -11 & -0.33 & -0.250 \\ 3 & 1.476 & -0.142 \\ 25 & -0.142 & 0.592 \end{bmatrix}$$

$$= -11 \begin{bmatrix} 1.476 & -0.142 \\ 0.142 & 0.592 \end{bmatrix} - 3 \begin{bmatrix} 0.33 & -0.250 \\ -0.142 & 0.592 \end{bmatrix}$$

$$+ 25 \begin{bmatrix} 0.33 & -0.250 \\ 1.476 & -0.142 \end{bmatrix}$$

$$= -11 (0.875 - 0.020) - 3 (-0.197 - 0.035) + 25 (0.047 + 0.36)$$

$$= -10.145 + 0.69 + 10.41$$
$$= 1.714$$

$$V_1 = \frac{1.714}{0.3167} = 5.412 \text{ V}$$

$$V_2 = \frac{1}{\Delta x} \begin{bmatrix} 0.583 & -11 & -0.250 \\ -0.333 & 3 & -0.142 \\ -0.250 & 25 & 0.592 \end{bmatrix}$$

$$= 0.583 \begin{bmatrix} 3 & -0.142 \\ 25 & 0.592 \end{bmatrix} + 11 \begin{bmatrix} -0.333 & -0.142 \\ -0.250 & 0.592 \end{bmatrix}$$

$$- 0.250 \begin{bmatrix} 0.333 & 3 \\ 0.250 & 25 \end{bmatrix}$$

$$= 0.583(1.778 + 3 \cdot 57.2) + 11(0.197 + 0.035) - 0.25(-8.332 + 0.75)$$

$$= 3.86 - 2.56 + 2.83$$

$$= 2.45$$

So

$$V_2 = \frac{2.45}{0.3167} = 7.73 \text{ V}$$

Now

$$V_3 = \frac{1}{\Delta x} \begin{bmatrix} 0.5833 & -0.333 & -11 \\ -0.33 & 1.476 & 3 \\ -0.250 & -0.142 & 25 \end{bmatrix}$$

$$0.583 \begin{bmatrix} 0.333 & -11 \\ -0.250 & 1.476 & 3 \end{bmatrix} - 0.33 \begin{bmatrix} 0.33 & 3 \\ -0.25 & 25 \end{bmatrix}$$

$$-11 \begin{bmatrix} 0.333 & 1.4762 \\ 0.250 & -0.142 \end{bmatrix}$$

$$= 0.583(15.238) + 0.333(-9.0825) - 11(0.107)$$

$$= 14.67$$

$$\text{So } V_3 = \frac{14.67}{0.316} = 46.32 \text{ V}$$

So


$$V_1 = 5.412 \text{ V}$$

$$V_2 = 7.73 \text{ V}$$

$$V_3 = 46.32 \text{ V}$$

Example 4.3

Determine the power supplied by the dependent source of figure.

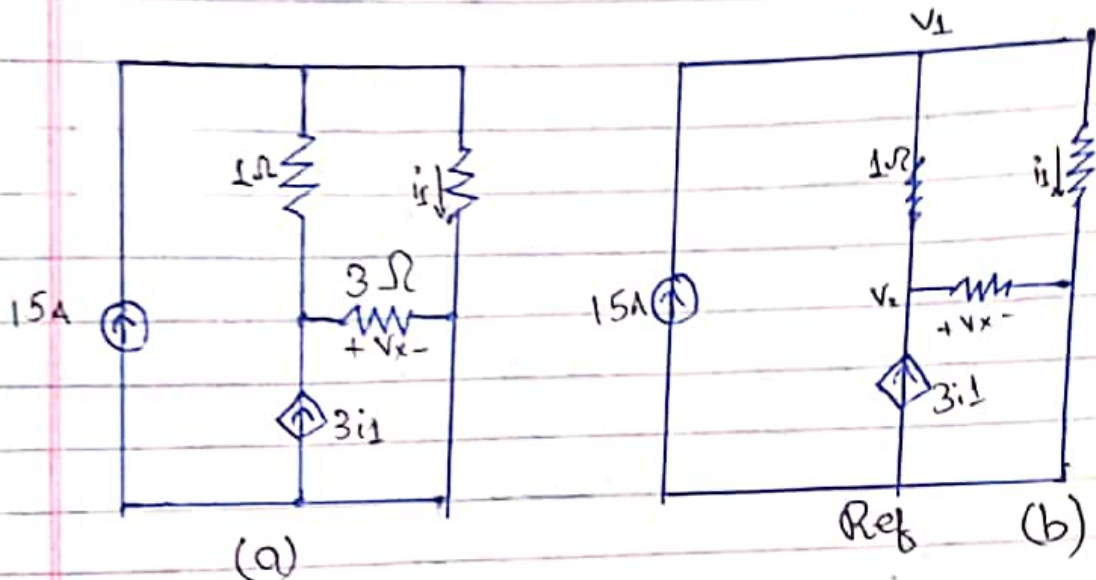

Example 4.3

Solution:

↳ Applying KCL on v_2

$$15 = v_1 - v_2 = \frac{v_1}{2}$$

$$15 = \frac{2v_1 - 2v_2 + v_1}{2}$$

$$30 = 3v_1 - 2v_2 \quad \text{--- (i)}$$

↳ Applying KCL on v_1

$$3i_1 = v_2 - v_1 + \frac{v_2}{3}$$

$$3i = 3v_2 - 3v_1 + v_2 \quad \dots (2)$$

i_1 is flowing across

$$\frac{v_1}{3\Omega} \text{ or } \frac{v_1}{2}$$

$$\text{So } i_1 = \frac{v_1}{2}$$

Put eq (2)

$$\frac{3v_1}{2} = \frac{3v_2 - 3v_1 + 2v_2}{3}$$

$$9v_1 = 6v_2 - 6v_1 + v_2$$

$$8v_2 + 15v_1 = 0$$

$$-15v_1 + 8v_2 = 0 \quad \dots (3)$$

Multiplying (5) with eq (i) by

Subtraction from eq (3)

$$\begin{array}{r} 15v_1 - 8v_2 = 0 \\ -15v_1 + 10v_2 = -30 \\ \hline 3v_2 = -30 \\ v_2 = -10 \end{array}$$

$$\text{Multiplying 5 with eq (i)} \\ 5 \times 3v_1 - 2v_2 = 30$$

$$= 15v_1 - 10v_2 = 150$$

(2)
Combining eq (1) and eq(3)

$$\begin{array}{r} 15v_1 - 10v_2 = 150 \\ -15v_1 + 8v_2 = 6 \\ \hline -2v_2 = -156 \end{array}$$

$$v_2 = 78$$

Putting in eq 3

$$\begin{array}{r} -15v_1 + 8(-78) = 6 \\ v_1 = -40 \end{array}$$

Now:

$$i_1 = \frac{v_1}{2} = \frac{-40}{2} = -20A$$


for Power, $P = iv$

$$P = (3i_1)(v) = +3(-20)(-75)$$

$$P = 4.5 \text{ KW.}$$

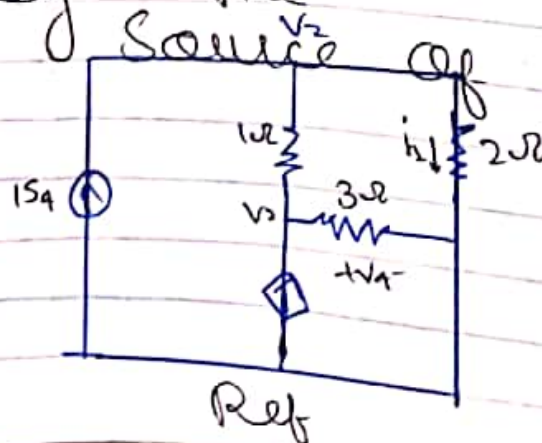Example 4.4

Determine the power supplied by the dependent source of figure



Applying KCL on v_1

$$15 = v_1 - v_2 + \frac{v_1}{2}$$

$$\begin{aligned} 30 &= 2v_1 - 2v_2 + v_1 \\ 30 &= 3v_1 - 2v_2 \quad \dots (i) \end{aligned}$$

Apply KCL on v_2

$$3v_2 = v_2 - v_1 + \frac{v_2}{3}$$

$$v_1 = \frac{v_2}{3}$$

$$\frac{3v_2}{3} = \frac{3v_2 - 3v_1 + v_2}{3}$$

$$-3v_1 + v_2 = 0 \quad \dots (2)$$

Combine eqn (i) and (2)

$$\begin{aligned} 3v_1 - 2v_2 &= 30 \\ -3v_1 + v_2 &= 0 \\ \hline v_2 &= 30 \end{aligned}$$

Example 4.5 :

Determine the value of unknown node voltage v_1 in the circuit of figure.

$$(28) (60) = -35V_1 + 80V_2 + 27V_3$$

$$1680 = -35V_1 + 80V_2 + 27V_3 \quad \text{--- (2)}$$

Multiply 5 eq (1)

$$35V_1 - 20V_2 - 15V_3 = -660 \quad \text{--- (3)}$$

Combining eq (2) and (3)

$$\begin{array}{r} -35V_1 + 80V_2 + 27V_3 = 1680 \\ 35V_1 - 20V_2 - 15V_3 = -660 \\ \hline 60V_2 + 12V_3 = 1020 \end{array}$$

We know from super node

$$V_2 + 22 = V_3 \quad \text{--- (4)}$$

Putting V_3 in eq (4)

$$60V_2 + V_2 + 22 = 1020$$

$$61V_2 = 998$$

Dividing both side by 61

$$\frac{61V_2}{61} = \frac{998}{61}$$

$$V_2 = 998/61$$

$$[Ax] = \begin{vmatrix} 7 & -4 & 4 \\ 0 & 6 & -3 \\ 7 & 0 & -1 \end{vmatrix}$$

$$= 7 \begin{vmatrix} 6 & -3 \\ 0 & -1 \end{vmatrix} + 0 + 7 \begin{vmatrix} -4 & 4 \\ 6 & -3 \end{vmatrix}$$

$$= 7(-6) + 7(12 - 24)$$

$$= -42 + 7(-12)$$

$$= -42 - 84$$

$$[Ax] = -126$$

$$Bx = \begin{vmatrix} 1 & 7 & 4 \\ -1 & 0 & -3 \\ 0 & 7 & -1 \end{vmatrix}$$

$$= 1 \begin{vmatrix} 0 & -3 \\ 7 & -1 \end{vmatrix} - 1 \begin{vmatrix} 7 & 4 \\ 7 & -1 \end{vmatrix} + 0$$

$$= 1(21) - 1(-7 - 28)$$

$$= 21 + 35$$

$$[Bx] = 56$$

next page

$$C_x = \begin{vmatrix} 1 & -4 & 7 \\ -1 & 6 & 0 \\ 0 & 0 & 7 \end{vmatrix}$$

$$= 1 \begin{vmatrix} 6 & 0 \\ 0 & 7 \end{vmatrix} + 1 \begin{vmatrix} -4 & 7 \\ 0 & 7 \end{vmatrix} + 0$$

$$= 1(42) + 1(28)$$

$$= 42 + 28$$

$$C_x = 70$$

$$C_x = \begin{vmatrix} 1 & -4 & 7 \\ -1 & 6 & 0 \\ 1 & 0 & 7 \end{vmatrix}$$

$$= 1 \begin{vmatrix} 6 & 0 \\ 0 & 7 \end{vmatrix} + 4 \begin{vmatrix} -1 & 0 \\ 1 & 7 \end{vmatrix} + 7 \begin{vmatrix} -1 & 6 \\ 1 & 0 \end{vmatrix}$$

$$= 1(42) + 4(-7) + 7(-6)$$

$$= 42 - 28 - 42$$

$$= -28$$

Now


$$i_1 = \frac{I_{Ax}}{I_A} = \frac{-126}{-14} = 9 \text{ A}$$

$$i_2 = \frac{I_{Bx}}{I_A} = \frac{-56}{-14} = 2.5 \text{ A}$$

$$i_3 = \frac{|C_x|}{|A|} = \frac{-28}{-14} = 2 \text{ A}$$

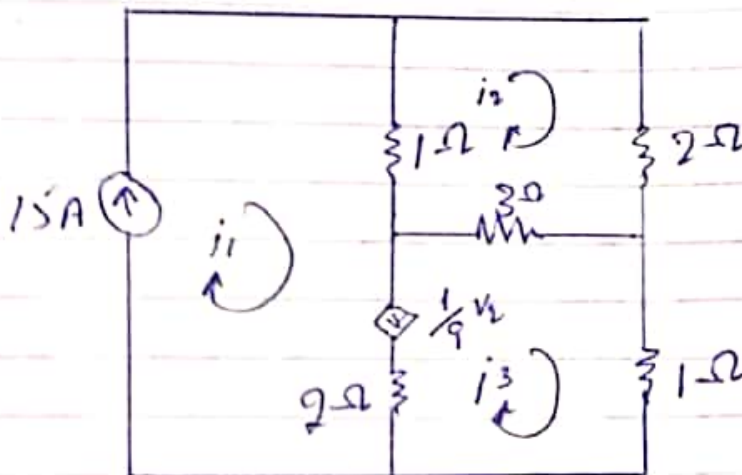Example 4.12

Evaluate the three unknown currents in the circuit.



Solution:

we have one dependent current and one independent source.

Now

we have the $v_1 = 15 \text{ A}$
we have to find two unknown source.

Apply KCL on a node
unknown is entering
next page.

$$i_2 + \frac{1}{9} v_x = i_3$$

$$\frac{v_x}{9} = i_3 - i_2$$

$v_x = 3(i_3 - i_2)$ From figure
putting in equation

$$\frac{3(i_3 - i_2)}{9} = i_3 - i_2$$

$$\frac{1}{3} i_3 - \frac{1}{3} i_2 = i_3 - i_2$$

$$-i_2 + i_3 + \frac{1}{3} i_2 - \frac{1}{3} i_3$$

$$-i_2 + \frac{1}{3} i_2 + \frac{2}{3} i_3 = 0$$

$$\boxed{i_2 = 15}$$

$$-15 + \frac{1}{3} i_2 + \frac{2}{3} i_3 = 0$$

$$\frac{1}{3} i_2 + \frac{2}{3} i_3 = 15 \quad \text{--- (A)}$$

$$i_2 + 2i_3 = 45 \quad \text{--- (1)}$$

Apply KVL on mesh 2

$$1(i_2 - i_2) + 2i_2 + 3(i_2 - i_3) = 0$$

$$i_2 - i_2 + 2i_2 + 3i_2 - 3i_3 = 0$$

$$-i_2 + 6i_2 - 3i_3 = 0$$

$$\boxed{i_2 = 15}$$

$$-15 + 6i_2 - 3i_3 = 0$$

$$6i_2 - 3i_3 = 15 \quad \text{--- (2)}$$

combining eq (1) and (2)

$$\begin{array}{r} 6i_2 + 12i_3 = 270 \\ -6i_2 - 3i_3 = -15 \\ \hline 9i_3 = 285 \end{array}$$

$$i_3 = \frac{285}{9}$$

$$i_3 = 28.33 \text{ A} \quad \text{and}$$


$$i_2 = 11 \text{ A}$$

part (ii)


Solve following example

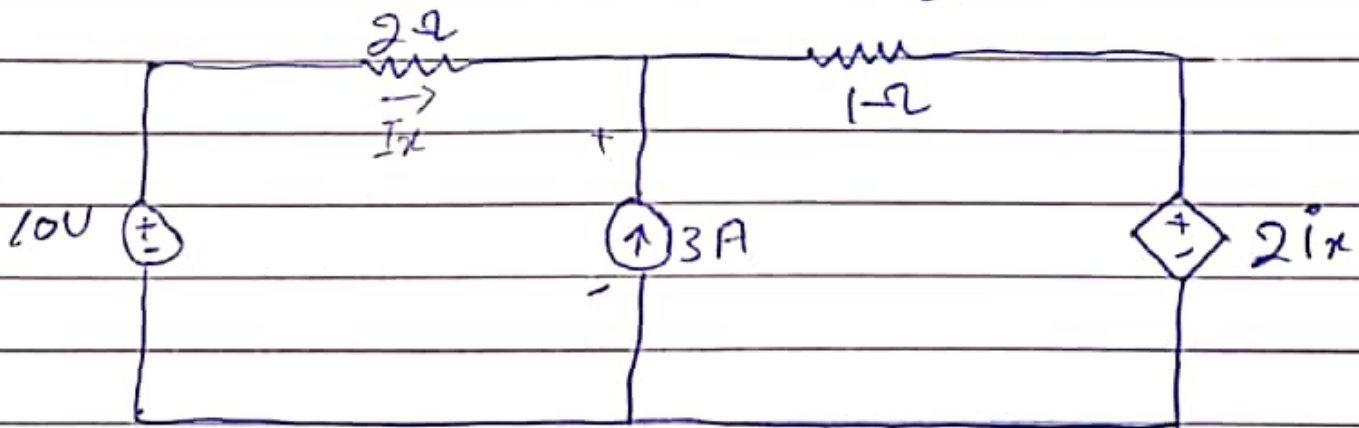Example 5.3 :-

Use the superposition principle to determine the value of i_x



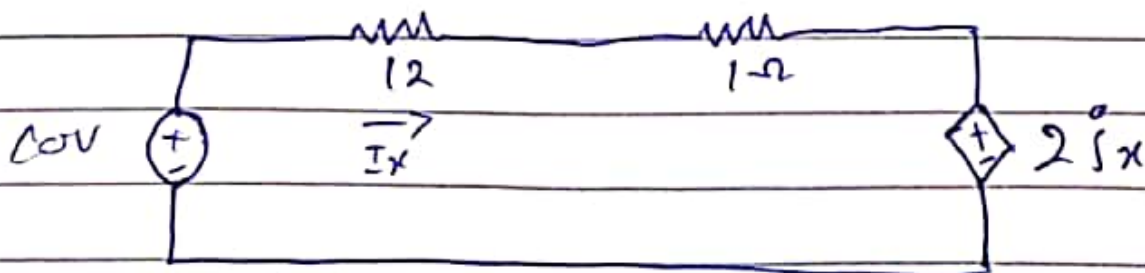Solution:- First we will remove current source and will make it in open circuit. Redrawing the circuit:




Apply KVL on mesh

$$2i_x' + 1i_x' + 2i_x' = 0$$

$$5i_x' = 10 \Rightarrow i_x' = 2A$$

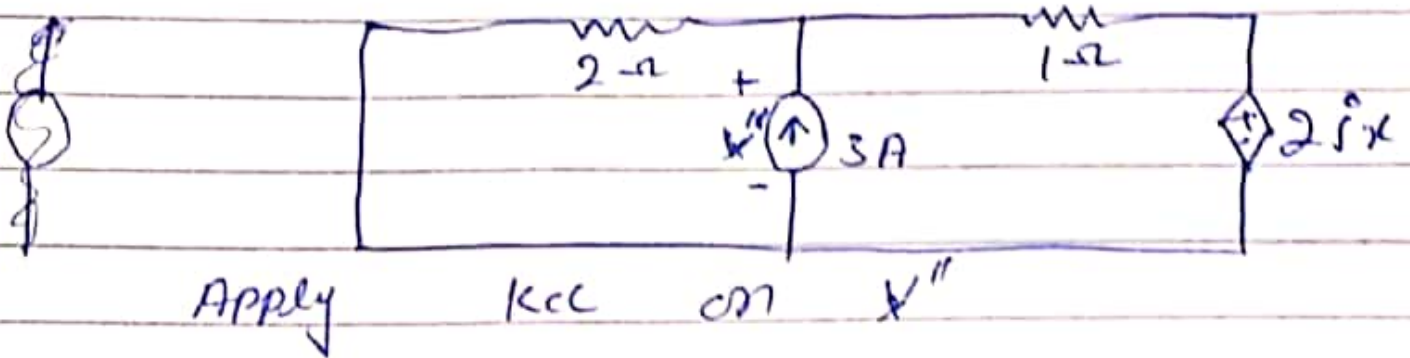Now we will remove voltage source and make it an open circuit.



$$\frac{V''}{2} + \frac{V'' - 2ix''}{1} = 3$$

$$\frac{V'' + 2V'' - 2ix''}{2} = 3$$

$$3V'' - 4ix'' = 6$$

We now from the figure

$$ix'' = -2ix''$$

$$3(1 - 2ix'') - 4ix'' = 6$$

$$-10ix'' = 6$$


$$ix'' = -0.6 \text{ A}$$

$$ix = ix' + ix''$$

$$= 2 + (-0.6)$$

$$i_x = 1.4 \text{ A}$$

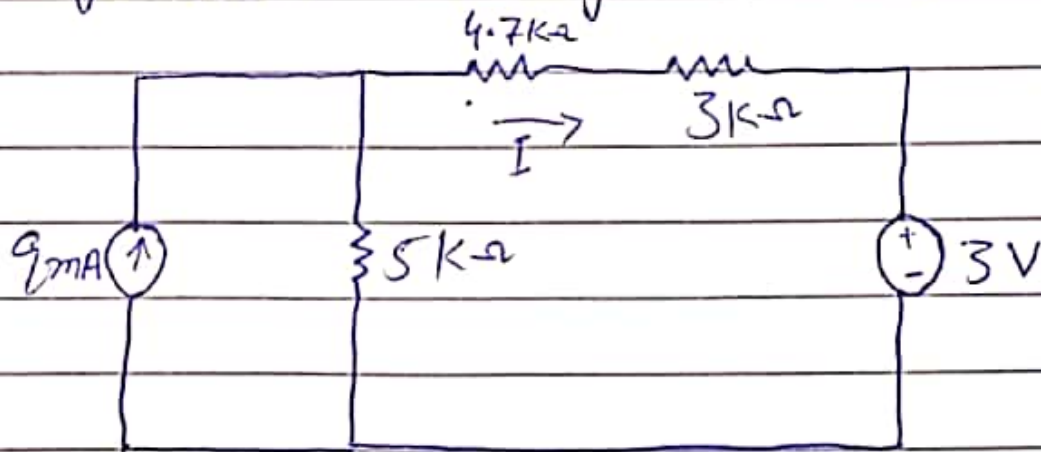Example 5.4: compute the current through the $4.7 \text{ k}\Omega$ resistor after transforming the 9 mA source into an equivalent voltage source.



Solution:


we know that

$$V = IR$$

$$V = (9 \times 10^{-3})(5000)$$
$$= (0.009)(5000)$$

$$V = 45$$

re drawing the circuit

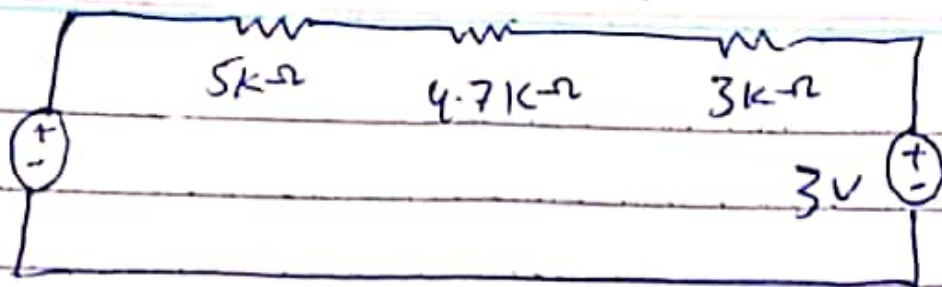


Apply KVL on mesh

$$5000i + 4700i + 3000i = 45 - 3$$


$$12700i = 42$$

$$i = 0.0033A$$

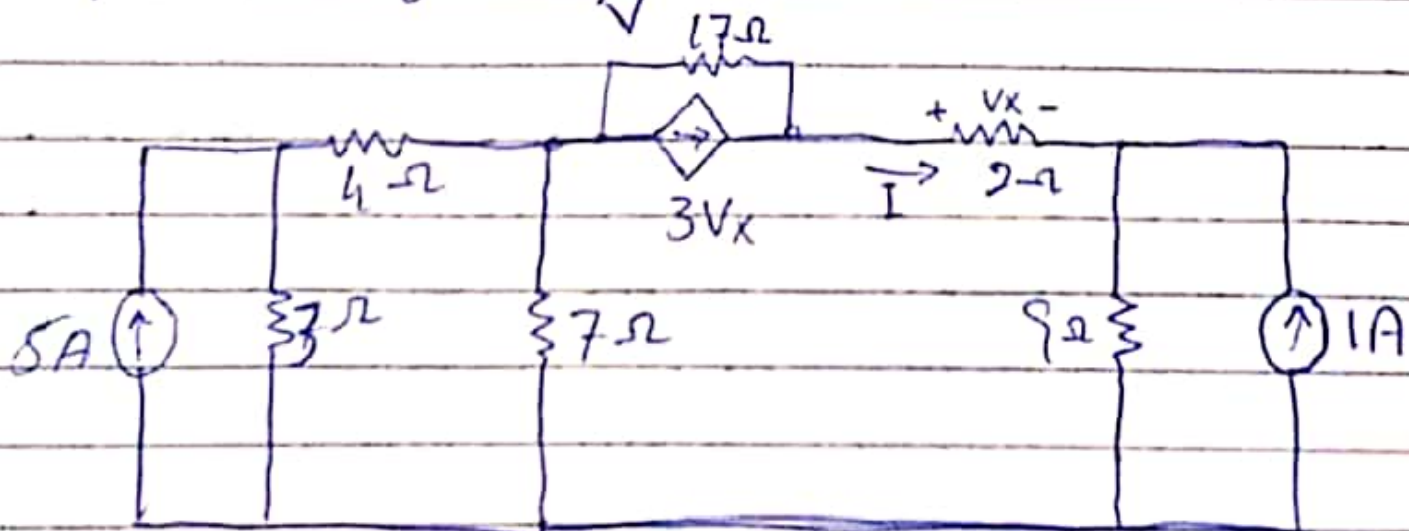Example 4.5: calculate the current through the 2Ω resistor by making use of source transformation to first simplify the circuit.



Re drawing a circuit

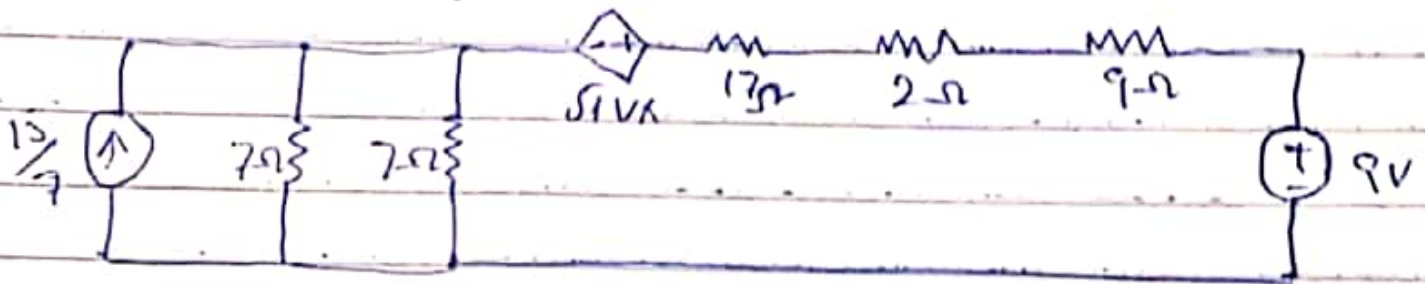


$$V = IR = \left(\frac{15}{7}\right) (7)$$

$$V = 7.5$$

$$R = 17 + 9$$

$$R = 26\Omega$$

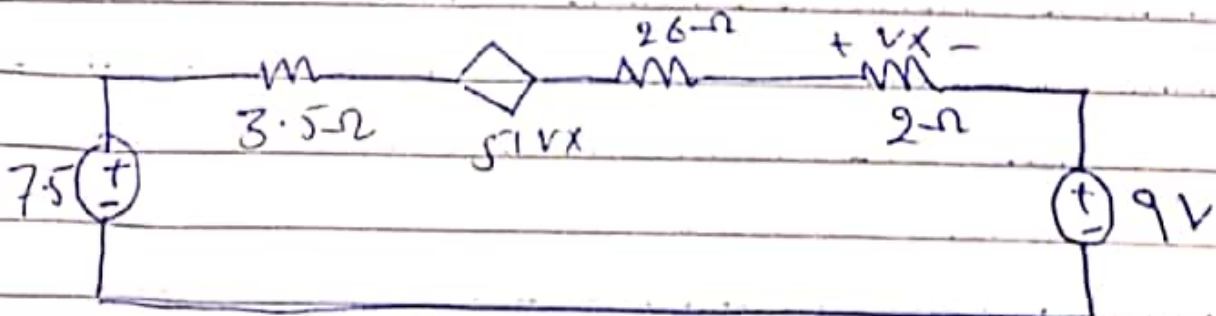

Apply KVL on mesh ;


$$3.5j - 51V + 28j = 7.5 - 9$$

$$V_x = 21$$

$$3.5j - 51(22)j + 28j = -1.5$$


$$j = \frac{-1.5}{-1039.5} \Rightarrow \boxed{j = 0.0014A}$$

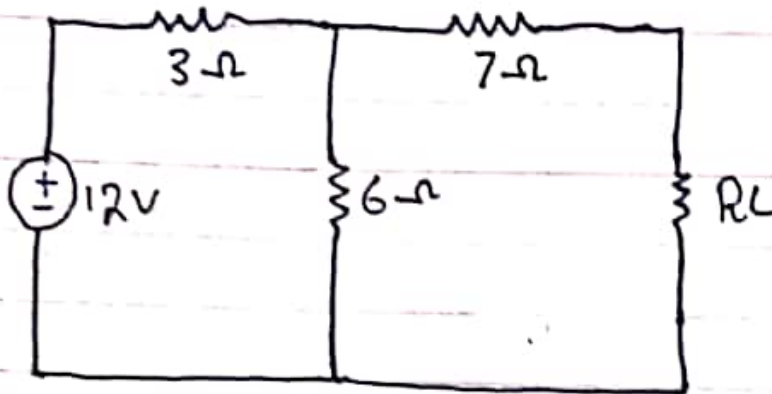Example 5.6: consider the circuit show in fig. Determine the Thévenin equivalent of network A, and compute the power delivered to the load resistor R_L .




Solution:

$$I = V/R = 12/3 = 4 \text{ A}$$

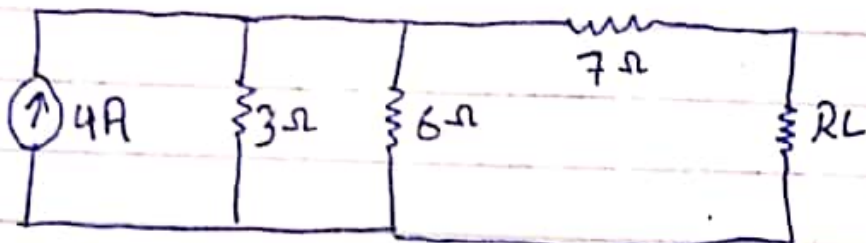

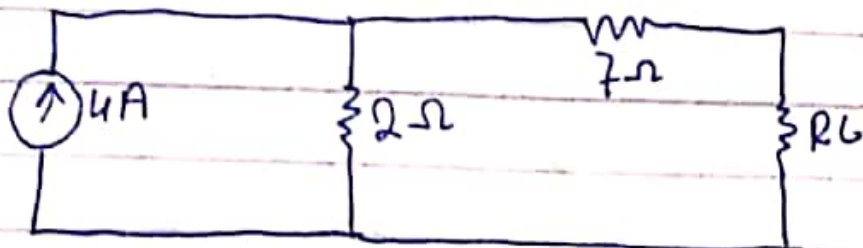
$$R_{eq} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2 \Omega$$




$$V = IR = 4(2)$$

$$V = 8 \text{ V}$$

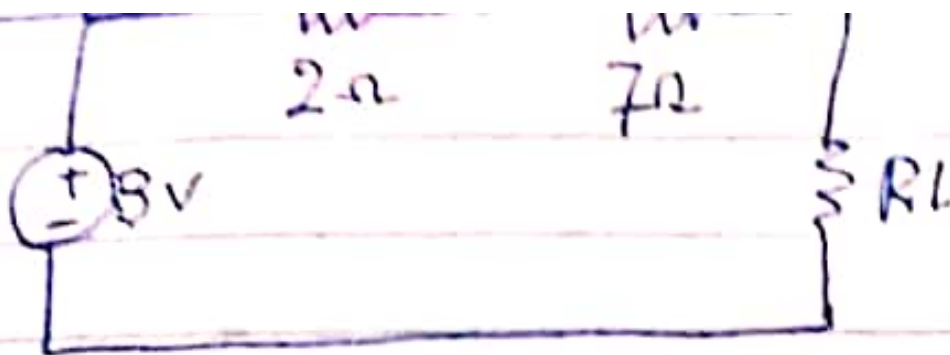

$$R = 2 + 7 = 9$$

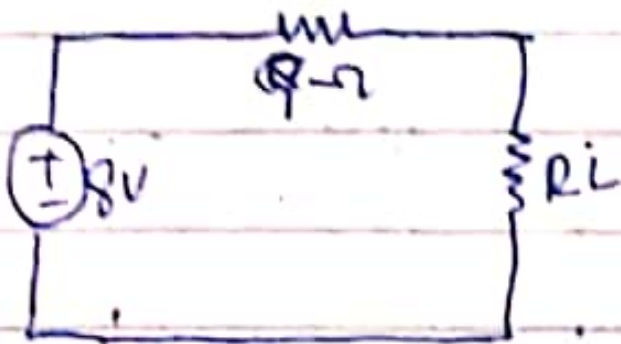


$$V_{TH} = 8V$$

$$R_{TH} = 9\Omega$$


$$R \cdot P = \left(\frac{8}{9 + R_{L}} \right)^2 R_{L}$$

For any value of R_L with different solution

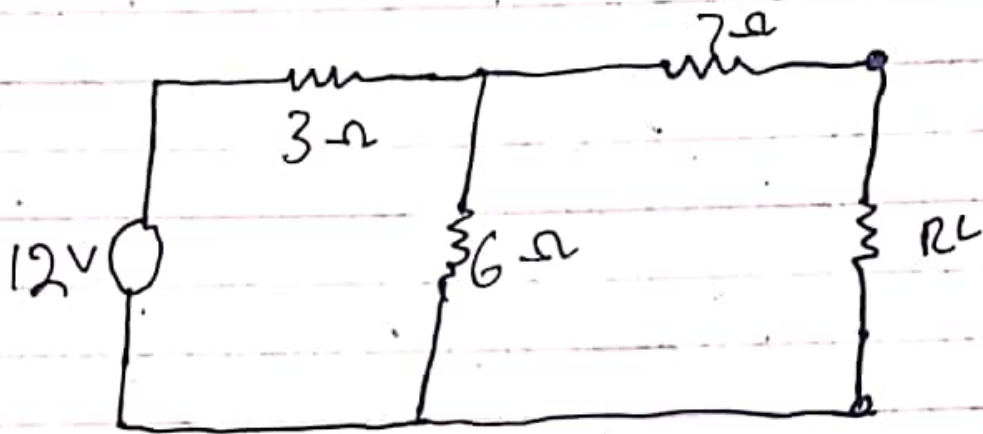Example 5.7: Use Thevenin's Theorem determine the Thevenin equivalent for that part of the circuit in to the left of R_L .



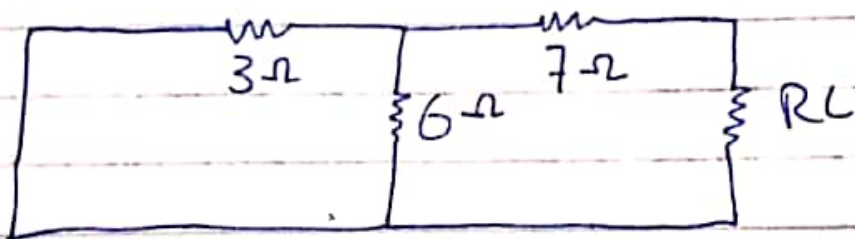For finding R_{Th} we will remove voltage source and make it is a short circuit.




For R_{Th} we will add all the resistor except R_L

$$R_{Th} = 3 \parallel 6 + 7$$


$$= \frac{18}{2} + 7$$

$$R_{Th} = 9$$

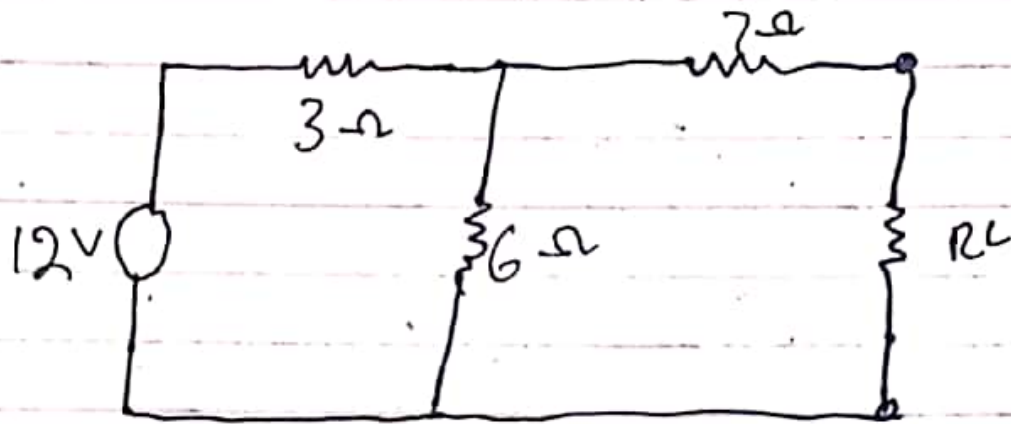Example 5.7: Use Thevenin's Theorem determine the Thevenin equivalent for that part of the circuit in to the left of R_L .



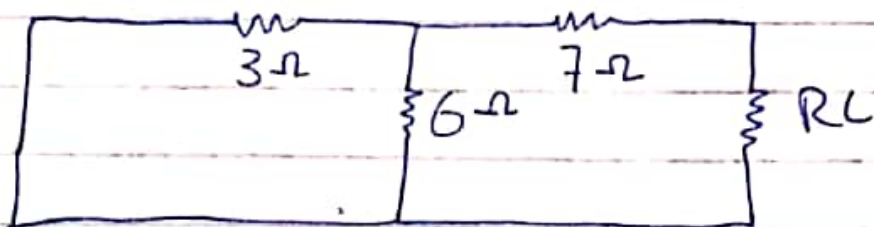For finding R_{Th} we will remove voltage source and make it is a short circuit.




For R_{Th} we will add all the resistor except R_L

$$R_{Th} = 3 \parallel 6 + 7$$

$$= \frac{18}{2} + 7$$

$$R_{Th} = 9$$

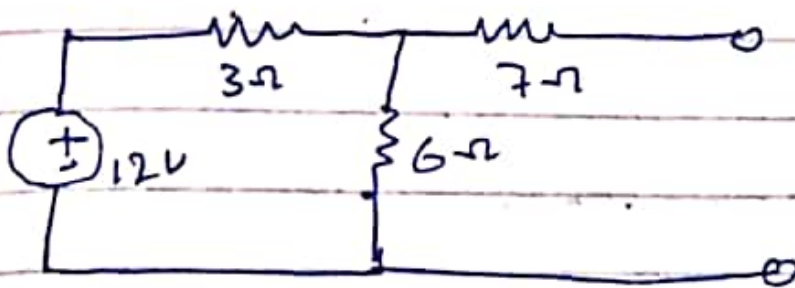For ~~Voc~~ Voc we will remove
RL and make it is an
open circuit.




$$V_{oc} = 12 \left(\frac{.6}{3+6} \right)$$

$$V_{oc} = 8V$$

Q5: Node voltage

(part b)

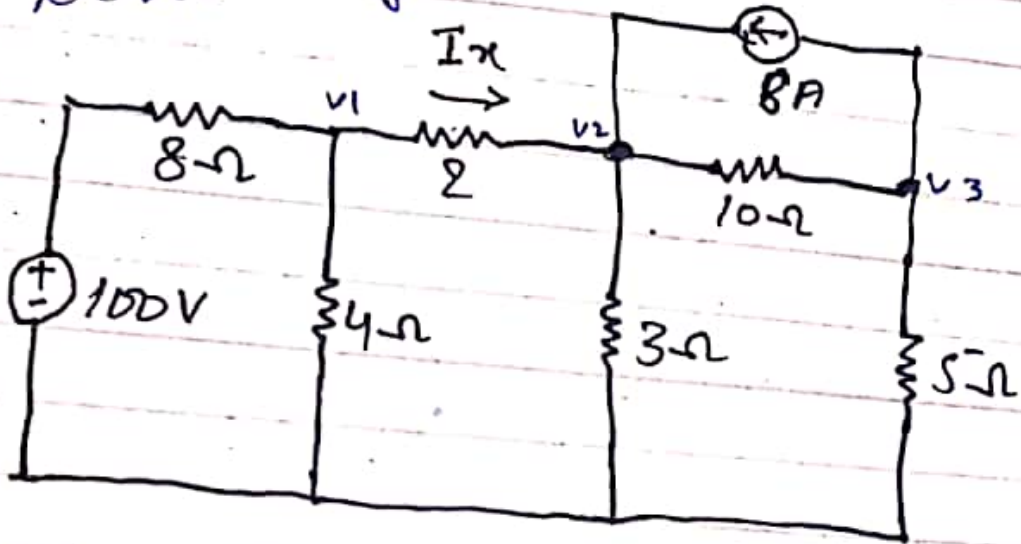

Solution:

Apply KCL on node 1:

$$\frac{v_1 - 100}{8} + \frac{v_1}{4} + \frac{v_1 - v_2}{2} = 0$$

$$\frac{v_1 - 100 + 2v_1 + 4v_1 - 4v_2}{8} = 0$$

$$7v_1 - 4v_2 = 100 \quad \text{--- (1)}$$

Apply KCL on node 2:

$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{18} = 8$$

$$\frac{30v_2 - 30v_1 + 20v_2 + 3v_2 - 3v_3}{60} = 8$$

Next page

$$-30V_1 + 53V_2 - 3V_3 = 480 \quad \text{--- (2)}$$

Apply KCL on node 3:

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Taking eq (2)

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

Putting eq (a) and (b) in eq (2)

$$-30(0.57v_2 + 14.28) + 53v_2 - 3(0.33v_2 - 26.67) = 480$$

$$-17.1v_2 - 428.4 + 53v_2 - 0.99v_2 + 80.01 = 480$$

$$34.91v_1 = 828.39$$

$$v_2 = \frac{828.39}{34.91}$$

$$v_2 = 20.31$$

putting in eq (a)


$$v_2 = \frac{4(20.31) + 100}{7}$$

$$v_2 = 25.89$$

$$i_x = \frac{v_1 - v_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

Mesh analysis

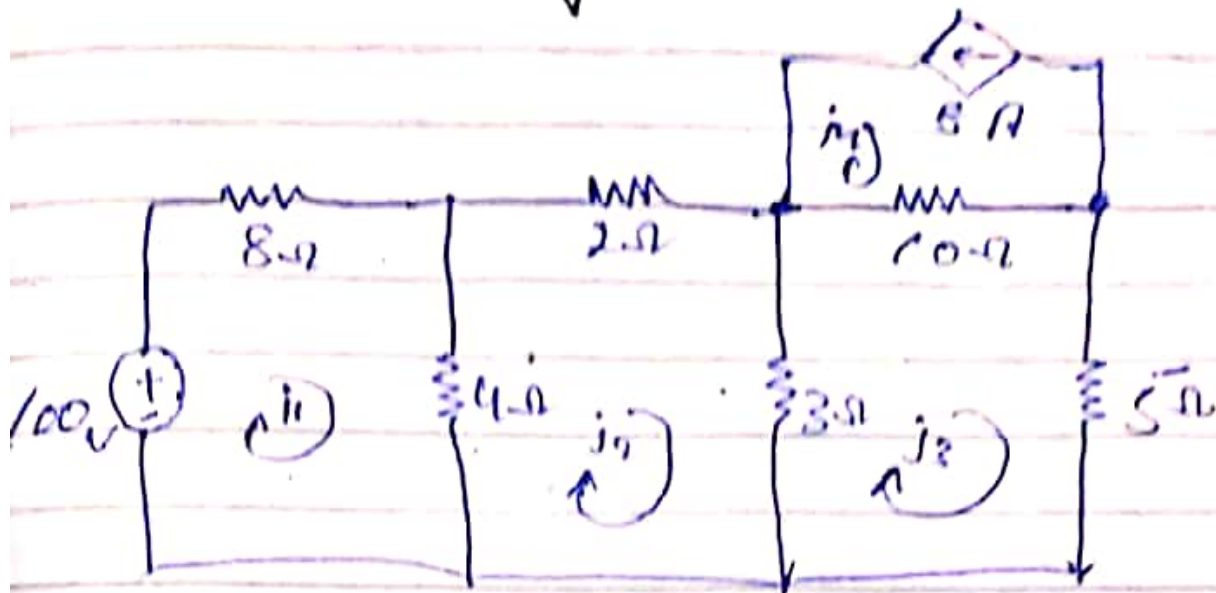

Apply KVL on Loop 1

$$8i_1 + 4(i_2 - i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_2 - 4i_2 = 100 \quad \text{--- (1)}$$

Apply KVL on Loop 2.

$$2i_2 + 4(i_2 - i_2) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_2 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop 3:

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (b)}$$

Putting eq (a) and (b) on eq (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$


$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$
$$7.2i_2 = -20$$

$$i_2 = 20/7.2 \Rightarrow i_2 = i_x$$

$$i_2 = 2.79 \text{ A} \Rightarrow \boxed{i_x = 2.79 \text{ A}}$$

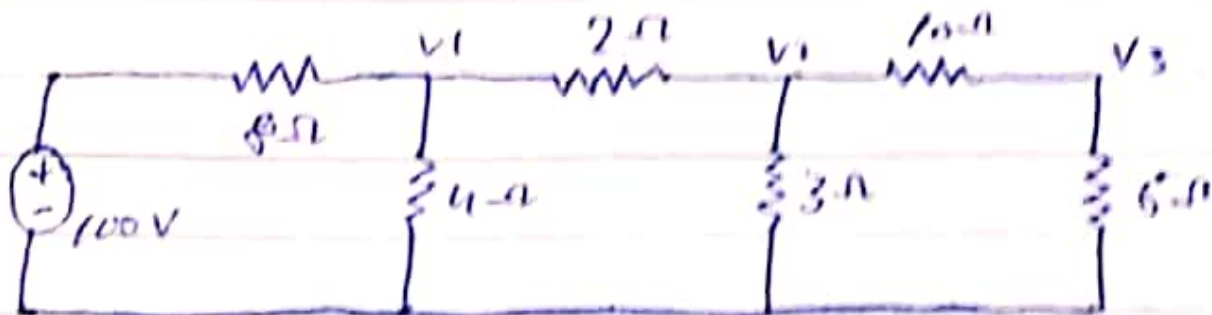ii) Superposition Theorem:

First removing the current source and making it an open circuit by drawing the circuit



Apply KCL on node 1

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$V_1 - 100 + 4V_1 - 4V_1 + 2V_3 = 0$$

$$7V_1 - 4V_2 = +100 \quad \text{--- (1)}$$

Apply KCL on node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 + 58V_2 - 3V_3 = 0$$

Apply KCL on node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + V_3}{10} = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) and (2)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Now $-V_2 + 3V_3 = 0$

$$V_3 = \frac{1}{3}V_2 \quad \text{--- (b)}$$

putting in eq (2)

$$-30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$-17.1V_2 - 428.4 - 4V_2 + 0.60V_2 = 0$$

$$20.44V_2 = -428.4$$

$$V_2 = -20.95$$

putting in eq (a)

(72)

Apply KVL on loop 2:

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop 3:

$$10i_3 + 5i_3 + 3i_3 - 2i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (b)}$$

$$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$$

$$j_2 = 1.354$$

Now

$$j_x = j_1 + j_2$$


$$j_x = 1.44 + 1.35$$

$$j_x = 2.79 \text{ A}$$

Result

$$j_x = 2.79 \text{ A}$$

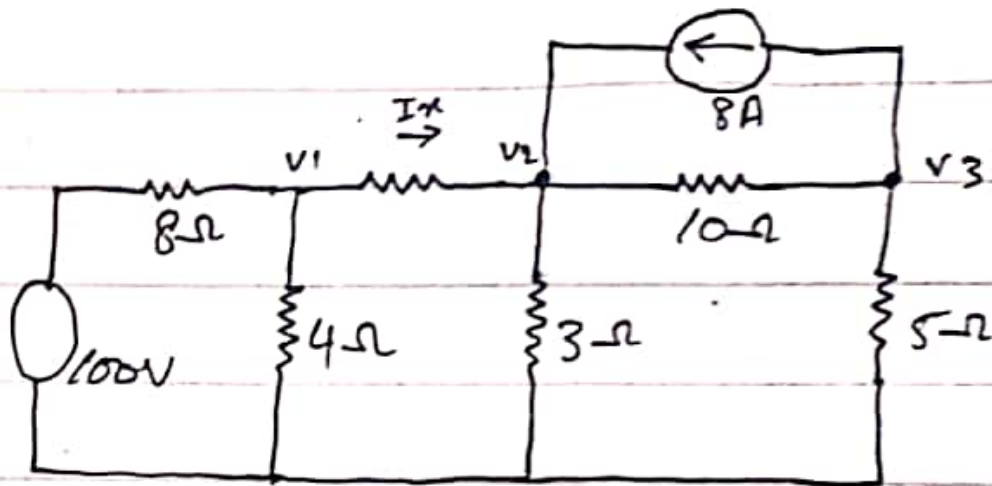compare the number of steps and degree of easiness of all the three methods with each other



Node analysis

Solution: Apply KCL on node 1:

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_1 - 100 + 2V_1 + 4V_1 - 4V_2}{8} = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Apply KCL node 2:

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_2 - V_3}{18} = 8$$

$$\frac{30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3 = 8}{60}$$

$$-30V_1 + 53V_2 - 3V_3 = 480 \quad \text{--- (2)}$$

Apply KCL on node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

~~$$7V_1 - 4V_2 = 100$$~~

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Taking eq (2)

$$-v_2 + 3v_3 = -80$$

$$v_3 = \frac{v_2 - 80}{3} \quad \text{--- (b)}$$

putting (a) and (b) in eq (2)

$$-30(0.57v_2 + 14.28) + 53v_2 - 3(0.33v_2 - 26.67) = 480$$

$$-17.1v_2 - 428.4 + 53v_2 - 0.99v_2 + 80.01 = 480$$

$$34.91v_2 = 828.39$$

$$v_2 = \frac{828.39}{34.91}$$

$$v_2 = 20.31$$

putting in eq (a)

$$v_2 = \frac{4(20.31) + 100}{7}$$


$$v_2 = 25.89$$

$$i_x = \frac{v_1 - v_2}{2}$$

$$i_x = \frac{25.89 - 20.31}{2}$$

$$i_x = 2.79 \text{ A}$$

Mesh analysis

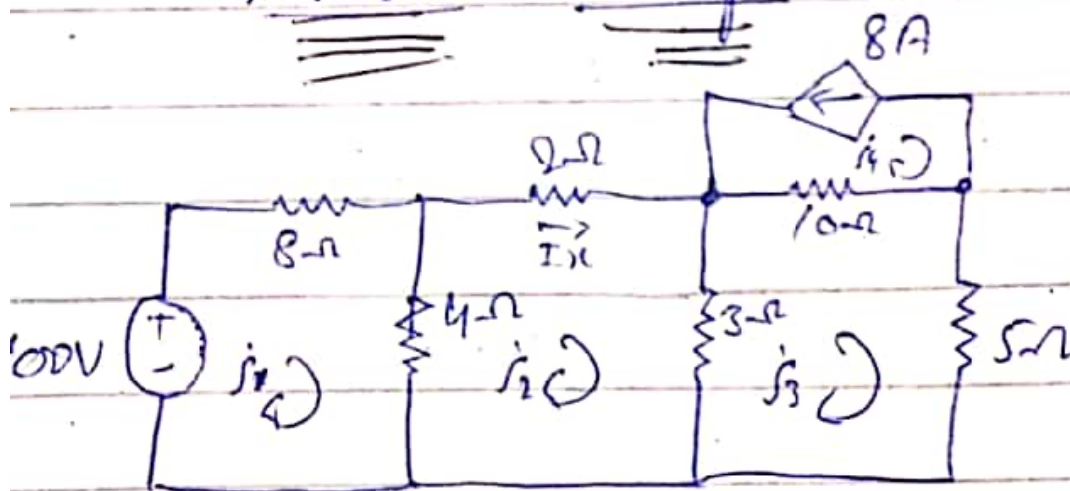

Apply KVL on loop 1

$$8i_1 + 4(i_2 - i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_2 - 4i_2 = 100 \quad \text{--- (1)}$$

Applying KVL on loop 2:

$$2i_2 + 4(i_2 - i_2) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_2 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop 3:

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_1 = \frac{4i_2 - 100}{12} \quad \text{--- (4)}$$

Taking eq (3)

$$-3j_2 + 18j_3 = -80$$

$$j_3 = \frac{-3j_2 + 80}{18} \quad \text{--- (b)}$$

Putting (a) and (b) in eq (2)

$$-4(0.33j_2 - 8.33) + 9j_2 - 3(0.16j_2 + 4.44) = 0$$

$$-1.32j_2 + 33.32 + 9j_2 - 0.48j_2 - 13.32 = 0$$

$$7.2j_2 = 20$$


$$j_2 = \frac{20}{7.2} \Rightarrow j_2 = 2.79 \text{ A}$$

$$j_x = j_2$$

$$\boxed{j_x = 2.79 \text{ A}}$$

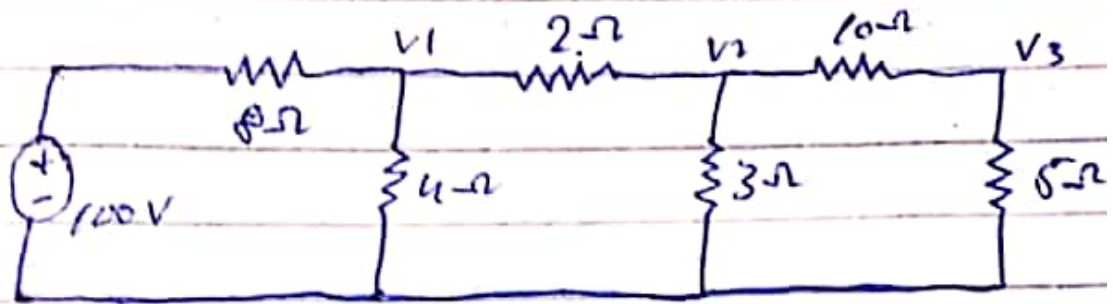i) Superposition Theorem:

First removing the current source and making it an open circuit. Re drawing the circuit



Apply KCL on node 1

$$\frac{-100 + V_1}{8} + \frac{V_1 - V_2}{2} + \frac{V_1}{4} = 0$$

$$\frac{V_1 - 100 + 4V_1 - 4V_1 + 2V_3}{8} = 0$$

$$7V_1 - 4V_2 = +100 \quad \text{--- (1)}$$

Apply KCL on node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 + 53V_2 - 3V_3 = 0 \quad \text{---}$$

Apply KCL on node 3.

$$\frac{v_3 - v_2}{10} + \frac{v_3}{5} = 0$$

$$\frac{v_3 - v_2 + v_3}{10} = 0$$

$$-v_2 + 2v_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) and (2)

$$7v_1 - 4v_2 = 100$$

$$v_1 = \frac{4v_2 + 100}{7} \quad \text{--- (a)}$$

Now $-v_2 + 3v_3 = 0$

$$v_3 = \frac{1}{3}v_2 \quad \text{--- (b)}$$

Putting in eq (2)

$$-30(0.57v_2 + 14.28) - 4v_2 + 2(0.33v_2) = 0$$

$$-17.1v_2 - 428.4 - 4v_2 + 0.60v_2 = 0$$

$$20.44v_2 = -428.4$$

$$v_2 = -20.95$$

Putting in eq (a)

Apply KCL on node 3.

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$\frac{V_3 - V_2 + V_3}{10} = 0$$

$$-V_2 + 2V_3 = 0 \quad \text{--- (3)}$$

Now taking eq (1) and (2)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \quad \text{--- (a)}$$

Now $-V_2 + 3V_3 = 0$

$$V_3 = \frac{1}{3} V_2 \quad \text{--- (b)}$$

Putting in eq (2)

$$30(0.57V_2 + 14.28) - 4V_2 + 2(0.33V_2) = 0$$

$$17.1V_2 - 428.4 - 4V_2 + 0.60V_2 = 0$$

$$20.44V_2 = 428.4$$

$$V_2 = -20.95$$


Putting in eq (a)

$$v_2 = 2.31$$

$$i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = 11.63$$

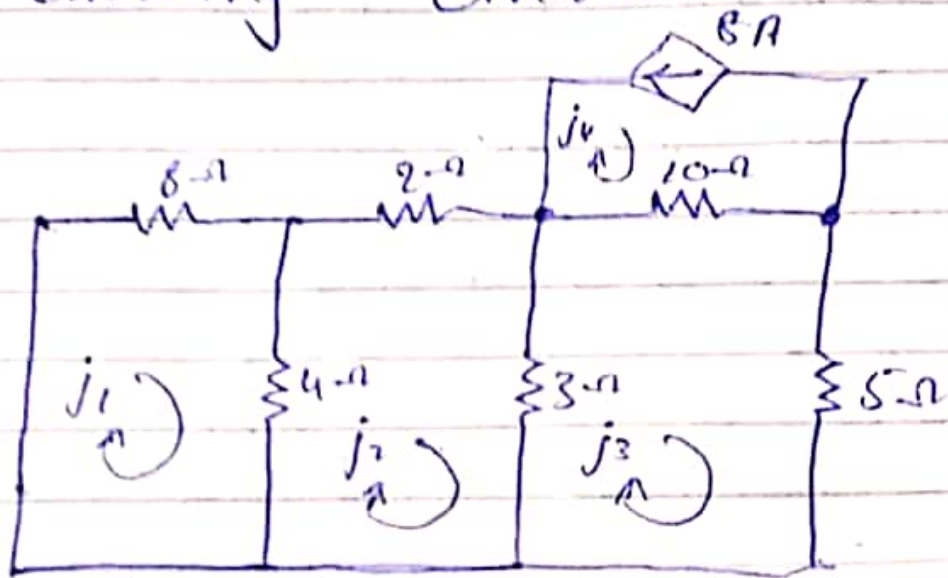Now Removing voltage source and making it short circuit. Re drawing circuit.



$$i_4 = 8A$$

Apply KVL on loop 1:

$$8i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0$$

(1)

Apply KVL on loop 2:

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop 3:

$$10i_3 + 5i_3 + 3i_3 - 2i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \quad \text{--- (a)}$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{3i_2 - 80}{18} \quad \text{--- (b)}$$

$$-4(0.33i_2) + 9i_2 - 3(0.16i_2 - 4.44) = 0$$

$$1.32i_2 + 9i_2 - 0.48i_2 + 13.32 = 0$$

$$j_2 = 1.354$$

Now

$$j_x = j_1 + j_2$$

$$j_x = 1.44 + 1.35$$

$$j_x = 2.79 \text{ A}$$

Result

$$j_x = 2.79 \text{ A}$$

Solution:

Solving by mesh analysis

Apply KVL on i_1

$$4i_1 + 1(i_1 - i_2) = 1$$

$$5i_1 - i_2 = 1 \quad \text{--- (1)}$$

Apply KVL on i_2 :

$$1(i_2 - i_1) + 5i_2 = 2$$

$$-i_1 + 6i_2 = 2 \quad \text{--- (ii)}$$

multiply 5 with eq (2)
So adding with eq (1)

$$5i_1 - i_2 = 1$$

$$-5i_1 + 30i_2 = 10$$

$$29i_2 = 11$$

$$i_2 = 11/29$$

$$i_2 = 0.379$$

putting in eq (1)

$$5i_1 = 1 + 0.379$$

$$i_1 = 0.275 \text{ A}$$