



DIGITAL LOGIC DESIGN

Synchronous Counter
Sir. Muhammad Amin
LAB# 11



HASSAN MEHDI

LAB# 11
Csc-201


SYNCHRONOUS COUNTER

AIM:

Realization of 3-bit synchronous counter design.

PROCEDURE:

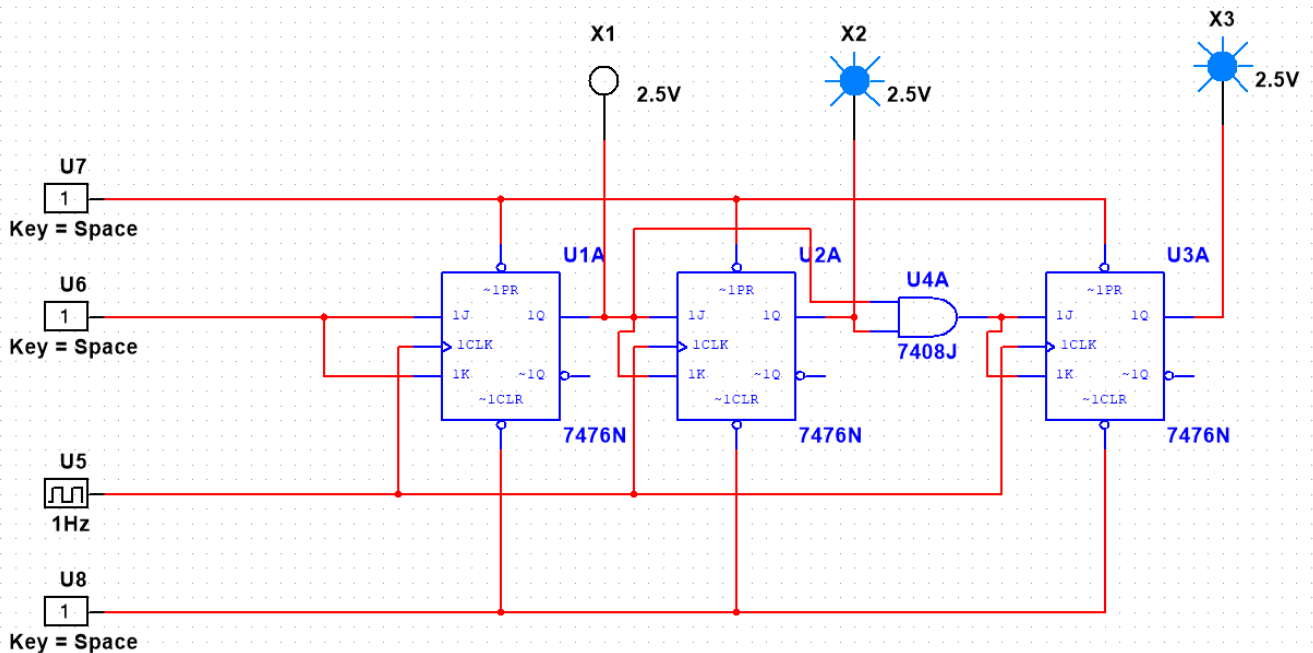- Connections are made as per circuit diagram.
- Clock pulses are applied one by one at the clock I/P and the O/P is observed at QA, QB & QC for IC 7476.
- Verify the Truth table.



CLK	Q ₀	Q ₁	Q ₂
Initial	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (Recycles)	0	0	0

CONCLUSION:

03-bit synchronous counter has been implemented and verified using ICs.