

(1)

Q.1:

Name Monsin Ali

25/8/2020

ID= 13746

electronic devices and circuit.

b)

Total Peak Secondary Voltage.

$$V_p(\text{sec}) = nV_p(\text{Pri})$$

$$= 0.25(50)$$


$$= 0.25(50)$$

$$= 12.5 \text{ V}$$


$$V_p(\text{sec}) = 12.5 \text{ V}$$

(c)

Half of The Secondary

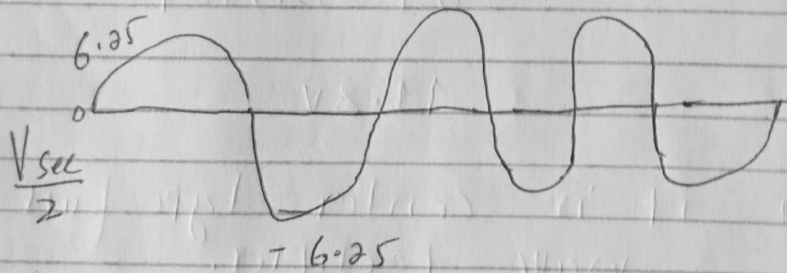

+5-55V

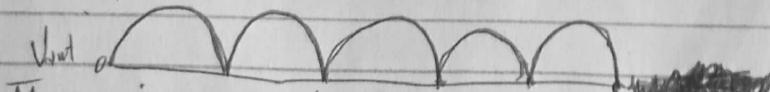

There is 6.25V peak to 0 peak voltage. The out put voltage has a peak value of 6.25-0.7 which is diod drop.

(2)

d) Peak Current Through each diode

$$I_f = \frac{V_p(\text{sec})}{2 R_L}$$

$$= \frac{5.55\text{V}}{10\text{K}\Omega}$$

$$= 0.000555$$

$$= 0.555 \text{ mA}$$

(e)

PIV rating must diode have

$$\text{PIV} = 2 V_p(\text{out}) + 0.7$$

$$= 2 (5.55\text{V}) + 0.7$$

$$= 11.8\text{V}$$

21 (a) it is center type full wave rectifier,

Q5

(3)

(a)

Power Supply filters:

The ripple components of output voltage is removed by placing a filter circuit. The output voltage of rectifier is pulsating in nature. Power supply filter consist of two parts

- 1) ~~Desire~~ Desire Dc components of voltage
- 2) unwanted ripple components

The unwanted components are removed by power supply filters.

In power supply capacitors are used to filter the pulsating Dc output so that constant Dc voltage is supplied to the load.

Filter capacitor reduces the ripple voltage to acceptable level.

In filter circuit capacitor is charged to peak of rectified input voltage during positive portion of voltage. When input become negative, the capacitor begins to discharge to load. The rate of discharge is determined by RC time constant.

The capacitance value for output current (I) and ripple current (dr)

P.10

is

(4)

$$C = \frac{I}{V_{rms} \times 4f}$$

$$\Rightarrow V_{rms} = V \frac{(P-P)}{2} \text{ for } f_{ac}$$


$$\Rightarrow C = \frac{2 \cdot 4f}{V_{rms}}$$

$$\Rightarrow I = DC \text{ load current}$$

$$C = \frac{I \times V_{dc}}{V_{rms} V_m 4} = V_{dc} = \frac{V_m + V_{P-P}}{2}$$

V_m = maximum voltage

V_{P-P} = Peak to Peak ripple voltage

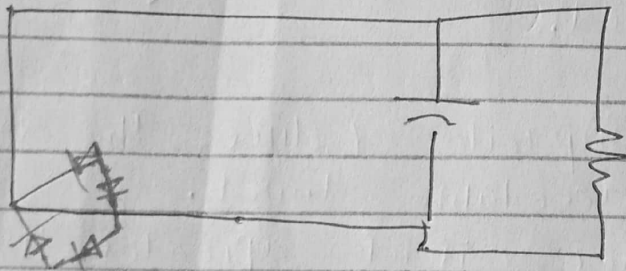

filtering:

Q5

(b)

Formation of P-type and N-type Semiconductors:

Q5:

(5)

(b) The extrinsic P-type Semiconductor is formed when a Trivalent Impurity is added to a pure Semiconductor in a small amount, and as a result, a large number of holes are created in it. A large number of holes are provided in the Semiconductor material by the addition of Trivalent Impurities like

Gallium and Indium.

N-TYPE:

Pentavalent Impurities atoms with 5 valence electrons produce n-type Semiconductor by contributing extra electrons.

When Semiconductor is doped with pentavalent Impurity then n-type Semiconductor is formed.

Q5:

(6)

(c)

Diode limiters

Diode limiter or diode clippers is a wave shaping circuit that takes an input wave form and cuts off its top-half bottom half or both halves together and produce wave form that resembles flattened version of the input. There are two types of clippers.

1) Positive Diode Limiters:

In this diode limiting circuit the diode is forward biased for the diode to become forward bias it must have the ~~same~~ input voltage magnitude greater than $+0.7$ volts.

A voltage bias is added in series with the diode.

Example:


If voltage bias is set 4 volt then the sinusoidal voltage, if the diode anode terminal must be greater than

$$4 + 0.7 = 4.7V$$

to become forward bias any voltage level above is

P.T.O

(7)

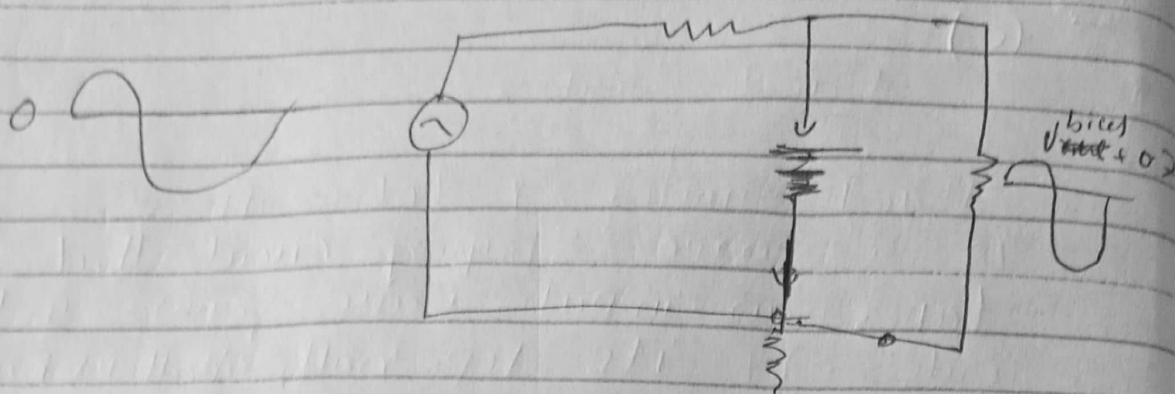


(2) Negative Diode Limiter

When the diode is forward Biased during a negative half of

the cycle and limits it $0.7V$ while allowing the positive half of the cycle is called negative limiter of the circuits

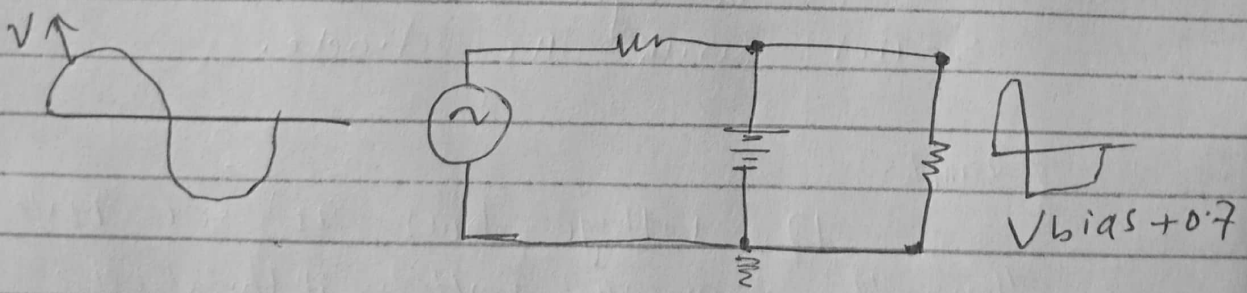the out put wave form is held to a level - bias $-0.7V$



Negative diode limiter

(8)

Q5 d)

Ans.

The capacitor effectively act as a battery in a clamping circuit.

Q5

(e)

Ans. The output frequency of half wave rectifier is same to input frequency,

so if 60Hz sinusoidal voltage is applied then the output frequency will also be 60Hz.

Q5 (f)

Ans. The ripple voltage and load resistance are inversely related to each other

Ripple voltage $\propto \frac{1}{\text{load resistance}}$

if The load resistance is decreased (\downarrow)
the applied voltage will be increased (\uparrow)

(9)

Q5

(9)

Difference b/w diode limiter and diode clamper.

Diode limiter

→ It limits the ~~amplitude~~ amplitude of output voltage
→ Output voltage less than the input voltage.

→ the change of voltage shape.

the shape of voltage changes.

→ if DC level remain same.

Diode clamper,

→ it shifts the DC level of output voltage


→ output voltage is multiple than the input voltage.

→ shape remain same




→ DC level gets shift

10)

Q3

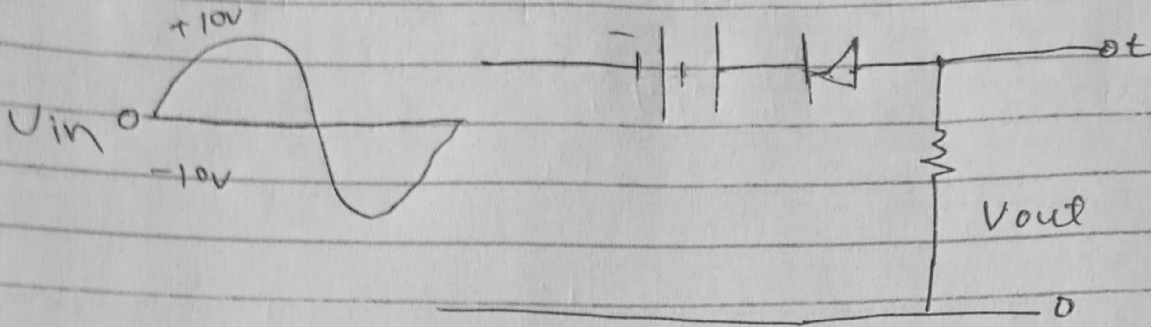

out put wave form of clipper circuit,

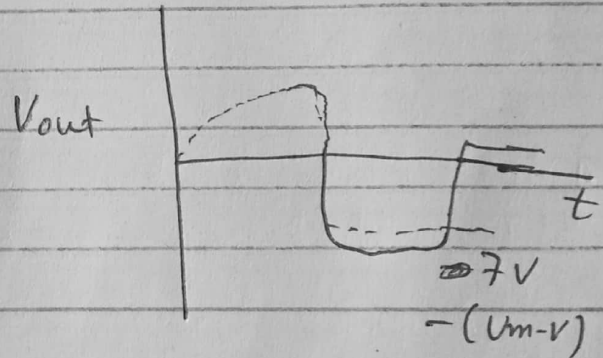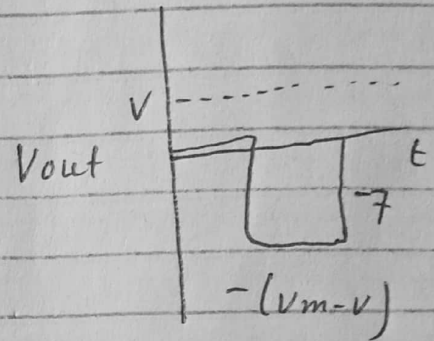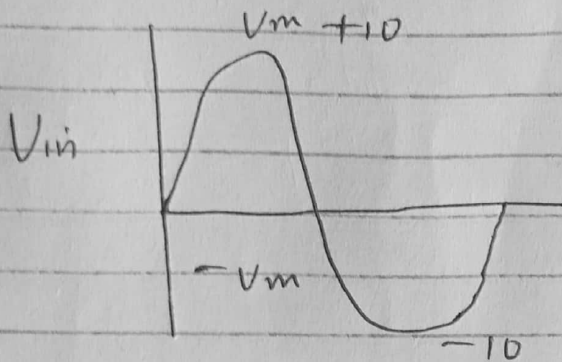

Q No 7

the transformer turn ratio is $n = 0.5$
the primary voltage is $V_p(\text{pri}) = 1.414 \text{ vrms}$
 $= 1.414 (120) = 170 \text{ V}$

the peak secondary voltage is
 $V_p(\text{sec}) = n V_p(\text{pri}) = 0.5(170) = 85 \text{ V}$

The unfiltered peak full wave rectified
voltage is

$$V_p(\text{rec}) = 85 - 1.4 \text{ V} = 83.6 \text{ V}$$

the frequency of a full wave rectifier

voltage is 120 Hz . The approximate
peak to peak ripple voltage at
out put is

$$V_r(\text{PP}) \approx \left(\frac{1}{f R_L C} \right) V_p(\text{rect})$$
$$= \frac{1}{120 \text{ Hz} (3.3 \text{ k}\Omega) 100 \mu\text{F}} \cdot 83.6 \text{ V}$$

$$V_r(\text{PP}) = 2.11 \text{ V}$$

the approximate dc value of the out put
voltage determine as follows

$$V_{DC} = \left(1 - \frac{1}{2f R_L C} \right) V_p(\text{rect})$$
$$= \frac{1 - 1}{(240 \text{ Hz})(3.3 \text{ k}\Omega)(100 \mu\text{F})} \cdot 83.6$$

p.to

$$= \left(1 - \frac{1}{39.6}\right) 83.6$$

$$V_{DC} = 81.48V$$

$$V_{DC} = 81.48V$$

The resulting ripple factor is

$$\gamma = \frac{V_r (PP)}{V_{DC}} = \frac{2.11}{81.48} = 0.026$$

The % ripple is = 2.62%

Q:4

