

Name: Ali Raza


ID No: 16309

Subject: linear Circuit Analysis

Date: 24 June, 2020

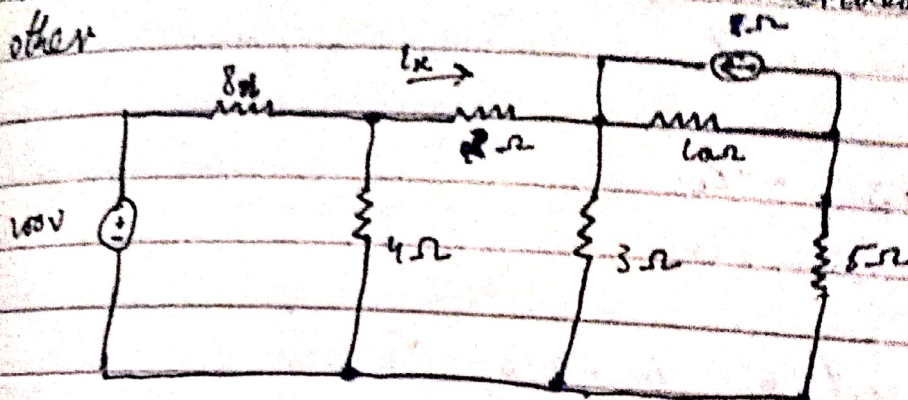Question no: 1

- Find the value of i_x for the circuit using
- 1) Nodal analysis
 - 2) Mesh Analysis
 - 3) Superposition analysis
 - 4) Compare the number of steps and degree of easiness of all the three methods with each other



Solution:

Applying KCL on node 1

$$\frac{V_1 - 100}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 - 100 + 2V_1 + 4V_2 - 4V_1 = 0$$

$$7V_1 - 4V_2 = 100 \rightarrow (1)$$

Applying KCL on node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 8$$

$$30V_2 - 30V_1 + 20V_2 + 3V_2 - 3V_3 = 80$$

$$-30V_1 + 53V_2 - 3V_3 = 80 \rightarrow (2)$$

Applying KCL on node 3

$$\frac{V_2 - V_1}{10} + \frac{V_2}{5} = 7$$

$$\frac{V_2 - V_1}{10} + 2V_2 = -8$$

$$-V_1 + 3V_2 = -80 \rightarrow (2)$$

Taking eq (1)

$$7V_1 = 4V_2 + 140 \rightarrow (a)$$

Taking eq (2)

$$-V_1 + 3V_2 = -80$$

$$V_1 = \frac{V_2 - 80}{3} \rightarrow (b)$$

Putting eq (a) and (b) in eq (2)

$$-30(0.5V_1 + 14.28) + 53V_2 - 3(0.33V_2 - 26.67) = 480$$

$$-17.1V_1 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_1 = 828.89$$

$$V_1 = 828.89$$

$$34.91$$

$$V_2 = 20.31$$

Putting in eq (a)

$$V_2 = \frac{4(20.31) + 140}{7}$$

$$V_2 = 25.89$$


$$I_x = \frac{V_1 - V_2}{2}$$

$$= \frac{25.89 - 20.31}{2}$$

$$I_x = 2.79A$$

MESH ANALYSIS

(2)

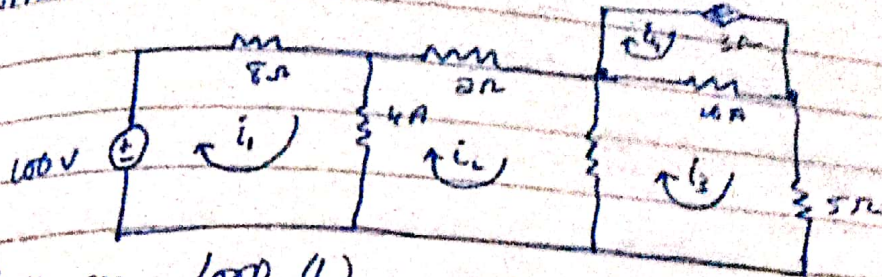

Applying KVL on loop (1)

$$8i_1 + 4(i_2 - i_1) = 100$$

$$8i_1 + 4i_2 - 4i_1 = 100$$

$$4i_1 + 4i_2 = 100 \rightarrow (1)$$

Applying KVL on loop (2)

$$2i_2 + 4(i_2 - i_1) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_1 + 3i_3 - 3i_2 = 0$$

$$-4i_1 + 4i_2 + 3i_3 = 0 \rightarrow (2)$$

Applying KVL on loop (3)

$$3(i_3 - i_2) + 10(i_3 - i_4) - 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

As $i_4 = 4$

$$= 3i_2 + 18i_3 = -80 \rightarrow (3)$$

Taking eq (1)

$$i_2 = \frac{100 - 4i_1}{4} \quad (a)$$

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 - 80}{18} \rightarrow (b)$$

Putting eq (a) and (b) on eq (2)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$

$$-1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.32 = 0$$

$$7Ri_2 = 120$$

$$\Rightarrow i_2 = 20/7.2$$


$$\Rightarrow i_2 = i_x$$

$$\Rightarrow i_x = 2.79 \text{ A}$$

$$\Rightarrow i_x = 2.79 \text{ A}$$

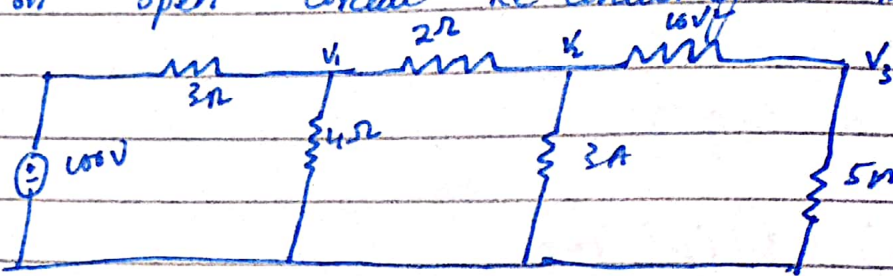iii) SUPERPOSITION THEOREM:

first we remove the current and then making it an open circuit re-drawing the circuit



Applying KCL on node 1

$$-\frac{100 + V_1}{3} + \frac{V_1 - V_2}{4} + \frac{V_1}{4} = 0$$

$$V_1 - \frac{100 + 4V_1 - 4V_2 + 2V_3}{8} = 0$$

$$7V_1 - 4V_2 + 100 \rightarrow (1)$$

Apply KCL on node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

$$-30V_1 + 53V_2 - 3V_3 = 0$$

Apply KCL on node 3

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

$$V_1 - V_2 + V_3 = 0$$

$$-V_2 + 2V_3 = 0 \rightarrow (2)$$

Now taking eq (1) and (2)

$$7V_1 - 4V_2 = 100$$

$$V_1 = \frac{4V_2 + 100}{7} \rightarrow (3)$$

$$\text{Now } -V_2 + 3V_3 = 0$$

$$V_3 = \frac{1}{3}V_2 \rightarrow (1)$$

Putting in eq (2)

$$-20(0.57V_2 + 4 \cdot 28) - 4V_2 + 2(0.33V_2) = 0$$

$$-11.4V_2 - 11.2 + 0.66V_2 = 0$$

$$V_2 = -20.95$$

Putting in eq (1)

$$V_3 = 2.31$$

$$i_1 = \frac{2.31 + 20.95}{2}$$

$$i_2 = 11.63$$


Putting in eq (1)

$$i_2 = 2.31$$

$$i_1 = \frac{2.31 + 20.95}{2}$$

$$i_1 = 11.63$$

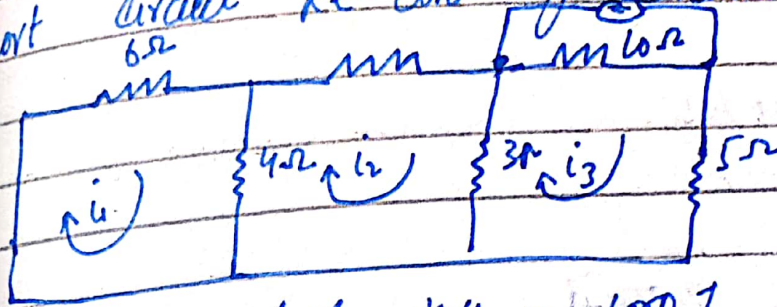by removing voltage source and making it short circuit Re-drawing circuit



$i_4 = 8A \Rightarrow$ apply KVL on loop 1

$$8i_1 + 4(i_1 - i_2) = 0$$

$$8i_1 + 4i_1 - 4i_2 = 0$$

$$12i_1 - 4i_2 = 0$$

$$3i_1 - i_2 = 0 \rightarrow (1)$$

Applying KVL on loop 2

$$2i_2 + 3(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$2i_2 + 3i_2 - 3i_3 + 4i_2 - 4i_1 = 0$$

$$-4i_1 + i_2 - 3i_3 = 0 \rightarrow (2)$$

Apply KVL on loop 3

$$10i_3 + 5i_3 + 3i_3 - 3i_2 + 8(10) = 0$$

$$-3i_2 + 18i_3 = -80 \rightarrow (3)$$

Taking eq (1)

$$3i_1 - i_2 = 0$$

$$i_1 = 0.33i_2 \rightarrow (4)$$

Taking eq (3)

$$-3i_2 + 18i_3 - 80$$

$$i_3 = \frac{3i_2 - 80}{18} \rightarrow (6)$$

$$-4(0.33i_2) + 9i_2 - 3(0.8i_2 - 4.44) = 20$$

$$-1.32i_2 + 9i_2 - 2.4i_2 + 13.32 = 20$$

$$i_2 = 1.354$$

Now $i_x = i_1 + i_2$

$$i_x = 1.44 + 1.35$$

$$i_x = 2.79 \text{ A}$$

$$\boxed{\text{Result } = i_x = 2.79 \text{ A}}$$

Compare the number of step and degree of easiness of all the three method with each other.

Solution:

The number of steps in nodal and mesh analysis are almost equal but in superposition the number of steps are almost of mesh and nodal analysis.

Degree of easiness:

According to opinion mesh analysis is easier than nodal analysis and superposition theorem.

Question # 2

Consider the 200 ohms resistor in figure as load resistor and develop

- i) Thevenin equivalent circuit
- ii) Norton equivalent circuit
- iii) Find out what value of Thevenin resistance should be used to deliver maximum power to the load


Thevenin's and Norton's Equivalent Circuit Tutorial :-

Thevenin's Theorem states that we can replace entire network by an equivalent circuit that contains only an independent voltage source in series with an impedance (resistor) such that the current-voltage relationship at the load is unchanged.


Norton's Theorem is identical to Thevenin's Theorem except that the equivalent circuit is an independent current source in parallel with an impedance (resistor)

Therefore, the Norton's equivalent is a source transformation of the Thevenin equivalent circuit.


original circuit

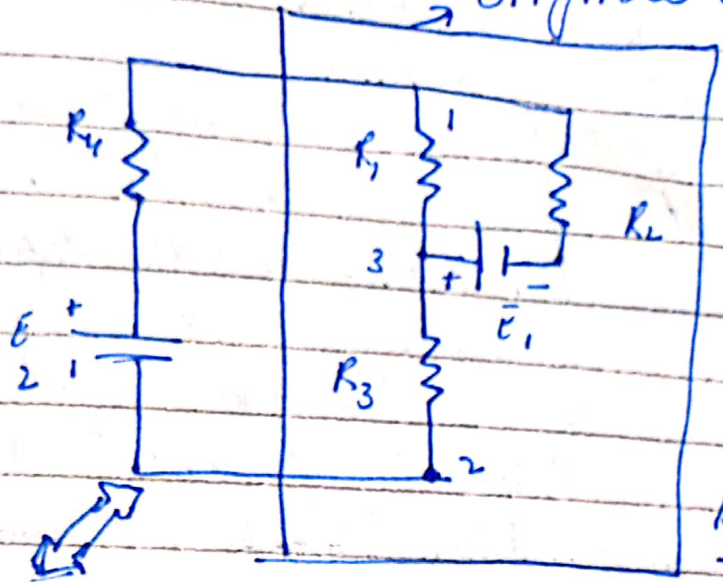

Thevenin's Equivalent Circuit

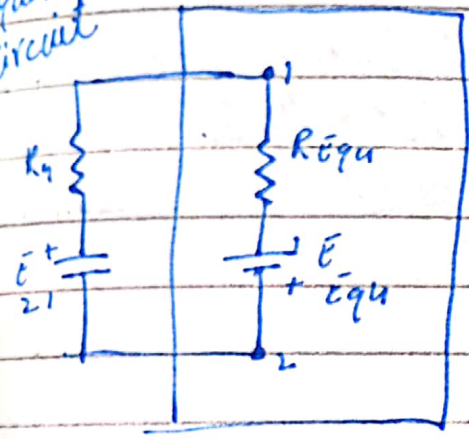

They are interchangeable

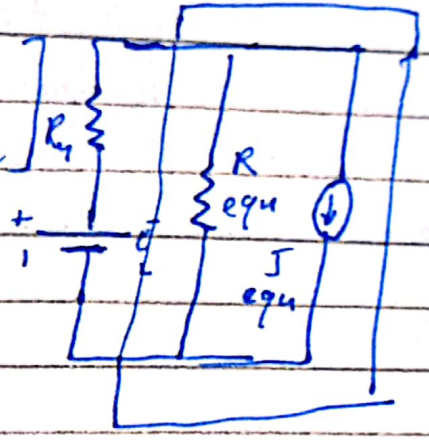

How to find Thevenin's Equivalent Circuit?

Norton's Equivalent Circuit


If the Circuit | You should do

Resistors and independent sources	<ol style="list-style-type: none"> 1) Connect an open circuit b/w a and b 2) Find the voltage across the open circuit which is $V_{oc} = V_{oc} = V_{th}$ 3) Deactive the independent sources voltage source \hat{I} open circuit 4) Find R_{Th} by circuit resistance reduction.
-----------------------------------	--

Resistors and dependent sources or independent sources

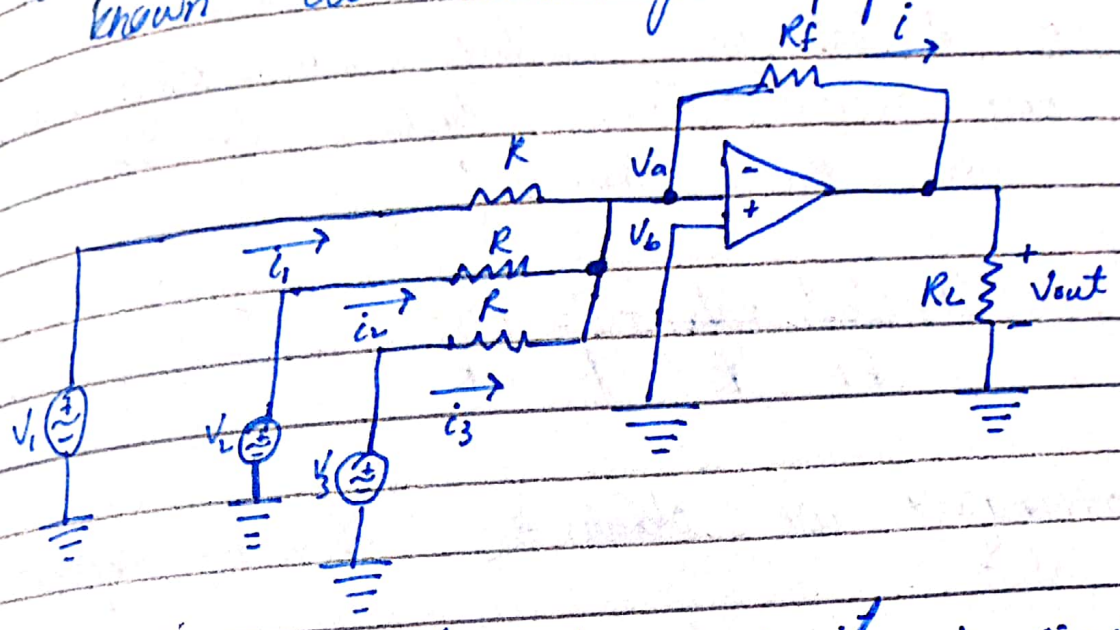- 1) Connect an open circuit between a and b.
 - 2) Find the voltage across the open circuit which is V_{oc} . $V_{oc} = V_{th}$ if there are both dependent and independent sources.
 - 3) Connect a short circuit between a and b.
 - 4) Determine the current between a and b.
 - 5) $R_{th} = V_{oc} / I_{ab}$
- If there are only dependent sources.
- 3) Connect 1 Ampere current source flowing from terminal b to a. $I_t = [1A]$
 - 4) Then $R_{th} = V_{oc} / I_t = V_{oc} / 1$

Q#3 Obtain an expression for v_{out} of v_1, v_2 , and also v_3 for the op amp circuit in figure known as summing amplifier.



We first note that this circuit is similar to the inverting amplifier circuit. & again, the goal is to obtain an expression for v_{out} (which in this case appears across a load resistor R_L) in terms of the inputs (v_1, v_2 and v_3)

Since no current can flow into the inverting input terminal we, can write

$$i_2 = i_1 + i_2 + i_3$$

Therefore we can write the following equation at the node labeled v_a :

$$0 = \frac{v_a - v_{out}}{R_f} + \frac{v_a - v_1}{R} + \frac{v_a - v_2}{R} + \frac{v_a - v_3}{R}$$

This equation contains both v_{out} and the input voltages but unfortunately it also contains the nodal voltage v_a . To remove this unknown quantity from our expression, we need to write an additional equation that relates

V_a to V_{out} the input voltages R_f and/or R .
 At this point we remember that we have
 not yet used ideal op amp rule 2 and
 that we will almost certainly require
 the use of both rules when analysing an
 op amp circuit. Thus since $V_a = V_b = 0$, we
 can write the following

$$0 = V_{out} + \frac{V_1}{R_f} + \frac{V_2}{R} + \frac{V_3}{R}$$

Re-arranging, we obtain the following expression
 for V_{out}

$$V_{out} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

In the special case where $V_2 = V_3 = 0$ we
 see that our result agrees with eq (8).
 which was derived for essentially the
 same circuit