

**Department of Electrical Engineering**  
**Assignment**  
**Date: 14/04/2020**

**Course Details**

<b>Course Title:</b>	Power Electronics	<b>Module:</b>	
<b>Instructor:</b>	Engr Shayan Tariq Jan	<b>Total</b>	30
		<b>Marks:</b>	

**Student Details**

**Name:** Muhammad Saqib Khalil \_\_\_\_\_ **Student ID:** 13342 \_\_\_\_\_

Note: Plagiarism of more than 20% will result in negative marking.


Similar answers of students will result in cancellation of the answer for all parties.

Q1	(a)	An appliance circuit has a R-L connected in series with a diode. After some time, modification is done to the circuit and a free-wheeling diode is added in parallel to the R-L. Will it have any impact on the performance and output of the circuit. Back your answer with before & after data, facts and figures. Does adding a free-wheeling diode in parallel to a R-C circuit have the same effect, different effect or no effect.	Marks 7
			CLO 1
	(b)	A Power Mosfet is connected in a circuit. The Drain to Source voltage, $V_{DS} = (\text{Last 2 digits of your student ID}) \text{ V}$ and Threshold Voltage, $V_T = (\text{Last 1 digit of your student ID}) \text{ V}$ . What is the minimum Gate to Drain Voltage, $V_{GS}$ required for the P.Mosfet to be in saturation mood.	Marks 3
			CLO 1
Q2	(a)	A Power Electronics appliance of 500W, 220V, 500KHz rating is using a Power Mosfet for switching purpose. If the P.Mosfet is replaced with a Power Bipolar Junction Transistor what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
	(b)	In the above appliance (Q2.a) if the P.Mosfet is replaced with a Silicon Controlled Rectifier what effect will it have on the performance, losses and efficiency of the appliance. Will any other changes to the circuit be required? Back your reasons with valid data, facts and figures.	Marks 5
			CLO 1
Q3	(a)	The bipolar transistor in the Figure below is specified to have $\beta_F$ in the range of 8 to 40. The load resistance, $R_C = (\text{Last 2 digits of your student ID}) \Omega$ .	Marks 10

The dc supply voltage,  $V_{CC} = (\text{Last 3 digits of your student ID}) \text{ V}$  and the input voltage to the base circuit,  $V_B = 10 \text{ V}$ .  
If  $V_{CE} = (\text{First digits of your student ID}) \text{ V}$  and  $V_{BE} = 1.5 \text{ V}$ , find

- The mode of operation of the transistor
- the value of  $R_B$  that results in saturation with an ODF of 5,
- the  $\beta_{\text{forced}}$ ,
- the power loss,  $P_T$  in the transistor.

CLO 1

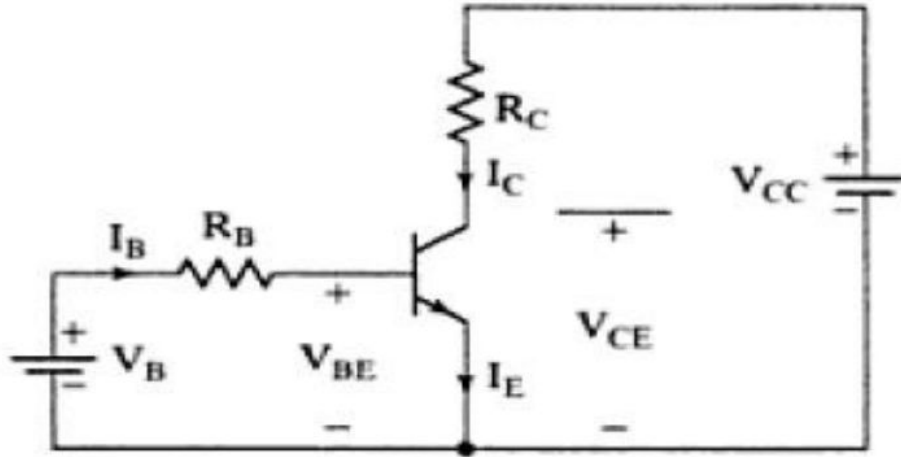

Name : M. SAQIB KHALK


ID : 13342

Subject : Power Electronics


Semester : 8th

Submitted to : Engr. Shayan Tariq Jan

## Question #1 (a)

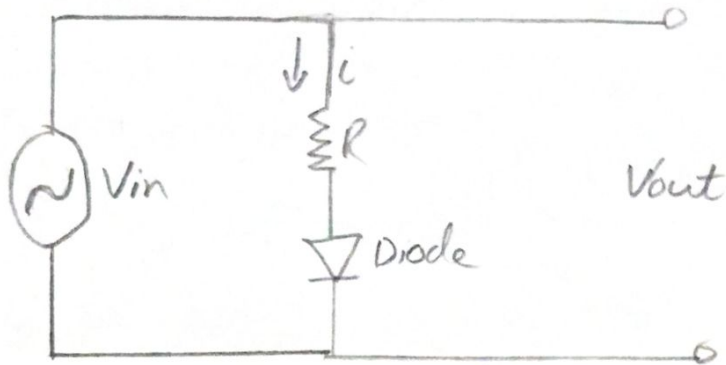

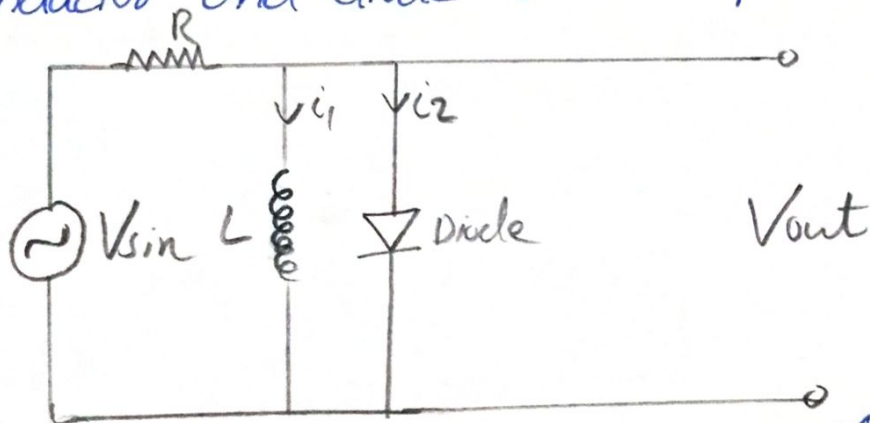When free wheeling diode is connected in series with RL circuit so, the flow of current through circuit will depend on forward & reverse bias of diode. The output voltage will be the combine voltage drop of inductor and diode barrier potential (0.7V)



When diode is connected in parallel of RL circuit so current flow will be depend of forward/Reverse bias of diode, current will flow that path which have minimum resistance. Output voltage will be only diode barrier potential (0.7V)

connecting free wheeling diode in parallel of RL circuit will have different effect then connecting the free wheeling diode is series of RL circuit.

Q.1 (b)

Given data

$$V_T = 2V$$

$$V_{DS} = 42V$$

$V_{GS}$  in saturation mode?

For saturation mode


$$V_{DS} = V_{GS} - V_T$$

$$V_{GS} = V_{DS} + V_T$$

$$V_{GS} = 42 + 2$$


$$\boxed{V_{GS} = 44V}$$

Q#2 (a)

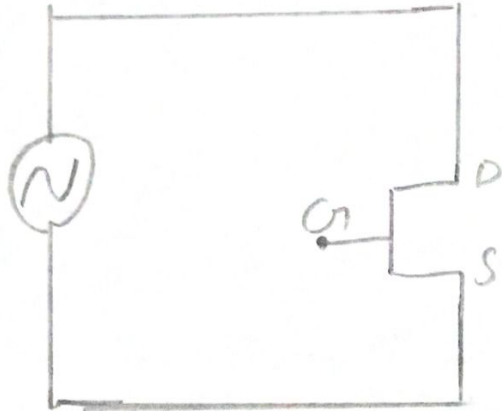


When power MOSFET is connected in power electronics circuit, it has fast switching, high efficiency and low losses.

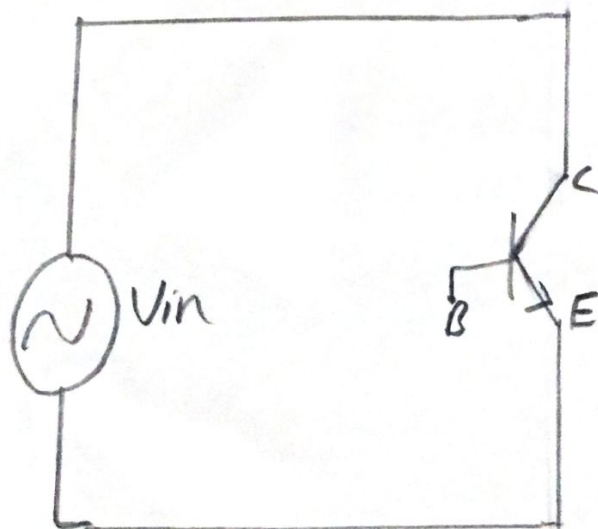When power MOSFET is replaced by power bipolar junction transistor, its switching speed decreases, efficiency decreases and its losses increase, as power bipolar junction transistor is mainly used for amplification.



Q#2 (b)

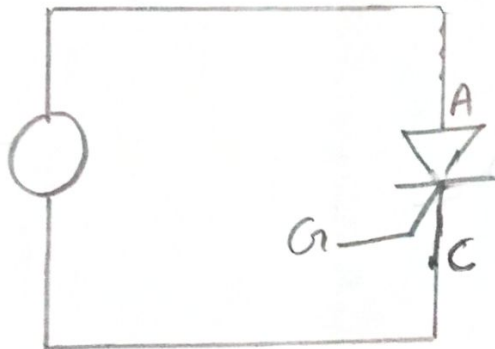When power bipolar junction transistor is replaced by silicon controlled rectifier so, on output we get controlled output voltage and switching



In case of silicon controlled rectifier we get fast switching than power BJT but less than power MosFET, variable efficiency and low losses

Q.3

(5)

18342

Given data

$$V_{CC} = 342V$$

$$V_B = 10V$$

$$V_{CE} = 1V$$

$$V_{BE} = 1.5V$$

$$R_C = 42\Omega$$

Part (a)

Saturation Mode

Part (b)

$$R_B = ?$$

$$I_{CS} = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C}$$

$$= \frac{342 - 1}{42}$$

$$= \frac{341}{42}$$



(6)

As

$$I_{BS} = \frac{I_{CS}}{\beta_{F(\min)}}$$

$$= \frac{8.1}{8}$$

$$\boxed{I_{BS} = 1.0125}$$

when know that

$$I_B = ODF \times I_{BS}$$

$$= 5 \times 1.0125$$

$$\boxed{I_B = 5.0625 \text{ A}}$$

we know that

$$R_B = \frac{V_B - V_{BE}}{I_B}$$

$$= \frac{10 - 1.5}{5.0625}$$

$$\boxed{R_B = 1.6790 \Omega}$$

c)

$$B_{force} = \frac{I_{cs}}{I_B}$$

$$= \frac{8.11}{5.0625}$$

$$B_{force} = 1.6019 \text{ A}$$

d)

$$P_T = ?$$

As

$$P_T = V_{BE} I_B + V_{CE} I_C$$

$$= \cancel{(1.5)(2.5)} + \cancel{(1)(8.11)}$$

$$= V_{BE} I_B + V_{CE} I_C$$

$$= (1.5)(5.0625) + (1)(8.11)$$

$$= 7.59375 + 8.11$$

$$P_T = 15.70375 \text{ watt}$$