

Course title :- Electrical Network  
analysis


Module :- 4<sup>th</sup>

Instructor :- Dr. Shahryar Saifque

Name :- Syed Muhammad Raza

Student ID :- 14620

Student Signature :-

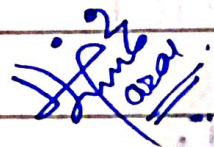

Date :- 13<sup>th</sup> April, 2020


Question No. 1 :-

The switch in figure has been in position 1 for a long time.

Switch moves to B.

Determine  $v(t)$  for  $t > 0$  & calculate its value at  $t = 8\text{ s}$ .

figure :-

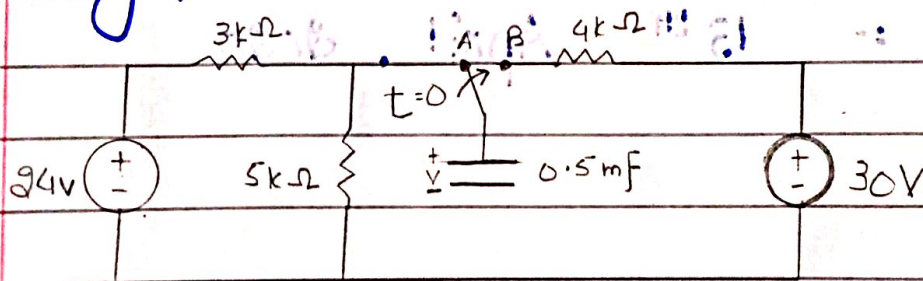

Solution :-

for  $t < 0$  :

The switch is at position A. The Capacitor

acts like an open circuit to dc, but  $V$  is the same as the voltage across  $5\Omega$  resistor. Hence the voltage across the capacitor just before  $t=0$  is obtained by voltage division as,

$$V(0) = \frac{5}{5+3} (24) = 15V$$

As the capacitor cannot change instantaneously.

$$V(0) = V(0) = 15V.$$

For  $t > 0$ :

The switch is in position B. The

$$R_{in} = 4k\Omega$$

Time constant is,

$$\tau = R_{in} C = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\tau = 2s$$

Since the Capacitor acts like an open circuit to dc at steady state,

$$V(\infty) = 30V$$

Thus

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$= 30 + (15 - 30) e^{-t/2}$$

$$= (30 - 15 e^{-0.5t}) V$$

At  $t = 2$  :

$$V(2) = 30 - 15 e^{-2/2}$$

$$= 30 - 15 e^{-1}$$

$$V(2) = 24.48 V$$

At  $t = 8$

$$V(8) = 30 - 15 e^{-8/2}$$


$$= 30 \cdot 15 e^{-4}$$

$$V(8) = 29.72$$

Question No :- 2

Determine the inductor current for both  $t > 0$  and  $t < 0$  for the circuit.

Figure :-

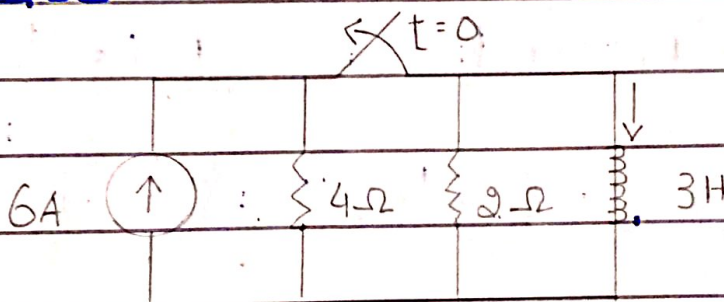

Solution :-

For  $t < 0$  :

The switch is closed and inductor acts as short circuit.

Therefore inductor current

$$i = 6A$$

For  $t > 0$  :

The switch is opened  
and time constant  
 $\tau = L/R$

$$\tau = 3/2$$

Now the inductance  
current  $i(t) = e^{-t/\tau}$


$$i(t) = 6e^{-t/3/2}$$

$$i(t) = 6e^{-2t/3} u(t) A$$

Question No : 5

find  $v(t)$  and  $i(t)$  in  
the circuit in  
figure

Figure :-

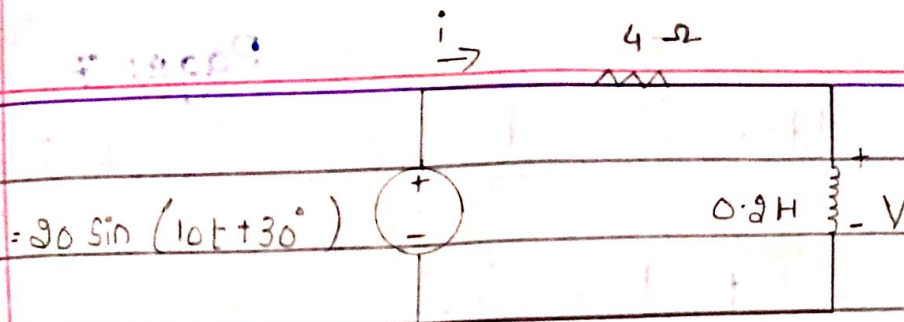

Solution :-

For  $i(t)$   
From the voltage source

$$V_s = 20 \sin(10t + 30^\circ) \text{ V}$$

$$V_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V}$$

$$V_s = 20 \cos(10t - 60^\circ) \text{ V}$$

$$V_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 10 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2 \text{ H} = j \times 10 \times 0.2$$

$$0.2 \text{ H} = j 2 \Omega$$

Given circuit can be represented as :

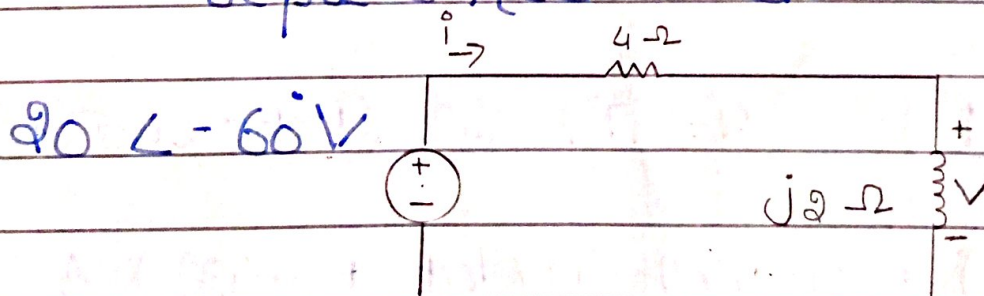

From the above circuit,

$$Z = 4 + j2 \Omega$$

Hence the current  $i(t)$  is

$$i = \frac{20 \angle -60^\circ}{4 + j2}$$

$$i = \frac{20 \angle -60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$

$$i = \frac{20 \angle -60^\circ}{4.472 \angle 26.57^\circ}$$

$$i = 4.472 \angle -86.57^\circ$$

Converting this into domain,

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$



For  $V(t)$ :

From the circuit voltage across the inductor is,

$$V = j\omega \times i$$

$$V = j\omega \times (4.472 \angle 86.57^\circ)$$

Converting polar form to rectangular form we get;

$$V = j\omega \times (0.26756 - j4.464)$$

$$V = 8.928 + j0.53512$$

Converting rectangular form to polar form

$$V = (\sqrt{8.926^2 + (0.53512)^2}) \angle \tan^{-1}\left(\frac{0.53512}{8.928}\right)$$

$$V = 8.944 \angle 3.4^\circ \text{ V}$$

Converting this into time domain

$$v(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(10t + 93.4^\circ) \text{ V}$$

Question No 3 :

A series RLC circuit is described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

find the response

when  $L = 0.5 \text{ H}$ ,  
 $R = 4 \Omega$  and  $C = 0.2 \text{ F}$ .

Let  $i(0) = 1 \text{ A}$ ,  $\frac{di(0)}{dt} = 0$

Solution :-

The step response of the branch voltage of the given RLC circuit is described by;

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by  $L$  ;

$$\frac{d^2 i}{dt^2} + R \frac{di}{L dt} + \frac{i}{LC} = \frac{10}{L}$$

Multiplying by  $\frac{L}{L}$  ;

$$\frac{d^2 i}{dt^2} + R \frac{di}{L dt} + \frac{i}{LC} = \frac{10L}{L}$$

As  $C = 0.2 F$ , thus ;

$$\frac{d^2 i}{dt^2} + R \frac{di}{L dt} + \frac{i}{LC} = 20$$

Substitute ;

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \dots (i)$$

The general form for source-free RLC is

given by,

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = I_s \dots (2)$$

Comparing 1 and 2 we get,

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \rightarrow (4)$$

$$\frac{I_s}{LC} = 20 \rightarrow (5)$$

From (3),  $\alpha$  is given by;

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/sec} \rightarrow (6)$$

The natural frequency  $\omega_0$  is given by;

Substitute  $t = 0$ ;

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute the values;

$$(-4 + \sqrt{6}) A_1 + (-4 - \sqrt{6}) A_2 = 0 \rightarrow (11)$$

Solving (10) and (11) simultaneously

$$A_1 = -1.316$$

$$A_2 = 0.316$$

Substitute in (9)

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t}$$

Question No 4 :-

A series RLC circuit has

$$R = 100 \Omega$$

$$L = 240 \text{ H}$$

$$C = 10 \text{ mF}$$

If the input voltage is  $v(t) = 10 \cos 2t$ , find the current flowing through the circuit.

Solution :-

The input voltage is,

$$v(t) = 10 \cos 2t \text{ V}$$

Amplitude =  $V_m = 10 \text{ V}$

Angular frequency =  $2 \text{ rad/s}$

Phase angle,  $\phi = 0^\circ$

So

Phasor for this voltage  $v(t)$ :

$$v(t) = 10 \angle 0^\circ \text{ V}$$

Now for inductive reactance

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

From (4)

$$\omega_0 = 10 \text{ rad/sec} \rightarrow (7)$$

From (6) and (7):

$\therefore$  The circuit is overdamped  $\because \alpha > \omega_0$

The root of the characteristic equation are given by;

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 + \sqrt{4^2 - 10^2}$$

$$= -4 + \sqrt{6} \text{ rad/sec}$$

And,

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$= -4 - \sqrt{4^2 - 10^2}$$

$$= -4 - 16 \text{ rad/sec}$$

From (5), the steady current is given by

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.8 = 8A \rightarrow (8)$$

The current for overdamped is given by ;

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

Substitute  $t = 0$  :

$$i(0) = I_s + A_1 + A_2$$

Substitute :

$$1 = 8 + A_1 + A_2$$

Thus,

$$A_1 + A_2 = -1 \rightarrow (10)$$

From 9, find  $\frac{di(t)}{dt}$ ,

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$



$$X_L = \omega L$$

So  $\omega = 2 \text{ rad/s}$ ,  $L = 240 \text{ H}$

$$X_L = \omega L$$

$$X_L = (2)(240)$$

$$X_L = 480 \Omega$$

Now for Capacitive reactance,

$$X_C = \frac{1}{\omega C}$$

$\omega = 2 \text{ rad/s}$ ,  $C = 10 \text{ mF}$

$$\frac{1}{2(10 \times 10^{-3})}$$

$$\frac{1}{2 \times 10^{-2}}$$

$$\frac{1 \times 10^2}{2}$$

$$X_C = 50 \Omega$$

Now for impedance ;

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, X_L = 480 \Omega, X_C = 50 \Omega$$

Putting in equation

$$Z = (100 + 480 - 50) \Omega$$

$$Z = (100 + j430) \Omega$$

Represent "Z" in Phasor form

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left( \frac{430}{100} \right)$$

$$= \sqrt{10,000 + 184,900} \angle \tan^{-1} (4.3)$$

$$= \sqrt{194,900} \angle \tan^{-1} (4.3)$$

$$Z = 441.47 \angle 76.90^\circ \Omega$$

Now for current flowing in the circuit ;  $\mathcal{O}$

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ, \quad Z = 441.47 \angle 76.90^\circ \Omega$$

Putting in equation

$$i = \frac{10 \angle 0^\circ \text{ V}}{441.47 \angle 76.90^\circ \Omega}$$

$$\tilde{i} = \frac{10}{441.47} \angle [0 - 76.90^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.90^\circ \text{ A}$$

$$= 22.6 \angle -76.90^\circ \text{ mA}$$

So, the general expression for "i"

$$i = 22.6 \cos(\omega t - 76.90^\circ) \text{ mA} .$$