

Department of Electrical Engineering

Assignment

Date: 24/06/2020

Course Details

Course Title: Electronic Circuit Design Module: 04
Instructor: _____ Total Marks: 50

Student Details

Name: _____ Student ID: _____

Q1.	(a)	Discuss the darlington connection for multistage amplifiers.	Marks 05+10
	(b)	The input of a certain regulator increases by 4.5 V. As a result, the output voltage increases by 0.062 V. The nominal output is 40 V. Evaluate the line regulation in both % and in %/V	CLO 2
Q2.		Explain Colpitts and Hartley oscillators.	Marks 10 CLO 2
Q3.	(a)	Describe the idea behind class B amplifiers.	Marks 06+06
	(b)	Explain the types of voltage regulators and their purposes.	CLO 2
Q4.		Explain the working of Flash ADC.	Marks 05 CLO 2
Q5.		Differentiate between the following:	Marks
	(a)	Low pass & high pass filters	04+04
	(b)	Active and passive filters	CLO 2

①

Name: Mazrat Bilal

ID: 14622

Course Title: Electronic circuit Module: 4th
Design

Instructor: eng Mujtaba
Insan Sir

Date: 24/06/2020

Department: electrical Engineering

ii ii ii ii ii ii

Q No 1a):- Discuss the darlington connection for multistage amplifiers.

Ans:- The main feature of Darlington connection of amplifiers is that the composite transistor acts as a single unit with a current gain that is the product of the current gains of the individual transistors. It provides high current gain than a single BJT.

The connection is made using two separate transistors having current gains of B_1 and B_2 .

So the current gain is

(2)



$$\beta_D = \beta_1 \beta_2$$

If $\beta_1 = \beta_2 = \beta$

The Darlington connection provides a current gain of

$$\beta_D = \beta^2$$

Circuit diagram :-

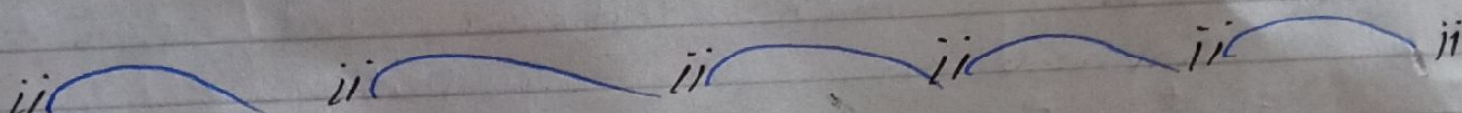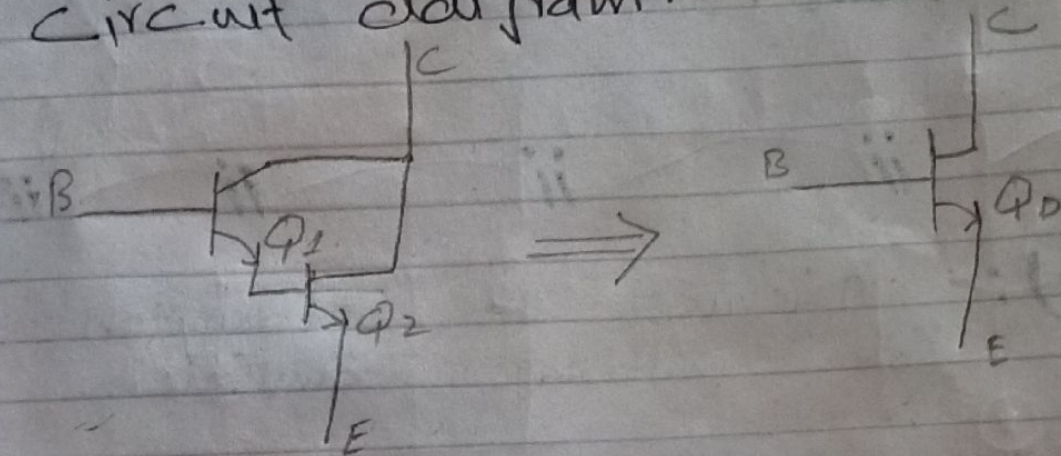


Q No 2 :- Explain Colpitts and Hartley oscillators.

Colpitts oscillators :-

A Colpitts oscillator is invented in 1918 by American engineer Edwin H. Colpitts. The Colpitts oscillator is one of a number of designs for LC oscillator. It is the electronic oscillator that uses a combination of inductor (L) and capacitor (C).

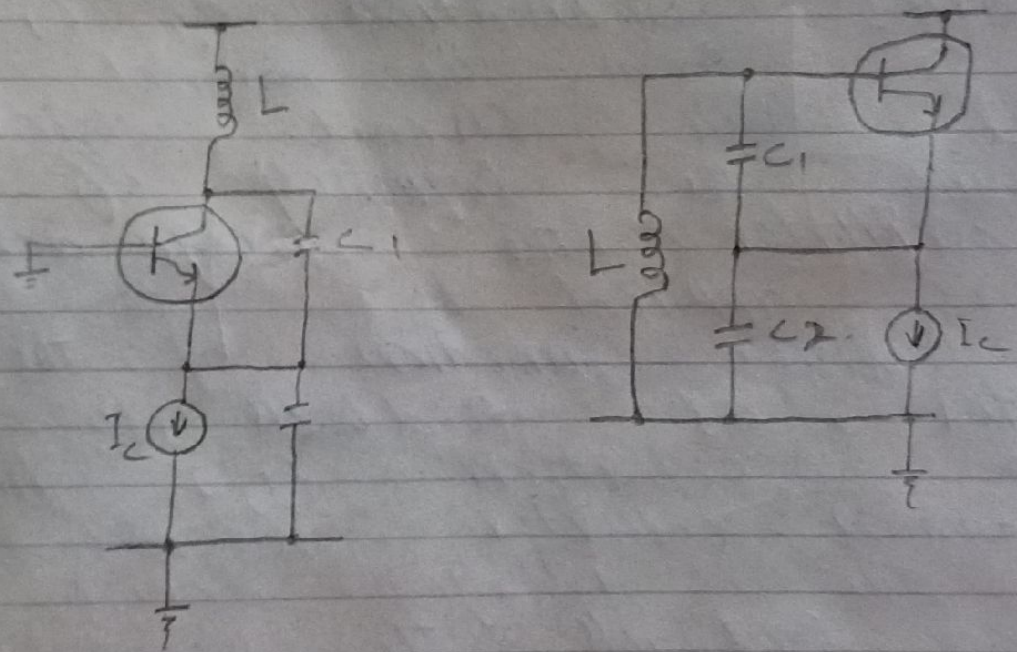and capacitor (C) to produce an oscillation at a certain frequency. The distinguishing feature of the Colpitts oscillator is that the feedback for the active device is taken from a voltage divider made of two capacitors in series across the inductor.



Common-base Colpitts biasing oscillator

Common collector Colpitts oscillator.

The Colpitts circuit, like other LC oscillators consist of a gain device with its output connected to its input in a feedback loop containing a parallel LC circuit which function as a band pass filter.

(4)

to set the frequency of oscillation.


A Colpitts oscillator is the electrical dual of a Hartley oscillator, where the feedback signal is taken from an inductive voltage divider consisting of two coils in series. L and the series combination of C_1 and C_2 form the parallel resonant tank circuit, which determine the frequency of the oscillator. The voltage across C_2 is applied to the base emitter junction of the transistor, as feedback to create oscillations. Fig 2 shows the common-collector version. Here the voltage across C_1 provides the feedback. The frequency of oscillation is approximately the resonant frequency of the series combination of the two capacitors and in parallel with the inductor.

$$f_0 = \frac{1}{2\pi \sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

(5)

Hartley oscillator:-

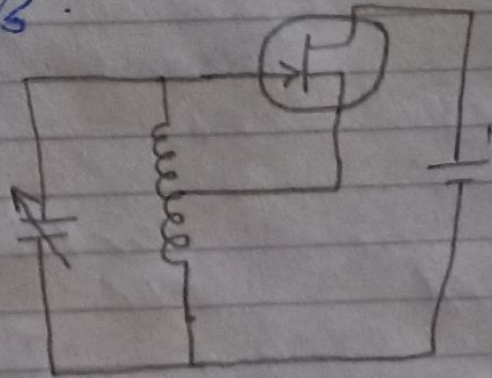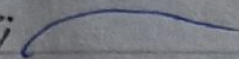
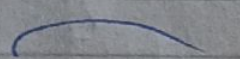

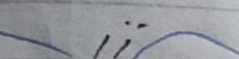
The Hartley oscillator is an electronic oscillator circuit in which the oscillation frequency is determined by a tuned circuit consisting of capacitor and inductors, that is an LC oscillator. The circuit was invented in 1915 by American engineer Ralph Hartley. The distinguishing feature of the Hartley is that the tuned circuit consists of a single capacitor in parallel with two inductors in series, and the feedback signal needed for oscillation is taken from the center connection of the two inductors.



The Hartley oscillator is distinguished by tank circuit consisting of two series connected coils in parallel with a capacitor, with

6

an amplifier between the relatively high impedance across the inductive LC tank and the relatively low voltage / high current point between the coils.

ii  ii  ii  ii  ii

Q No 3 a) :-

Describe the idea behind class B amplifiers.

Ans :-


CLASS B Amplifier :-

Class B amplifier is the type of power amplifier where the active ~~device~~ device (transistor) conducts only for one half cycle of the input signal. That means the conduction angle is 180° for class B amplifier.

Since the active device is switched off for half the input cycle, the active device dissipates less power and hence the efficiency is improved. The theoretical maximum efficiency of class B power amplifier is 78.5%. The schematic

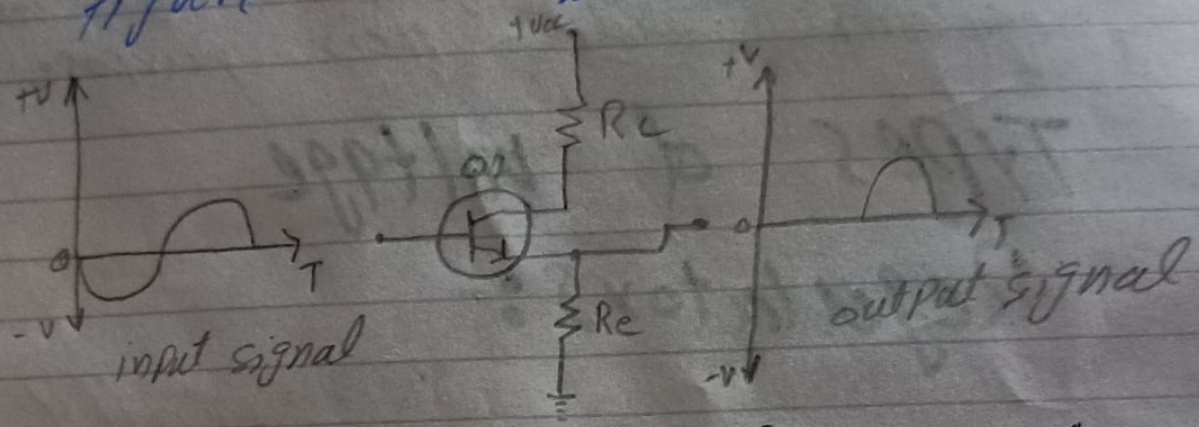(7)

of class B single ended amplifier and its input, output waveforms are shown in the figure below.



single ended class B amplifier.

From the above circuit it is clear that the base of the transistor Q1 is not biased and the negative half cycle of the input waveform is missing in the output. Even though it improves the power efficiency it creates a lot of distortion. The information present in the input will be available in the output and that is a bad thing. Single ended class B amplifiers are not used in present day practical audio.

amplifier application.

ii ii ii ii ii ii

Q No 3 b):- Explain the types of voltage regulators and their purpose.

Ans:- TYPES of voltage

Regulators:-


Basically there are two types of voltage regulators. The one is linear voltage regulator and the other one is switching voltage regulator. There are two types of series and shunt voltage regulator.

Linear Regulators:-

Linear regulators act as voltage divider in the ohmic region. It uses FET. The resistance of FET varies with constant voltage load. Resulting output voltage.


Series voltage Regulator:-

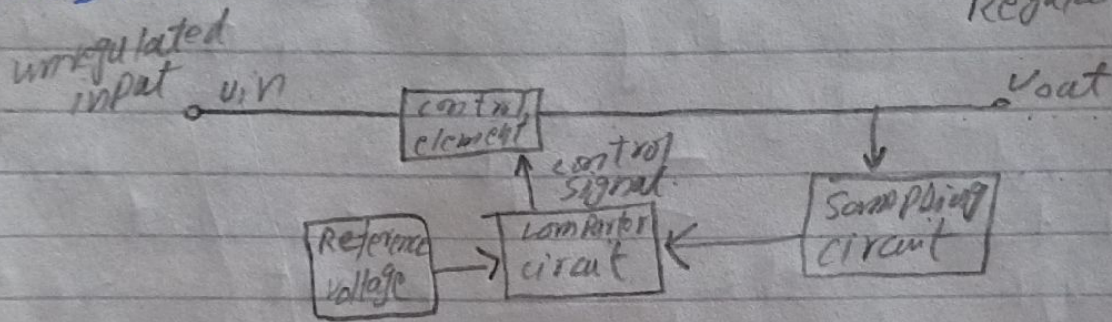Series voltage regulator uses a variable element placed in series with the load. By changing the resistance of the series element, the voltage drop across it can be changed. And the voltage across the load remain constant.



The amount of current drawn is effectively used by the load. This is the main advantage of the series voltage regulator. Even when the load does not require current, the series regulator does not draw full current. There fore is the series regulator more efficient than shunt regulator.

(19)

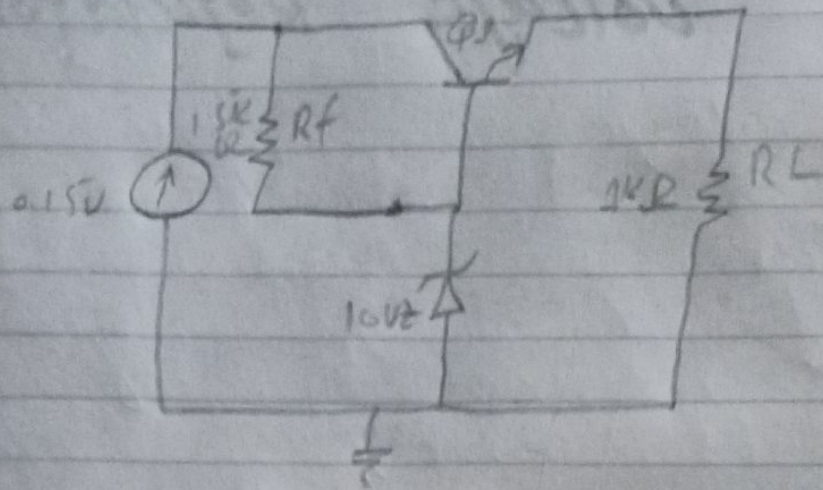

Shunt voltage Regulator:-

A shunt voltage regulator works by providing a path from the supply voltage to ground through a variable resistance. The current through the shunt regulator is diverted away from the load and flows uselessly to the ground. It is, however, simpler sometimes consisting of just a voltage-reference diode and is used in very low powered circuits where the wasted current is too small to be of concern.

Shunt regulators are used in

* Low output voltage switching

(11)

power

supplies.

Current



Source and Sink circuits

Error
voltage

amplifiers.
monitoring etc.

Switching voltage regulator:-

Switching regulators are a series of rapidly switching devices on and off. The duty cycle sets the amount of charge transferred to the load. This is controlled by a feedback mechanism similar to a linear regulator. Switching regulators are efficient because the series element is either fully conducting or switched off because it dissipates almost no power. Switching regulators generate output voltages that are higher than the input voltage or of opposite polarity, unlike linear regulators.

ii  ii  ii  ii

(12)

Q No 1 b) :- The input of a certain regulator increase by 4.5 V. As a result the output voltage increase by 0.062 V. The nominal output is 40 V. Evaluate the line regulation in both % and in μV .

Sol: -

$$\text{Line Reg} = \frac{0.062}{4.5} \times 100\%$$
$$= 1.377\%$$

&

$$\text{Line Reg} = \frac{0.062}{40} \times 100\%$$
$$= 0.034 \mu\text{V}$$

ii ii ii ii ii

Q No 4 :- Explain the working of Flash ADC.

Ans: Flash ADC :- series of

(13)

comparators, each one compares input to a unique reference voltage. comparator outputs connect to a priority encoder circuit.

working of Flash ADC:-

As the ~~analog~~ analog input voltage exceeds the reference voltage at each comparators, the comparator outputs will sequentially saturate to a high state.

The priority encoder generates a binary number based on the highest order active input, ignoring all other inputs.

ii ~~~~~ ii ~~~~~ ii ~~~~~ ii

Q Nos:- Differentiate between the following.

Q):- Low Pass & High Pass filters:-

The difference between low pass filter and high pass filter mainly includes definitions, circuit architecture, significance, operating frequency and application.

Low Pass filter

Low pass filter allows the frequency underneath cut-off frequency for flowing through it.

it can be built with a resistor which is followed by a capacitor.

it is important in eliminating the aliasing effect.

it is less than the cut-off frequency

The LPF can be used as an anti-aliasing filter in communication circuit.

High Pass filter

High pass filter allows the frequency over cut-off frequency for flowing through it.

it can be built with a capacitor which is followed by a resistor.

it is important whenever the distortion occurs because of low-frequency signal like noise to be detached.

it is higher than the cut-off frequency.

The HPF can be used in amplifiers like low noise, audio, etc.

b) Difference B/W Active & Passive Filter.

The major difference between active and passive filter is that an active filter uses active components like transistor and op-amp for the filtering of electronic signals. As against, a passive filter uses passive component like resistor, inductor and capacitor to generate a signal of a particular band.

Comparison chart.

Basis of comparison	Active filter	Passive filter.
Composed of	Active component like resistor inductor etc transistor etc.	Passive component like resistor inductor etc.
cost	high	comparatively low.
circuit	more complex	less complex than active filter.

