

Department of Electrical Engineering
Sessional Assignment
Date: 04/05/2020

Course Details

Course Title: Electronic Circuit Design **Module:** 04
Instructor: Engr. Mujtaba ihsan **Marks:** 20

Student Details

Name: M.yasir shah **Student ID:** 13172

Q1.	<p>Explain the trans conductance curve for n-channel JFET given below</p> <div style="text-align: center;"> </div>	<p>Marks 04 CLO 1</p>
Q2.	<p>State the characteristics of a practical operational amplifier.</p>	<p>Marks 04 CLO 1</p>
Q3.	<p>Calculate output voltage for summing amplifier if $V_1 = 0.2V$, $V_2 = 0.5V$ and $V_3 = 2V$ and $R_1=R_2=R_3=R_f = 6k\Omega$</p>	<p>Marks 05 CLO 2</p>
Q4.	<p>(a) You are working on an audio circuit in the lab. Which class of power amplifier will you not consider for your work? Justify your answer with reason.</p> <p>(b) Outline the differences between an amplifier and a rectifier.</p>	<p>Marks 04 CLO 2 Marks 03 CLO 2</p>

Name M. Yasir Shah


ID 13172

Subject ECD

Assignment # 02 (Sessional)

Submitted to Engr Mujtaba Ihsan

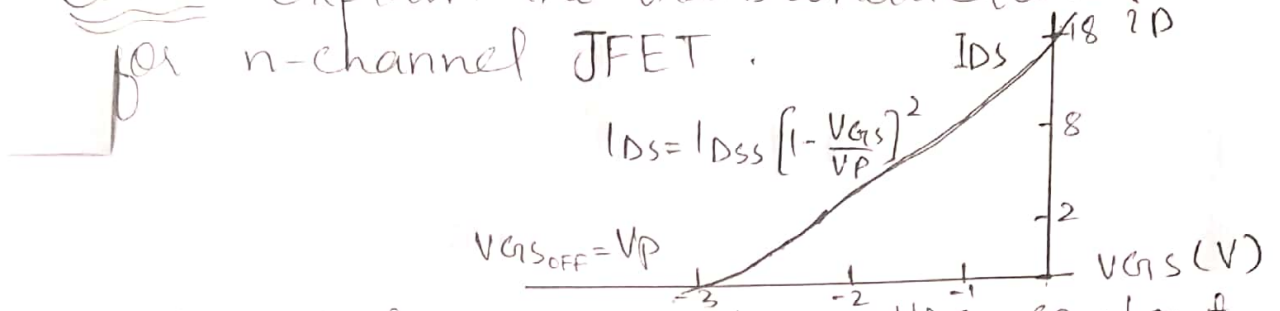Q# 1: Explain the transconductance curve for n-channel JFET.



→ Keeping drain source voltage, V_{DS} constant and determining drain current, I_D for various values of gate source voltage V_{GS} .

→ The circuit diagram shows, The curve is plotted between gate-source voltage V_{GS} and drain current, I_D .

→ It is observed that

- (i) Drain current decreases with the increase in negative gate-source bias.
- (ii) Drain current, $I_D = I_{DSS}$ when $V_{GS} = 0$.
- (iii) Drain current, $I_D = 0$ when $V_{GS} = V_P$.

→ It may be noted that a P-channel JFET operates in the same way and have the similar characteristics as an N-channel JFET except that channel carriers are holes instead of electrons and the polarities of V_{GS} and V_{DS} are reversed.

Q#02:

State the characteristics of a practical operational amplifier?

- (i) The open loop voltage gain A_0 is maximum and finite, typical value for the practical op-amplifier is considered to be 200,000.
- (ii) The input impedance is maximum and is finite i.e. in the order of $100k$ or more.
- (iii) The output impedance is minimum, in the order of 100 or less.
- (iv) The CMRR is maximum and finite.
- (v) Bandwidth is maximum and finite i.e. it can amplify dc to $1MHz$ signal.
- (vi) A slight drift of characteristics due to the change in temperature, not null.
- (vii) Two terminals may be virtually ground, not $V_d = 0$ exactly, for all conditions.
- (viii) Maximum slew-rate and has the finite value.
- (ix) The output is negligible due to dc-bias when input is zero.

Q#03:

Calculate the output voltage for summing amplifier.

Given data

$$V_1 = 0.2 \text{ V}$$

$$V_2 = 0.5 \text{ V}$$

$$V_3 = 2 \text{ V}$$

$$R_f = R_1 = R_2 = R_3 = 6 \text{ k}\Omega$$

Solution:

formula $V_{out} = - (R_f/R) * (V_1 + V_2 + V_3)$

$$V_{out} = - (6/6) * (0.2 + 0.5 + 2)$$

$$V_{out} = - 2.7 \text{ V}$$

Answer.

Q # 04 (a)

- I will not consider class 'C' of power amplifier for working on an audio circuit in the lab.
- Because class C amplifiers are never used for audio circuits.
- They are commonly used in RF circuits.
- Class C amplifiers operate the output transistor in a state that results in tremendous distortion. It would be totally unsuitable for audio circuit.
- Class C output devices conduct for less than 180 degrees (100 to 150 degrees typically for radio frequencies only), cannot be used for audio.

Q#04 (b)

An Amplifier: An amplifier is an electronic device that can increase the power of a signal (a time varying voltage or current). It is a two port electronic circuit that uses electric power from a power supply to increase the amplitude of a signal applied to its input terminals.

A Rectifier: A rectifier is an electrical device that converts alternating current (AC) to direct current (DC) which flow in one direction.

This process is known as rectification.