

Department of Electrical Engineering

Assignment

Date: 13/04/2020

Course Details

Course Title: Linear Circuit Analysis

Module: 2

30


Instructor: Sir Sohail Imran



Total Mark




Student Details

Name: Hasnat Khan

Student ID: 16631

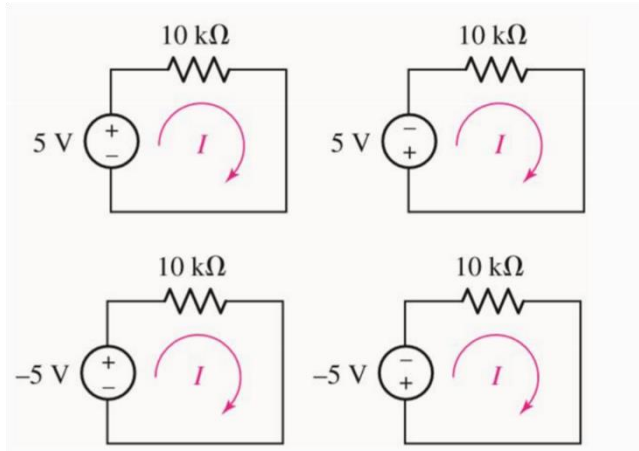
Q1	(a)	For each of the circuits in figure, find the current $I$ and compute the power absorbed by the resistor	Marks 3 PLO1
			
	(b)		Marks 4

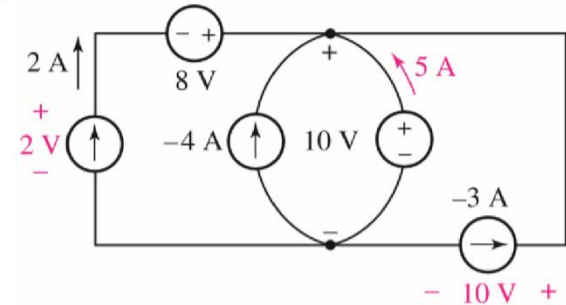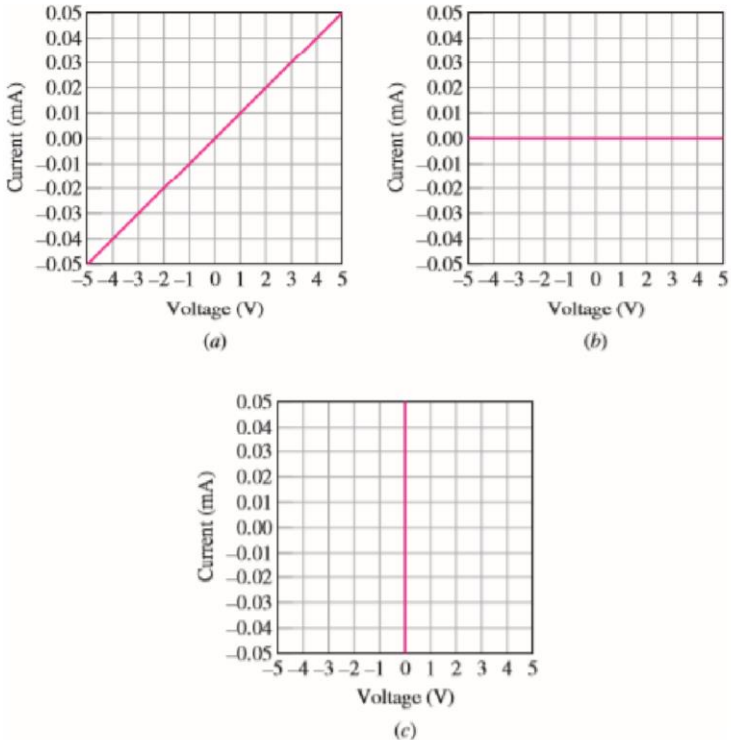	<p>Determine the power supplied by the leftmost element in the circuit of following figure</p> 	PLO1
(c)	<p>Following figure depicts the current-voltage characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.</p>	Marks 3 PLO1
	 <p>(a) A graph showing a linear relationship between current and voltage. The x-axis is Voltage (V) from -5 to 5, and the y-axis is Current (mA) from -0.05 to 0.05. The line passes through the origin (0,0) and has a positive slope, indicating a resistor.</p> <p>(b) A graph showing a constant current of 0 mA for all voltages from -5 V to 5 V. This represents an ideal current source.</p> <p>(c) A graph showing a constant current of 0 mA for all voltages from -5 V to 5 V. This represents an ideal current source.</p>	
Q2	<p>(a) Refer to the circuits of following figures, and answer the following: 1. How many distinct nodes are contained in the circuit?</p>	Marks 4

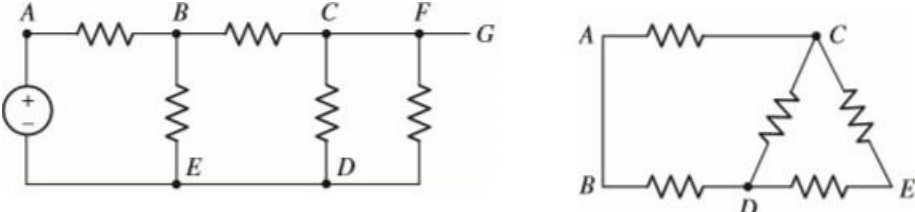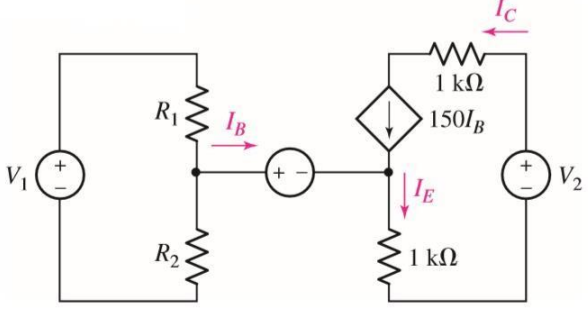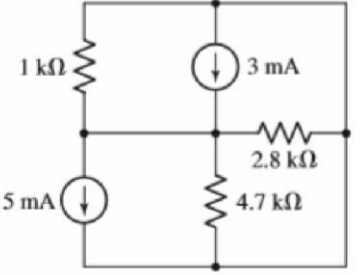	<p>2. How many elements are contained in the circuit?  3. How many branches does the circuit have?  4. Determine if each of the following represents a path, a loop, both, or neither:</p> <p>i. A to B  ii. B to D to C to E  iii. C to E to D to B to A to C  iv. C to D to B to A to C to E</p> 	PLO2
(b)	<p>For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region), <math>I_B</math> is measured to be <math>100 \mu\text{A}</math>. Determine <math>I_C</math> and <math>I_E</math></p>	Marks 6 PLO2
		
Q3	<p>(a) Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.</p> <p>a. Determine the power absorbed by each resistor.  b. Determine the power supplied by each current source.  c. Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).</p> 	Marks 5 PLO1
(b)		Marks 5

Determine the power absorbed by the  $15\ \Omega$  resistor in the circuit of following figure

PLO1

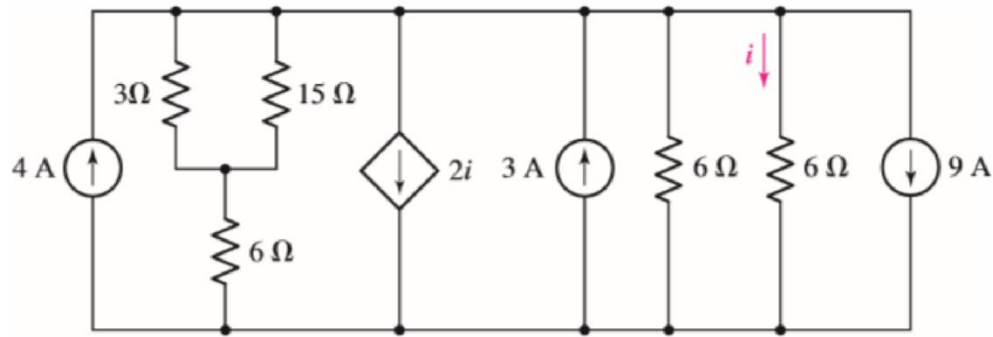

**Ans 1(a):-**

First we have to use Ohm's Law

$$V = IR$$

$$I = \frac{V}{R}$$

First find Power :

$$P = VI$$

To find first circuit. So we have to take the current in opposite side means with negative sign

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{5v}{10000\Omega}$$

$$I = 0.0005A$$

$$I = 0.5mA$$

Now for Power

$$P = VI$$

$$P = 5 \times 0.5 \times 10^{-3}$$

$$P = 2.5 \times 10^{-3}$$

$$P = 0.25mW$$

Now for 2<sup>ND</sup> circuit:

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{-5v}{10000\Omega}$$

$$I = -0.0005A$$

$$I = -0.5mA$$

For power

$$P = VI$$

$$P = 5(-0.5 \times 10^{-3})$$

$$P = -2.5 \times 10^{-3}$$

$$P = -0.0025W$$

$$P = -0.25mW$$

For 3<sup>rd</sup> circuit:

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{-5v}{10000\Omega}$$

$$I = -0.0005A$$

$$I = -0.5mA$$

Then Power

$$P = VI$$

$$P = 5(-0.5 \times 10^{-3})$$

$$P = -2.5 \times 10^{-3}$$

$$P = -0.25mW$$

Now Circuit 4<sup>th</sup>:

$$V = IR$$

$$I = \frac{V}{R}$$

$$I = \frac{5v}{10000\Omega}$$

$$I = 0.5mA$$

For Power

$$P = VI$$

$$P = 5(0.5 \times 10^{-3})$$

$$P = 2.5 \times 10^{-3}$$

$$P = 0.25mW$$

**Ans 1(b):**

We know that

$$P = VI$$

$$P = 2v \times 2A$$

$$P = 4W$$

In this circuit voltage and current are given

We will multiply two factors to find power

$$2v \times 2A = 4w$$

This 4w is supplied. And we will take current with positive sign.

**Ans 1(c):**

For this we have to use Ohm's Law

$$V = IR$$

$$OR \quad R = \frac{V}{I}$$

To find R take the value of I and V from the graph

**Solution (a)****Given that**

$$I = 0.01mA$$

$$V = 1V$$

$$R = ?$$

**Calculation:**

Using Ohm's Law

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{0.5A}{5V}$$

$$R = 10\mu S$$

$$R = \frac{1v}{0.01 \times 10^{-3}}$$

$$R = 100 \times 10^3$$

$$R = 100k\Omega$$

**Solution (b)****Given that:**

From graph we know that current is zero

$$V = 1v$$

$$I = 0$$

$$R = ?$$

**Calculation:**

We know that

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{1v}{0}$$

$$R = \infty$$

**Solution (c)****Given that:**

From this graph we come to know that the current is infinite

$$V = 1v$$

$$I = \infty$$

$$R = ?$$

**Calculation:**

We know that

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{1}{\infty}$$

$$R = 0 \quad \text{So, we have zero resistance}$$

**Ans 2(a):**

- 1) Number of nodes = 4
- 2) Number of elements = 5
- 3) Number of branches = 5



4)

- i. Neither
- ii. Only path
- iii. Path and loop
- iv. neither

**Ans 2(b):**

We know that KCL tells us that

Total current entering a node = total current leaving a node

So by this equation;

$$I_B + I_C = I_E$$

Or

$$I_E = I_B + I_C \Rightarrow I_C = 150.I_B$$

$$I_C = 15mA$$

Now,

$$I_E = 150 \times 10^{-3} + 100 \times 10^{-6}$$

$$I_E = 15.1mA$$

**Ans 3(a):**

We know that

$$V=IR$$

So

$$V=2 \times 637 \times 10^{-3} \Rightarrow 1.274V$$

Now find current I of each

$$V=IR$$

$$I = \frac{V}{R}$$

Let

$$I_x = \frac{1.274v}{1000\Omega}$$

$$I_x = 0.001274A$$

$$I_x = 1.274mA$$

Now

$$I_y = \frac{1.274v}{2800\Omega}$$

$$I_y = 0.000455A$$

$$I_y = 0.455mA$$

Then

$$I_z = \frac{1.274v}{4700\Omega}$$

$$I_z = 0.000271A$$

$$I_z = 0.271mA$$

Now to find Power,

We know the equation

$$P = VI$$

$$\begin{aligned} \Rightarrow P(2.8k) &= (1.274v)(0.455) \\ &= 0.5797mW \end{aligned}$$

$$\begin{aligned} \Rightarrow P(4.7k) &= (1.274)(0.271) \\ &= 0.3452mW \end{aligned}$$

$$\begin{aligned} \Rightarrow P(1k) &= (1.274)(1.274) \\ &= 1.6230mW \end{aligned}$$

$$\begin{aligned}\Rightarrow P(5\text{mA}) &= (1.274)(-5) \\ &= -6.37\text{mW} \\ \Rightarrow P(3\text{mA}) &= (1.274)(3)\end{aligned}$$

**Ans 3(b):**

In this circuit first we will calculate the source and equivalences:

$$\begin{aligned}i_{eq} &= 4 - 2i + 3 - 9 \\ &= 4 - 2i - 6 \\ i_{eq} &= -2 - 2i \\ R_{eq} &= (6 + 3 \parallel 5) \parallel 6 \parallel 6 \\ R_{eq} &= 8.5 \parallel 3 = 2.217\Omega\end{aligned}$$

Now find voltage V:

$$\begin{aligned}V &= i_{eq} \cdot R_{eq} \\ V &= (-2 - 2i)(2.217\Omega)\end{aligned}$$

From diagram;

$$\begin{aligned}V &= 6i \\ 6i &= (-2 - 2i)(2.217) \\ 6i &= -4.434 - 4.434i \\ 6i + 4.434i &= -4.434 \\ 10.434i &= -4.434 \\ i &= \frac{-4.434}{10.434} \\ i &= -0.424\text{A}\end{aligned}$$

$$v = -2.55\text{v}$$

So,

$$\begin{aligned}P &= \frac{V^2}{R} \\ P_{15\Omega} &= \frac{(-2.55)^2}{15} \\ V_{15\Omega} &= \frac{6}{6.25} \\ V_{15\Omega} &= 1.8\text{v}\end{aligned}$$

*Now Power,*

$$\begin{aligned}P_{15\Omega} &= \frac{V^2}{R} \\ &= \frac{(1.8)^2}{15\Omega} \\ &= \frac{3.24}{15} \\ P_{15\Omega} &= 0.216W\end{aligned}$$

**Finished !**