

NAME

Muhammad Ilyas

ID NO

15392

Degree

B.S (software engr)

Teacher


Sir M. Amin

Assignment


DLD

# Assignment 2

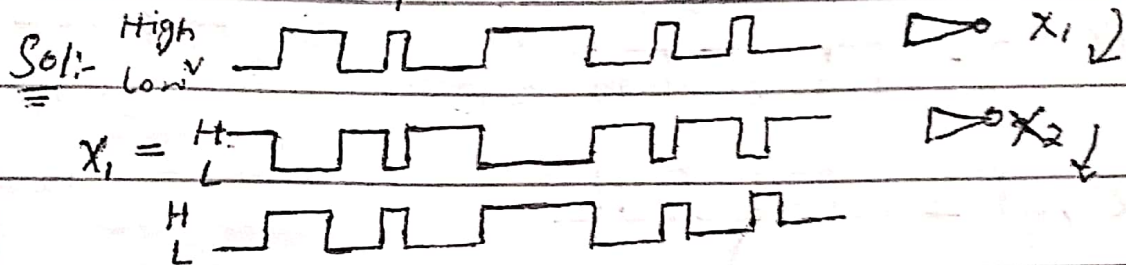Q1:- The input waveform in figure is applied to a system of two inverters connected in series. Draw the output waveform across each inverter in proper relation to the input.



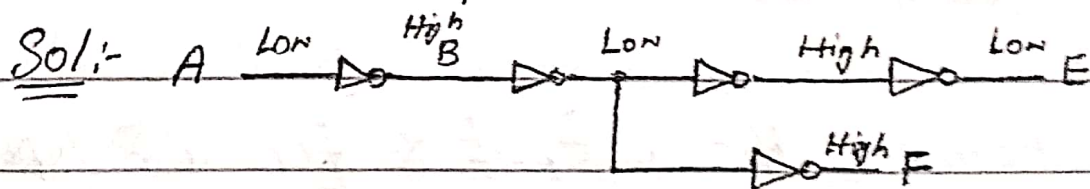Q2:- A combination of inverters is shown in figure. If a low is applied to the point A, determine the output at point E and F.




$E = \text{LOW}$

$F = \text{high}$


Q3: if waveform in Q.1 is applied to figure in Q.2 at point A. Determine the waveform from point B to F.

Sol:-

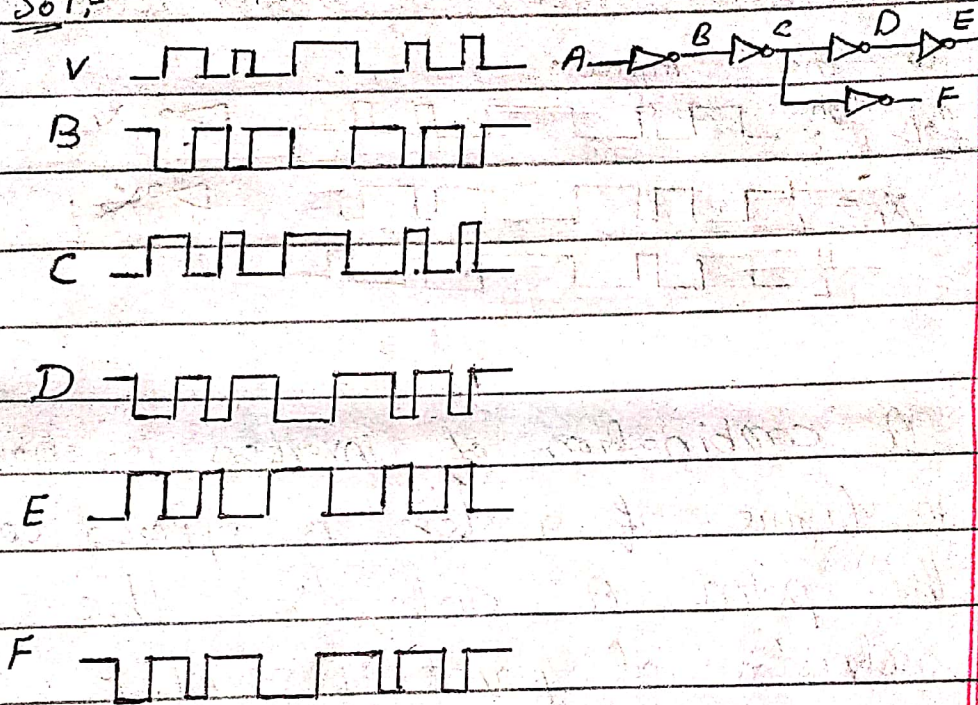


Q4:- Determine the output x for a 2 input AND gate with the input waveform.


Sol:-

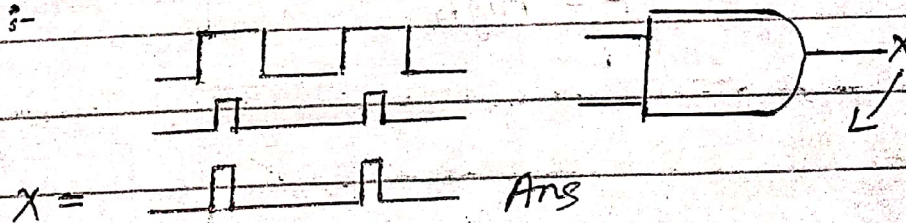

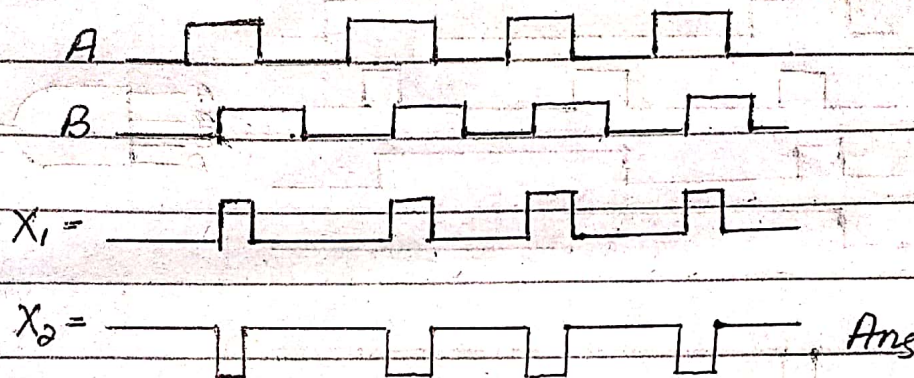
Q5: The waveform in figure are applied to point A & B at a 2-input AND gate followed by inverter. Draw the output waveform.



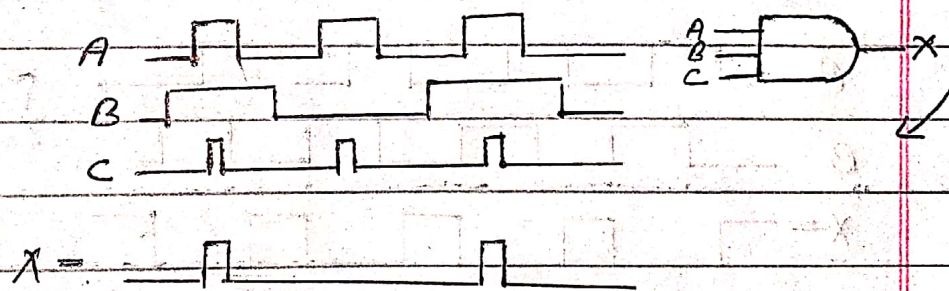Q6: The input waveform applied to 3-input AND gate ~~are~~ as indicated in figure. Show the output waveform in proper relation to inputs with a timing diagram.




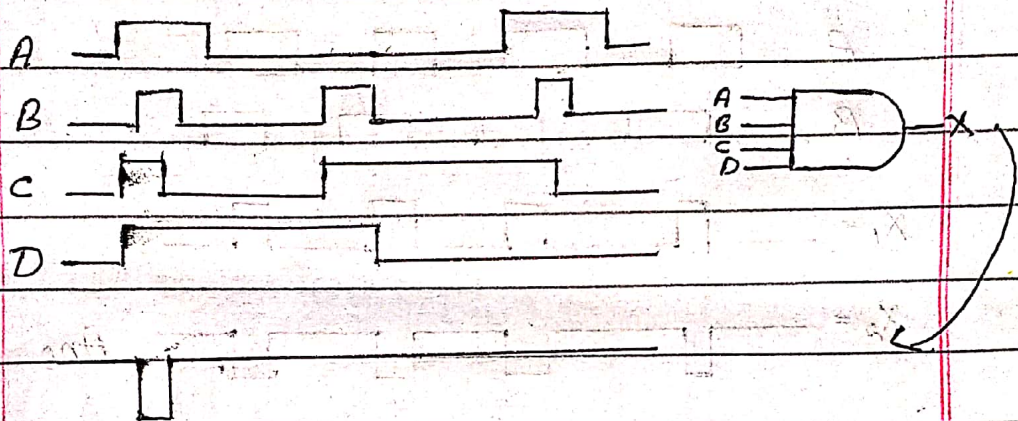Q7:- The input waveform applied to a 4 input AND gate as indicated in figure the output is fed to inverter. Draw the net output waveform of this system.




Ans

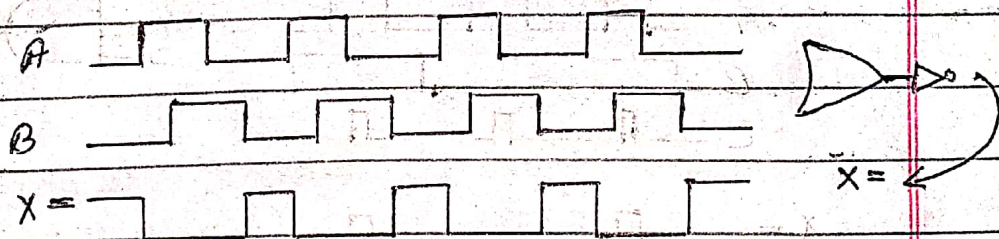
Q8:- Determine the output for a two input OR gate when the input waveform are as in figure 04 and draw a timing diagram.



Q9: Repeat Q.6 for 3-input OR gate.

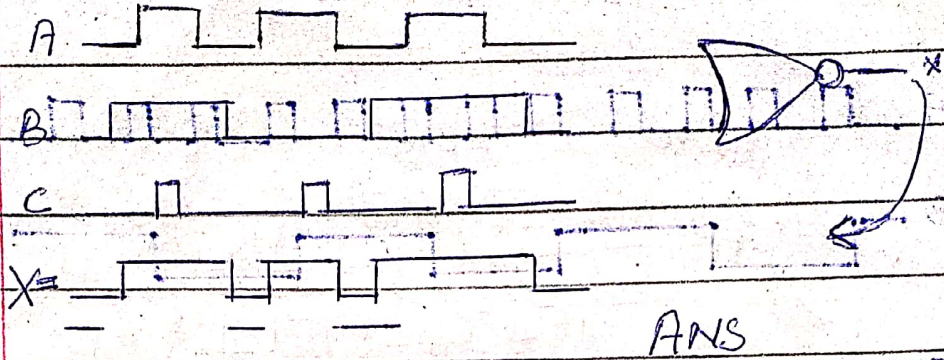


Q10 Repeat Q.7 for 4-input OR gate.

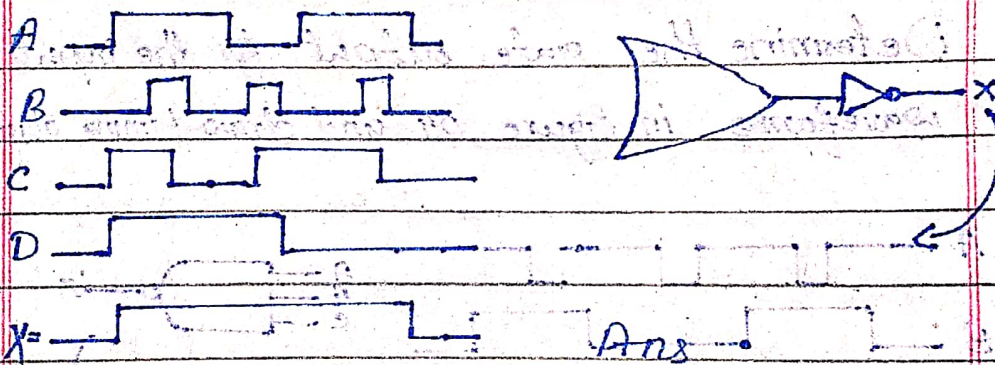


Q12: Show that truth table for a system of a 3-input OR gate followed by inverter


A	B	C	$A+B+C$	$\neg(A+B+C)$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

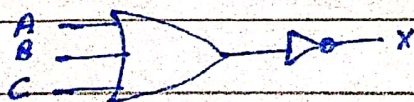

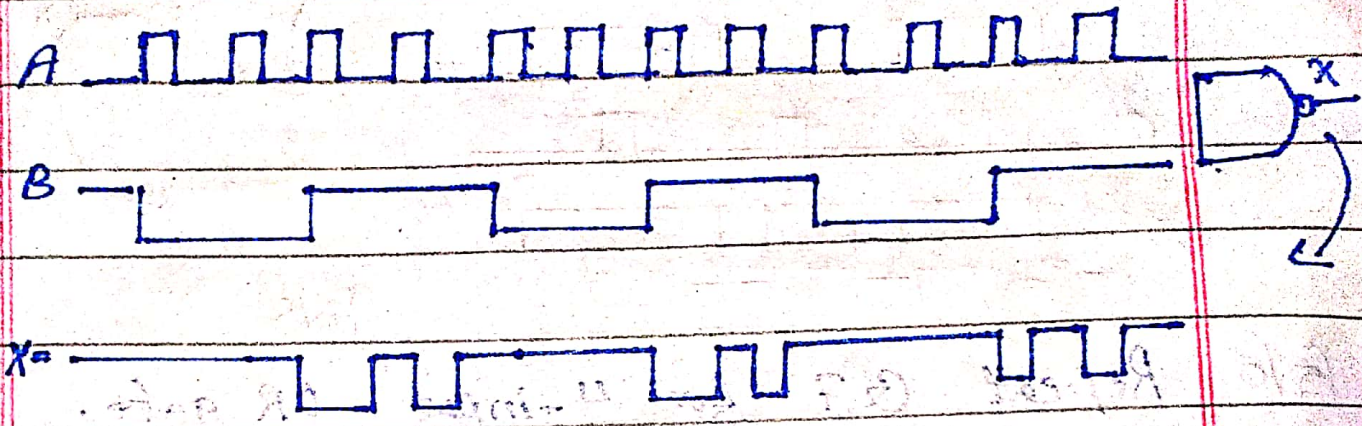Q 13:- For the set of input waveforms, Determine the output for the gate show in timing diagram.




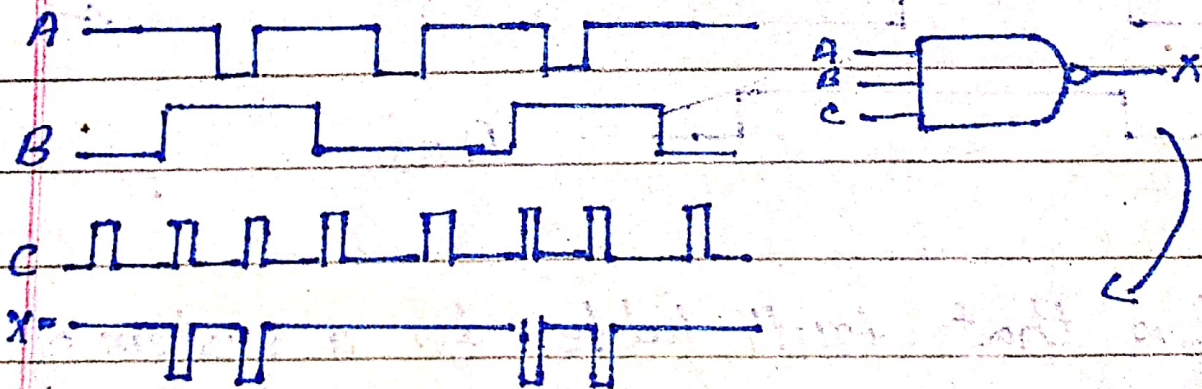Q 14 Determine the gate output for the input waveforms in figure 09 and draw timing diagram.






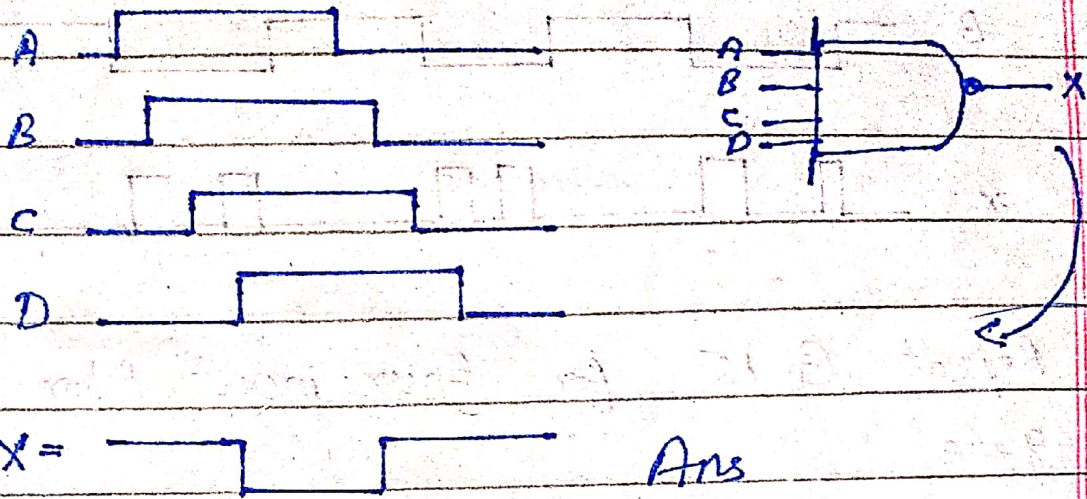Q15: Determine the output waveform in figure 10.




Q16: The two logic symbols shown in figure 11 represent equivalent operation. The difference between the two is strictly from a functional viewpoint. For the NAND symbol. Look for two 1 highs on the inputs to give low output. For the negative-OR, look for at least one low on the inputs to give a high on the output.

Ans:-


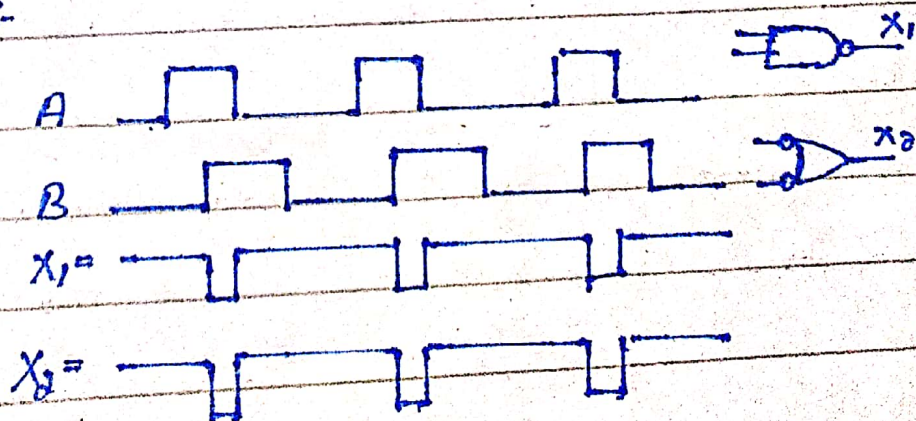


Q17: Repeat Q13 for 2 input Nor gate.

Ans:-

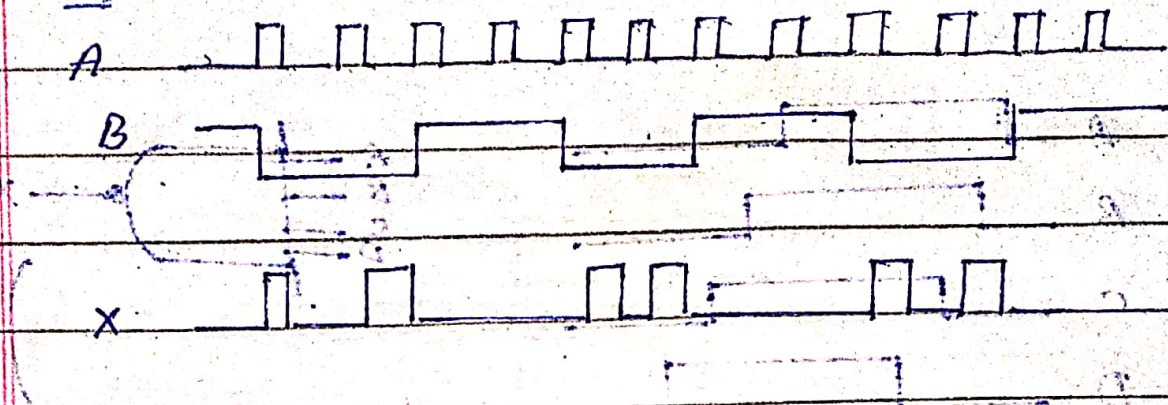


Q18: Repeat Q15 for four input Nor gate

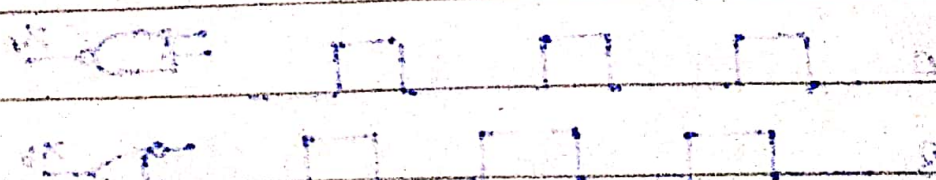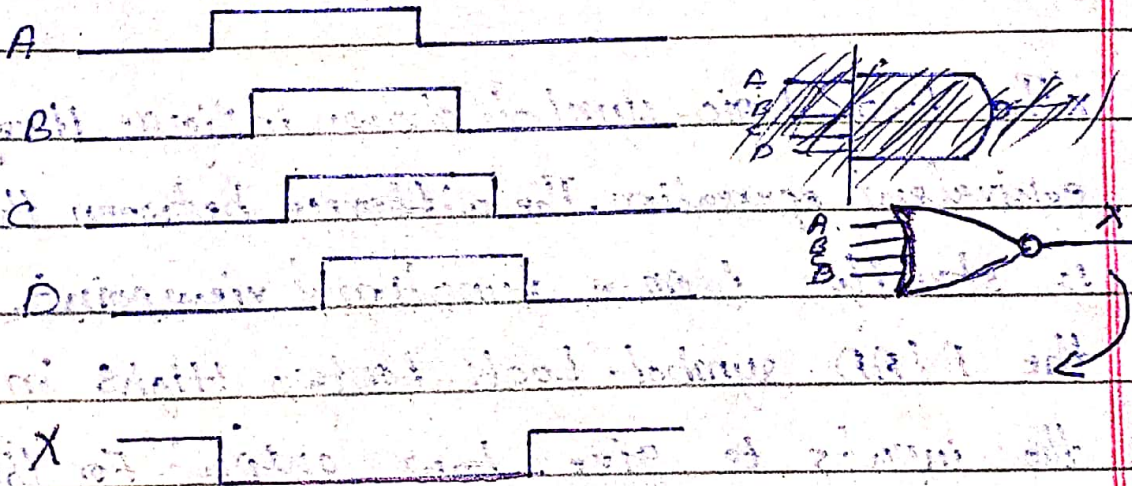


Q19: Determine the output waveform in figure 12 and draw timing diagram.

Ans:-

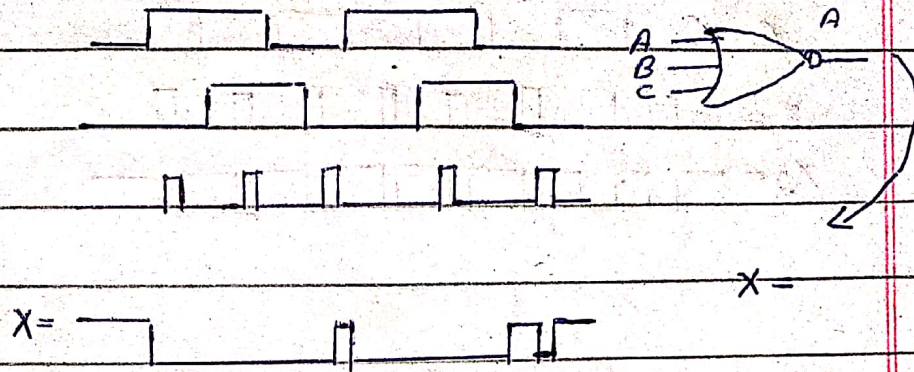


Q20: The NOR and the negative-AND symbols represent equivalent operations but they are functionally different. For the NOR symbol, look for at least one High on the inputs to give a low on the inputs. For the negative-AND, look for two Lows on the inputs to give high output. Using these two functional points of view, show that both gates in figure 12 will produce the same output.

Ans:-

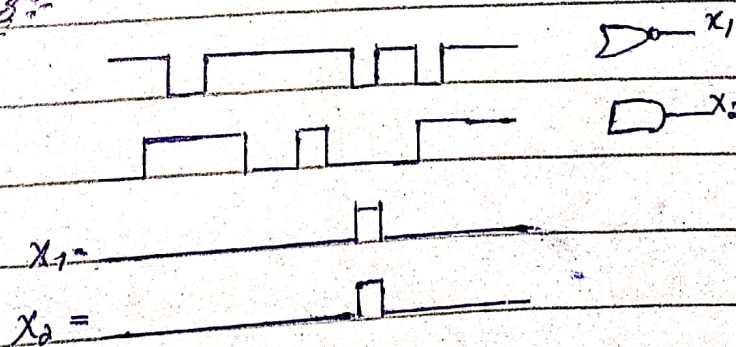


Q21: Repeat Q.5 for an Exclusive OR gate

Ans:-

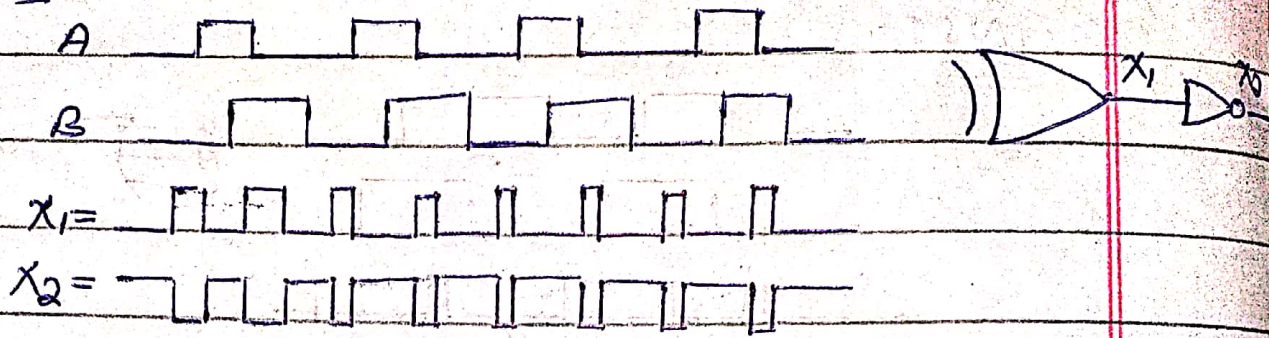

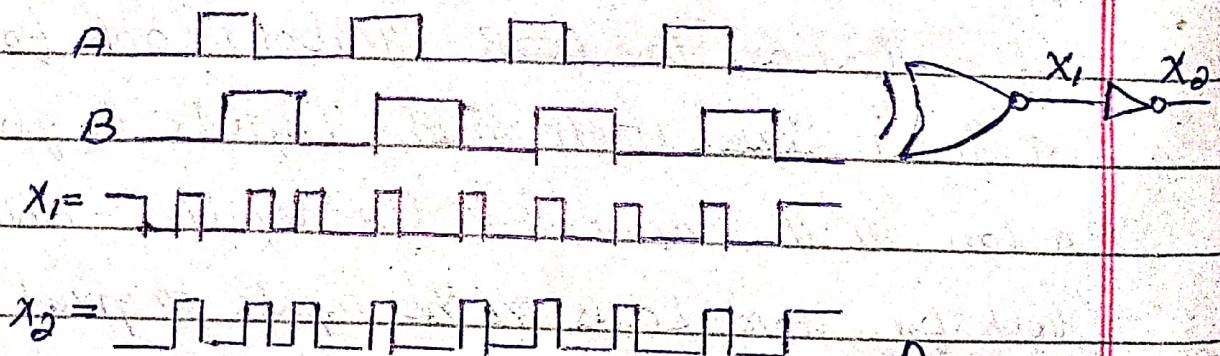Q22: Repeat Q.5 for an Exclusive NOR gate



ANSWER

