

# Lab: 3 Full Adder

Observation Table:

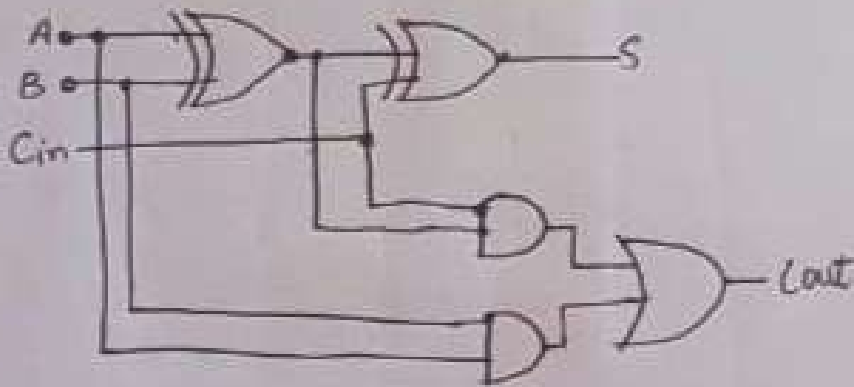


Table 3-1:

Inputs			Outputs	
A	B	C <sub>i</sub>	Sum(S)	Carry(A <sub>1</sub> )
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1