

* NAME M. SALMAN NASIR

* ID 16664

* SEMESTER 2ND

* LCA ASSIGNMENT

* DEPARTMENT BE ELECTRICAL

* SUBMITTED TO:-

"SIR SOHAIL

IMRAN"

* DATED :: 20-JUNE-2020

* _____ *

(1)

Chapter # 4

Q101: Find The determinant:

(a)

$$\begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}$$

let

$$A = \begin{vmatrix} 2 & 1 \\ -4 & 3 \end{vmatrix}$$

$$|A| = (2 \times 3) - (-4 \times 1)$$

$$|A| = 6 - (-4) = 6 + 4$$

$$\boxed{|A| = 10}$$

(b)

$$\begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

let

$$B = \begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

(2)

$$|B| = \begin{vmatrix} 0 & 2 & 11 \\ 6 & 4 & 1 \\ 3 & -1 & 5 \end{vmatrix}$$

Expanding Row 1:

$$|B| = 0 \begin{vmatrix} 4 & 1 \\ -1 & 5 \end{vmatrix} - 2 \begin{vmatrix} 6 & 1 \\ 3 & 5 \end{vmatrix} + 11 \begin{vmatrix} 6 & 4 \\ 3 & -1 \end{vmatrix}$$

$$= 0 - 2(30 - 3) + 11(-6 - 12)$$


$$= -2(27) + 11(-18)$$

$$= -54 - 198$$

$$= -252$$

$$|B| = 252$$

Q No 2:-

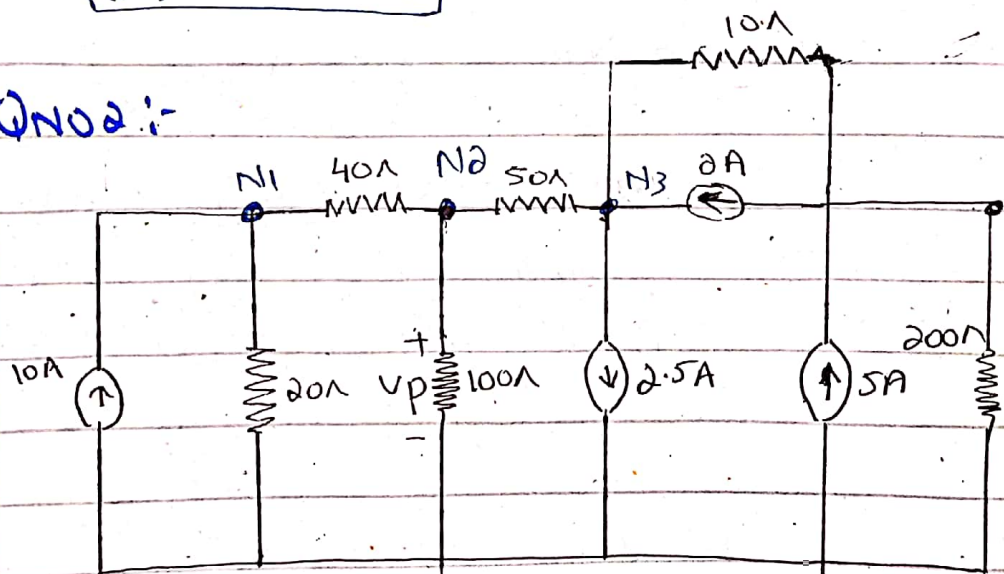

Find v_p through 100Ω resistor
analysis.

(3)

Applying KCL ON NODE 1

$$I_{20\Omega} + I_{40\Omega} = I_s \quad ; \quad I = V/R$$

$$\frac{V_1}{20} + \frac{V_1 - V_2}{40} = 10A$$

$$\frac{V_1}{20} + \frac{V_1 - V_2}{40} = 10$$

$$\frac{V_1}{20} + \frac{V_1 - V_2}{40} = 10$$

$$\frac{2V_1 + V_1 - V_2}{40} = 10$$

$$3V_1 - V_2 = 400 \rightarrow (1)$$

at Node (2)

$$\frac{V_2 - V_1}{40} + \frac{V_2}{100} + \frac{V_2 - V_3}{50} = 0$$

$$\frac{5V_2 - 5V_1 + 2V_2 + 4V_2 - 4V_3}{200} = 0$$

$$-5V_1 + 11V_2 - 4V_3 = 0 \rightarrow (2)$$

At Node 3:

$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_4}{10} = 2 - 2.5$$

$$\frac{5V_3 - 5V_2 + 5V_3 - 5V_4}{50} = -0.5$$

$$-V_2 + 6V_3 - 5V_4 = -25 \rightarrow (3)$$

(4)

at node (4)

$$\frac{V_3 - V_2}{10} + \frac{V_3}{200} = 5 - 2$$

$$\frac{20V_3 - 20V_2 + V_3}{200} = 3$$

$$\frac{-20V_2 + 21V_3}{200} = 3$$

$$-20V_2 + 21V_3 = 600 \rightarrow (4)$$

by ~~solving~~ eq (1) (2) (3) & (4)
we get.

$$\begin{array}{cccc|c|c|c} 3 & -1 & 0 & 0 & V_1 & & 400 \\ -5 & 11 & -4 & 0 & V_2 & = & 0 \\ 0 & -1 & 6 & -5 & V_3 & & -25 \\ 0 & -20 & 21 & 0 & V_4 & & 600 \end{array}$$

by solving matrix we get

$$V_1 = 18.46 \text{ V}, V_2 = 141.3 \text{ V}$$


$$V_3 = 163.2 \text{ V}, V_4 = 172.5 \text{ V}$$

from Fig $V_2 = V_P$

Hence $V_P = 141.3 \text{ V} \rightarrow \text{ANS.}$


(5)

Q NO3:-

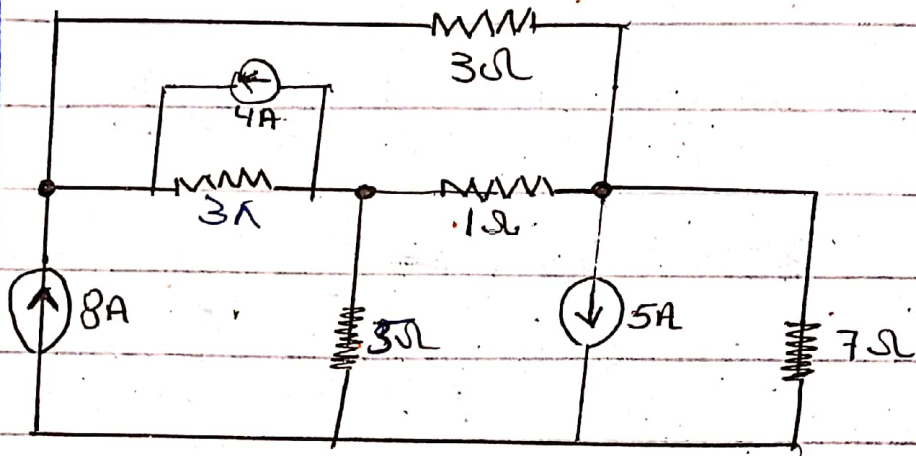

Find voltage across 3Ω
& power dissipated by 7Ω .

Re draw circuit & identify nodes

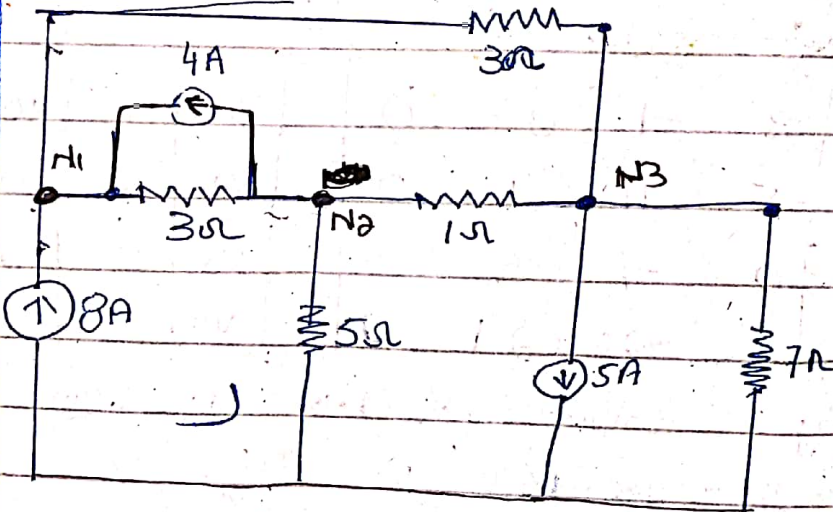

At Node 1 (N_1) Apply KCL

$$\cancel{V_3} + \cancel{V_3} + \cancel{V_3} = 0$$

Net power.

⑥

$$\frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{3} = 8 + 4$$

$$\frac{V_1 - V_2 + V_1 - V_3}{3} = 12$$

$$2V_1 - V_2 - V_3 = 12 \times 3$$

$$2V_1 - V_2 - V_3 = 36 \rightarrow (1)$$

at node 1:-

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - V_3}{1} = 4$$

$$\frac{5V_2 - 5V_1 + 3V_2 + 15V_2 - 15V_3}{15} = 4$$

$$-5V_1 + 23V_2 - 15V_3 = -60 \rightarrow (2)$$

at node 3:-

$$\frac{V_3 - V_2}{1} + \frac{V_3 - V_1}{3} + \frac{V_3}{7} = 5$$

$$\frac{21V_3 - 21V_2 + 7V_3 - 7V_1 + 4V_3}{21} = 5$$

$$-7V_1 - 21V_2 + 31V_3 = -105$$

(7)

Write 3 eq. in form of matrix

$$\begin{bmatrix} 2 & -1 & -1 \\ -5 & 2 & -10 \\ -7 & -21 & 31 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 26 \\ 4 \\ 105 \end{bmatrix}$$

A X B

$$AX = B$$

$$A^{-1}AX = A^{-1}B$$

$$IX = A^{-1}B$$

$$X = A^{-1}B \rightarrow$$

by solving above matrix by inversion method we get

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \rightarrow \begin{bmatrix} 26.7 \\ 8.8 \\ 8.6 \end{bmatrix}$$

Here $V_{sR} = V_2$
voltage across $sR = 8.8V$


$$\boxed{V_{sR} = 8.8V} \rightarrow \text{ANS}$$

Now

$$P_{7\Omega} = \frac{V_3^2}{R}$$
$$= \frac{(8.6)^2}{7} = \frac{74.8}{7}$$

$$\boxed{P_{7\Omega} = 10.64} \rightarrow \text{ANS}$$

Q4:- (8)

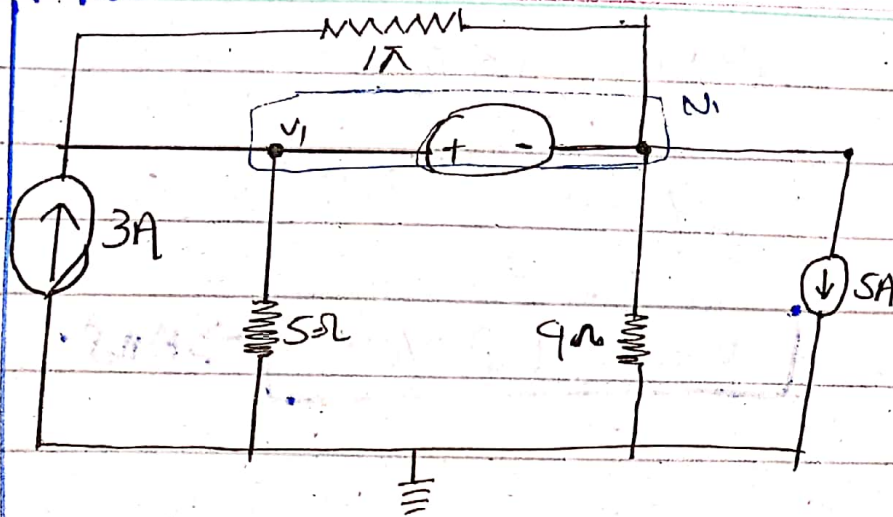

Find V_1

Apply KCL on ~~the~~ supernode

$$\frac{(V_1 - V_0)}{1} + \frac{V_1}{5} + \frac{V_0 - V_1}{1} + \frac{V_0}{9} = 3 - 5$$

$$4.5V_1 - 4.5V_0 + 9V_1 + 4.5V_0 - 4.5V_1 + 5V_0 = -2$$

$$9V_1 + 5V_0 = -90 \rightarrow (1)$$

Here

$$V_1 - V_0 = 9 \rightarrow (2)$$

multiply 5 eq (2) & Add eq (1)

$$9V_1 + 5V_0 = -90$$

$$+ 5V_1 - 5V_0 = +45$$

$$14V_1 = 135$$

$$V_1 = \frac{135}{14}$$


(9)

$$14V_1 = 130$$

$$V_1 = 130/14$$

$$V_1 = 9.2 \text{ Volt} \rightarrow \text{Ans.}$$

Q105:-

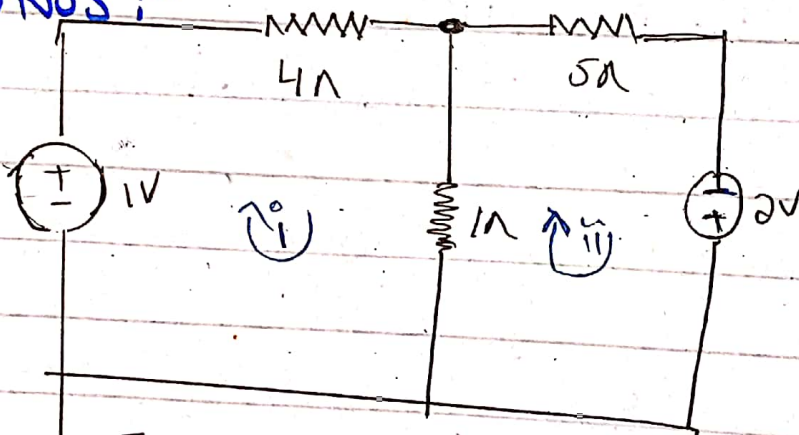

Find current flowing out from +ive terminal of each voltage source.

by mesh analysis

Apply KVL on loop 1

$$1V - 4i_1 - (i_1 - i_2) = 0$$

$$1 = 4i_1 + i_1 - i_2$$

$$5i_1 - i_2 = 1 \rightarrow \text{①}$$

(10)

at loop (2)

$$1(\dot{i}_2 - \dot{i}_1) + 5\dot{i}_2 = 2$$

$$6\dot{i}_2 - \dot{i}_1 = 2 \quad \text{--- (i)}$$

~~6i~~

$$-\dot{i}_1 + 6\dot{i}_2 = 2 \quad \text{--- (ii)}$$

multiply 5 by eqv (ii)
Add with eqv (i)

$$5\dot{i}_2 + 30\dot{i}_2 = 10$$

$$5\dot{i}_1 - \dot{i}_2 = 1$$

$$29\dot{i}_2 = 11$$

$$\dot{i}_2 = 11/29$$

$$\dot{i}_2 = 0.37 \text{ A} \rightarrow \text{Ans.}$$

put value of i_2 in

eqv (i)


$$5\dot{i}_1 - 0.37 = 1$$

$$5\dot{i}_1 = 1 + 0.37$$


$$\dot{i}_1 = 0.27 \text{ A} \rightarrow \text{Ans.}$$

(11)

Q NO 6:-

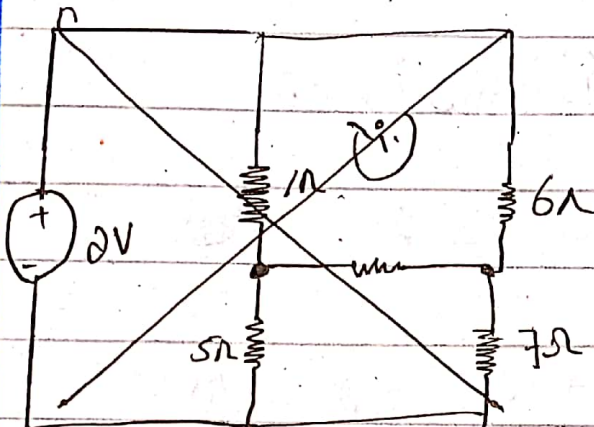

Q NO 6:-

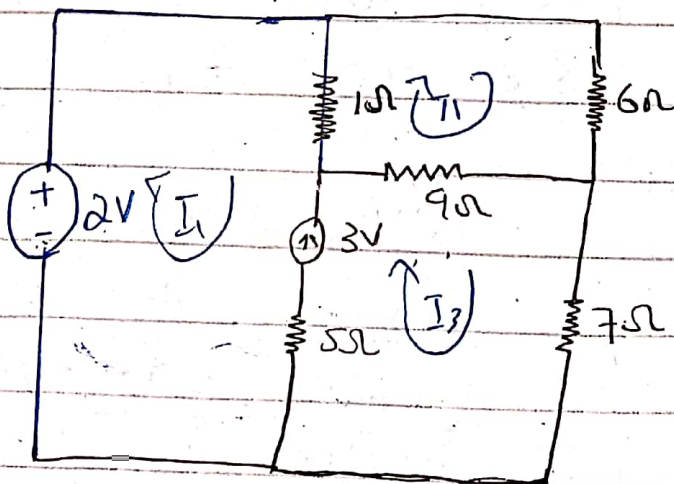

From loop I1-

$$-2 + 1(i_1 - I_2) - 3 + 5(i_1 - I_3) = 0$$

$$6i_1 - I_2 - 5I_3 = 5 \quad \rightarrow (i)$$

From loop (ii)

$$1(I_2 - I_1) + 6I_2 + 9(I_2 - I_3) = 0$$

$$-I_1 + 16I_2 - 9I_3 = 0 \quad \rightarrow (ii)$$

(12)

from loop 3:-

$$5(z_3 - z_2) + 9(z_3 - z_2) + 7z_3 = -3$$

$$-5z_2 - 9z_2 + 21z_3 = -3 \rightarrow \text{iii}$$

From eqv (i) (ii) & (iii)

$$\begin{bmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{bmatrix} \begin{bmatrix} z_1 \\ z_2 \\ z_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ -3 \end{bmatrix}$$

A.

Solve by Cramer's rule.

$$|A| = \begin{vmatrix} 6 & -1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{vmatrix}$$

Further simplification

$$|A| = 1015$$

$$\text{Now } A_x = \begin{vmatrix} 5 & -1 & -5 \\ 0 & 16 & -9 \\ -3 & -9 & 21 \end{vmatrix}$$

$$|A_x| = 1008$$

$$A_x = \begin{vmatrix} 6 & 5 & -5 \\ -1 & 0 & -9 \\ -5 & -3 & 21 \end{vmatrix}$$

(13)

$$|A_1| = 153$$

$$A_2 = \begin{vmatrix} 6 & -1 & 5 \\ -1 & 16 & 0 \\ -5 & -9 & -3 \end{vmatrix}$$

$$|A_2| = 730$$

$$\text{Now } \frac{|A_x|}{|A|} = \frac{1008}{1015}$$

$$\dot{z}_1 = 0.9 \text{ A}$$

$$\dot{z}_2 = \frac{|A_1|}{|A|} = \frac{153}{1015}$$

$$\dot{z}_3 = 0.150 \text{ A}$$

$$\dot{z}_3 = \frac{|A_2|}{|A|} = \frac{730}{1015}$$

$$\dot{z}_3 = 0.71 \text{ A}$$


$$i_1 = 0.9 \text{ A}$$

$$i_2 = 0.15 \text{ A} \rightarrow \text{ANS.}$$

$$i_3 = 0.71 \text{ A}$$

(14)

Q NO 71-

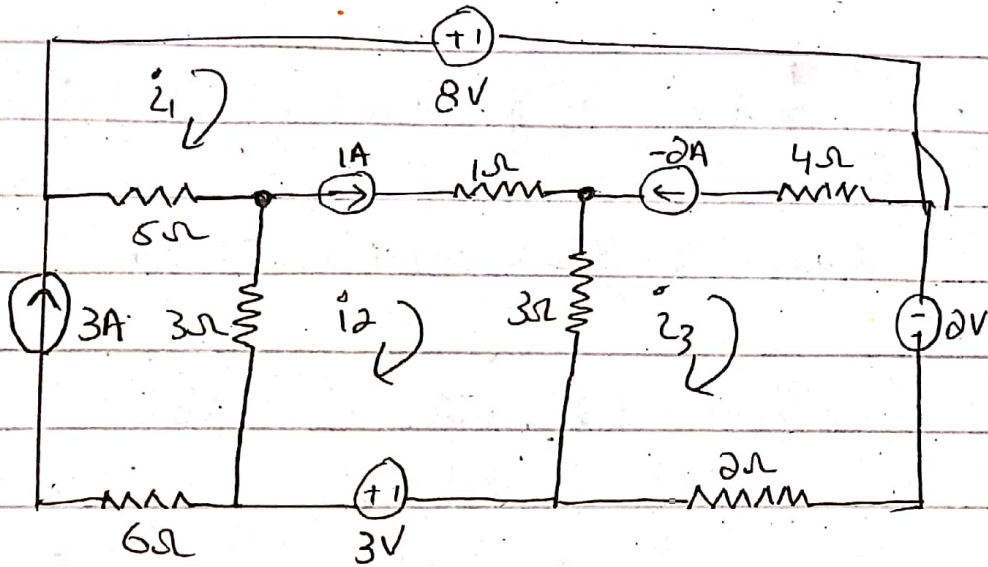

Let i_1, i_2 & i_3 As a supernode
 and Apply KCL to it.

$$5(i_1 - 3) + 3(i_2 - 3) + 2i_3 = 3 + 2 - 8$$

$$5i_1 - 15 + 3i_2 - 9 + 2i_3 = -3$$

$$5i_1 + 3i_2 + 2i_3 = -3 + 15 + 9$$

$$5i_1 + 3i_2 + 2i_3 = 21 \rightarrow (i)$$

We know that

$$i_2 - i_1 = 1$$

$$\text{where } i_2 = 1 + i_1 \rightarrow (ii)$$

$$i_2 - i_3 = -2$$

$$-2i_3 = -2 - i_2$$

$$i_3 = 1 + i_2 \rightarrow (iii)$$

$$i_3 = 2 + i_1 \rightarrow (iv)$$

(15)

put eq (ii) & (iii) in (i)

$$5i_1 + 3(1 + 2i_2) + 2(2 + i_1) = 12$$

~~$$5i_1 + 3 + 3i_2 + 4 + 2i_1 = 12$$~~

$$5i_1 + 3 + 3i_1 + 2i_2 + 4 = 12$$

$$10i_1 = 2i_2 + 5$$

$$i_1 = 2.1 \text{ A}$$

put value of i_1 in eq (ii) & (iii)

$$i_2 = 1 + 2 \cdot 1$$

$$i_2 = 3.1 \text{ A}$$

$$i_3 = 2 + 2 \cdot 1$$


$$i_3 = 4.1 \text{ A}$$

$i_1 = 2.1 \text{ A}$
$i_2 = 3.1 \text{ A}$
$i_3 = 4.1 \text{ A}$

→ Ans.

(18)

Q No 8:-

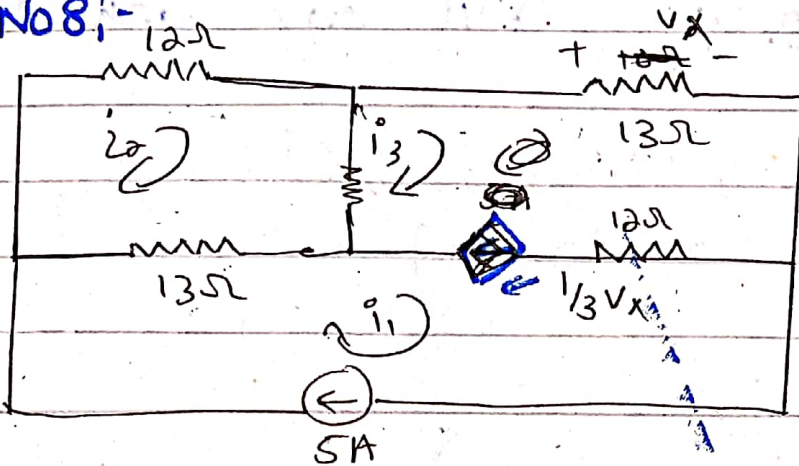

from the fig
we know that
5A current flowing through
 i_1

$$i_1 = 5A$$

Now these is dependent
of source b/w i_1 & i_3

$$i_1 - i_3 = \frac{1}{3} v_x$$

$$\therefore v_x = 18 i_3$$

$$-i_3 = \frac{13 i_3}{3} + 5$$

$$i_3 = -1.5A$$

now on i_2 :-

(17)

$$13(i_2 - i_1) + 11(i_2 - i_3) + 12i_2 = 0$$

$$13i_2 - 13i_1 + 11i_2 - 11i_3 + 12i_2 = 0$$


$$36i_2 - 13(5) - 11(-1.5) = 0$$

$$36i_2 - 65 + 16.5 = 0$$

$$36i_2 = 65 - 16.5$$

$$i_2 = \frac{48.5}{36}$$

$$i_2 = 1.37A$$

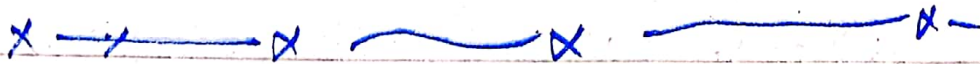


(18)

Chapter # 5:-

Q No 1:-

Figure:-

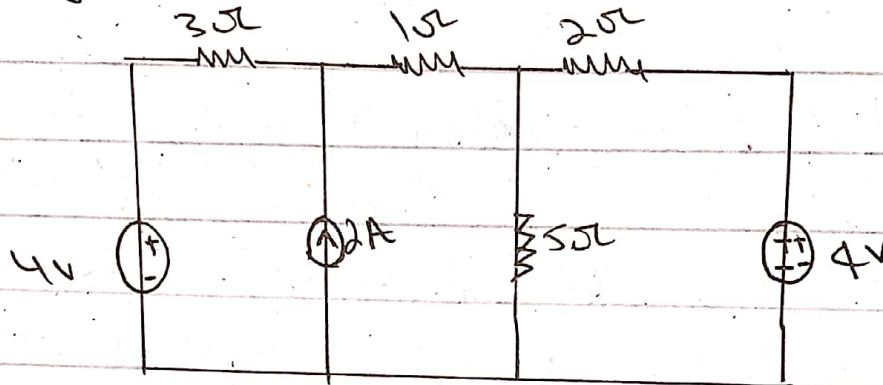

*Solution

Since there are three sources V_1, V_2, V_3

$$V_x = V_1 + V_2 + V_3$$

where V_1, V_2 and V_3 are the contribution due to the left 4V voltage source - 2A current source and the right 4V voltage source respectively.

To obtain V_1 we set the 2A and the right 4V source to zero as shown below -

(19)

Apply mesh analysis to the two meshes 1 and 2, we obtain the following matrix equation.

$$\begin{bmatrix} 3 + 1 + 5 & -5 \\ -5 & 5 + 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix}$$


we find

$$i_2 = \frac{14}{19} \text{ A}$$

For 2Ω resistor, ohm's law gives

$$V_1 = 1 \cdot i_2 = \frac{14}{19} \text{ V} \approx 736.84 \text{ mV}$$

$$V_1 = 736.84 \text{ mV}$$

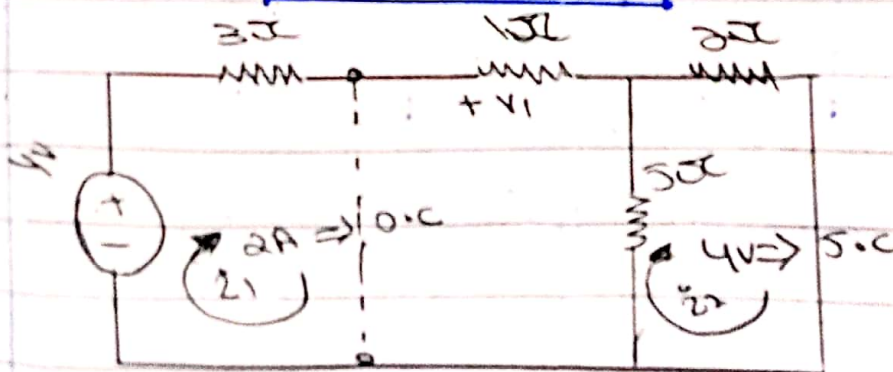

To obtain V_2 we set the two 4V source to zero as shown below. Apply nodal analysis to

(20)

The two node v_a and v_b
we obtain the following
matrix equation -


$$\begin{bmatrix} \frac{1}{3} + 1 & -1 \\ -1 & 1 + \frac{1}{3} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} 2 \\ 9 \end{bmatrix}$$

matrix equation we find
 $v_a = 51$ and $v_b = 21$

By inspection it is clear
that.

$$v_a = v_a - v_b = \frac{51}{19} - \frac{30}{19} = \frac{21}{19}$$

$$v_a = 1.05 \text{ V}$$

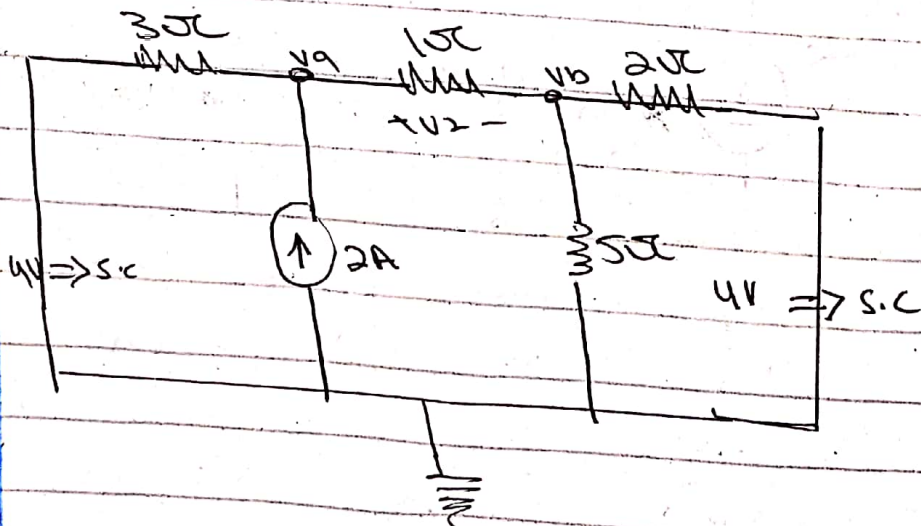

(21)

To obtain V_3 we set the ~~20~~ and the left 40 source to zero as shown below. Apply mesh analysis to the two meshes and we obtain the following matrix equation -

$$\begin{bmatrix} 3+1+5 & -5 \\ -5 & 5+2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 6 \\ 4 \end{bmatrix}$$

The matrix equation we find

$$i_1 = \frac{-10}{19} \text{ A}$$

For the 1 ohm resistor ohm's law gives:-

$$V_3 = 1 \cdot i_1 = \frac{-10}{19} \text{ V}$$

$$V_3 = -526.32 \text{ mV}$$


Therefore

$$V_1 = V_0 + V_2 + V_3$$

(22)

$$V_x = 736.84 \mu\text{V} + 1.05 \text{V} - 526.32 \mu\text{V}$$

$$V_x = 1.0316 \text{V}$$

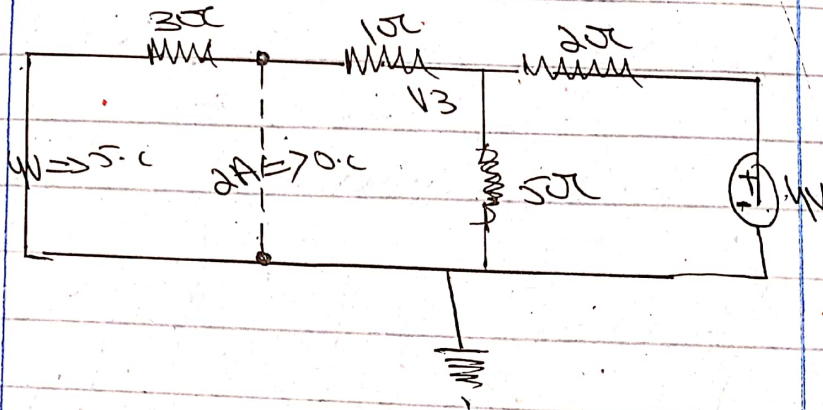

it is required to evaluate the values of the current source that results in reducing the V_x value by 10%. let the new values of V_x is V_x' . the current source values affects only its contribution which is V_2 . let the new values of V_2 is V_2' .

23

$$V_1 = 0.91V = 0.91 \cdot 316V$$

$$V_X = 1.1844V$$

and

$$V_2 - V_1 - (V_1 + V_3) = 1.1844V - (736.84 \mu V) - 526.30 \mu V = 9.7388 \text{ mV}$$

Apply nodal analysis to the two nodes V_a and V_b in the circuit shown below gives.

$$1cs = \left(1 + \frac{1}{3}\right) V_a - V_b \quad \text{--- (1)}$$

$$0 = -V_a + \left(1 + \frac{1}{5} + \frac{1}{2}\right) V_b \quad \text{--- (2)}$$


we have

$$V_a - V_b = V_2 = 9.7388 \text{ mV} \quad \text{--- (3)}$$

Solving the three equations

(1), (2) and (3) we have

$$1cs = 1.7623A$$

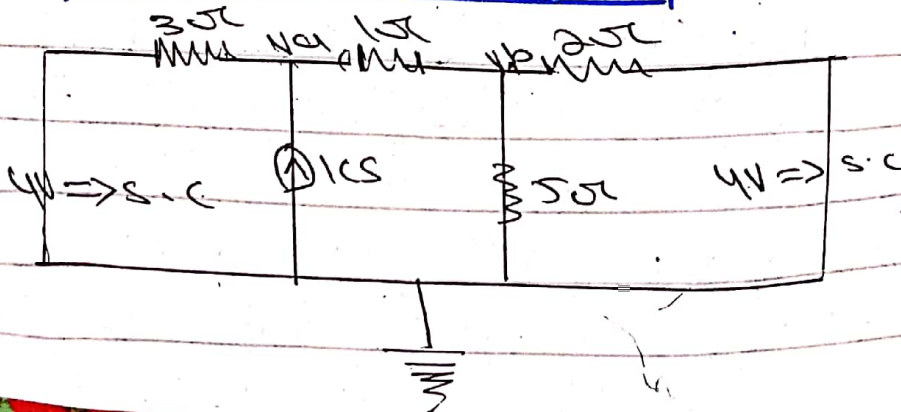


we verify our results
in part (a) using
resistor as shown below
we obtain:-

$$V_x = 6.053 - 4.737$$
$$= \boxed{1.316V}$$

* * *
Q No 2:-

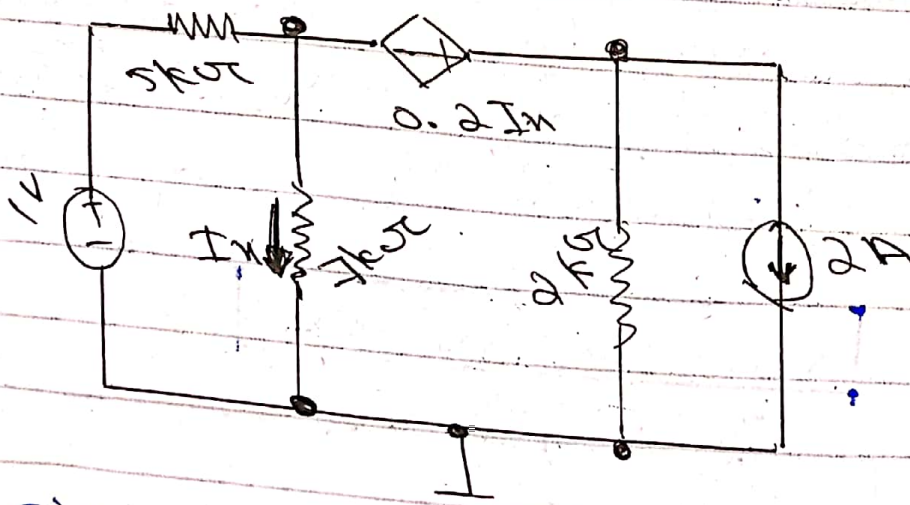employ superposition principle
to obtain the current
 I_x as labeled.



Since there are two
independent sources -
let us find I_x and

(25)

I_{n2} are the contribution due to voltage source and 2A current source respectively.

To obtain I_{n1} we set the 2A current source to zero (replacing it with an open circuit) as shown below.

Apply KCL to the superposition x gives.

$$\frac{V_1 - I}{5000} + \frac{V_1}{7000} + \frac{V_2}{2000} = 0$$

But

$$V_2 = V_1 + 0.2 I_{n2} \text{ here}$$

$$\frac{V_1 - I}{5000} + \frac{V_1}{7000} + \frac{V_1 + 0.2 I \times 1}{2000} = 0$$

But

$$V_1 = 7000 I_{n2} \text{ hence}$$


(20)

$$\frac{7000 I_{N1} - 2 + 7000 I_{N1}}{5000} + \frac{7000 I_{N1}}{7000}$$

$$+ \frac{7000 I_{N1} + 0.2 I_{N1}}{2000} = 0$$

Then

$$I_{N1} = 38.9 \mu A$$

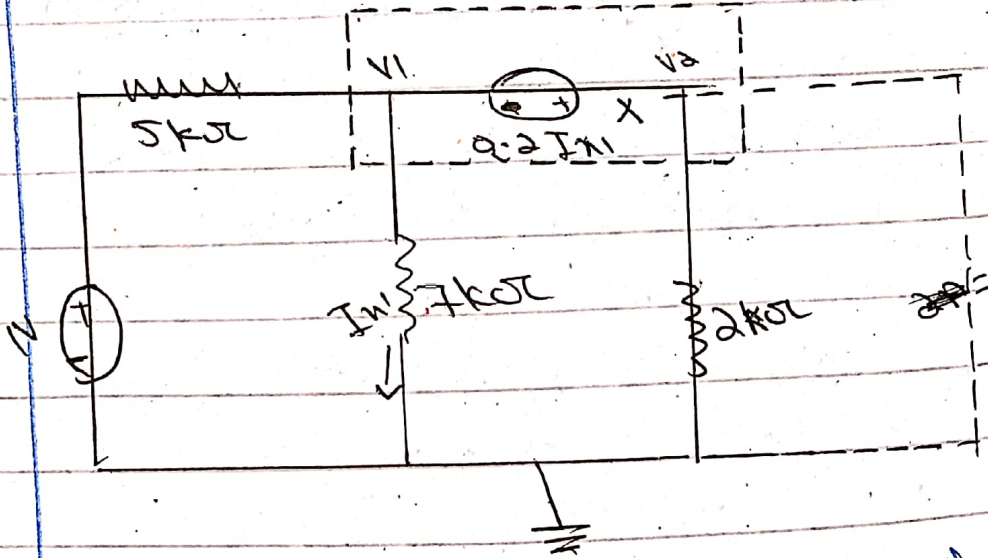

To obtain I_{N2} we set the (v) voltage source to zero as shown below.

Apply KCL to the super node γ given

$$\frac{V_1}{5000} + \frac{V_1}{7000} + \frac{V_2}{2000} = -2$$

But

$$V_1 = 7000 I_{N2} \text{ hence}$$

(27)

$$\frac{7000 I_{n1} + 7000 I_{n2} + 7000 I_{n2}}{5000}$$

$$= -2$$


Thus

$$I_{n2} = -338.98 \text{ mA}$$

Therefore,

$$I_n = I_{n1} + I_{n2} \\ = 33.9 \mu\text{A} + (-338.8 \text{ mA})$$

$$I_n = -338.95 \text{ mA}$$

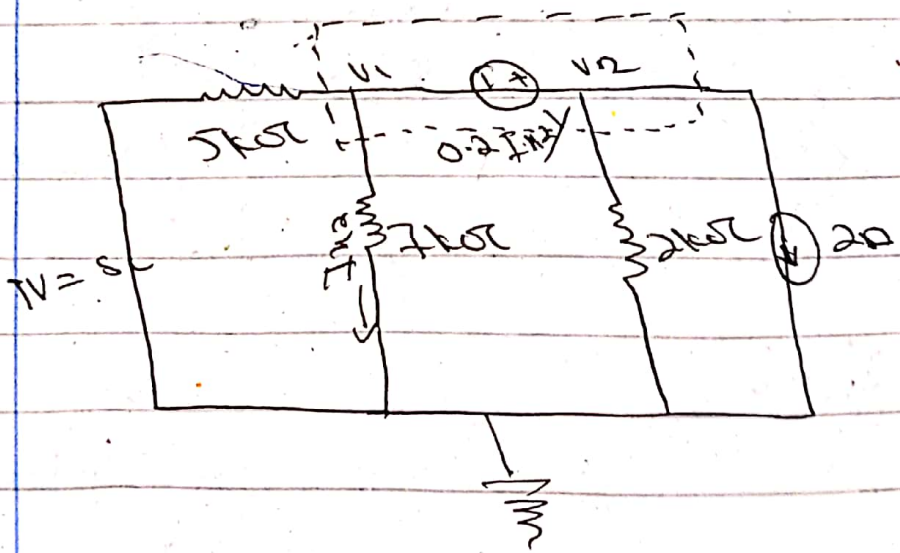



Result

$$I_n = -338.95 \text{ mA}$$

* ————— *

Q No 3:-

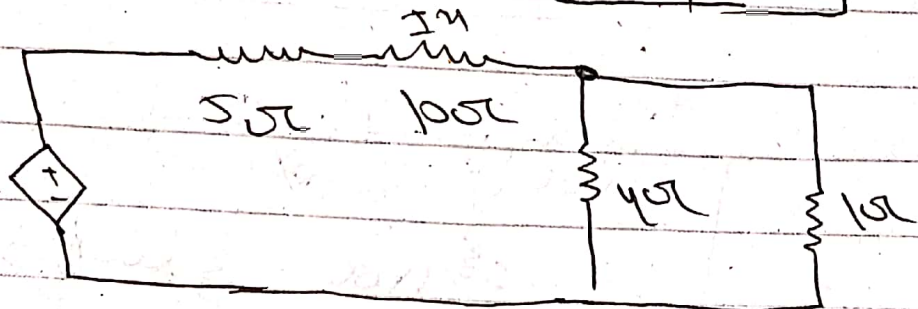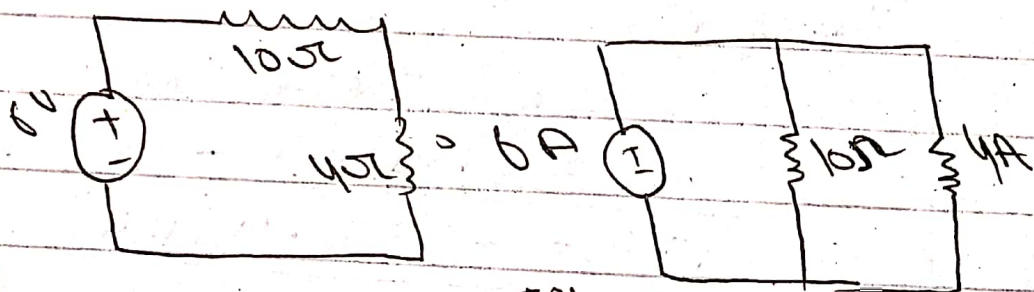perform an appropriate source transformation on each of the circuit depicted in 5.58, taking care to retain 4Ω resistor in each final circuit.



Solution

To get the value of the new source we use-

$$I = \frac{V}{R}$$


$$I = \frac{6}{10}$$

$$I = 0.6A$$

(29)

And

we can draw the circuit as:

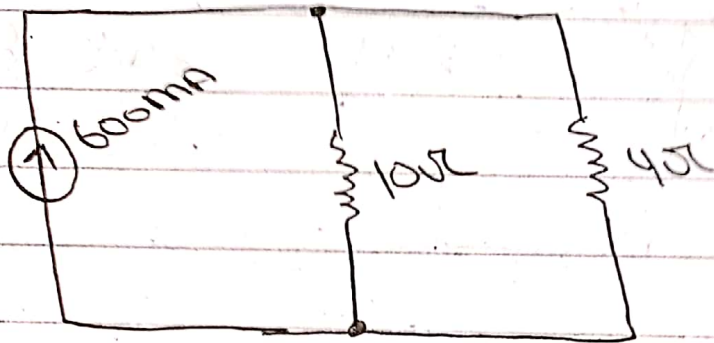


The new voltage source will have the of:

$$V = 10 \cdot I$$

$$V = 600$$

And

we draw it as:

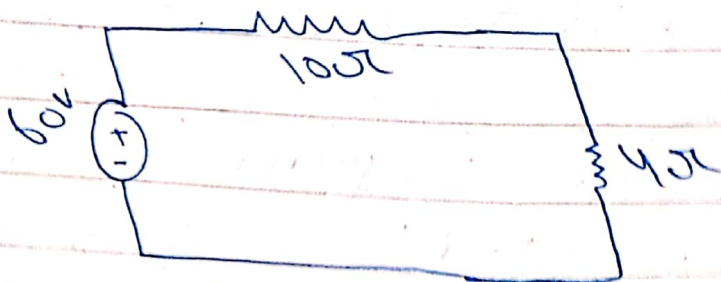


To get the value of the new current source we use

$$I = \frac{V}{R}$$

$$I = \frac{60}{14}$$

$$I = 4.2857$$

and we draw it as:

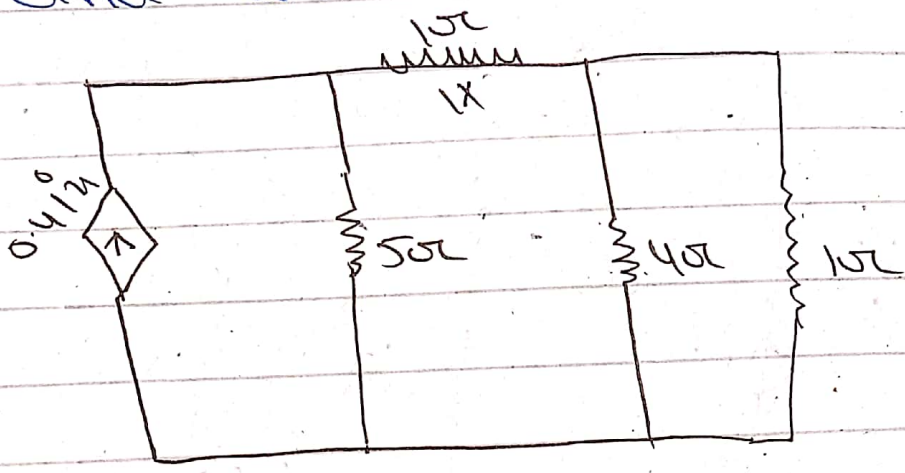

Results:-

(a) we replace the ~~100Ω~~ resistor and the voltage source with a $600mA$ current source in parallel with a 100Ω resistor.

(b) we replace the 100Ω resistor and a current source with a steady voltage ($60V$) source in series with a 100Ω resistor.

(c) we replace the 50Ω resistor and the

(31)


dependent voltage source
with a dependent current
source labeled $0.4i_x$ in
parallel with a 5Ω resistor



Q No 4:-

(a) Determine the Thevenin
equivalent of the network
to R_L .

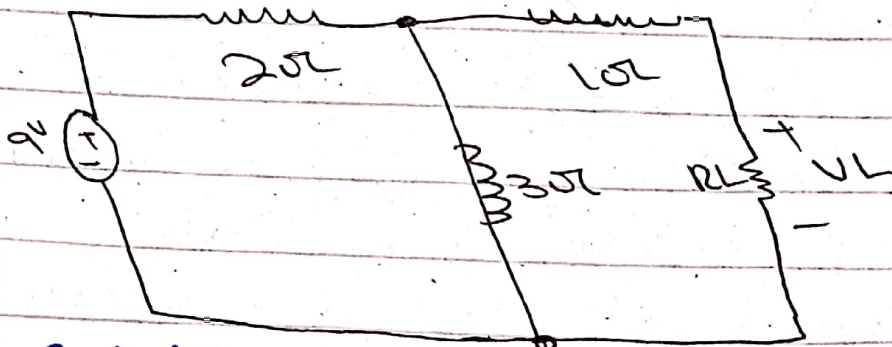(b) Determine V_L for R_L
 $= 1\Omega, 3.5\Omega, 6.25\Omega$ and 9.8Ω



Solution :-

To get V_{TA} we
disconnect R_L and find
the voltage b/w the
two disconnected point - As
we can see. This voltage
is the one in the 3Ω

30

$$V_{Th} = 9V \cdot \frac{3}{11}$$

$$V_{Th} = 5.4V$$

We can calculate R_{Th} as:-

$$R_{Th} = 1 + 3 \parallel 2$$

$$R_{Th} = 2.2 \Omega$$

Then

we calculate V_L as:

$$V_L = V_{Th} \cdot \frac{R_L}{R_L + R_{Th}}$$

for each value of R_L we get

$$R_L = 1 \Omega \Rightarrow V_L = 1.688V$$

$$R_L = 3.5 \Omega \Rightarrow V_L = 3.316V$$

$$R_L = 9.8 \Omega \Rightarrow V_L = 4.41V$$

$$R_L = 6.257 \Omega \Rightarrow V_L = 3.995V$$

Result:-

$$V_{Th} = 5.4V, R_{Th} = 2.2 \Omega$$


$$V_L = 1.688V, 3.316V, 3.995V$$

and 4.41V

33

Q No 5:-

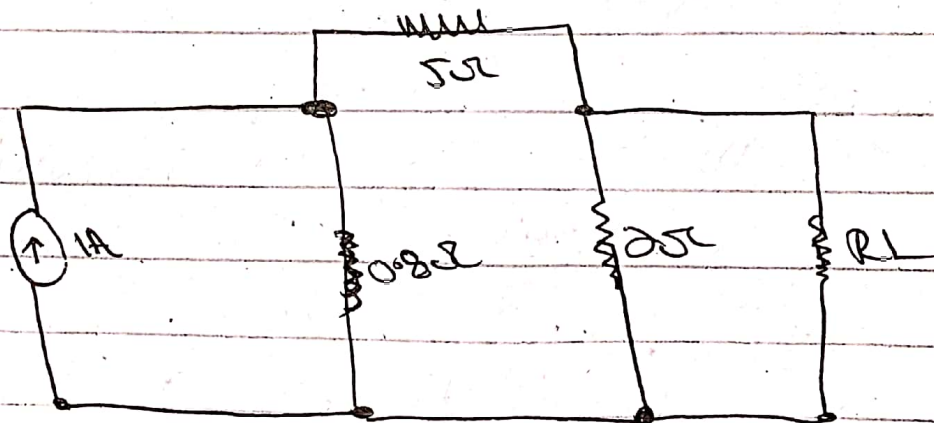- (a) obtain the Norton equivalent of the network connected to R_L
- (b) obtain Thevenin equivalent of the same network -
- (c) Use either to calculate it for $R_L = 0.5\Omega, 1\Omega, 4.923\Omega$ and 8.107Ω .



Solution

(a) we calculate R_N as:

$$R_N = (0.8 + 5 \parallel 2) \parallel 1$$

$$R_N = 3.311\Omega$$

$$R_N = 1.245\Omega$$

36

For i_N we have:

$$i_N = \frac{0.8}{0.8 + 2.5}$$

$$i_N = 0.242 \text{ A}$$

(b)

Now we can V_{Th} as:
 $V_{Th} = i_N \cdot R_N$

$$V_{Th} = 0.302 \text{ V}$$

(c)

Using Thevenin equivalent
we get.

$$i_L = \frac{V_{Th}}{R_{Th} + R_L}$$

for each value of R_L
giving as

(1) $R_L = 0 \Omega \Rightarrow i_L = 0.243 \text{ A}$

(2) $R_L = 1 \Omega \Rightarrow i_L = 0.135 \text{ A}$

(3) $R_L = 4.923 \Omega \Rightarrow i_L = 0.049 \text{ A}$

35

$$\textcircled{1} R_L = 8.107 \Omega \Rightarrow i_L = 0.032 \text{ A}$$

Result:-

(a)

$$i_N = 0.242 \text{ A}, R_N = 1.245 \Omega$$

(b)

$$V_{Th} = 0.302 \text{ V}, R_{Th} = 1.245 \Omega$$

(c)

$$i_L = 0.243 \text{ A}, 0.135 \text{ A}, 0.049 \text{ A}, 0.032 \text{ A}$$




(36)

Question nodi-


part 1:

E.g 4.21-

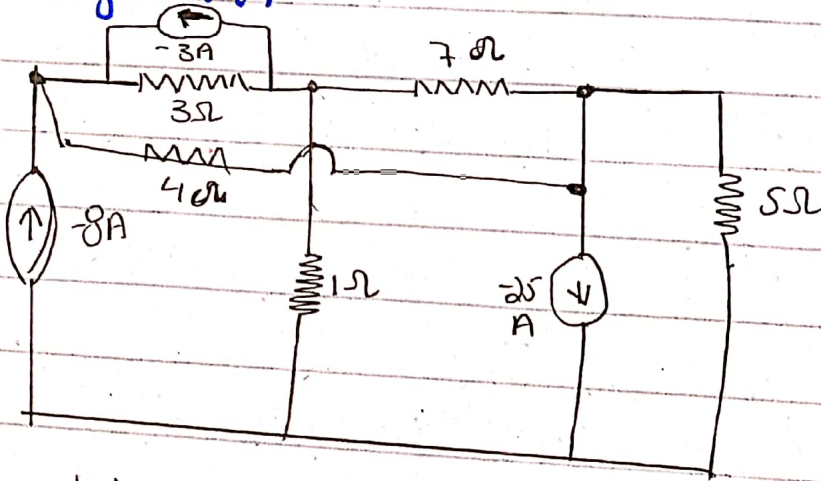

determine the nodal voltage for the circuit as referenced to the bottom node.

by simplifying the diagram.

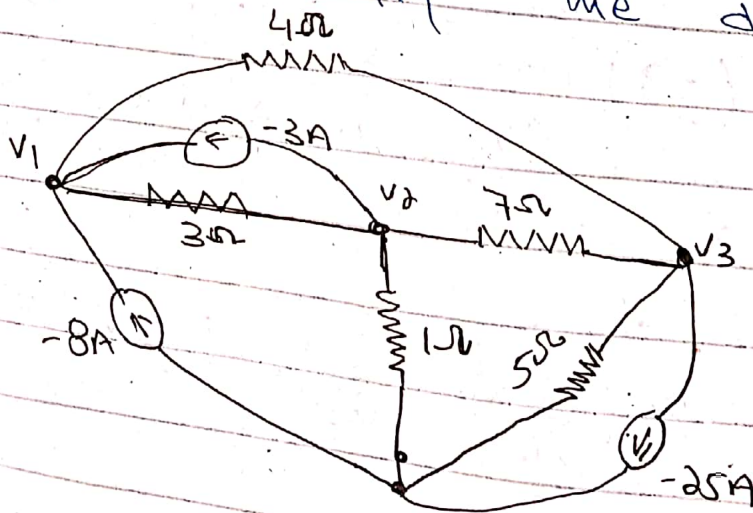

(37)

Now Apply KCL at V_1 :-

$$-8 - 3 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4}$$

$$-11 = \frac{4V_1 - 4V_2 + 3V_1 - 3V_3}{12}$$

$$\frac{7V_1 - 4V_2 - 3V_3}{12} = -11$$

$$7/12 V_1 - 4/12 V_2 - 3/12 V_3 = -11$$

$$0.58V_1 - 0.33V_2 - 0.25V_3 = -11 \rightarrow (1)$$

at V_2 :-

$$-(-3) = \frac{V_2 - V_1}{3} + \frac{V_2}{1} + \frac{V_2 - V_3}{7}$$

$$3 = \frac{7V_2 - 7V_1 + 21V_2 + 3V_2 - 3V_3}{21}$$

$$\frac{31}{21} V_2 - \frac{7}{21} V_1 - \frac{3}{21} V_3 = 3$$

$$-0.25V_1 + 1.4V_2 - 0.14V_3 = 3 \rightarrow (2)$$

(38)

at v_3 :-

$$-(-25) = \frac{v_3}{5} + \frac{v_3 - v_2}{7} + \frac{v_3 - v_1}{4}$$

$$= \cancel{25}$$

$$\Rightarrow -0.25v_1 - 0.14v_2 + 0.59v_3 = 25 \rightarrow (3)$$

write eqv ① ② ③ in
matrix form

$$\begin{bmatrix} 0.58 & -0.33 & -0.25 \\ -0.25 & 1.47 & -0.14 \\ -0.25 & -0.14 & 0.59 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -11 \\ 3 \\ 25 \end{bmatrix}$$

A

Now $|A|$ $\begin{vmatrix} 0.58 & -0.33 & -0.25 \\ -0.25 & 1.47 & -0.14 \\ 0.25 & -0.14 & 0.59 \end{vmatrix}$

$$|A| = 0.316$$

$$Ax = b \Rightarrow \begin{vmatrix} -11 & -0.33 & -0.25 \\ 3 & 1.47 & -0.14 \\ 25 & -0.14 & 0.59 \end{vmatrix}$$

$$|Ax| = 1.714$$

(39)

$$A_1 = \begin{bmatrix} 0.58 & -11 & -0.28 \\ -0.33 & 3 & -0.28 \\ -0.28 & 25 & 0.09 \end{bmatrix}$$

$$|A_1| = 2.4$$

$$|A_2| = \begin{bmatrix} 0.58 & -0.33 & -11 \\ -0.33 & 1.47 & 3 \\ -0.28 & -0.14 & 25 \end{bmatrix}$$

$$|A_2| = 14.6$$

Now

from Cramer's Rule

$$V_1 = \frac{|A_x|}{|A|} = \frac{1.714}{0.316} = 5.41$$

$$V_1 = 5.41V$$

$$V_2 = \frac{|A_y|}{|A|} = \frac{2.4}{0.316} = 7.73V$$

$$V_2 = 7.73V$$

$$V_3 = \frac{|A_z|}{|A|} = \frac{14.6}{0.316} = 46.3V$$

$$V_3 = 46.3V$$


(40):

Result


$$V_1 = 5.41 \text{ V}$$

$$V_2 = 7.73 \text{ V}$$

$$V_3 = 46.3 \text{ V}$$

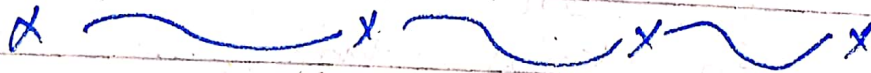

Example: 4.31:

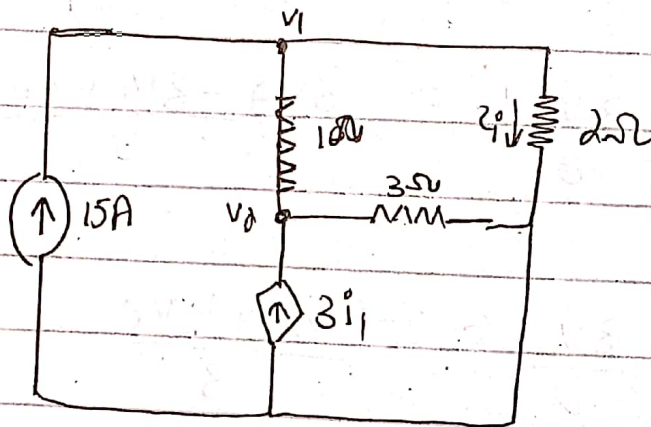

Find power supply
by dependent source.

Apply KCL at V_1

$$15 = \frac{V_1 - V_2}{1} + \frac{V_1}{2}$$

$$15 = \frac{2V_1 - 2V_2 + V_1}{2}$$

$$15 = 3V_1 - 2V_2 \rightarrow \textcircled{1}$$

(41)

at v_2 :-

$$3i_1 = \frac{v_2 - v_1}{1} + \frac{v_2}{3}$$

$$3i_1 = \frac{3v_2 - 3v_1 + v_2}{3}$$

$$3i_1 = 3$$

We know that

i_1 is current pass through 2Ω resistor

$$i_1 = v_1/2 \quad \text{put in eq}$$

$$\frac{3v_1}{2} = \frac{3v_2 - 3v_1 + v_2}{3}$$

$$\frac{3v_1}{2} = \frac{-3v_1 + 4v_2}{3}$$

$$9v_1 = -6v_1 + 8v_2$$

$$8v_2 = 9v_1 + 6v_1$$

$$8v_2 = 15v_1$$

$$-15v_1 + 8v_2 = 0 \rightarrow \textcircled{3}$$

now

multiply 5 by eq 1

subtract from eq 3

(42)

$$5(3V_1 - 2V_2 = 15) \quad \text{--- (1)}$$

8

$$15V_1 - 10V_2 = 75$$

$$-15V_1 + 8V_2 = 0$$

$$\hline -2V_2 = 75$$

$$V_2 = -37.5$$

$$\boxed{V_2 = -37.5 \text{ V}}$$

put $V_2 = -37.5 \text{ V}$ in

(3)

$$-15V_1 + (8 \times -37.5) = 0$$

$$-15V_1 - 300 = 0$$

$$-15V_1 = 300$$

$$-V_1 = 20$$

$$\boxed{V_1 = -20 \text{ V}}$$

now we know that

$$I_1 = V_1 / 2$$

$$I_1 = \frac{-20}{2}$$

$$\boxed{I_1 = -10}$$

(43)

power ~~absorbed~~ supplied
by variable source.

$$P = 1.0 \text{ V}$$

$$P = (3I_1)(-37.5)$$


$$= (3(18.5)) \times -37.5$$

$$56.2 \times -37.5$$

$$P = 2.1 \text{ kW}$$



Ex 4.41-

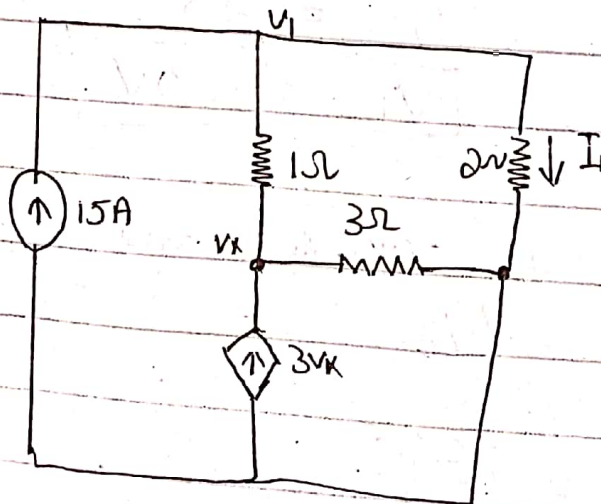

Find Power supplied by
dependent source

(44)

Apply KCL at (V_0)

$$15 = \frac{V_1 - V_0}{1} + 2$$

$$15 = \frac{2V_1 - 2V_0 + V_1}{2}$$

$$3V_1 - 2V_0 = 30 \rightarrow (1)$$

at V_1 :

$$3V_0 = \frac{V_0 - V_1}{1} + \frac{V_0}{3}$$

$$3V_0 = \frac{3V_0 - 3V_1 + V_0}{3} \rightarrow (2)$$

We know that

$$V_0 = \frac{V_2}{3} \text{ put } (1)$$

$$3 \frac{V_0}{3} = \frac{3V_0 - 3V_1 + V_0}{3}$$

$$3V_0 = 4V_0 - 3V_1$$

$$V_0 - 3V_1 = 0 \rightarrow (3)$$

(45)

Add eq ① & ③

$$3V_1 - 2V_2 = 30$$

$$-3V_1 + V_2 = 0$$

$$V_2 = 30$$

here $V_2 = V_x$

Power

Supply

$$P = \frac{V^2}{R} = \frac{(30)^2}{12}$$

$$\text{Power} = (3V_x)(V_x)$$


$$= (3 \times 30)(30)$$

$$P = 400 \times 30$$

$$P = 8 \text{ kW}$$

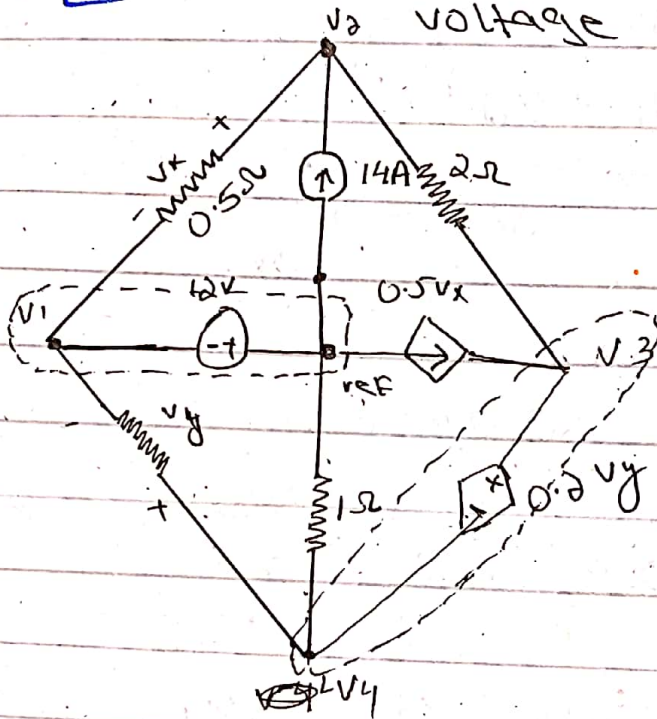(46)

Ex 4.61: Determine the node-to-refer voltage in the circuit.



As from Fig

$$v_1 = 12V$$

Apply KCL at v_2

$$\frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 14$$

$$\frac{4v_2 - 4v_1 + v_2 - v_3}{2} = 14$$

$$\cancel{3} - 4v_1 + 5v_2 - v_3 = \cancel{28} \rightarrow \text{D}$$

$$-2v_1 + 2.5v_2 - 0.5v_3 = 14 \rightarrow \text{D}$$

(47)

at Supper node v_3 & v_4

$$0.5V_X = \frac{v_3 - v_2}{2} + \frac{v_4 - v_1}{2.5} + \frac{v_4}{1}$$

$$0.5x = \frac{5v_3 - 5v_2 + 4v_4 - 4v_1 + 10v_4}{10}$$

$$0.5V_X = \frac{-4v_1 - 5v_2 + 5v_3 + 14v_4}{10} \quad \text{--- (i)}$$

From Fig

$$0.5V_X = 0.5(v_2 - v_1) \quad \text{put (i)}$$

$$0.5(v_2 - v_1) = \frac{-4v_1 - 5v_2 + 5v_3 + 14v_4}{10}$$

$$0.5v_2 - 0.5v_1 = -4v_1 - 5v_2 + 5v_3 + 14v_4$$

$$-9v_1 + 10v_2 + 5v_3 + 14v_4 = 0 \quad \text{--- (ii)}$$

$$0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 = 0 \rightarrow \text{iii}$$

Now use node

$$-2v_1 - 2.5v_2 - 0.5v_3 = 14 \rightarrow \text{a}$$

$$0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 = 0 \rightarrow \text{b}$$

$$v_1 = 12 \rightarrow \text{c}$$

$$0.2v_1 + v_3 - 1.2v_4 = 0 \rightarrow \text{d}$$

(48)

by solving these equation.

$$V_1 = 12V$$

$$V_2 = -4V$$

$$V_3 = 24V$$


$$V_4 = 1$$

x ~~~~~ x ~~~~~ x ~~~~~ x

Example 4.11 :-

Next - page -

(49)

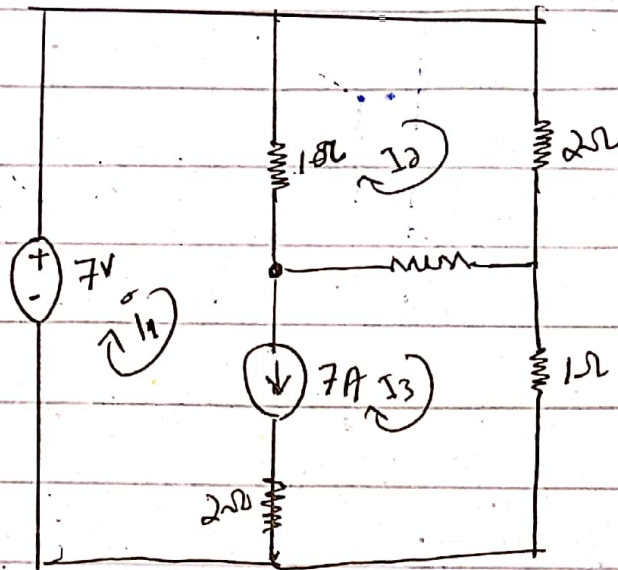

Determine the mesh current.

From Fig

The 7A independent current source is common b/w two meshes so it will be considered as super mesh.

~~Apply KVL to it.~~

at mesh 2:-

$$1(I_2 - I_1) + 3(I_2 - I_3) + 2I_2 = 0$$

$$I_2 - I_1 + 3I_2 - 3I_3 + 2I_2 =$$

$$-I_1 + 6I_2 - 3I_3 = 0 \rightarrow \text{①}$$

(50)

at mesh (2) super mesh.

~~(I₂-I₁)~~

$$-7 + 1(I_1 - I_2) + 3(I_3 - I_2) + 1I_3 = 0$$

$$\Rightarrow \cancel{I_1} - \cancel{4I_2} + 4I_3$$

$$I_1 - I_2 + 3I_3 - 3I_2 + I_3 = 7$$

$$\cancel{I_1} + \cancel{6I_2} - \cancel{3I_3} = \dots$$

$$I_1 - 4I_2 + 4I_3 = 7 \rightarrow \textcircled{\text{ii}}$$

& From Fig its clear

$$\textcircled{\text{iii}} \quad I_1 - I_3 = 7 \quad (\text{iv})$$

Now write (3) eq in matrix.

$$\begin{bmatrix} 1 & -4 & 4 \\ -1 & 6 & -3 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 7 \\ 0 \\ 7 \end{bmatrix}$$

$$|A| = \begin{vmatrix} 1 & -4 & 4 \\ -1 & 6 & -3 \\ 1 & 0 & -1 \end{vmatrix}$$

$$1(-6-0) - (-4)(1-(-3)) + 4(0-6)$$

$$= -6 + 4(1+3) + 4(-6)$$

$$-6 + 16 - 24$$

(57)

$$|A| = -30 + 16$$

$$|A| = -14$$

$$|Ax| = \begin{vmatrix} 7 & -4 & 4 \\ 0 & 6 & -3 \\ 7 & 0 & -1 \end{vmatrix} \text{ Expand column 1}$$

~~by 7~~

$$= 7(-6 - 0) + 0 + 7(12 - 24)$$

$$= -42 + 0 - 84$$

$$|Ax| = -126$$

$$|Ay| = \begin{vmatrix} 1 & 7 & 4 \\ -1 & 0 & -3 \\ 0 & 7 & -1 \end{vmatrix}$$

$$1(0 - (-28)) - 1[-7 - 28] + 0$$

$$|Ay| = 21 - 1(-35)$$

$$= 21 + 35$$

$$|Ay| = 56$$

(52)

$$|A_2| = \begin{vmatrix} 1 & -4 & 7 \\ -1 & 6 & 0 \\ 0 & 0 & 7 \end{vmatrix}$$

$$|A_2| = 1(42) - (-1)28 + 0$$

$$|A_2| = 42 + 28$$

$$|A_2| = 70$$

NOW

$$I_1 = \frac{|A_2|}{|A|} = \frac{70}{7} = 10$$

$$I_1 = 10$$

$$I_2 = \frac{|A_1|}{|A|} = \frac{+56}{+14} = 4$$

$$I_2 = 4$$

$$I_3 = \frac{14}{-14} = -1$$

$$I_3 = -1$$


$$\begin{array}{l} I_1 = 10 \\ I_2 = 4 \\ I_3 = -1 \end{array}$$

Example.

(53)

4.12 :-

Find unknown element of circuit.

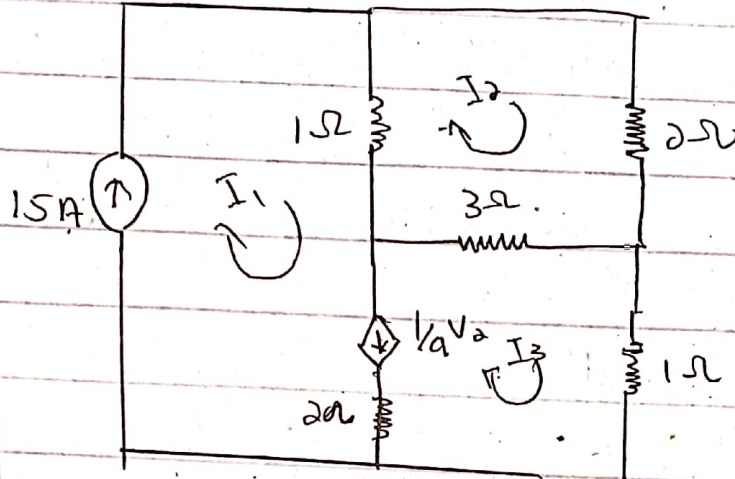

It is clear from circuit

$$I_1 = 15A$$

&

~~Now Apply KVL at I3~~

$$\frac{V_x}{9} = \frac{I_3 - I_1}{1} = \frac{3(I_3 - I_2)}{9}$$

$$I_1 + \frac{1}{9} V_x = I_3$$

$$I_1 + \frac{I_3 - I_2}{3} = I_3$$

$$I_1 + \frac{I_3 - I_2}{3} = I_3$$

(54)

$$\frac{1}{3} I_2 - I_3 \frac{1}{3} - 2I_1 + I_3 = 0$$

$$-I_1 + \frac{1}{3} I_2 + \frac{2}{3} I_3 = 0$$

As $I_1 = 15$

$$-15 + \frac{1}{3} I_2 + \frac{2}{3} I_3 = 0$$

$$\frac{1}{3} I_2 + \frac{2}{3} I_3 = 15$$

$$\Rightarrow I_2 + 2I_3 = 45 \rightarrow \textcircled{1}$$

Apply KVL at mesh 2.

$$1(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) = 0$$

$$I_2 - I_1 + 2I_2 + 3I_2 - 3I_3 = 0$$

$$6I_2 - I_1 - 3I_3 = 0$$

$$6I_2 - 15 - 3I_3 = 0$$

$$6I_2 - 3I_3 = 15 \rightarrow \textcircled{2}$$

(35)

$$I_2 + 2I_3 = 45 \rightarrow \textcircled{1}$$

$$6I_2 - 3I_3 = 15 \rightarrow \textcircled{2}$$

multiply 6 by eq ①
& subtract from ②

$$\begin{array}{r} 6I_2 + 12I_3 = 270 \\ 6I_2 - 3I_3 = 15 \\ \hline -15I_3 = 255 \end{array}$$

$$15I_3 = 255$$

$$I_3 = 17A$$

put $I_3 = 17$ in eq ①

$$I_2 + 3(I_3) = 45$$

$$I_2 + (17 \times 3) = 45$$

$$I_2 = 45 - 51$$


$$I_2 = -6A$$

$$\begin{array}{l} I_1 = 15A \\ I_2 = 17A \\ I_3 = -6A \end{array}$$

(56)

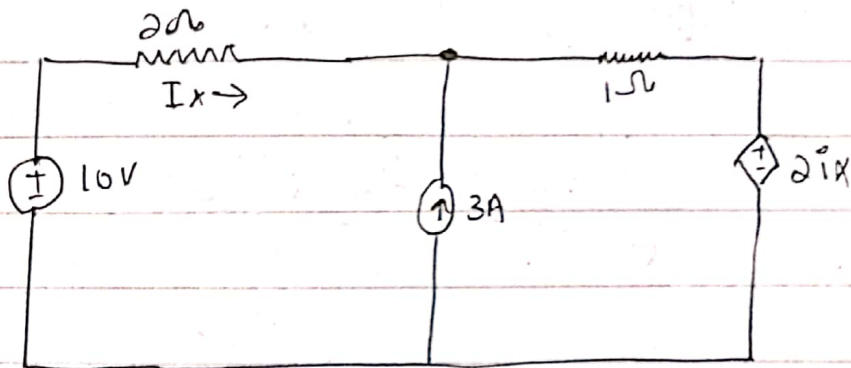
Example 5.31-

Use super position theorem
to determine the value of
 I_x .



Solution:-

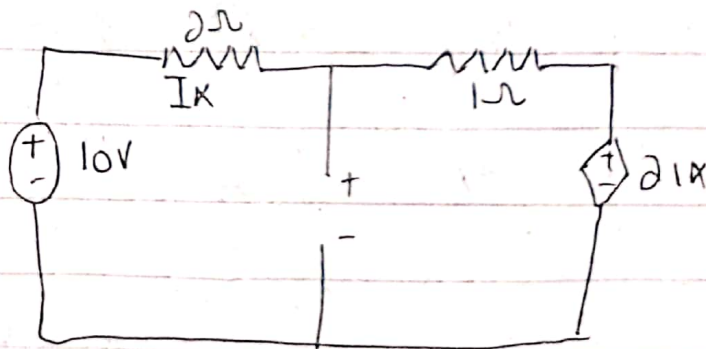first we remove current
source make it open circuit



now apply KVL

~~$2I_x$~~ +

$$-10 + 2I_x' + 1I_x' + 2I_x' = 0$$


$$2I_x' + I_x' + 2I_x' = 10$$

$$5I_x' = 10$$

$$\boxed{I_x' = 2A}$$

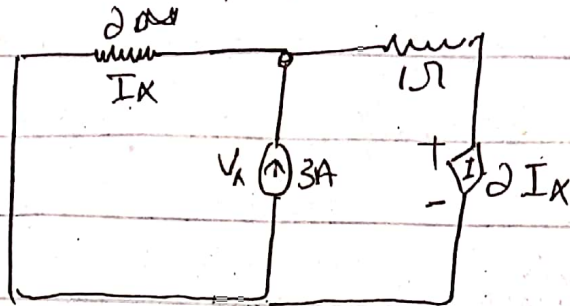(5.7)

NOW we will remove voltage source by short circuit



$$\frac{V_x''}{2} + \frac{V_x'' - 2I_x''}{1} = 3$$

$$\frac{V_x + 2x - 4I_x''}{2} = 3$$

$$3V_x - 4I_x'' = 6 \rightarrow \textcircled{1}$$

NOW

$$V_x = 2(-I_x'') \text{ put in } \textcircled{1}$$

$$V_x = 2(-2)$$

$$3(2 - I_x'') - 4I_x'' = 6$$

$$-6I_x'' - 4I_x'' = 6$$

$$-10I_x'' = 6$$

$$I_x'' = 6/10$$

$$\boxed{I_x'' = -0.6}$$

(58)


Now

$$I_x = I_x' + I_x''$$

$$= 2 + (-0.6)$$

$$= 2 - 0.6$$

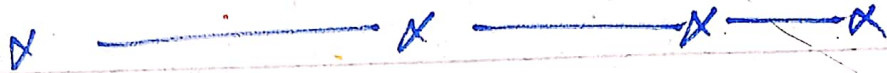
$$I_x = 1.4 \text{ A} \rightarrow \text{Ans}$$



Example

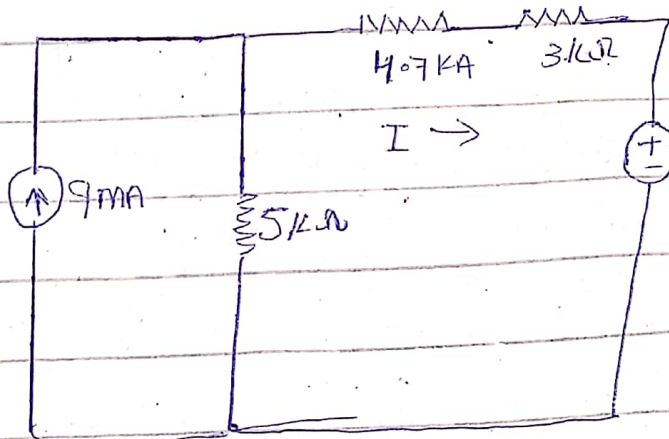(5.4)

Find the current through $4.7 \text{ k}\Omega$ after transforming the 9 mA source into the equivalent voltage source.



Solution:

We know that

$$V = IR$$


$$V = (9 \times 10^{-3}) (5 \times 10^3)$$

$$V = 45 \text{ Volt}$$


(59)

~~Now remove current source~~

~~by open circuit.~~

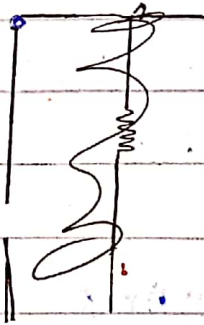

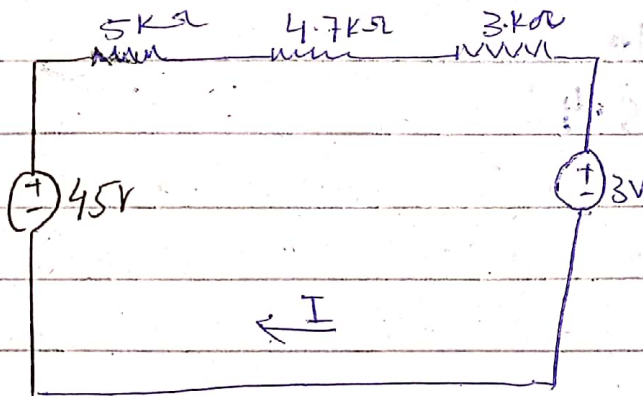Now replace 9A source with 45V source & redraw circuit.



$$AS = V = IR$$

Apply KVL

$$-45 + 5 \times 10^3 I + 4.7 \times 10^3 I + 3 \times 10^3 I + 3 = 0$$

$$5 \times 10^3 I + 4.7 \times 10^3 I + 3 \times 10^3 I = 45 - 3$$

$$(5 + 4.7 + 3) \times 10^3 I = 42$$

$$12.7 \times 10^3 I = 42$$


$$12700 I = 42$$

$$I = 0.0033A \rightarrow \text{Ans.}$$

(60)

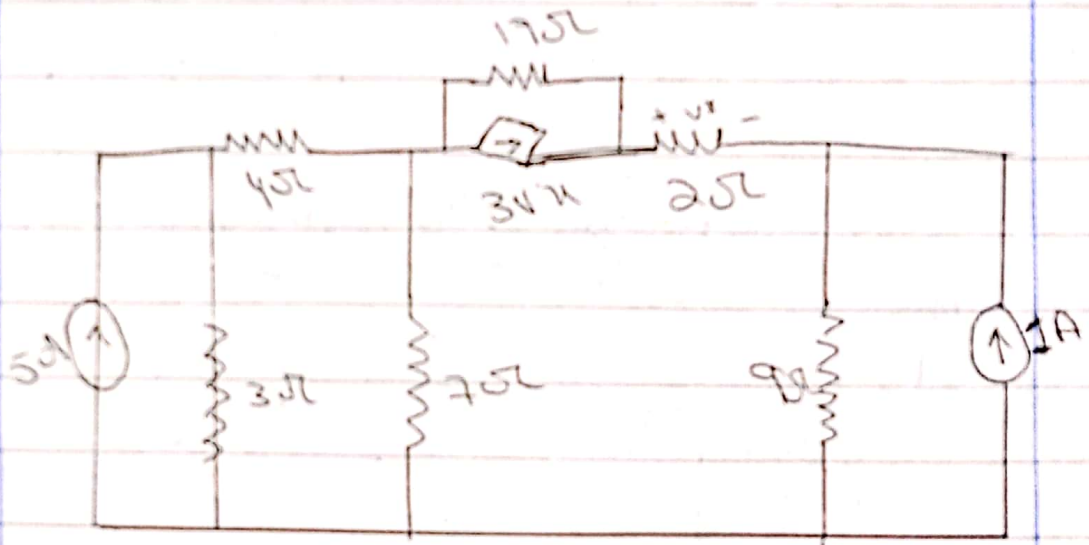Example 4.5i-

calculate the current through the 2Ω resistor by making use of source transformation to first simplify the circuit.



$$V = IR$$


$$V = 5(3)$$

$$V = 15V$$

$$V_x = 3(17)$$

$$V_x = 51$$

Re-drawing a circuit

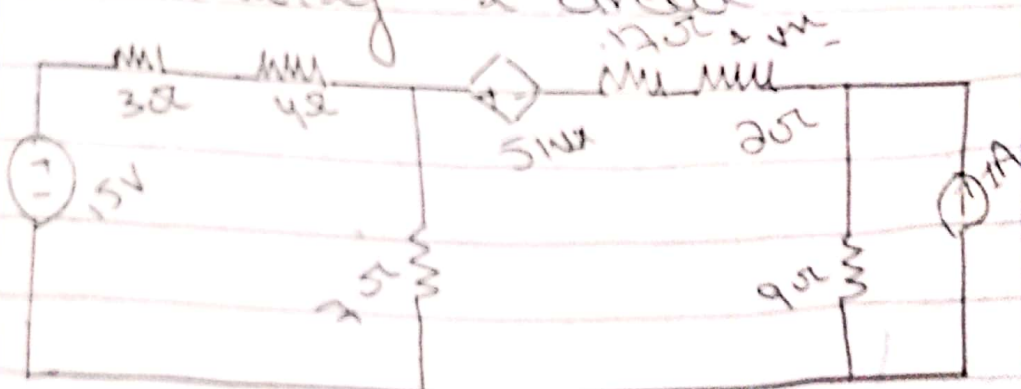

(61)

$$R = 3 + 4$$

$$R = 7\Omega$$


$$I = \frac{V}{R} = \frac{15}{2} = 7.5$$

$$V = IR$$

$$V = 9(1)$$

$$V = 9$$

Re-drawing a circuit.

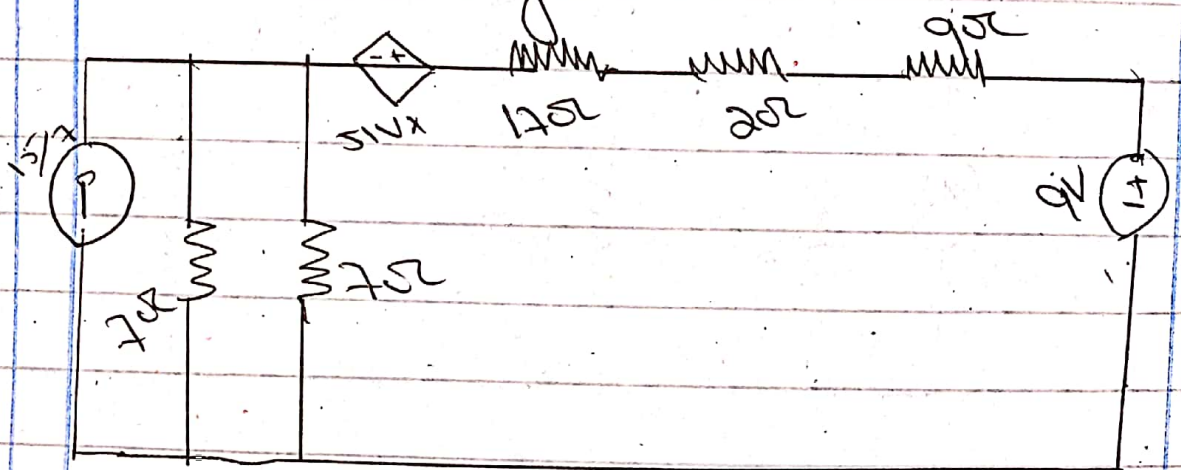

$$V = IR = \left(\frac{5}{17}\right)(7)$$


$$V = 7.5$$

But

$$R = 17 + 9$$

$$R = 26\Omega$$

(62)

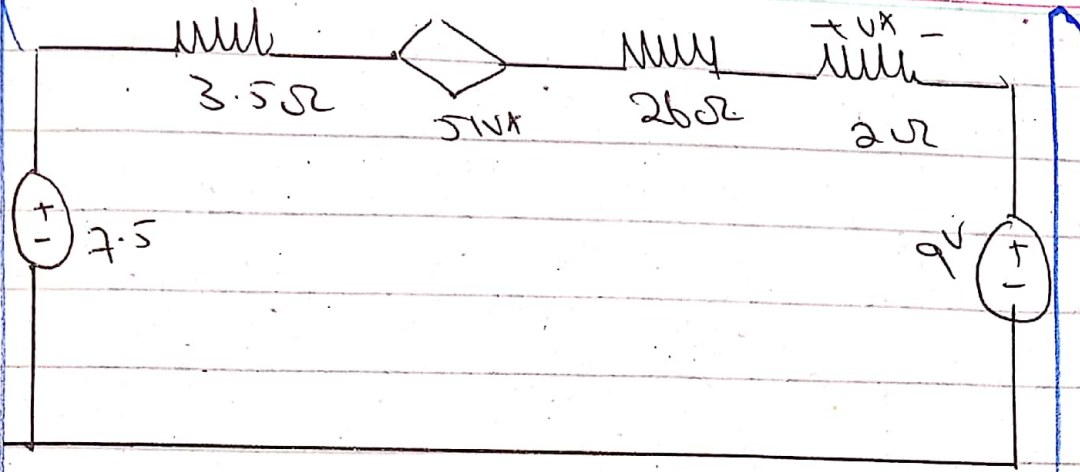

Applying KVL on mesh i

$$3.5i - 5V + 28i = 7.5 - 9$$

$$Vx = 21$$

$$3.5i - 5(22)i + 28i = -1.5$$


$$i = \frac{-1.5}{-10395}$$

$$\Rightarrow i = 0.0014A$$

Example 5.6:-


consider a circuit shown in figure - determine the Thevenin equivalent of network A, and compute the power delivered to the load resistor R_L .

(63)

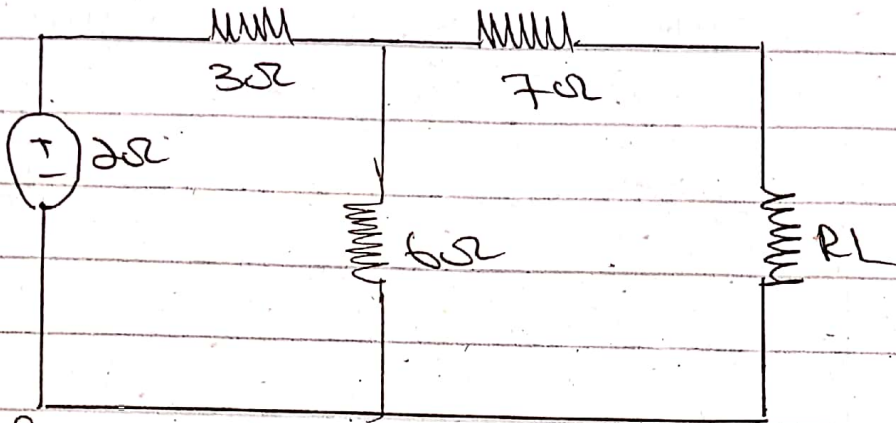


Solution

$$I = \frac{V}{R} = \frac{12}{3} = 4A$$

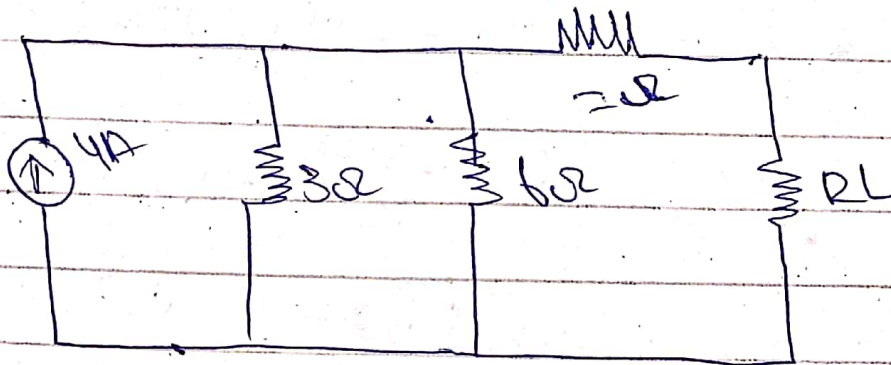

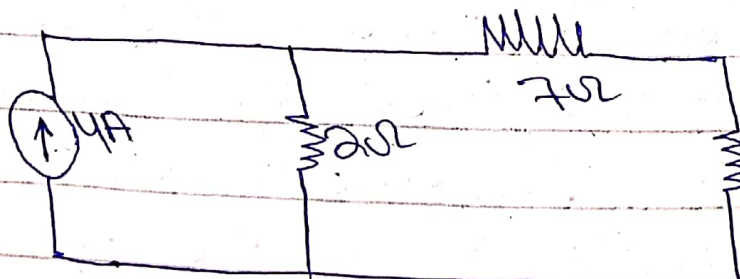
$$R_{eq} = \frac{3 \times 6}{3 + 6} = 2\Omega$$




$$V = IR = 4(2)$$

$$V = 8V$$

(64)

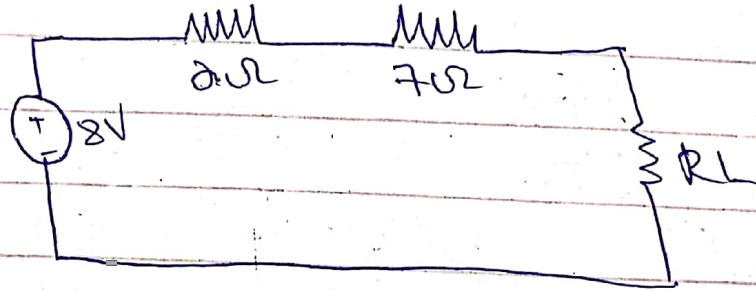

$$R = 2 + 7 = 9\Omega$$

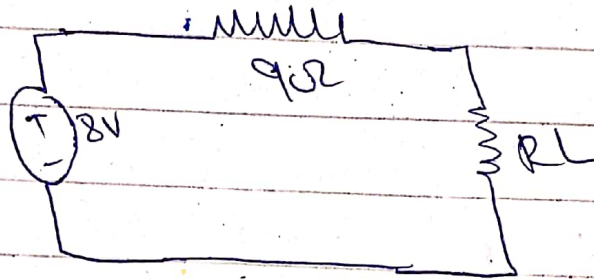

$$V_{Th} = 8V$$

$$R_{Th} = 9\Omega$$

$$R_{op} = (8)^2 RL$$


$$7TRL$$

For any value of R_L
with have different
solution.


Example 5.7:-

Use Thevenin's Theorem
determine the Thevenin
equivalent for that part
of the circuit in to
the left of R_L .

(65)

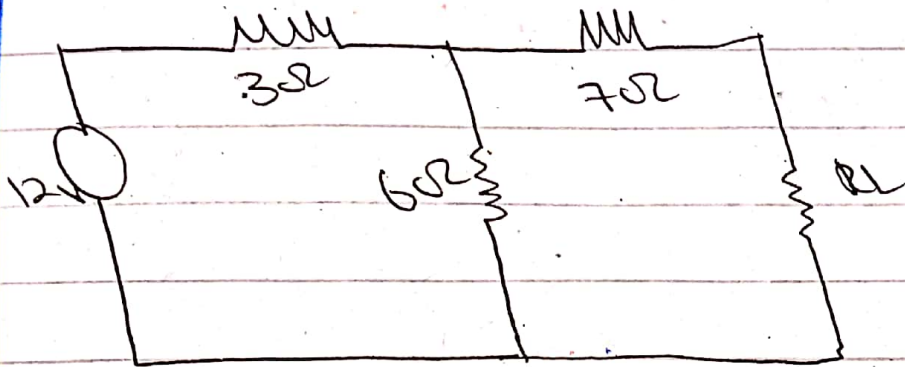

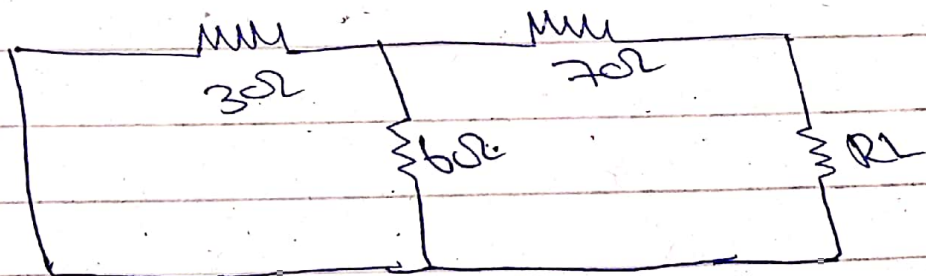For finding R_{Th} we will remove voltage source and make it is a short circuit.



For R_{Th} we will add all the resistors except


R_L -

$$R_{Th} = 3 \parallel 6 + 7$$
$$= \frac{18}{2} + 7$$

$$R_{Th} = 9$$

For V_{oc} we will remove R_L and make it's an open circuit -

(16)

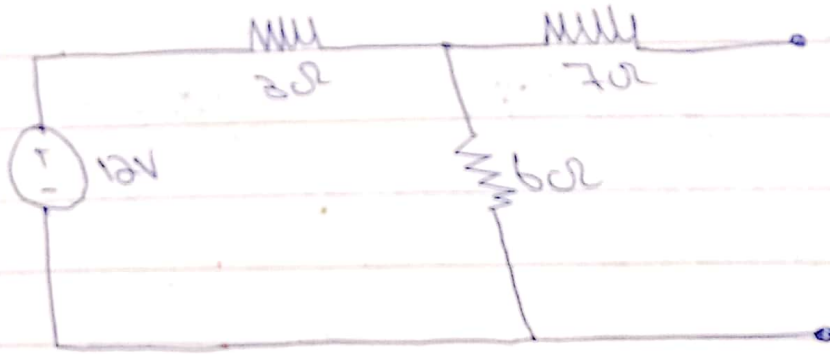


$$V_{oc} = 12 \left(\frac{6}{3+6} \right)$$

$$V_{oc} = 8V$$

* ————— *


Q No 3i:

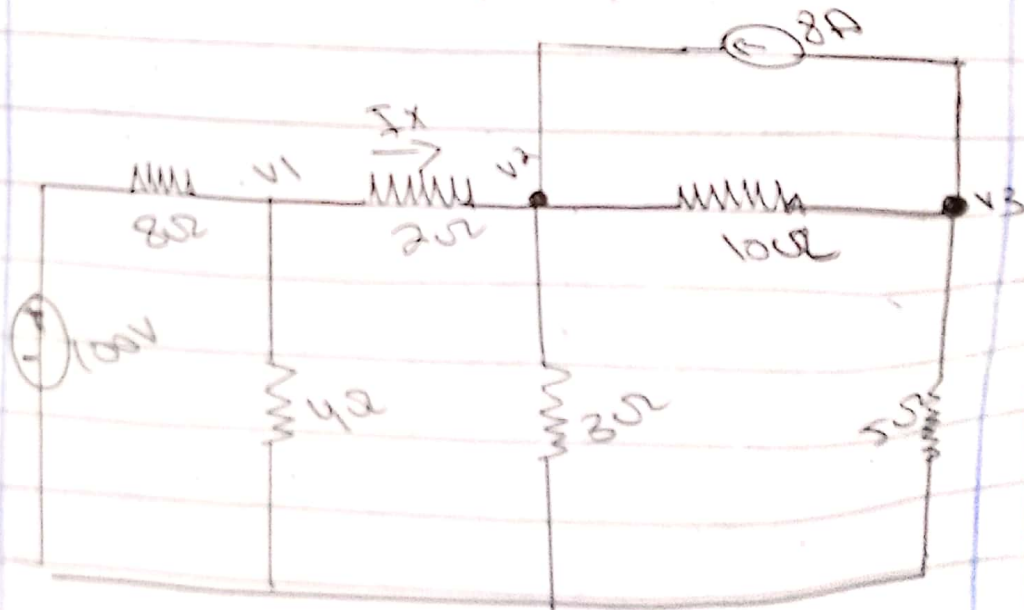Find the value of I_x for the circuit using nodal analysis, mesh analysis and superposition theorem.



(67)

Nodal Analysis :-

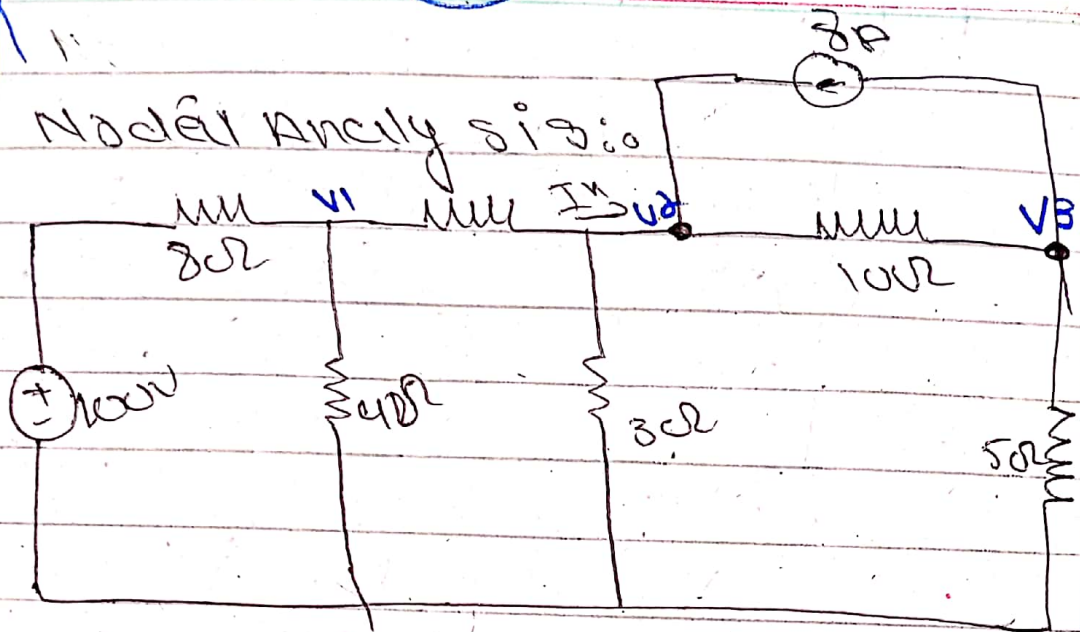

Solution:-

1) Apply nodal analysis (KCL) on node 1 (V1).

$$\frac{V_1 - 100}{2} + \frac{V_1}{4} + \frac{V_1 - V_2}{3} = 0$$

$$3V_1 - 100 + 2V_1 + 4V_1 - 4V_2 = 0$$

$$7V_1 - 4V_2 = 100 \quad \text{--- (1)}$$

Apply KCL on node 2 (V2).

$$\frac{V_2 - V_1}{3} + \frac{V_2}{10} + \frac{V_2 - V_3}{18} = 8$$

$$30V_2 - 30V_1 + 20V_2 + 3V_2 + 3V_3 = 8 \times 60$$

(b8) $P = I \cdot V$
=

$$-30V_1 + 53V_1 - 3V_3 = 480 \quad \text{--- (i)}$$

Apply KCL on node 3
i.e. V_3 :-

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = -8$$

$$\frac{V_3 - V_2 + 2V_3}{10} = -8$$

$$\frac{-V_2 + 3V_3}{10} = -8$$

$$-V_2 + 3V_3 = -80 \quad \text{--- (ii)}$$

Taking eq (i)

$$7V_1 - 4V_2 = 120$$

$$V_1 = \frac{4V_2 + 120}{7} \quad \text{--- (a)}$$

Taking eq (ii)

$$-V_2 + 3V_3 = -80$$

$$V_3 = \frac{V_2 - 80}{3} \quad \text{--- (b)}$$

putting eq (a) and (b) on eq (i)

$$-30(0.571V_2 + 17.14) + 53V_2 - 3(0.333V_2 - 26.67) = 480$$

(69)

$$-17.1V_2 - 428.4 + 53V_2 - 0.99V_2 + 80.01 = 480$$

$$34.91V_2 = 828.39$$

$$V_2 = \frac{828.39}{34.91}$$

$$V_2 = 20.31$$

Putting in eq (a)

$$V_1 = 4(20.31) + 100$$


$$V_1 = 25.89$$

$$i_N = \frac{V_1 - V_2}{2} = \frac{25.89 - 20.31}{2}$$

$$i_N = 2.79A$$

Ans:

Mesh analysis

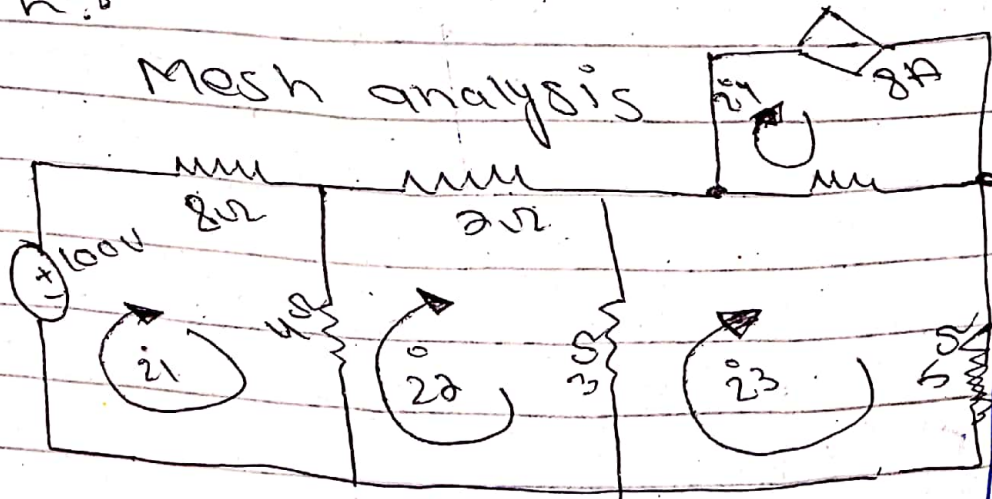

70

Apply KVL on loop I:

$$8i_1 + 4(i_2 + i_2) = 100$$

$$8i_1 + 4i_2 - 4i_2 = 100$$

$$12i_2 - 4i_2 = 100 \quad \text{--- (1)}$$

Apply KVL on loop II:-

$$2i_2 + 4(i_2 - i_2) + 3(i_3 - i_2) = 0$$

$$2i_2 + 4i_2 - 4i_2 + 3i_3 - 3i_2 = 0$$

$$-4i_2 + 9i_2 - 3i_3 = 0 \quad \text{--- (2)}$$

Apply KVL on loop III:-

$$3(i_3 - i_2) + 10(i_3 - i_4) + 5i_3 = 0$$

$$3i_3 - 3i_2 + 10i_3 - 10i_4 + 5i_3 = 0$$

$$\text{As } i_4 = 8$$

$$-3i_2 + 18i_3 = -80 \quad \text{--- (3)}$$

Taking eq (1)

$$i_1 = 4i_2 - 100 \quad \text{--- (4)}$$

12

Taking eq (3)

$$-3i_2 + 18i_3 = -80$$

$$i_3 = \frac{-3i_2 + 80}{18} \quad \text{--- (5)}$$

18

Putting eq (4) and (5) in eq (2)

(71)

$$-4(0.33i_2 - 8.33) + 9i_2 - 3(0.16i_2 + 4.44) = 0$$


$$\Rightarrow -1.32i_2 + 33.32 + 9i_2 - 0.48i_2 - 13.21 = 0$$

$$7.2i_2 = -10.11$$

$$i_2 = \frac{-10.11}{7.2} \Rightarrow i_2 = -1.404A$$

$$i_2 = 2.79A \Rightarrow \boxed{i_x = 2.79A}$$

3: Superposition Theorem.

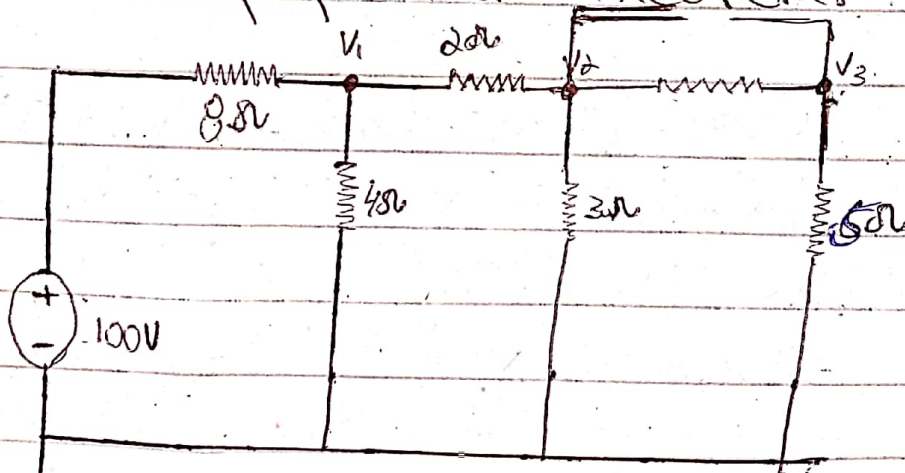

rem: redraw circuit by remove current source by open circuit.

Apply KCL on Node 1 v_1 :

$$\frac{-100 + v_1}{8} + \frac{v_1 - v_2}{2} + \frac{v_1}{4} = 0$$

(7a)

$$\frac{V_1 - 100 + 4V_1 - 4V_2 + 2V_1}{8} = 0$$

$$7V_1 - 4V_2 = 100 \rightarrow (i)$$

Apply KCL on Node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{3} + \frac{V_2 - V_3}{10} = 0$$

~~$5V_2 = 5V_1$~~

$$\frac{15V_2 - 15V_1 + 10V_2 + 3V_2 - 3V_3}{30} = 0$$

$$-15V_1 + 23V_2 - 3V_3 = 0 \rightarrow (ii)$$

at Node 3:

$$\frac{V_3 - V_2}{10} + \frac{V_3}{5} = 0$$

~~$2V_3 = 2V_2$~~

~~$\frac{V_3 - V_2 + 2V_3}{10} = 0$~~

$$-V_2 + 3V_3 = 0 \rightarrow (iii)$$

(73)

Now From eqn (1) &

$$7V_1 - 4V_2 = 100$$

~~$$-4V_2 = 100 - 7V_1$$~~

$$7V_1 = 100 + 4V_2$$

$$100 + 4V_2$$

$$V_1 = \frac{100 + 4V_2}{7}$$

$$V_1 = \frac{100 + 4V_2}{7} \rightarrow (2)$$

From eqn (2) :

$$-V_2 + 3V_3 = 0$$

$$+V_2 = +3V_3$$

$$V_3 = \frac{1}{3} V_2$$

Put in eqn (1)

$$-15V_1 + 23V_2 - 3V_3 = 0$$

$$-15 \left(\frac{100 + 4V_2}{7} \right) + 23V_2 - 3 \left(\frac{1}{3} V_2 \right) = 0$$

$$-15(14.2 + 0.5V_2) + 23V_2 - V_2 = 0$$

$$-213 - 7.5V_2 + 22V_2$$

(74)

$$-7.5V_0 + 22V_0 = 213$$

$$14.5V_0 = 213$$

$$V_0 = 14.6 \text{ V}$$

put $V_0 = 14.6 \text{ V}$

in

$$V_3 = \frac{1}{3} V_0$$

$$V_3 = \frac{14.6}{3}$$

$$V_3 = 4.8 \text{ V}$$

$$V_1 = \frac{100 + 4(14.6)}{7}$$

$$\frac{100 + 58.4}{7}$$

$$V_1 = 22.06 \text{ Volt.}$$

(75)

Now from Figure 1


$$I_{x'} = \frac{V_1 - V_2}{2}$$

$$= \frac{22.6 - 14.6}{2}$$

8/2

$$I_{x'} = 4A \rightarrow *$$

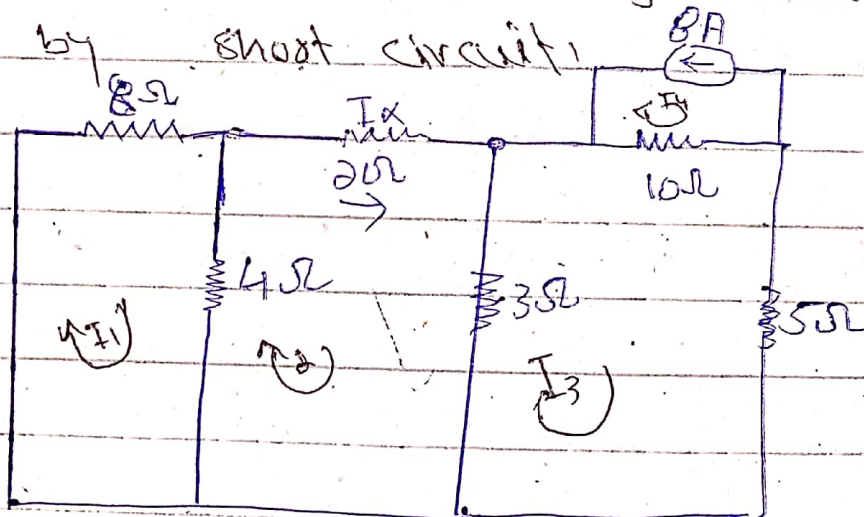Now remove voltage source
by short circuit,



Here

$$I_4 = 8A$$

Apply KVL at loop 1

$$8I_1 + 4(I_1 - I_2) = 0$$

$$8I_1 + 4I_1 - 4I_2 = 0$$

$$12I_1 - 4I_2 = 0$$

$$3I_1 - I_2 = 0 \rightarrow \textcircled{i}$$

at loop 2:

$$2I_2 + 3(I_2 - I_3) + 4(I_2 - I_1) = 0$$

$$2I_2 + 3I_2 - 3I_3 + 4I_2 - 4I_1 = 0$$

$$-4I_1 + 9I_2 - 3I_3 = 0 \rightarrow \textcircled{ii}$$

at loop 3:

$$10I_3 + 5I_3 + 3(I_3 - I_2) = 0$$

$$10I_3 - 10(8) + 5I_3 + 3I_3 - 3I_2 = 0$$

$$10I_3 - 80 + 5I_3 + 3I_3 - 3I_2 = 0$$

$$-3I_2 + 18I_3 = 80 \rightarrow \textcircled{iii}$$

From eq ①

$$3I_1 - I_2 = 0$$

$$I_1 = \frac{1}{3}I_2 \rightarrow \textcircled{a}$$

77

From eq (3)

$$-3I_2 + 18I_3 = -80$$

$$I_3 = \frac{3I_2 - 80}{18} \rightarrow (b)$$

put (a) & (b) in eq (2)

$$-4\left(\frac{1}{3}I_2\right) + 9I_2 - 3\left(\frac{3I_2 - 80}{18}\right) = 0$$

$$-\frac{4}{3}I_2 + 9I_2 - \frac{1}{2}(I_2 - 40) = 0$$

$$-1.33I_2 + 9I_2 - 0.5I_2 + 20 = 0$$

$$7.17I_2 = -20$$

$$I_2 = -2.8 \text{ A}$$

Now

$$I_1 = -\frac{1}{3}I_2$$

$$I_1 = +0.93 \text{ A}$$

NOW

$$I_{x''} = I_1 + I_2$$

$$I_{x''} = +0.6 \phi 1.8$$

$$\boxed{I_{x''} = 1.08} \rightarrow \text{***}$$

From ***

$$I_x = I_{x'} + I_{x''}$$

$$= 4 - (1.08)$$

$$= 4 - 1.08$$

$$\boxed{I_x = 2.92} \rightarrow \text{ANS}$$

x — x — x — x — x

Q3 part 2:-

Compare numbers of steps & easiness in above 3 method -

(1) Nodal Analysis:-

In nodal analysis

we apply KCL on each

node (i.e. 3 node)

which give us three

equation. which can be solved by solving

these three equation

(79)

we find I_x . Nodal analysis completed more than 5 steps and its ~~quite~~ quite a bit difficult to identify nodes for such complex circuit and solve these complicated equation by this method. the question become too lengthy and difficult.

mesh analysis

by mesh analysis also the question became too difficult b/c in this method we apply KVL on 4 loop & that give us ~~more~~ 4 equation by solving these 4 equation we get require result. it also too lengthy and difficult.

superposition theorem:

superposition theorem quite easy way to solve such complicated circuit but b/c in this method we not take current

(80)

Source and voltage source
simultaneously. we remove
~~for~~ one source & solve
the circuit and then
other due to ~~this~~ this
the circuit became to
easy - and it's not
too lengthy like other
method -

x — x — x — x — x

END