

Department OF Electrical

Assignment

Date: 20/04/2020

Course detail

Course title: Power System

Analysis

Instructor:

Engr. Amir Aman

Module:

6th

Student detail

Name:

Kamran Khan

ID:

6990

Q1 A 3 ϕ transformer is connected with a residential load of 28.56KV. The primary side of a transformer is connected with 130KV feeder while secondary side is stepped down to 10KV. The transformer is rated with 30MVA. Find Impedance! Z_b

Ans

Given data!

A 3 ϕ is connected to with residential load 28.56KV.

Primary side T/P 130KV
feeder

Secondary side is stepped down
10KV.

Transformer rated 30MVA

Required data!

Find the Impedance
 Z_b .

1093

Kamran Khan # 6990

Q1/b

Find the per unit equivalent impedance of an 11/132 KV transformer having 60Ω and 1440Ω . The equivalent impedance the primary and secondary currents are 909 Amp and 75.75 Amps respectively.

Ans

Given data:

11/132 KV transformer have 60Ω and 1440Ω equivalent impedance. Primary & secondary currents are 909 Amp & 75.75 Amp respectively.

Required data:

Find the per unit equivalent impedance of an 11/132 KV transformer. are the above data.

Solution:

Primary 11/132 KV
Secondary

10/29/24

Camron Khan # 10#6990

$$I_{base1} = \frac{S_{base1}}{V_{base1}}$$

$$\begin{aligned} S_{base1} &= V_{base1} \times I_{base1} \\ &= 11 \times 10^3 \times 99 \text{ Amb} \end{aligned}$$

$$S_{base1} = 9999000$$

* $S_{base2} =$

$$\begin{aligned} S_{base2} &= V_{base2} \times I_{base2} \\ &= 132 \times 10^3 \times 75.75 \text{ Amb} \end{aligned}$$

$$S_{base2} = 9999000$$

* $Z_{base1} =$

$$Z_{base1} = \frac{(V_{base1})^2}{S_{base1}} = \frac{(11 \times 10^3)^2}{9999000}$$

$$= 12.101$$

$$Z_{base1} = 12.101$$

1095

Now Z_{base2}

$$Z_{base2} = \frac{(V_{base2})^2}{S_{base2}} = \frac{(132 \times 10^3)^2}{1742.574}$$

$$Z_{base2} = 1742.574$$

* For the per unit equivalent impedance,
for Z_{base1} .

$$* Z_{base1} \text{ eq. p.u.} = \frac{Z_{eq1}}{Z_{base1}} = \frac{10 \Omega}{12.104}$$

$$Z_{base1} \text{ eq. p.u.} = 0.826$$

* for the Z_{base2}


$$Z_{base2} \text{ eq. p.u.} = \frac{Z_{eq2}}{Z_{base2}} = \frac{1440 \Omega}{1742.574}$$

$$= 0.826$$


$$/ Z_{base2} = \text{eq. p.u.} = 0.826 /$$

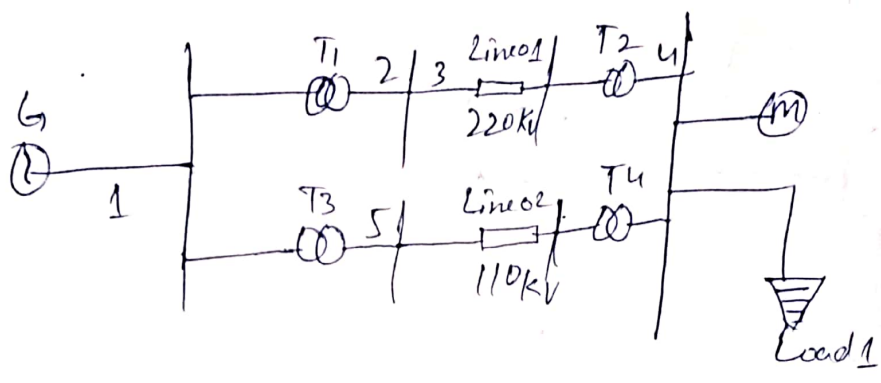(Q2) (a)

Single line diagram of a 3 ϕ Power System is shown in the below figure. Draw an Impedance and reactance diagram in Pu.



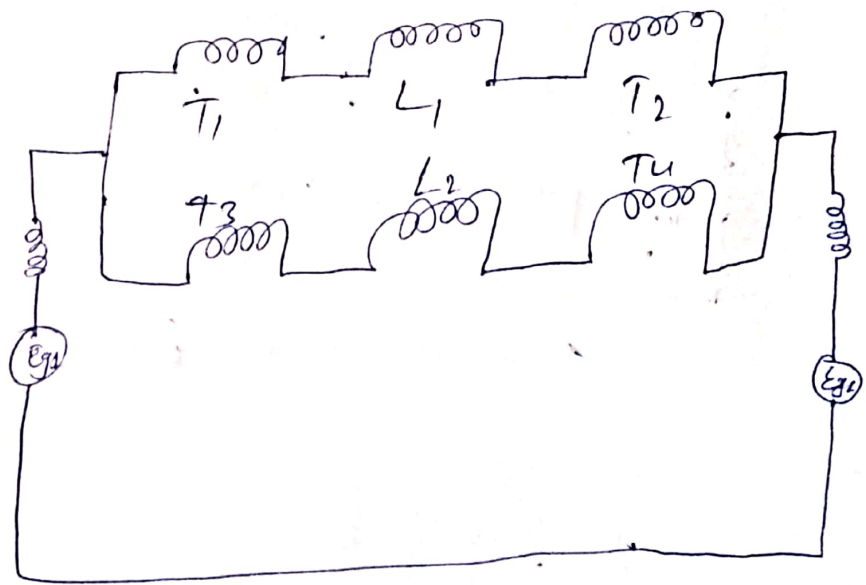
* This diagram will be converted into Reactance diagram



Pg 7/


Kamran # ID# 6990

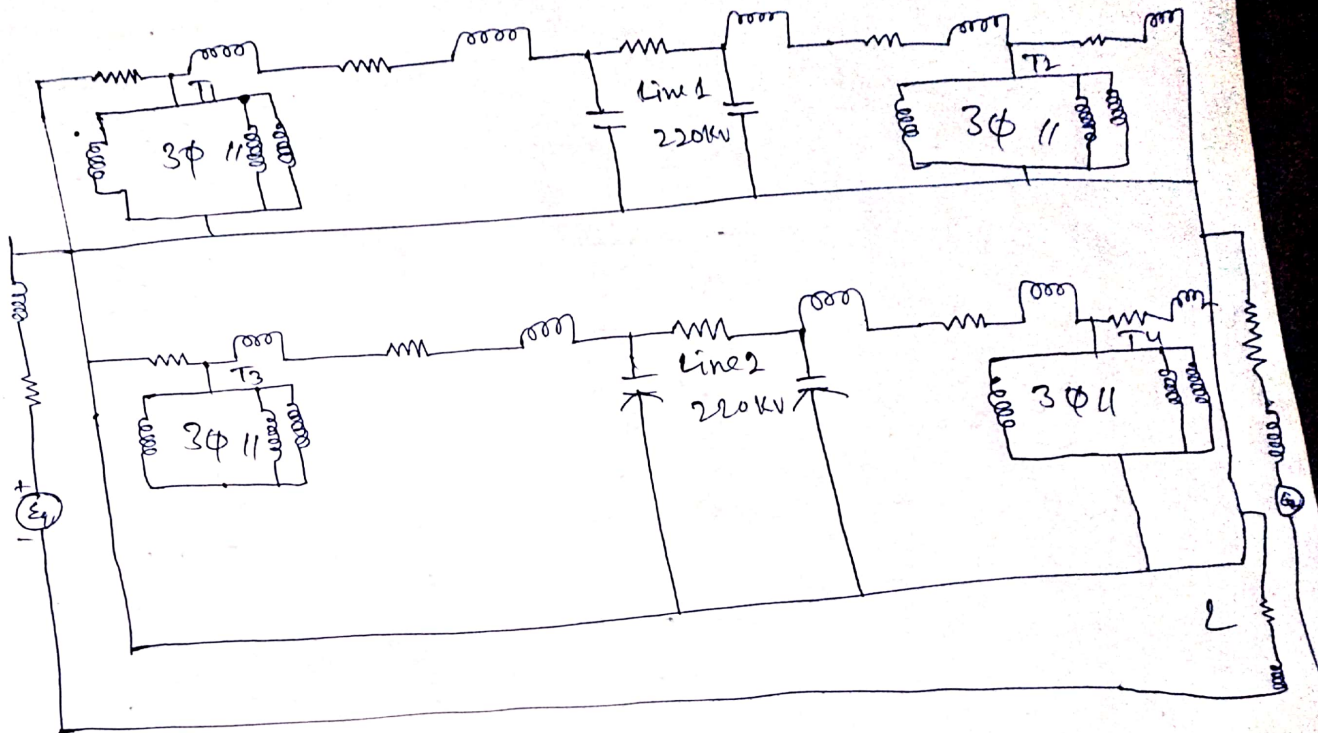single line
diagram
convert to
the impedance
diagram.



Q3/2017


For the single line diagram shown below generators are connected to high tension buses 1 and 2 and supply load connected at bus 3. Find the reactance diagram, then convert into equivalent current source and shunt admittance. Then find the admittance matrix and find the total current.

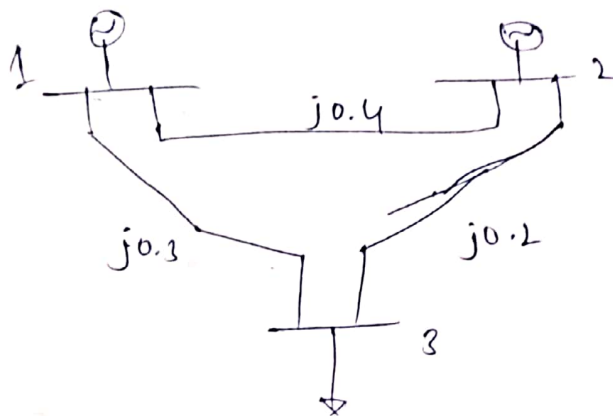Ans!Given data!

- Single line diagram
- connected with Bus 1 & 2
- supply load connected at bus 3.

Required data!

- Find the reactance diagram converted into equivalent current source and shunt admittance.
- Find shunt admittance matrix find the total current.

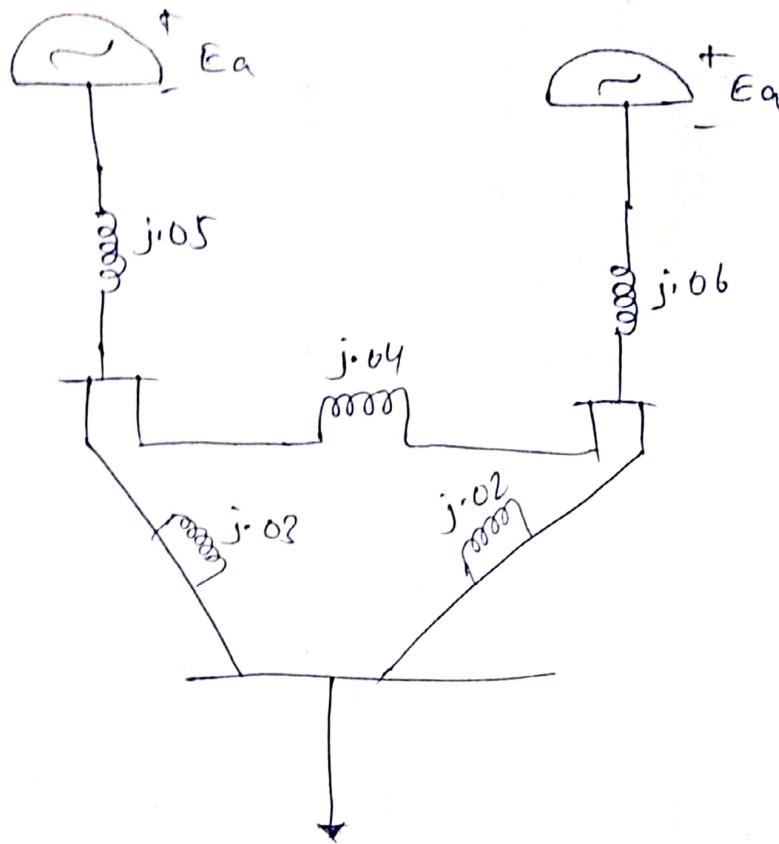Solution!Now Calculation!

$$\frac{1}{j \cdot 0.06} = 160 \quad \frac{1}{j \cdot 0.05} = 2 \quad \frac{1}{j \cdot 0.4} = 2.5 \quad \frac{1}{j \cdot 0.3} = 333$$

$$\frac{1}{j \cdot 0.2} = 5$$

* So now we convert reactance diagram into admittance.

Pg 101

Kamran # 10 # 6990

