

**Department of Electrical Engineering**

**Assignment**

**Date: 23/06/2020**

**Course Details**

Course Title: Instrumentation and Measurement  
 Instructor: \_\_\_\_\_

Module: 6<sup>th</sup> (BE)  
 Total Marks: 50

**Student Details**

Name: mohsin ali

Student ID: 13746

**Note: Draw neat diagrams where necessary. Assume missing details if required.**

Q1.	A student has connected two voltmeters in series and have applied 500V across them. Both voltmeters have the same range of 0-300V. What will be their readings if their internal resistances are 25kΩ and 15 kΩ respectively?	Marks 10
		CLO 2
Q2.	A dynamometer type wattmeter has two current coils each having a resistance of 0.5Ω. Both of the coils are connected in parallel. The wattmeter voltage coil is connected to the supply side. The wattmeter shows a reading of 200W while the reading on the ammeter is 4A which is connected in series with the current coil of the wattmeter. Calculate the following parameters: a) Power dissipated in the wattmeter b) True load power c) Percentage error due to the connection of wattmeter	Marks 10
		CLO 2
Q3.	(a) What is the difference between Kelvin's bridge and Wheatstone bridge? Explain briefly.	Marks 05
	(b) Explain how the potential on the upper (top) node in a DM <sup>3</sup> bridge is equal to the potential on the lower (bottom) node?	Marks 05
		CLO 3


Q4.	(a) Why the energy meters designed for DC circuits cannot be used for AC circuits?	Marks 05
	(b) What will happen if the phase difference between two alternating fluxes in an induction type energy meter is zero degrees?	Marks 05
		CLO 03
Q5.	(c) Why the series magnet is wound with a wire of few turns as compared to shunt magnet in an induction type energy meter?	Marks 05
	(d) What is the significance of meter constant in an energy meter?	Marks 05
		CLO 03

Given Data:

Two Voltmeter range = 0-300V

$$R_1 = 25\text{ k}\Omega$$

$$R_2 = 15\text{ k}\Omega$$

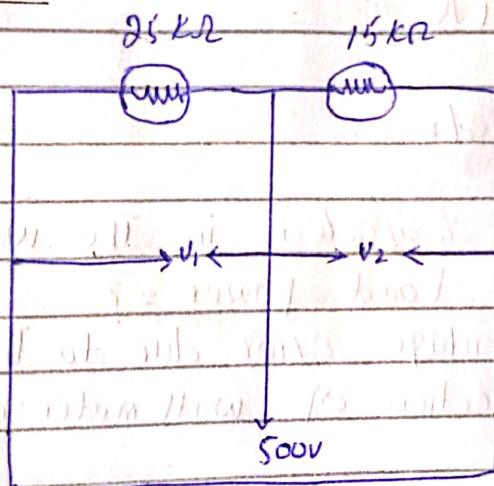Total Voltage  $V = 500\text{V}$ Required:Voltage reading in 1st voltmeter =  $V_1$ ?Voltage reading in 2nd voltmeter =  $V_2$ ?Diagram:Solution

Here we use voltage divider rule  
The reading of the two voltmeter are.

$$V_1 = \frac{25\text{ k}\Omega}{25\text{ k}\Omega + 15\text{ k}\Omega} \times 500$$

$$V_1 = 312.5\text{V}$$

②

$$V_2 = \frac{15 \text{ k}\Omega \times 500 \text{ V}}{25 \text{ k}\Omega + 15 \text{ k}\Omega}$$

$$V_2 = 187.5 \text{ V}$$

Q9Given data:

$$R_1 = 0.5 \Omega$$


$$R_2 = 0.5 \Omega$$

$$\text{Power } P = 200 \text{ W}$$

$$I = 4 \text{ A}$$

Required:

- 1) Power dissipated in the wattmeter = ?
- 2) True Load power = ?
- 3) percentage error due to the connection of watt meter = ?

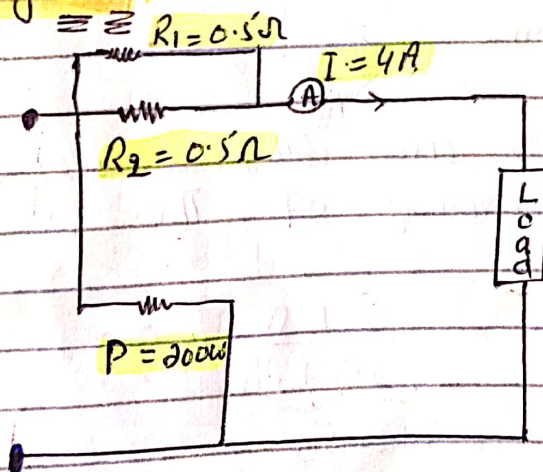Diagram:

P.T.O

(3)

13746

Solution,

Resistance of current coils

$$R_e = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_e = \frac{0.5 \times 0.5}{0.5 + 0.5}$$

$$R_e = \frac{0.25}{1} = 0.25 \Omega$$

(a) Power dissipated in wattmeter —

$$P = I^2 R_e$$
$$= (4)^2 \times 0.25$$

$$= 16 \times 0.25$$

$$P = 4 \text{ W}$$

$$P = 4 \text{ W}$$

(b) True load power = 200 - 4

$$= 196 \text{ W}$$

(c)

$$\% \text{ error} = \frac{P - \text{True load}}{\text{True load power}} \times 100$$

$$= \frac{200 - 196}{196} \times 100 = 2.0408$$

$$\% \text{ error} = 2.0408$$

Q 3

①

What is The difference b/w Kelvin's bridge and wheat stone Bridge? explain briefly.


ANS.

A Wheat stone bridge measures electrical resistance by balancing a bridge ckt. The circuit has two legs, of which one contain the unknown resistance of value between 1 ohm to 10 ohms. A part from resistance, this setup can also measure Impedance, capacitance and Inductance. The W.S bridge is the combination of 4 resistance forming a bridge.

The kelvin bridge is more advance and helps in measuring resistance less than 1 ohm, however, it has two more resistors than the wheatstone bridge. The kelvin bridge use for measuring unknown resistance having value

Diagrams:

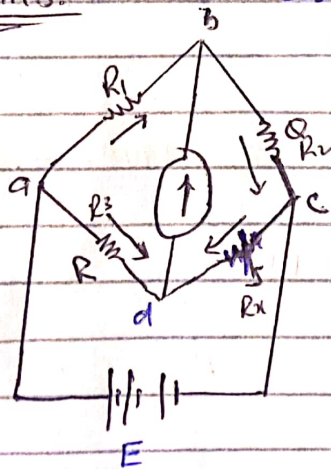Less than  $1 \Omega$  it is modified form of



Wheat stone bridge

(5)


In kelven's bridge This bridge is modification of wheat stone bridge and is used to measure low resistance very accurately

→ When we are implementing wheatstone bridge in the laboratory, we connect all the ~~resistance~~ resistance through connecting wires.

→ Hence these connecting wires also have some resistance and in order to measure it we will use kelvin's bridge

from w.s bridge we know that
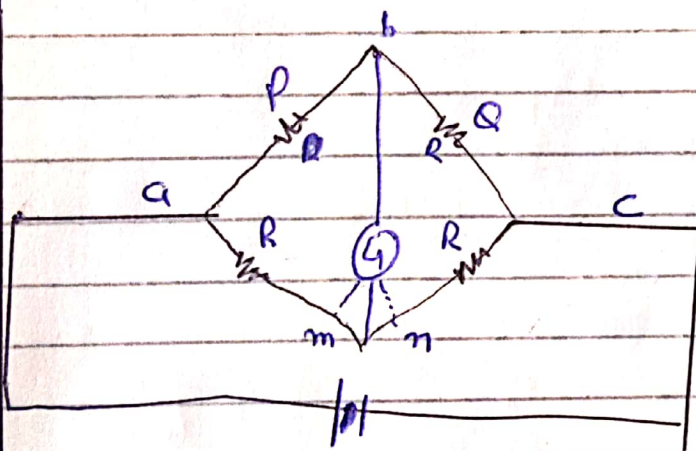
$$R = \frac{P \times S}{Q} \rightarrow \textcircled{1}$$



kelven's bridge



Q3

(b)

ANS:

Bridge circuit are particularly useful in connecting resistance changes in to voltage bridge that can be in put directly in to automatic control system.

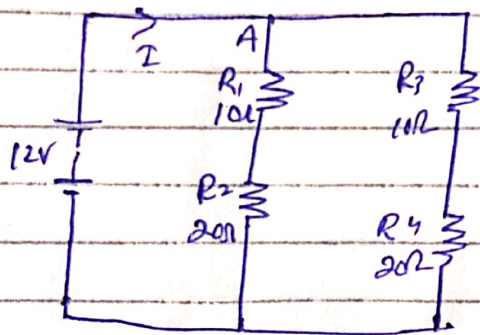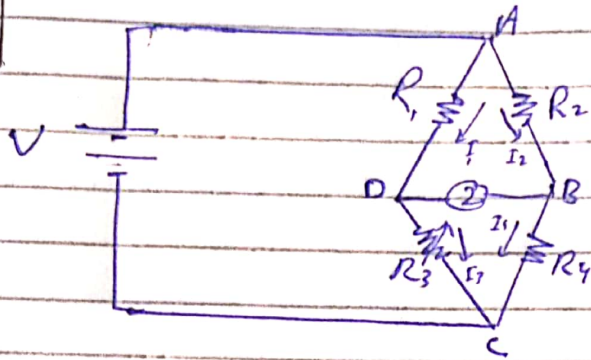The difference in potential crucial current flows not the value of the potential to ground of end points.



$$I_1 = \frac{V}{R} = \frac{12}{20+10} = \frac{12}{30} = 0.4 \text{ A}$$

$$V_{R2} = I \times R_2 = 0.4 \times 20 = 8 \text{ Volt} = 8 \text{ V}$$

P.T.O

(7)

$$I_0 R_1 = 0.4 \times 10 = 4V$$

$$V_{R_1} = 4V \text{ and } V_{R_2} = 8V$$

Both point have same value of  
8 volt and  $c = D = 8 \text{ volts}$

the difference is 0 volts

When this happens both side of  
the parallel network are said to  
be balanced because the voltage  
at point 'C' is the same  
value as the voltage at point 'D'



Q4

①

(a)

Why the energy meter design for DC circuit cannot be used for AC circuit?

Ans:

Energy meter designed for DC circuit not AC because AC energy work due to involvement of two alternating magnetic fields produced by AC quantities (voltage and current) that interacts with an aluminium disk causing eddy current to induced in the disk. In DC such induction effect and eddy current not produced.

Q4

(b)

What will be happen if the phase difference b/w two alternating fluxes in an induction type energy meter is zero.

Ans

it should be noted that when  $\phi = 0$  (i.e. two fluxes are in phase) then deflecting torque is zero or no torque can be produced.

Torque will be maximum when  $\phi = 90^\circ$

Q.5

(8) (9)  
(a) Why The Series magnetic is wound with a wire of few turns as compare to shunt magnet~~ic~~ in an Induction type energy meter.

ANS: The Series magnetic is wound with a wire of few turns connected in series with load it carries the load current. The coil of this magnetic is highly non inductive.

(b) what is The Significance of meter constant in an energy meter.

ANS:

$N \propto \text{energy}$

$N = K \text{ energy}$

K is constant called meter constant

$$K = \frac{N}{\text{energy}} = \frac{\text{number of revolution}}{\text{kWh}}$$

Hence The number of revolutions made by The disk for 1 kWh of energy consumption is called meter constant

for example: if ~~the~~ meter constant of energy meter is 1500 rev/kWh



10

it means that for consumption  
of 1kwh The disk will make 1500  
revolution.



END