

Department of electrical Engineering Assignment

COURSE detail





Instruction	Shail Imran
Subject	LCA
Module	2 nd
Total marks	30

Student detail

Name	M. Zeeshan
ID	16529

Q 1. For each of the following circuits in figure. Find the current I and compute the power absorbed by the resistor.

Page No
(1)

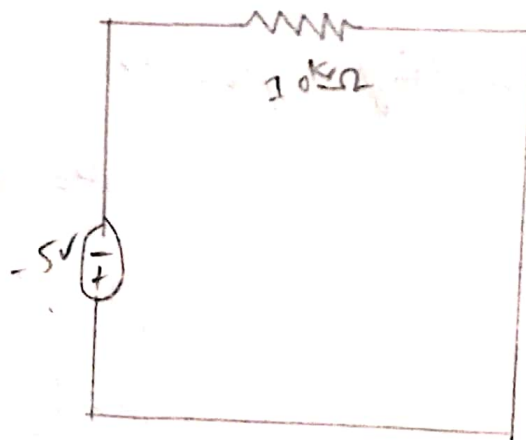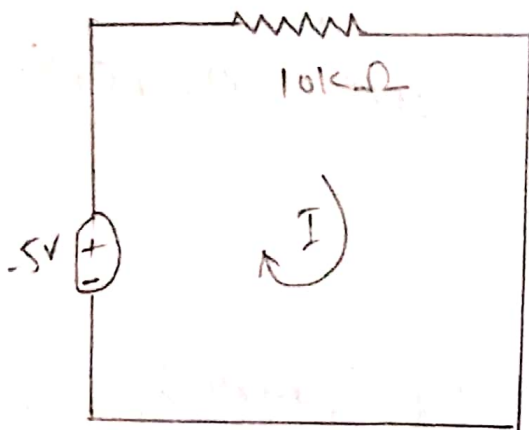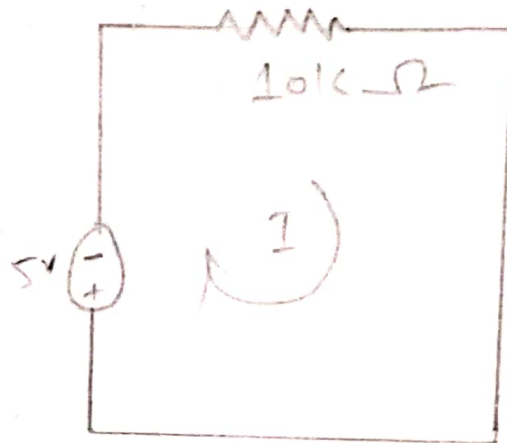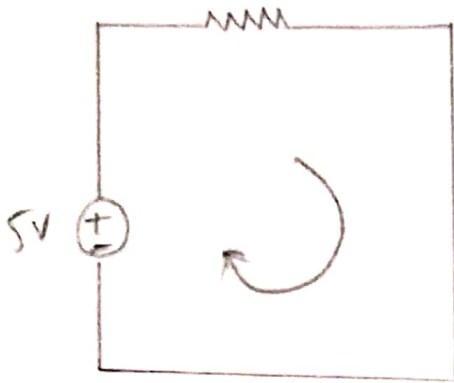

Ans

Applying ohm law for finding circuit.

$$V = IR$$

$$I = V/R$$

For find power in the circuit we use

$$P = VI \text{ or } P = I^2R$$

To obtain result so we need to Page
Perment a given value for each circuit. #2
so if current.

$$V = IR$$

$$I = VR$$

$$I = \frac{5V}{10000 \Omega}$$

$$I = 0.0005 A$$

$$I = 0.5 mA$$

For finding power we use $P = I^2 R$

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

$$P = (0.5 mA)^2 \times (10000)$$

$$P = 0.0025$$

$$P = 0.25 \times 10^{-3}$$

P.T.O

For Finding Second circuit.
current and power

Page

we apply ohm law for finding current (3)

$$V = IR$$

$$I = V/R$$

$$I = V/R$$

$$I = -5V / 10000 \Omega$$

$$I = -0.0005A$$

For Finding power we use = $P = I^2 R$

$$P = I^2 R$$

$$P = (-0.0005)^2 (10000)$$

$$P = -0.0025W$$

$$P = -0.25mW$$

For finding current and power Page
in 4th circuit # 5

First of all we find the current:

we Applying ohm law $V = IR$

$$I = V/R$$

$$I = 5V/10000 \Omega$$

$$I = 0.0005A$$

$$I = 0.5 mA$$

For finding power in a circuit

we Applying $P = I^2 R$

~~$P = VI$~~ $P = (0.0005A)^2 (10000 \Omega)$


~~$P = 5 \times 5$~~

$$P = 0.0025$$

$$P = 0.0025$$

$$P = 0.25 mW$$

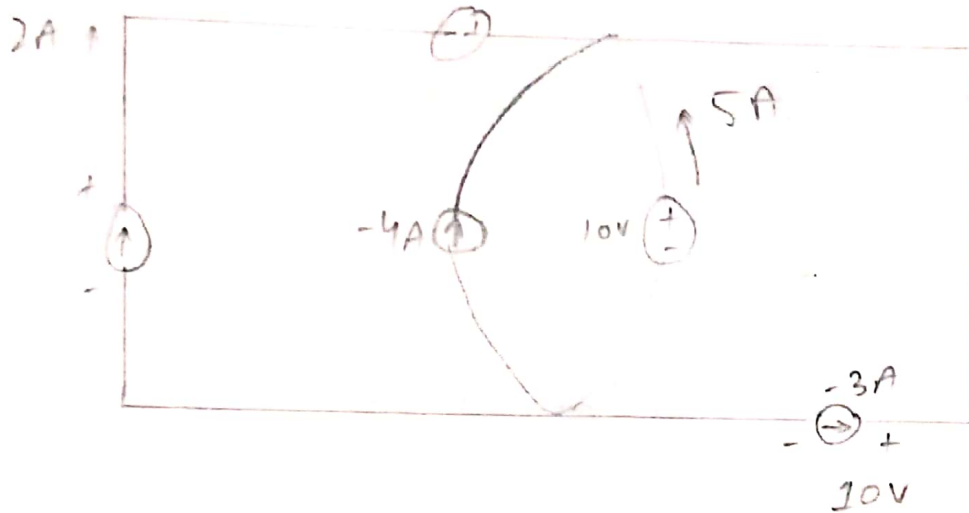Q(b) Determine The power supplied by the left most element in the circuit of following figure: Page # 6



Solution we apply $P = VI$ for finding power:

Given: The voltage and current are given below: we can find the power in leftmost element in

$$P = VI$$

$$P = 2V \times 2A$$

$$P = 4W \text{ Supplied}$$

Don't forget that the 4W is supplied power in the current direction conflicts with passive sign


Q 1(c) Following figure depicts the circuit voltage characteristic of three different resistive element. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.

Solution

use Applying Ohm law $V = IR$ (or)

$$R = V/I$$

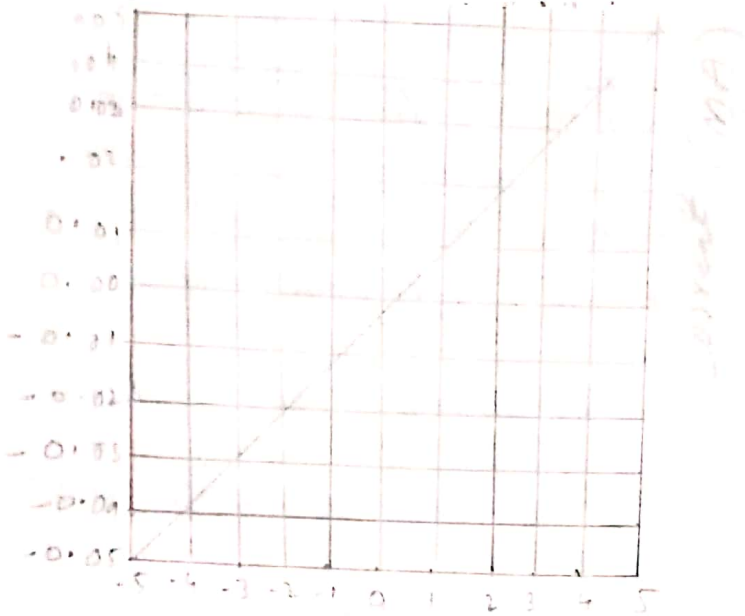So we calculate R from the slope on the graph. we can take any point on the line to get the values of ' I ' and ' V '



(a) Voltage (V)

Solution

$$I = 0.01 \text{ mA}$$

$$V = 1 \text{ V}$$

$$R = ?$$

Applying Ohm law


$$V = IR$$

$$R = V/I$$

$$R = \frac{0.5 \text{ A}}{5 \text{ V}} = > 10 \mu\text{s}$$

$$R = 1 \text{ V} / 0.01 \times 10^{-3}$$

$$R = 100 \text{ k}\Omega$$

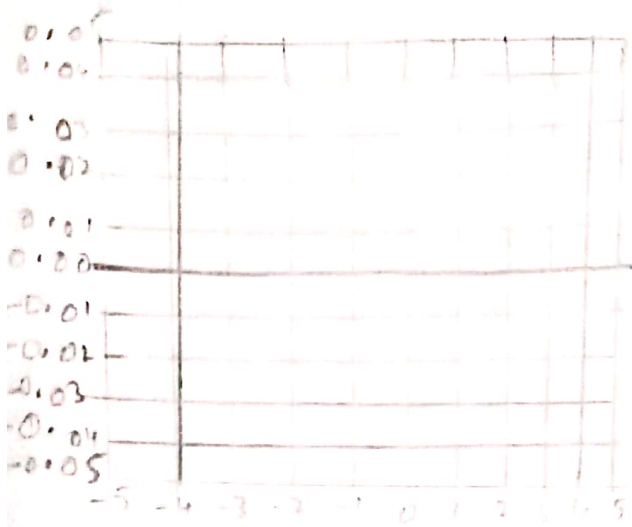

Solution
(B)

Voltage (V)

Through difficulty to see. The current is zero. as slope as zero

$$V = IR \Rightarrow R = V/I$$

$$R = \frac{1V}{0} \Rightarrow \boxed{R = \infty}$$



Voltage

(Solution) c

Through difficulty to see the current infinite as slope is

$$I (A)$$


$$R = \frac{1}{I}$$

OR

$$R = 0$$

we hence this is zero resistance

$$R = 0$$

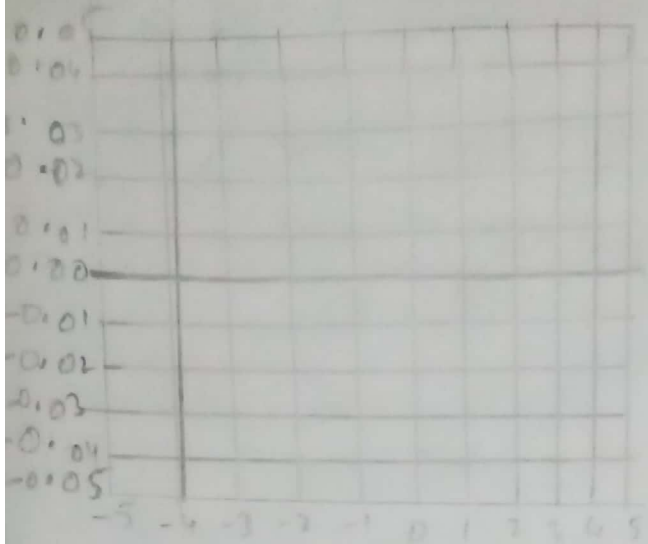

Voltage (V)


Solution

(B)

Through difficulty to see. The current is zero. as slope as zero

$$V = IR \Rightarrow R = V/I$$
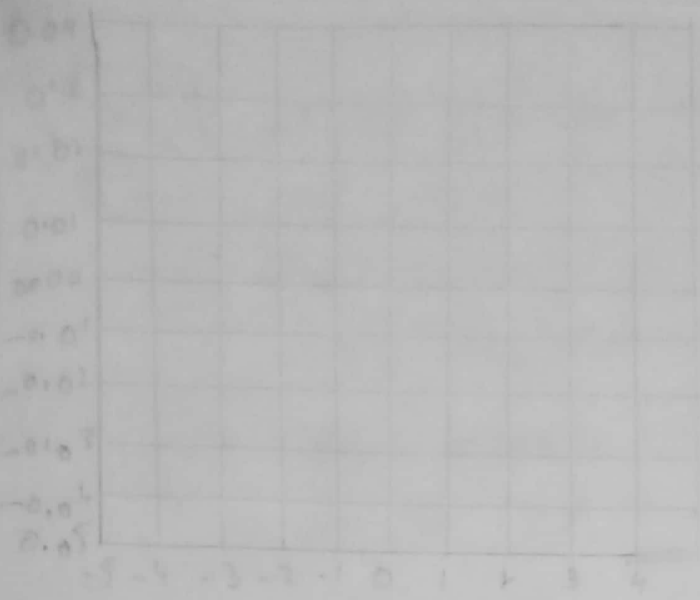
$$R = 1V/0 \Rightarrow \boxed{R = \infty}$$



voltage
(c)

(Solution) c

Through difficulty to see the current infinite as slope is

$$\infty (\Omega)$$

$$R = \frac{V}{I}$$

OR

$$R = 0$$


we hence this is zero resistance


$$\boxed{R = 0}$$

Q2a) Refer to the circuit of following figure and answer the following:

- (1) How many distinct nodes are contained in the circuit.
- (2) How many element are contained on the circuit.
- (3) How many branch does the circuit have?
- (4) Determine if each of the following represent a path, a loop, both or neither.

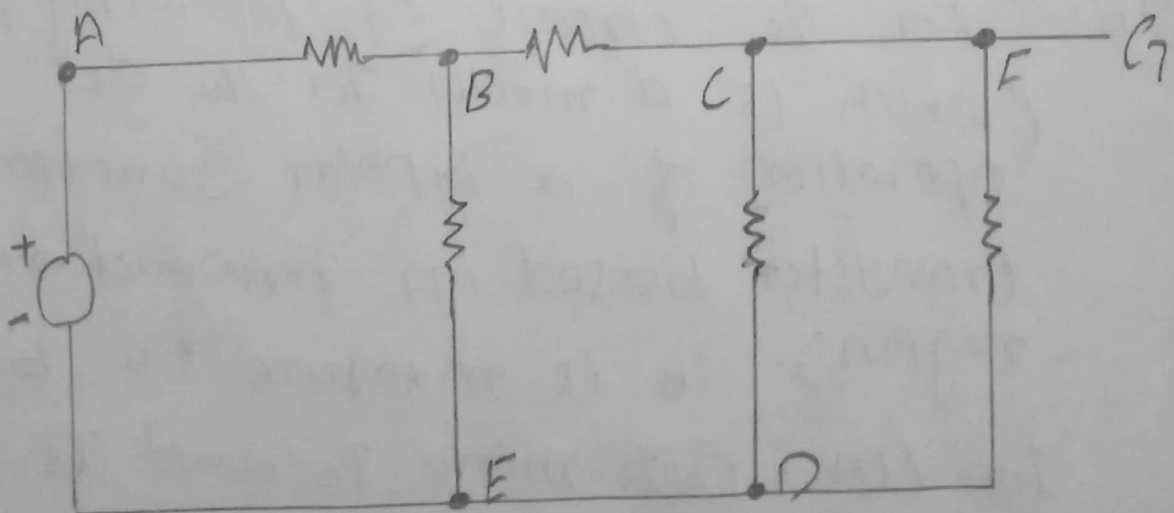
- (i) A to B
- (ii) B to D to C to E
- (iii) C to E to D to B to A to C
- (iv) C to D to B to A to C to E



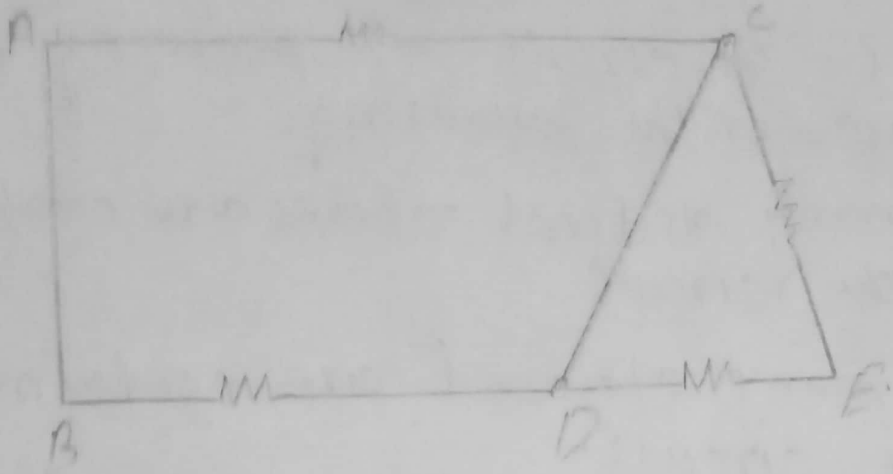

- Ans 2(a)
- (1) Nodes = 4
 - (2) Element = 5
 - (3) Branch = 5
 - (4)
 - (i) neither
 - (ii) only path
 - (iii) path and loop
 - (iv) neither.

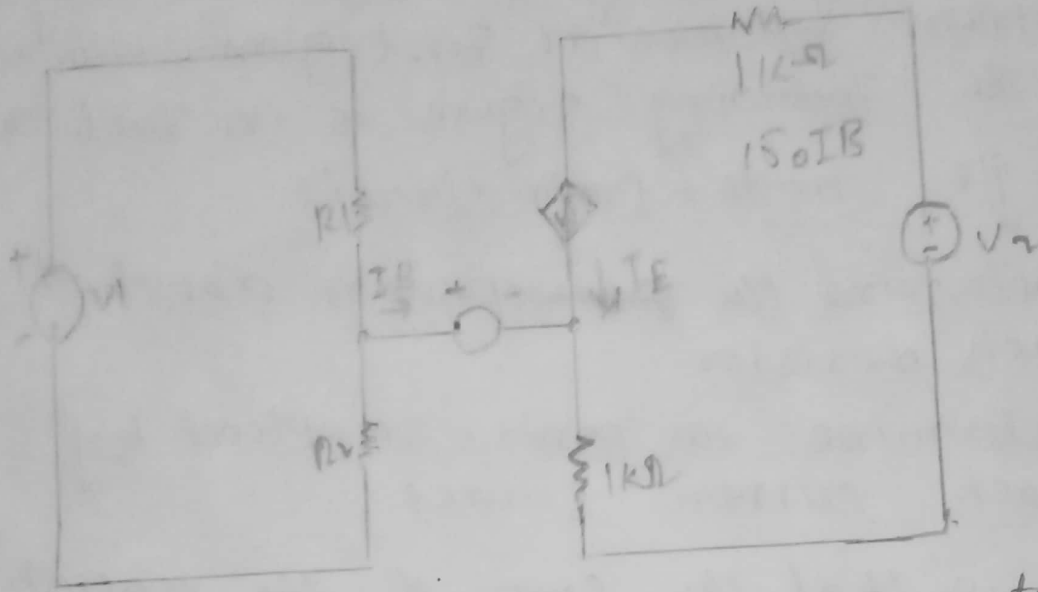Q2b: For the circuit of following figure (which is a model for the dc operation of a bipolar Junction transistor biased in forward active region). I_B is measure to be $100 \mu A$. Determine I_C and I_E .




Ans KCL total current entering
a node = total current
leaving a node

$$I_C = 150 \times I_B = 150 \times 100 = \boxed{15 \text{ mA}}$$

$$I_E = 15 + 0.1 = \boxed{15.1 \text{ mA}}$$

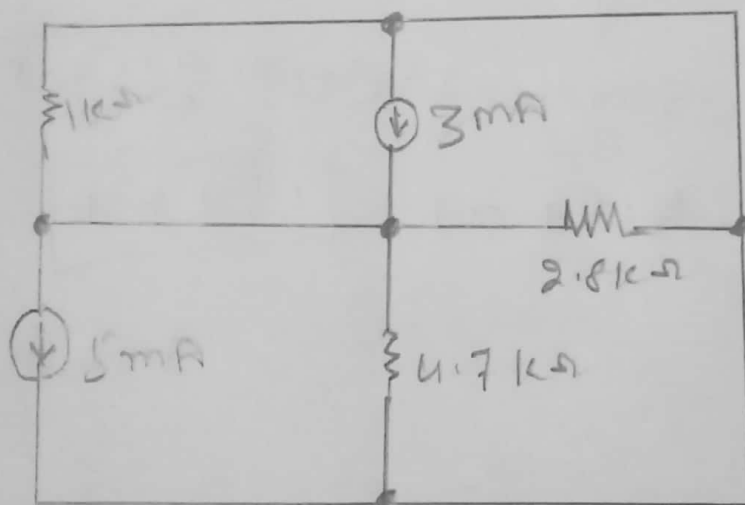Q3a: Although draw so that it may not appear obvious at first glance, the circuit of the following figure is in fact a single node-pair circuit.

- Determine the ~~total~~ power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculate in (a) is equal to the sum of the supplied power calculate in (b)



We use ohm's law

$$V = IR$$

$$V = 2 \times 10^{-3} \times 637$$

$$V = 1.274V$$

Find current

page 15

$$V = IR$$

$$I = V/R$$

$$\Rightarrow I_1 = V/R_1 \Rightarrow \frac{1.274}{1000} = \boxed{1.274 \text{ mA}}$$

$$\Rightarrow I_2 = V/R_2 = \frac{1.274}{2800 \Omega} \Rightarrow \boxed{0.455 \text{ mA}}$$

$$\Rightarrow I_3 = V/R_3 = \frac{1.274}{4700} \Rightarrow \boxed{0.271 \text{ mA}}$$

Find power:

$$\Rightarrow P(1k) = (1.274)(1.274) = \boxed{1.623 \text{ mW}}$$

$$\Rightarrow P(4.7k) = (1.274)(0.271) = \boxed{0.345 \text{ mW}}$$


$$\Rightarrow P(2.8k) = (1.274)(0.271) = \boxed{0.345 \text{ mW}}$$

$$\Rightarrow P(5\text{mA}) = (1.274)(-5) = \boxed{-6.37\text{mW}}$$

$$\Rightarrow P(3\text{mA}) = (1.274)(3) = \boxed{3.822\text{mW}}$$

Page
16

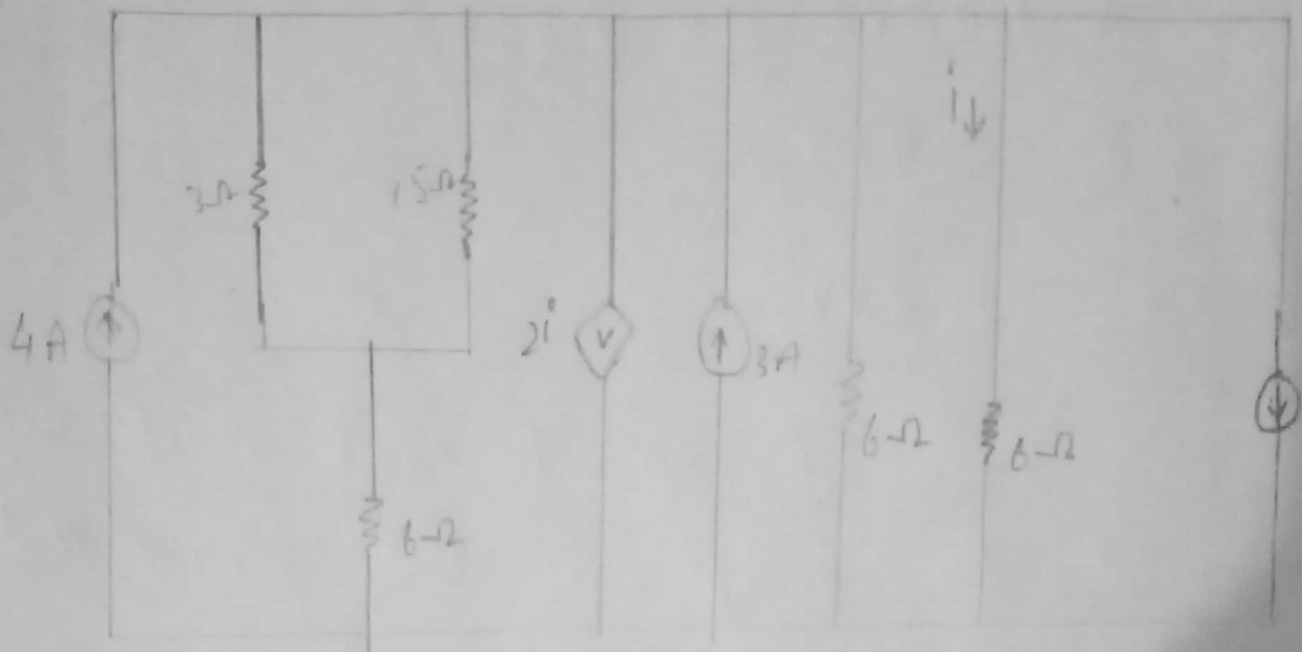Q 3b; Determine the power absorbed by the $15\text{-}\Omega$ resistor on the circuit of the following figure: page 17



Ans 3 (b) First simplify the circuit by calculating source and resistance equivalence

$$I_{eq} = 4 - 2i^\circ + 3 - 9 = 2 - 2i^\circ$$

$$R_{eq} = (6 + 3 // 15) // 6 // 6$$

$$R_{eq} = 8.5 // 3 = 2.2174\text{-}\Omega$$

Now we can calculate voltage:

$$V = I_{eq} \times R_{eq}$$

$$V = (-2 - 2i^\circ) \times (2.2174\text{-}\Omega)$$

and from the diagram we can see that

$$V = 6i$$

page
18

$$= 6i = (-2 - 2i) + 2 \cdot 2.174$$

$$= 10.4348 \times i = -4.4348$$

$$I = 0.42 \text{ A}$$

$$V = -2.55 \text{ V}$$

power consumed by the $15\text{-}\Omega$ resistor will need the voltage on that resistor that

$$P = V^2/R$$

$$P_{15\text{-}\Omega} = \frac{V^2_{15\text{-}\Omega}}{15\text{-}\Omega}$$

$$V_{15\text{-}\Omega} = \frac{6}{6+2.5} \text{ V}$$

$$V_{15\text{-}\Omega} = 1.08 \text{ V}$$

and power is:

$$P_{15\text{-}\Omega} = \frac{1.08^2}{15\text{-}\Omega}$$

$$P_{15\text{-}\Omega} = 0.216 \text{ W}$$

Thank you
sir!