

Course title:-

Electrical Networks
Analysis

Module :-

4th

Instructor:-

Dr. shahriyar

Name :-

Ali Davish Kayani

Student ID :-

15243

Student Signature :-

Date:-

13th April 2020


Ali Davish Kayani

P. 1

Question No 2:-

Determine the inductor current for both $t > 0$ & $t < 0$ for the circuit.

Figure:-

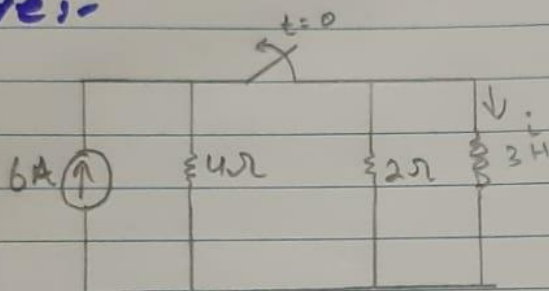

Solution:-

For $t < 0$:

The switch is closed & inductor acts as a short circuit;

Therefore inductor current
 $\therefore i = 6A$

A. (2)

For $t > 0$:

The switch is open
up the time constant

$$\tau = \frac{L}{R}$$

$$\tau = \frac{3}{2}$$

Now the inductor current

$$i(t) = \frac{-t}{\tau}$$

$$i(t) = b e^{-\frac{t}{\tau/2}}$$

$$i(t) = b e^{-2t/3} (t) A.$$

Q 3:-

A series RLC circuit is
described by

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Find the response when $L = 0.5 H$.

$$R = 4 \Omega \text{ \& } C = 0.2 F.$$

P. (3)

$$\text{Let } i(0) = 1A, \quad \frac{di(0)}{dt} = 0$$

Solutions:-

The step response of the branch voltage of the given RLC circuit is describe by;

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 10$$

Divide by L ;

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10}{L}$$

multiplying by $\frac{C}{C}$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{10C}{LC}$$

As $C = 0.2F$; thus;

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{2}{LC}$$

P. (4)

Substitute:

$$\frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + 10i = 20 \quad (1)$$

The general form of source-free

RLC is given by;

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = \frac{I_s}{LC} \quad (2)$$

Comparing (1) & (2) we get.

$$\frac{R}{L} = 8 \rightarrow (3)$$

$$\frac{1}{LC} = 10 \rightarrow (4)$$

$$\frac{I_s}{LC} = 20 \rightarrow (5)$$

From 3, α is given by;

$$\alpha = \frac{R}{2L} = \frac{8}{2} = 4 \text{ rad/sec} \rightarrow (6)$$

P. (5)

The frequency ω_0 is given by;

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

From 4, $\omega_0 = \sqrt{10} \text{ rad/sec} \quad (7)$

From (b) & (7)

$$\therefore \alpha > \omega_0$$

\therefore The circuit is overdamped

The roots of characteristic equation are given by;

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 + \sqrt{4^2 - 10} \\ &= -4 + \sqrt{6} \text{ rad/s} \end{aligned}$$

$$\begin{aligned} \text{And } s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \\ &= -4 - \sqrt{4^2 - 10} \\ &= -4 - \sqrt{6} \text{ rad/s} \end{aligned}$$

P. (6)

From (5), the steady current is given by;

$$I_s = 20 \times LC = 20 \times 0.5 \times 0.2 = 2A \rightarrow (8)$$

The current i of over damped is given by;

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad t > 0 \rightarrow (9)$$

Substitute $t = 0$:

$$i(0) = I_s + A_1 + A_2$$

Thus,

$$A_1 + A_2 = -2 \rightarrow (10)$$

From 9, find $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute, -

$$2 = 2 + A_1 + A_2$$

Then,

$$A_1 + A_2 = -2 \rightarrow (10)$$

D. (7)

From a, Find $\frac{di(t)}{dt}$

$$\frac{di(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Substitute: $t = 0$:

$$\frac{di(0)}{dt} = A_1 s_1 + A_2 s_2$$

Substitute values,

$$(-4 + \sqrt{6})A_1 + (-4 - \sqrt{6})A_2 = 0 \rightarrow (11)$$

Solving (10) & (11)

$$A_1 = -1.316$$

$$A_2 = 0.316$$


Substitute: (9)

$$i(t) = 2 - 1.316 e^{(-4 + \sqrt{6})t} + 0.316 e^{(-4 - \sqrt{6})t}$$

P. (8)
Question No 1:-

The switch in figure has been in position A for a long time. At $t=0$ for $t > 0$ calculate its value at $t = 2s$ & $8s$.

Figure:-

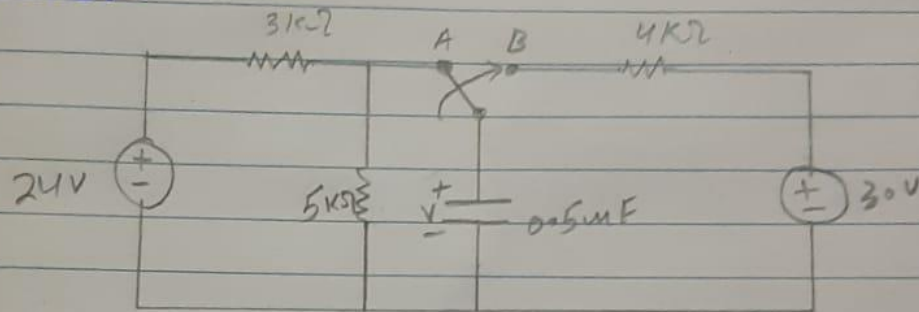

Solution:-

For $t < 0$:

The switch is at position A. The capacitor acts like an open circuit to dc, but V is the same as the voltage across $5k\Omega$ resistor. Hence the voltage across the capacitor just before $t=0$ is obtained by voltage division as;

P. (9)

$$v(0^-) = \frac{5}{5+3} (24) = 15V$$

As the capacitor can't change instantaneously.

$$v(0) = v(0^+) = 15V$$

For $t > 0$;

The switch is in position B. The $R_{th} = 4k\Omega$

Time constant is;

$$\tau = R_{th} C = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\tau = 2s$$

Since the capacitor acts like an open circuit to dc at steady state;

$$v(\infty) = 30V.$$

Thus;

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$= 30 + (15 - 30) e^{-t/2}$$

$$= (30 - 15 e^{-0.5t}) V$$

P. (10)

At $t = 2$:

$$\begin{aligned}V(2) &= 30 - 15e^{-\frac{2}{2}} \\ &= 30 - 15e^{-1} \\ V(2) &= 24.48 \text{ V}\end{aligned}$$

At $t = 8$:

$$\begin{aligned}V(8) &= 30 - 15e^{-\frac{8}{2}} \\ &= 30 - 15e^{-4}\end{aligned}$$

$$V(8) = 29.72.$$

Question 4:

A series RLC circuit has

$$R = 100 \Omega$$

$$L = 240 \text{ H}$$

$$C = 10 \text{ mF}.$$

17 the input voltage is $v(t) = 10 \cos 2t$, find the current flowing through the circuit.

D. (11)

Solution:-

The input voltage,

$$v(t) = 10 \cos 2t \text{ V}$$

$$\text{Amplitude} = V_m = 10 \text{ V}$$

$$\text{Angular Frequency} = 2 \text{ rad/s}$$

$$\text{Phase angle, } \phi = 0^\circ$$

So,

Phasor for the voltage $v(t)$:

$$v(t) = 10 \angle 0^\circ \text{ V.}$$

Now for inductive reactance.

$$X_L = \omega L$$

Now for inductor

$$\text{So } \omega = 2 \text{ rad/s, } L = 240 \text{ H}$$

$$X_L = (2)(240)$$

$$X_L = 480 \Omega$$

P. (12)

Now for capacitive Reactance

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2 \text{ rad/s}, C = 10 \mu\text{F}$$

$$\frac{1}{2(10 \times 10^{-6})}$$

$$\frac{1}{2 \times 10^{-2}}$$

$$\frac{1 \times 10^2}{2}$$

$$X_C = 50 \Omega$$

Now for impedance

$$Z = R + jX_L - jX_C$$

$$R = 100 \Omega, X_L = 480 \Omega, X_C = 50 \Omega$$

putting in eq

$$Z = (100 + 480 - 50) \Omega$$

$$Z = (100 + j430) \Omega$$

D. (13)

Represent "Z" in Phasor form

$$Z = \sqrt{(100)^2 + (430)^2} \angle \tan^{-1} \left(\frac{430}{100} \right)$$

$$= \sqrt{10,000 + 184,900} \angle \tan^{-1} (4.3)$$

$$= \sqrt{194,900} \angle \tan^{-1} (4.3)$$

$$Z = 441.47 \angle 76.90^\circ \Omega$$

Now for current flowing in the circuit

$$i = \frac{v(t)}{Z}$$

$$i = \frac{v(t)}{Z}$$

$$v(t) = 10 \angle 0^\circ, Z = 441.47 \angle 76.90^\circ \Omega$$

putting in eq

$$i = \frac{10 \angle 0^\circ V}{441.47 \angle 76.90^\circ \Omega}$$

P. (14)

$$i = \frac{10}{441.47} \angle [0 - 76.90^\circ] \text{ A}$$

$$= 22.6 \times 10^{-3} \angle -76.90^\circ \text{ A}$$

$$= 22.6 \angle -76.90^\circ \text{ mA}$$

So,

The general expression
for "i"


$$i = 22.6 \cos(2t - 76.90^\circ) \text{ mA.}$$

P. (15)

Question 5:-

Find $v(t)$ & $i(t)$ in the circuit in figure

Figure:-

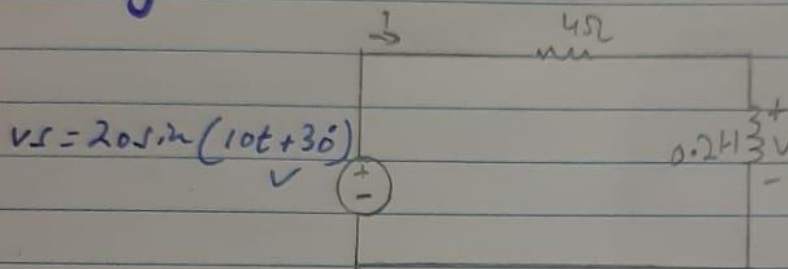

Solution:-

For $i(t)$
From the voltage source

$$v_s = 20 \sin(10t + 30^\circ) \text{ V}$$

$$v_s = 20 \cos(10t + 30^\circ - 90^\circ) \text{ V}$$

$$v_s = 20 \cos(10t - 60^\circ) \text{ V}$$

$$v_s = 20 \angle -60^\circ \text{ V}$$


$$\omega = 10 \text{ rad/sec}$$

$$X_L = j\omega L$$

$$0.2H = j \times 10 \times 0.2 \Rightarrow 0.2H = j2\Omega$$

P. (16)

Given circuit can be represented

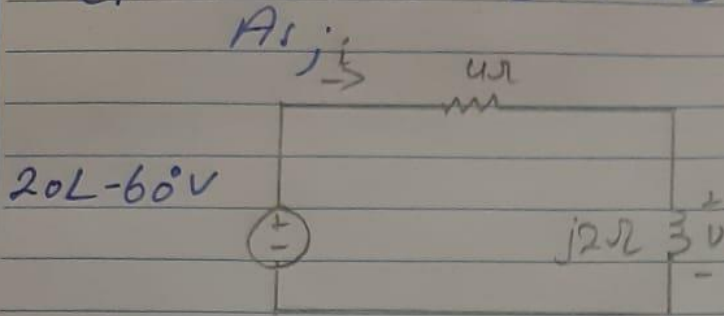

From the above circuit,

$$Z = 4 + j2\Omega$$

Hence the current is,

$$i = \frac{20\angle-60^\circ}{4 + j2}$$

$$i = \frac{20\angle-60^\circ}{\sqrt{4^2 + 2^2} \angle \tan^{-1}\left(\frac{2}{4}\right)}$$

$$i = \frac{20\angle-60^\circ}{4.472 \angle 26.57^\circ}$$

$$i = 4.472 \angle -86.57^\circ$$

P. (17)

Converting this into time domain.

$$i(t) = 4.472 \cos(10t - 86.57^\circ)$$

$$i(t) = 4.472 \sin(10t - 86.57^\circ + 90^\circ)$$

$$i(t) = 4.472 \sin(10t + 3.43^\circ) \text{ A}$$

For $v(t)$:

From the circuit voltage across the inductor is,

$$v = j\omega \times i$$

$$v = j2 \times (4.472 \angle 86.57^\circ)$$

Converting polar form to rectangular form we get

$$v = j2 \times (0.26756 - j4.464)$$

$$v = 8.928 + j0.53512.$$

Convert rectangular form to polar form.

P. (18)

$$V = \sqrt{(8.926)^2 + (0.53512)^2} \angle \tan^{-1}$$

$$\left(\frac{0.53512}{8.928} \right)$$

$$V = 8.944 \angle 3.4^\circ$$

Converting this in time domain.

$$v(t) = 8.944 \cos(10t + 3.4^\circ)$$

$$v(t) = 8.944 \sin(10t + 3.4^\circ + 90^\circ)$$

$$v(t) = 8.944 \sin(10t + 93.4^\circ)$$