

-: COURSE DETAILS:-

Course title :- EDC


Module :- 3rd

Instructor :- Dr-Shahryar

-: STUDENT DETAILS:-

Name :- Naveed Alam

Student ID :- 14965

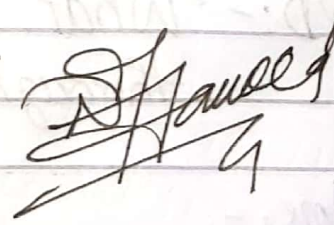Student Sign :- 

Q No. 1:-

The IN4747A zener used in the regulator circuit of Figure 1 is a 20V diode, determine the following-

(a) :- Determine V_{out} at I_{zk} and at I_{zm} .

Sol:- $V_{out} = V_z - \Delta I_z r_z$

$$V_{out} = 20 - (I_z - I_{zk}) r_z$$

$$V_{out} = 20 - (12.25)(22\ \Omega)$$

$$V_{out} = 20 - (0.01225)(22)$$

$$V_{out} = 20 - 0.2695$$

$$V_{out} = 19.7305\text{ V}$$

Know calculate zener max current the maximum power dissipation is 1W.

$$I_{zm} = \frac{P_o(\text{max})}{V_z} = \frac{1\text{ W}}{20} = 0.066667$$

$$I_{zm} = 50\text{ mA.}$$

$$I_{zm} = 50\text{ mA.}$$

for I_{zm}

$$\begin{aligned}V_{out} &= V_z + \Delta I_z z_z \\&= 20V + (50mA - 12.5mA) 22 \Omega \\&= 20V + (37.5mA) 22 \\&= 20V + 0.825\end{aligned}$$

$$V_{out} = 20.825V$$


(B) calculate the value of R for maximum zener current as shown in figure.

$$R = \frac{V_{in} - V_{out}}{I_{zm}}$$

$$= \frac{24V - 20.825V}{50mA}$$

$$R = 63.5 \Omega$$
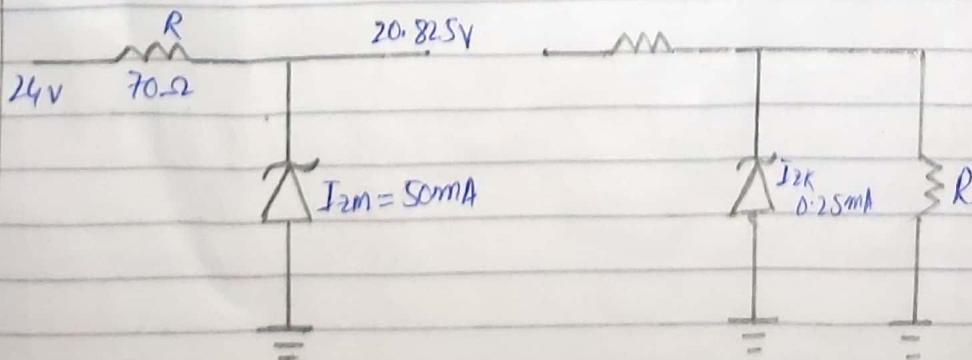
$$R = 70 \Omega \text{ (Nearest largest standard)}$$



Q: for maximum load Resistance (maximum current) the zener diode current minimum ($I_{zk} = 0.25$).

$$I_T = \frac{V_{in} - V_{out}}{R}$$

$$I_T = \frac{24V - 19.73V}{70\Omega}$$

$$I_T = 0.061A$$

$$I_T = 61mA$$

$$I_L = I_T - I_{zk}$$

$$I_L = 61 - 0.25mA$$

$$I_L = 60.75mA$$

$$R_L = \frac{V_{out}}{I_L} = \frac{19.3}{60.75} = \frac{19.3}{60.75mA}$$

$$R_L = \frac{19.3}{0.0675}$$

$$R_L = 285.92\Omega$$

$$R_L = 286\Omega$$

Q NO. 2:- Determine $I_B, I_C, I_E, V_{BE}, V_{CE}$
and V_{CB} in the circuit shown
in Figure 2.

Solution:-

Given $V_{BE} = 0.7V$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{3.9K\Omega}$$

$$I_B = 1102\mu A$$

$$I_C = \beta_{DC} \cdot I_B = (150)(1102\mu A) = 165.3\text{mA}$$

$$I_C = 165.3\text{mA}$$

$$I_E = I_C + I_B = 1653\text{mA} + 1102\mu A$$

$$I_E = 166.4\text{mA}$$

Solve for the V_{CE} and V_{CB}

$$V_{CE} = V_{CC} - I_C R_C = 15V - (165.3\text{mA})(180\Omega) \\ = 15V - 29.7V$$

$$V_{CE} = -14.7V$$

$$V_{CB} = V_{CE} - V_{BE} = -14.7V - 0.7V$$

$$V_{CB} = -15.4V$$

Since the collector is at a lower voltage
than the base, the collector-base junction
is forward-biased.

Q. NO. 3:-

Bipolar Junction Transistor:


BJT:-

Transistor as


- Invented in Dec 1947 at bell labs at USA-
- BJT is a three terminal device and it is used in amplification of weak signals used in switching operation-

→ Physical structure:-


NPN

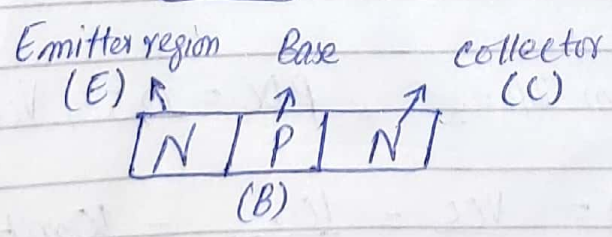


PNP

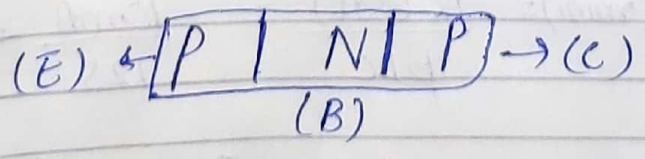

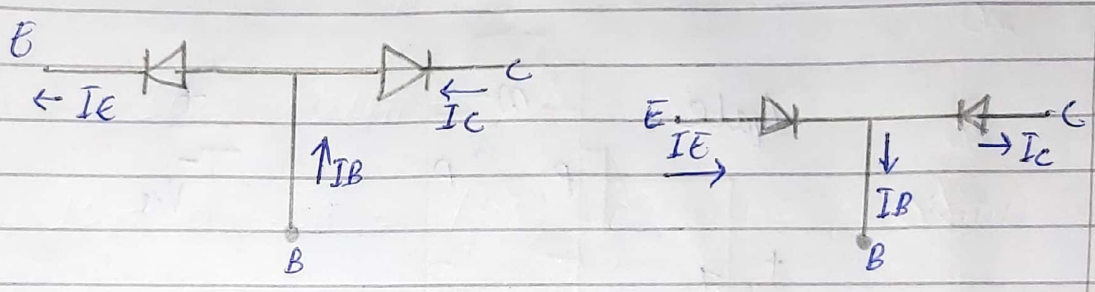
- 2 junction (N)
- 1 junction (P) width $C > E > B$
- J_1 → emitter-Base deping $E > C > B$
- J_2 → collector → Base
- There is depletion Region at J_1
- There is depletion region at J_2



↳ Section View:-

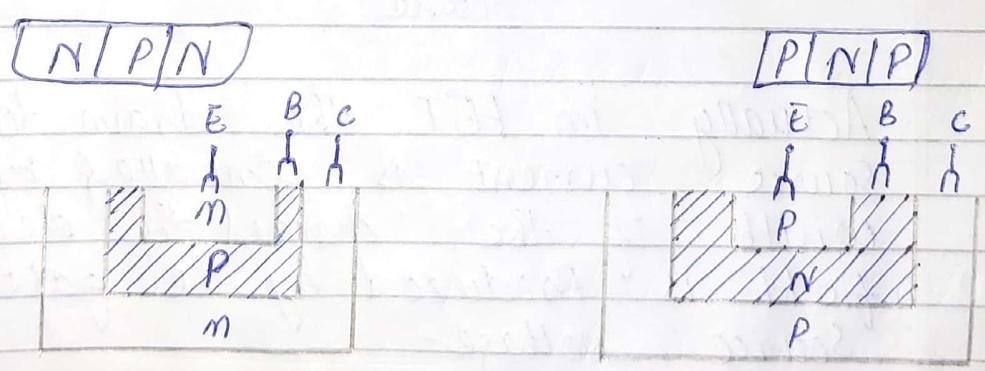


↳ Symbol:-

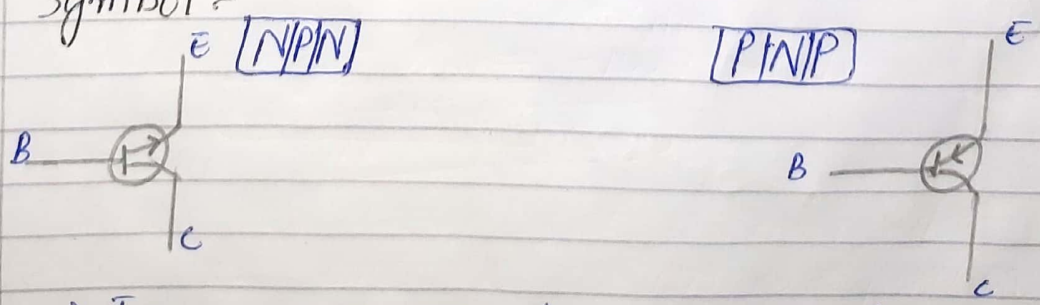

→ Increase of NPN these will more from B → E.

3

Diagram-

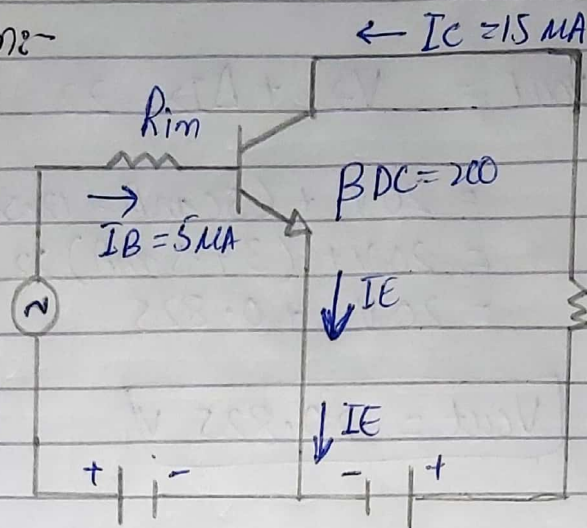

So this is common emitter configuration of transistor which has both voltage and current amplification.


$$\begin{aligned} I_C &= \beta \cdot I_B \\ &= 200 \cdot 5 \mu A \\ I_C &= 200 \cdot 0.00005 A \end{aligned}$$

$$\begin{aligned} I_E &= I_C + I_B \\ I_E &= 200 \cdot 0.00005 A + 5 \mu A \end{aligned}$$

$$I_E = 200 \cdot 0.00002$$


Q NO. 4:-

For a transistor to act as a "switch", you need to join each of the following conditions on the left to "NO" or "OFF" state -

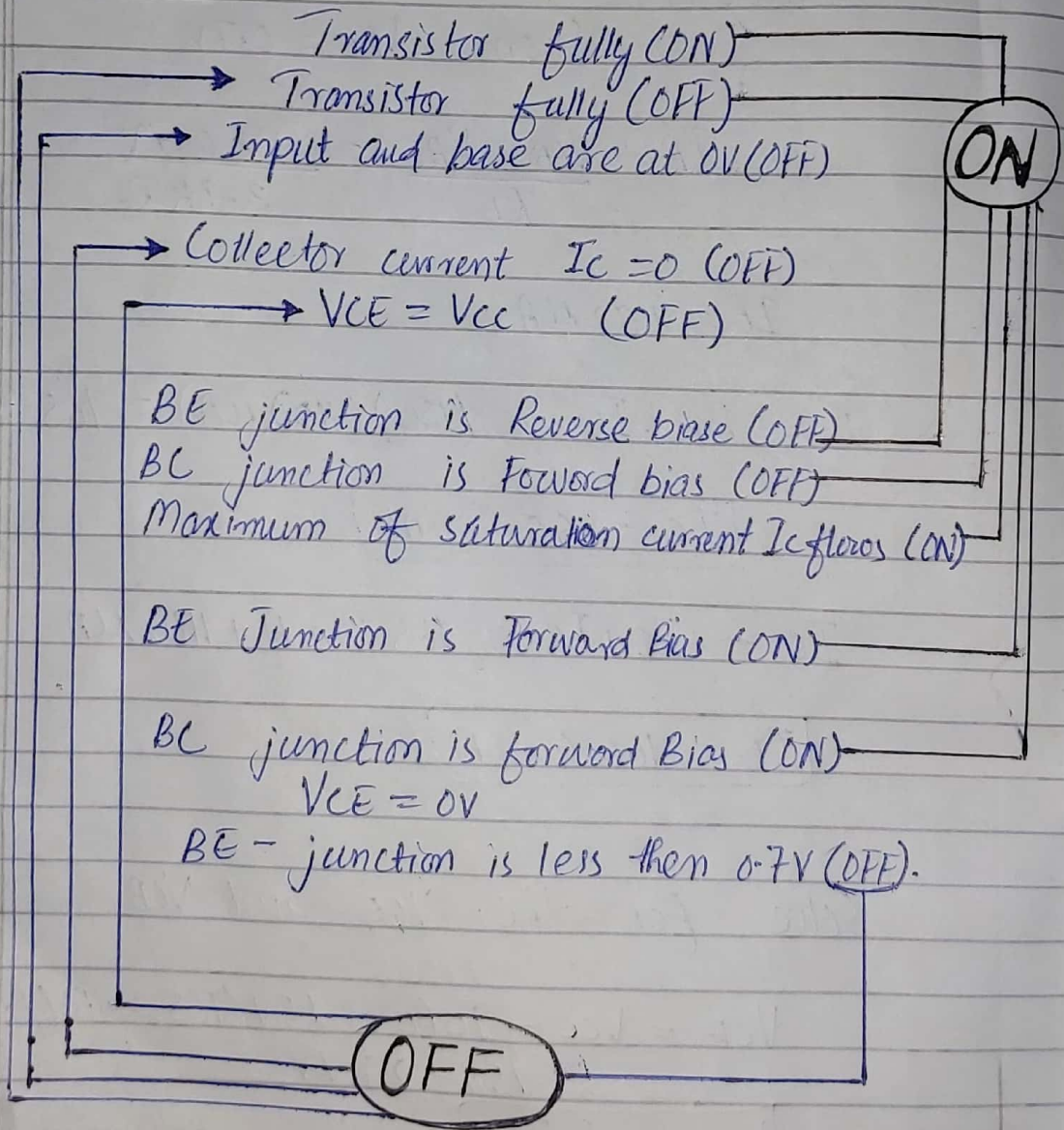


QNO.5:-

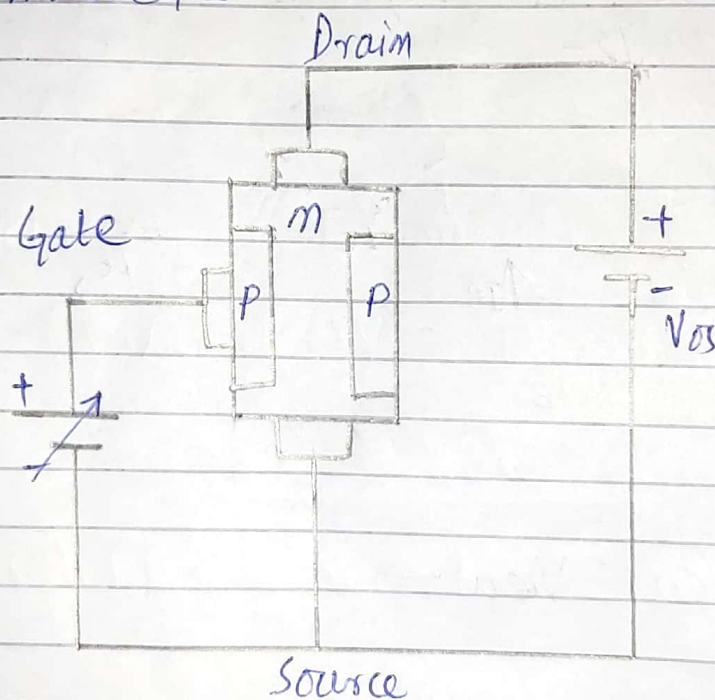
JFET is a type of ~~transistor~~ junction field effect transistor which is voltage controlled device as differ from BJT which is current controlled -



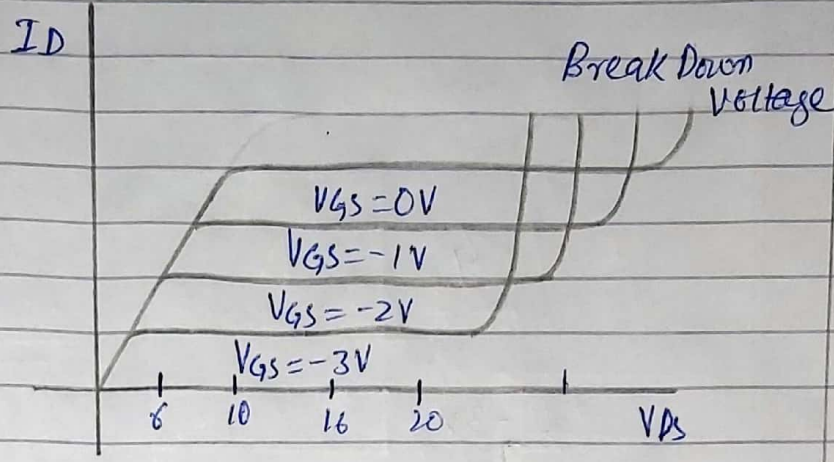
Actually in FET the drain to source current is controlled by the width of the channel the electric field is produced by the gate to source voltage -



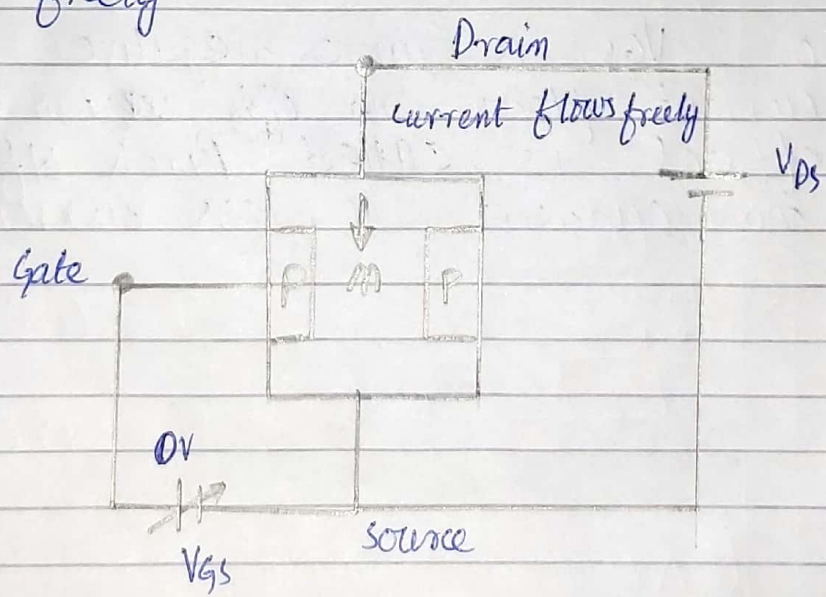So if we see to the graph with the no voltage applied to the gate the current flows freely



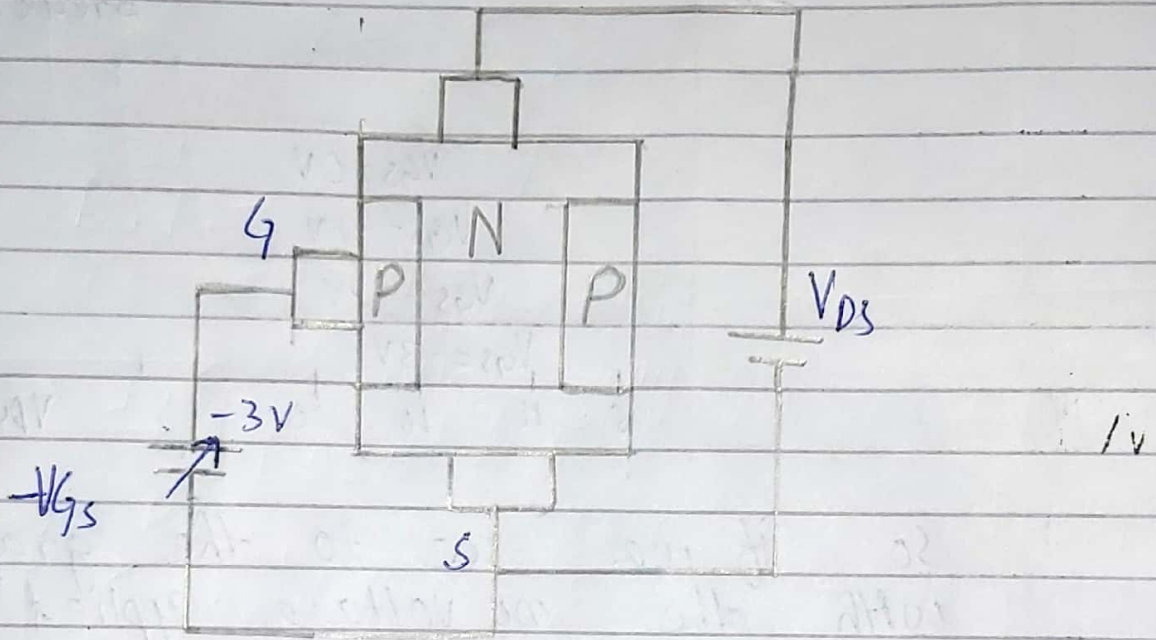The channel are wider and Drain current moves freely - If we move V_{GS} to negative value the channel width start to decrease and current cannot moves -



So V_{GS} is more negative so no current flows and ~~off region~~ this effect is called Pinch off region no current or less current flows.

Q NO. 6 :-

For the transistor circuit given in Fig 3, calculate the following -

(A) What is V_{CE} when $V_{IN} = 0V$?

Sol:- When $V_{IN} = 0V$, so transistor is in cut OFF mode and

$$V_{CE} = V_{CC} = 10V$$

(B) Determine the minimum value of I_B is required to ~~start~~ saturate this transistor if β_{DC} is 125 and $V_{CE(sat)}$ is $0.4V$.

Sol:- $\text{min } I_B = ?$, $\beta_{DC} = 125$, $V_{CE(sat)} = 0.4V$

$$I_C(sat) = \frac{V_{CC}}{R_C} = \frac{10V}{1.0K\Omega} = 10mA$$

$$I_B(\text{min}) = \frac{I_C(sat)}{\beta_{DC}} = \frac{10mA}{125} \rightarrow \text{scribbled out}$$

$$I_B(\text{min}) = \text{scribbled out } 80\mu A.$$

$$\therefore \boxed{I_B(\text{min}) = 80\mu A} \text{ :-}$$