


Department of Electrical Engineering
Assignment
Date: 14/04/2020

Course Details

Course Title: Electronic Circuit Design **Module:** 04
Instructor: ENGINEER MUJTABA **Total Marks:** 30

Student Details

Name: Asfandyar Awais **Student ID:** 11461

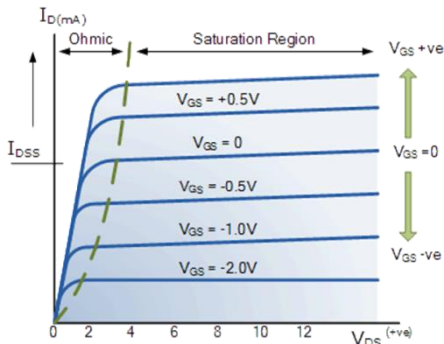Q1	(a)	<p>Explain the drain characteristic curve of D-MOSFET given below.</p> 	Marks 07
			CLO 1
	(b)	<p>Sketch the hybrid model and write equations for the transistor in common emitter configuration.</p>	Marks 06
			CLO 1
Q2		<p>A certain operational amplifier has a common mode gain of 0.6 and an open loop differential voltage gain of 400,000. Evaluate the CMRR & express it in decibels.</p>	Marks 05
			CLO 2
Q3	(a)	<p>Explain the concept behind negative feedback in operational amplifiers.</p>	Marks 06
			CLO 2
	(b)	<p>State the following statement as True or False and also give the reason for your answer: "The output of a summing amplifier is positive"</p>	Marks 06
			CLO 2

Answer to question 1(a):


Drain characteristics are the characteristics between the drain current I_d and the voltage v_{ds} for various voltage v_{gs} if we see I_d , v_{ds} and v_{gs} we will find that the i_d is the output current, v_{ds} is the output voltage and v_{gs} is the input voltage. Y axis is for the drain current I_d in milli amperes (mA) and X axis is for the voltage v_{ds} in volts. The figure shows that initially the v_{ds} is at zero potential so the drain current I_d is also at zero potential. As we increase the v_{ds} the drain current I_d starts increasing linearly. Now at a certain value of v_{ds} the i_d becomes constant, it is because of the pinch off. Here v_{gs} is 0volts. In depletion type MOSFETS we can increase and decrease the v_{gs} . In the graph when the v_{gs} is increased to $=0.5v$ we can see that the drain current I_d also increases. It is because the gate terminal becomes positive and attracts more electrons and as a result the drain current I_d increases. Now when the v_{gs} is decreased to $-0.5v$ and so on we can see that the I_d also decreases. It is because the gate terminal becomes negative and repels the electrons hence I_d decreases. And if in case the v_{gs} becomes equal to pinch off then the I_d will be zero at any value of v_{ds} .

In case of $v_{gs}=0v$ the saturated drain current which is the maximum drain current is called I_{DSS} as shown in figure.

Answer to Question 1(b):

In common emitter transistor configuration, the input signal is applied between the base and emitter terminals of the transistor and output appears between the collector and emitter terminals. The input voltage (V_{be}) and the output current (i_e) are given by the following equations:

FIG 1

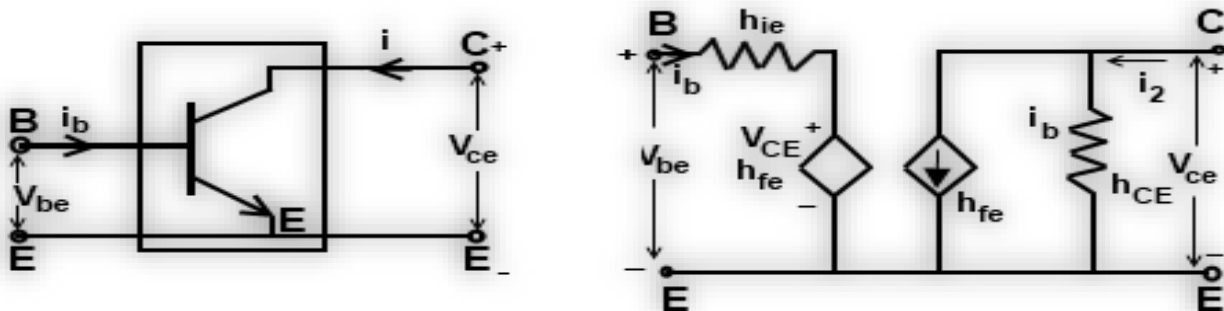

$$V_{be} = h_{ie} \cdot i_b + h_{re} \cdot V_c$$

$$i_e = h_{fe} \cdot i_b + h_{oe} \cdot V_c$$


$$\text{Where } h_{ie} = (\partial f_1 / \partial i_B) V_c = (\partial v_B / \partial i_B) V_c = (\Delta v_B / \Delta i_B) V_c = (v_b / i_b) V_c$$

$$h_{re} = (\partial f_1 / \partial v_c) I_B = (\partial v_B / \partial v_c) I_B = (\Delta v_B / \Delta v_c) I_B = (v_b / v_c) I_B$$

$$h_{fe} = (\partial f_2 / \partial i_B) V_c = (\partial i_c / \partial i_B) V_c = (\Delta i_c / \Delta i_B) V_c = (i_c / i_b) V_c$$

$$h_{oe} = (\partial f_2 / \partial v_c) I_B = (\partial i_c / \partial v_c) I_B = (\Delta i_c / \Delta v_c) I_B = (i_c / v_c) I_B$$

FIG 2

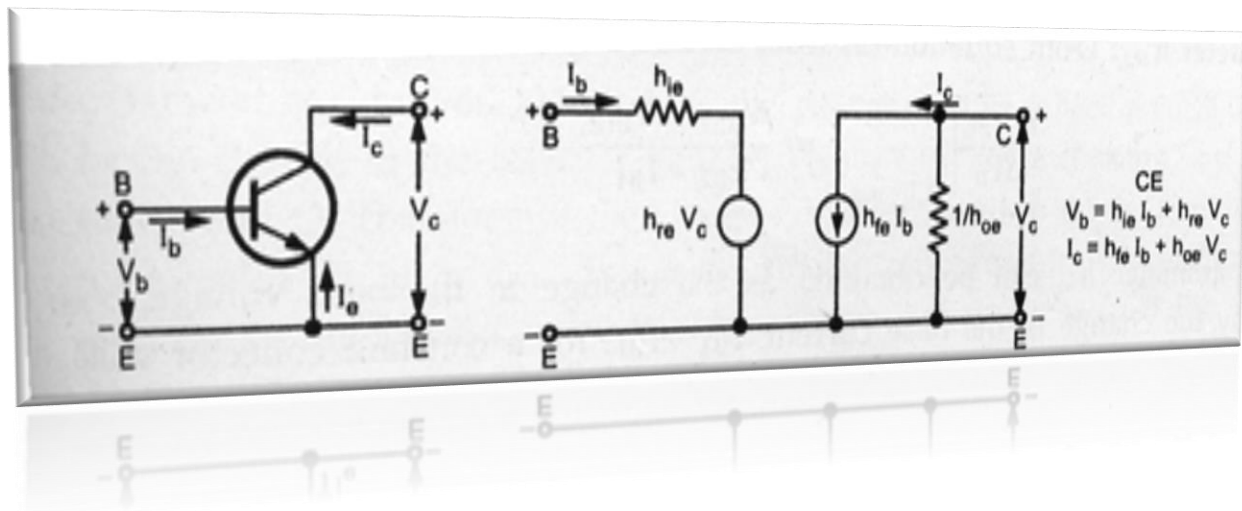

Answer to question 2:

Given:

Aol=Open loop differential voltage gain= 400000

Acm=Common mode gain=0.6

Required:

CMPR=?

Solution:

FORMULA: CMPR=Aol/Acm

Therefore

CMPR=400000/0.6

$$=666666.666$$

CMPR in decibels:

Formula:

$$\text{CMPR} = 20 \log(A_{ol}/A_{cm})$$

$$= 20 \log(666666.666)$$


$$= 116.47 \text{ dB}$$

Answer to question 3 (a):

Negative feedback is the process whereby a portion of the output voltage of an amplifier is returned to the input with a phase angle that opposes (or subtracts from) the input signal.

Inverting (-) input effectively makes the feedback signal 180° out of phase with the input signal.

A negative feedback amplifier is an amplifier that subtracts a fraction of its output from its input, so that the negative feedback opposes the original signal, the applied negative feedback can improve its performance (gain stability, linearity, frequency response, step response) and reduces sensitivity to the parameter variations due to malfunctioning or environment. Because of these advantages, many amplifiers and control system use negative feedback.

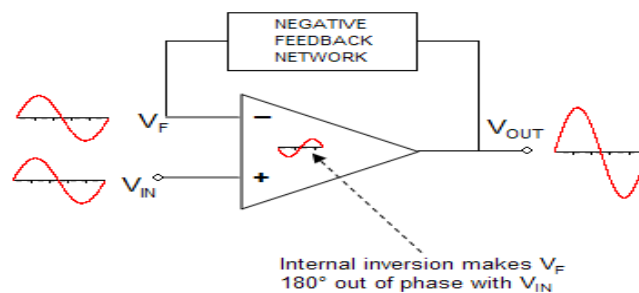

Answer to question 3 (b):

The statement is not true. The reason is that whenever the summing point is connected to the inverted input of the operational amplifier the circuit will produce the negative sum of any number of input voltages. Similarly, when the summing point is connected to the non-inverting input of the operational amplifier a positive sum of all the input voltages will be produced.