

Name Zia Us Rehman

①

ID 11473

Course Electronic devices and circuits

Q1

$$V_z = 20$$

$$I_z = 12.5$$

$$\text{see } Z_z = 22\Omega$$

$$I_{zk} = 0.25$$

a) for $I_{zk} =$ $V_{out} = V_z = \Delta I_z Z_z$

$$= 20 (12 - I_{zk}) Z_z$$

$$= 20 (12.25 \text{ mA}) (22\Omega)$$

$$= 20 \text{ V} (0.01225) (22)$$

$$= 20 \text{ V} (0.2695)$$

$$\boxed{= 19.7305 \text{ V}}$$

Calculating Zener max current, the maximum power dissipation is 1W.

$$I_{zm} = \frac{P_o (\text{max})}{V_z} = \frac{1 \text{ W}}{20} = 0.05 \text{ A}$$

$$\boxed{I_{zm} = 0.05 \text{ A}}$$

for I_{zm} : $V_{out} = V_z + \Delta I_z Z_z$

$$= 20 + \Delta I_z Z_z$$

$$= 20 \text{ V} + (I_{zm} - I_z) Z_z$$

$$= 20 \text{ V} + (54.2 \text{ mA}) (22\Omega)$$

$$= 20 \text{ V} + (0.0542) (22\Omega)$$

(2)



$$= 20V + 1.1924$$

$$V = 21.1924V$$

④ Calculating value of R for max Zener current that occurs when there is no load.

$$R = \frac{V_{in} - V_{out}}{I_{zm}} = \frac{24V - 21.1924V}{66.7mA} = \frac{2.808}{66.7mA}$$

$$R = 44\Omega$$

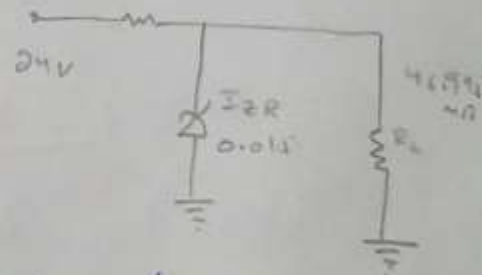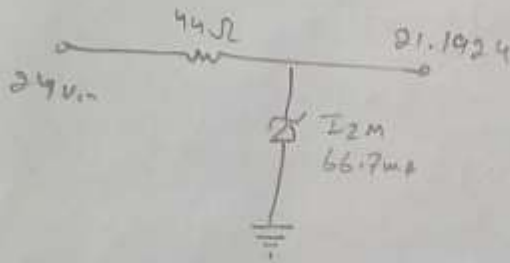

⑤ For the maximum load resistance (maximum load current) the Zener current is $(I_{zk} = 0.025mA)$

$$I_T = \frac{V_{in} + V_{out}}{R} = \frac{24 - 19.7305}{44}$$

$$I_T = 0.0970 = 97.034mA$$

$$I_L = I_T - I_{zk} = 97.034 - 0.025 = 96.784mA$$

$$R_L (min) = \frac{V_{out}}{I_L} = \frac{19.7305}{96.784mA} = \frac{19.7305}{0.096784}$$


$$R_L (min) = 203.97\Omega$$

Q2

$$V_{BE} = 0.7V$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$
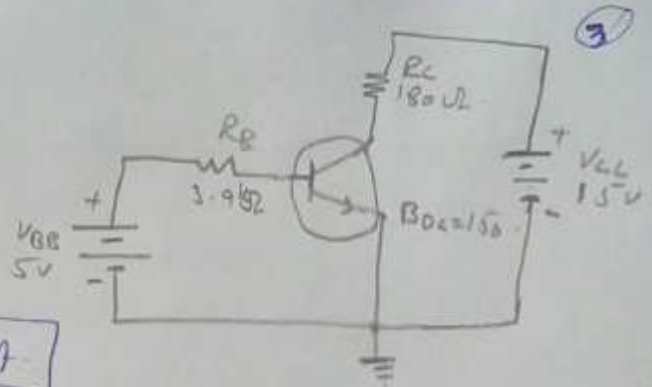
$$= \frac{5V - 0.7V}{3.9k\Omega} \rightarrow \boxed{1102\mu A}$$



$$I_C = B_{DC} I_B \Rightarrow (150)(1102\mu A) = \boxed{165.3mA}$$

$$I_E = I_C + I_B = 165.3mA + 1102\mu A \rightarrow \boxed{166.4mA}$$

for: V_{CE} , V_{CB}

$$V_{CE} = V_{CC} - I_C R_C = 15V - (165.3mA)(180\Omega) \\ = 15V - 29.7V = \boxed{-14.7V}$$

$$V_{CB} = V_{CE} - V_{BE} = -14.7V - 0.7V$$


$$\boxed{V_{CB} = -15.4V}$$

since the collector is at a lower voltage than the base, the collector base junction is forward-biased.


Q3 Discuss how is BJT used as an amplifier with the help of schematic diagram for a basic BJT amplifier? (4)

Ans: BJT (Bipolar junction transistor) are widely used as amplifiers, physical structure



NPN

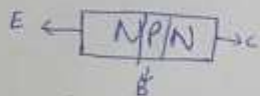

PNP

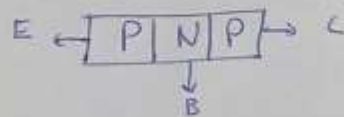


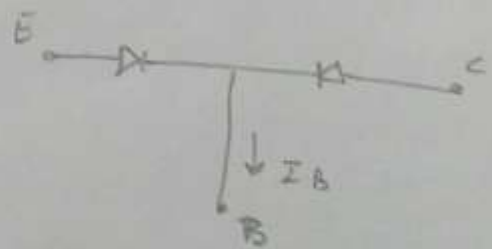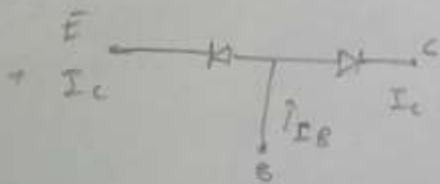- 2 junction (N)
- 1 junction (P)
- $J_1 \rightarrow$ emitter Base
- $J_2 \rightarrow$ collector base
- There is depletion region at J_1
- There is depletion region at J_2




Symbol:


NPN

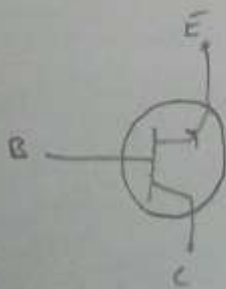

PNP

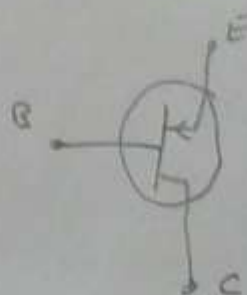

Q4

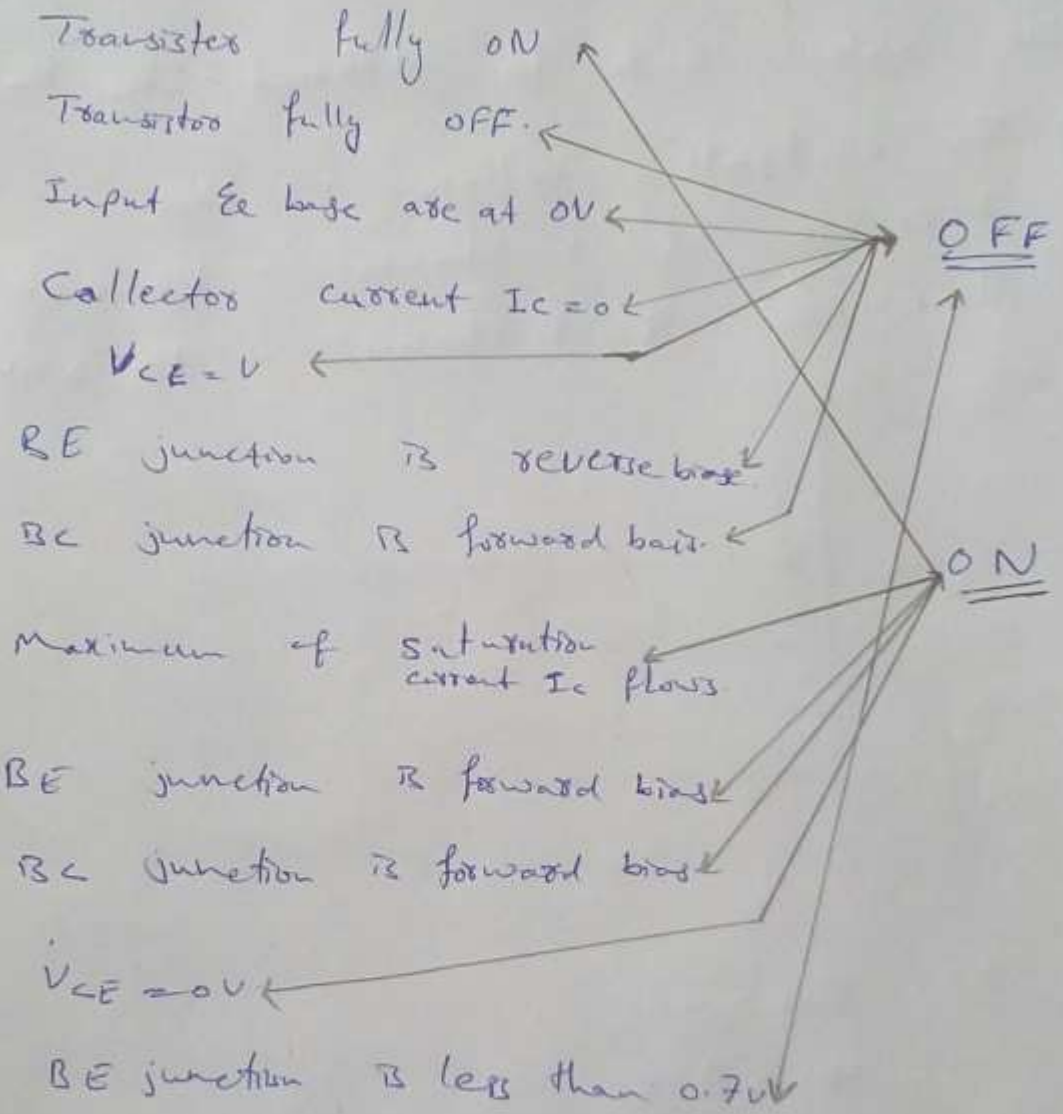

''-----''

6

Q5 Discuss that how JFET (n-channel) can be used as voltage control device.

Ans: The magnitude of the current flowing through the channel between Drain and the Source terminals is controlled by a voltage applied to the Gate terminal which is reverse-biased. In an N-channel JFET this Gate voltage is negative while for a P-channel JFET the Gate voltage is positive.

The JFET operation can be compared to that of a garden pipe. The flow of water through a pipe can be controlled by crushing it to reduce the cross section and the electric charge flow through a JFET is controlled by forcing the current carrying channel. The current also depends on the electric field between the source and the discharge (similar to the pressure difference on both ends of the tube). Conduction of conducting channel is performed using the field effect. A voltage between the gate and the source is applied to reverse the gate n-source pn

⑦

Pn -junction, thereby widening the junction layer invading channel conduction and limiting its cross-sectional area. The depletion layer is so called because it is depleted of mobile carriers and is therefore electrically non-conductive for practical purpose.

When the drainage layer extends along the width of the conduit channel, reduction is achieved and drain-to-source conduction is interrupted. Pinching occurs at a particular reverse polarization (V_{GS}) of the gate-source junction. The switch-off voltage (V_P) varies considerably, even between devices of the same type. For example, $V_{GS}(\text{off})$ for the Texas J102 device varies from $-0.8V$ to $-4V$. The typical value from $-0.3V$ to $-1.0V$.


To turn off a channel device n requires a negative gate-source voltage (V_{GS}). Conversely to turn off a p -channel device, a positive V_{GS} is required.

In normal operation, the electric field developed by the gate blocks, to some extent the conduction of the source-drain. Some JFET devices are symmetrical with respect to origin and discharge.

Characteristics of JFETs (N-channel).

we obtain both for different V_{GS} values.

- The controlling voltage is V_{GS} .
- Increase of n-channel → $V_{GS} < 0V$.
- Increase of p-channel → $V_{GS} > 0V$.

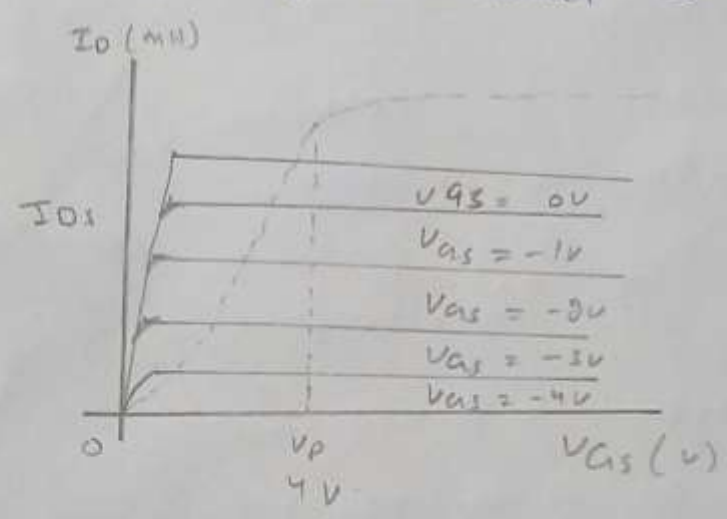

Case 1: $V_{GS} = 0V$

$V_{GS} > I_{VB}$

$I_{DSS} = 8mA$
 $V_p = -4$

Case 2: $V_{GS} = -1V$

Case 3: $V_{GS} = -3$

Case 4: $V_{GS} = -4$

Case 5: $V_{GS} = -5$

Q 6

9

a) $V_{CE} = ?$ $V_{in} = 0V$

when $V_{in} = 0V$ so transistor is in cut-off mode and $V_{CE} = V_{CC} = 10V$

b) = Min. $I_B = ?$ $\beta_{DC} = 125$ $V_{CE(sat)} = 0$

$$I_C(sat) = \frac{V_{CC}}{R_C} = \frac{10V}{10k\Omega} = 1mA$$

$$I_B(min) = \frac{I_C(sat)}{\beta_{DC}} = \frac{1mA}{125} = 0.008mA$$

c) Max R when $V_{in} = 5V$

$V_{BE} = 0.7V$ then $R_B = ?$


$$V_{RB} = V_{in} - V_{BE} = 5V - 0.7V = 4.3V$$

Now we solve for max value of R_B needed to allow a min I_B of $0.008mA$ using.


Ohm's Law

$$R_B(max) = \frac{V_{RB}}{I_B(min)} = \frac{4.3V}{0.008mA} = \boxed{537.5k\Omega}$$


Q6

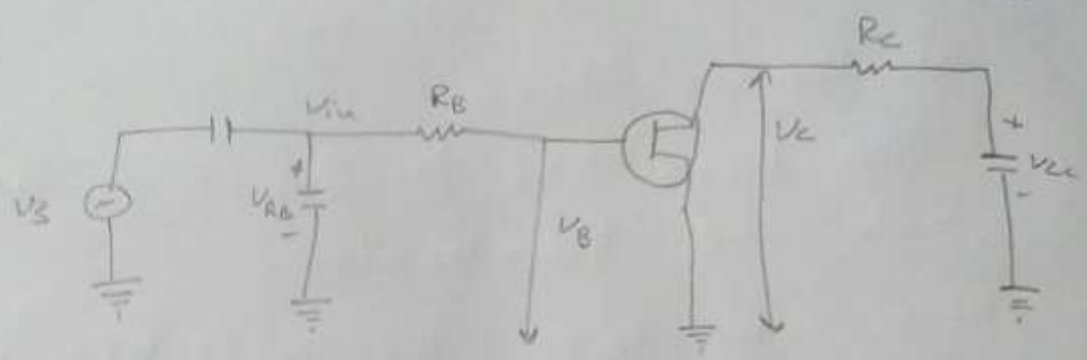

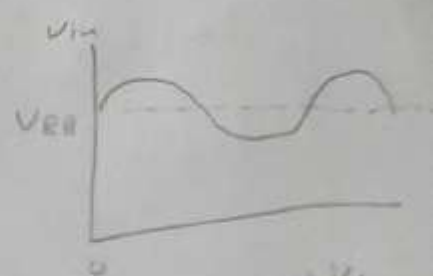The ac base volt = $v_b = I_{e r_e}$
 The collector volt is = $v_c = I_c R_c$
 since $I_c \approx I_e$ the ac collector
 voltage is $v_c \approx I_e R_c$



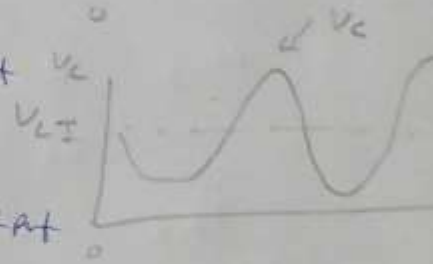Consider v_b as transistor input
 volt. and $v_b = v_s - I_b R_B$



Consider v_c as transistor output
 volt

Volt gain is $A_V = \frac{v_c}{v_b} = \frac{I_e R_c}{I_e r_e}$

So $A_V = \frac{R_c}{r_e}$

// ----- //