

NAME : FAWAD REHMAN

ID : S053

PAPER : POWER ELECTRONICS

INST : ENGR. SHAYAN

DATE : 27/06/2020

Question No : 01

Answer:

* 1- \otimes half wave and Full wave
bridge Rectifiers:


→ Half wave rectifier which convert only one half of the AC cycle into pulsating DC while Full wave rectifier is an electronic circuit which converts entire cycle AC into pulsating DC.

→ Half wave utilize only half of AC cycle for the conversion while Full wave utilize Full wave of AC cycle.


→ Half wave is unidirectional the conduction is one directional only either convert positive or negative, that why called half wave. While Full wave is bidirectional

It conduct positive half as well as negative half cycle.

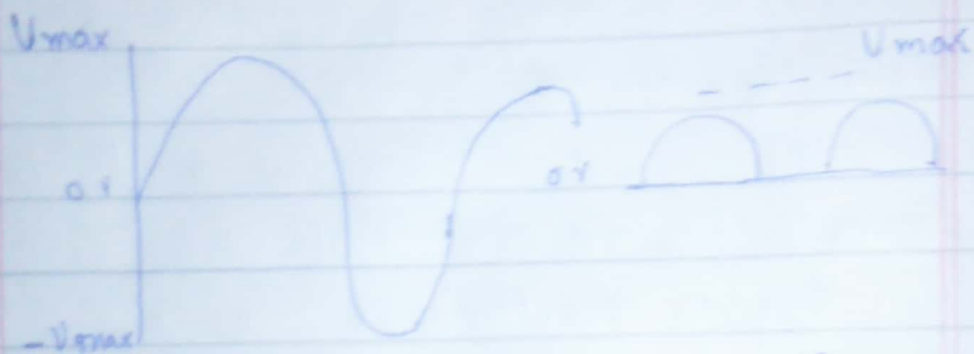→ Output wave form of single phase half wave rectifier



→ Single Phase Full wave rectifier

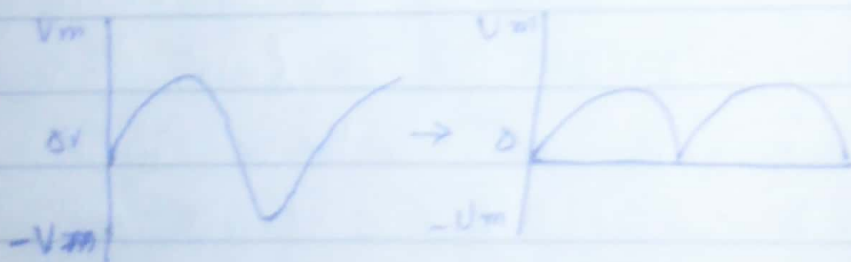

→ Number of diode in half wave is 1 while in full wave is 4.

→ Both utilize single phase for operation.

→ Peak inverse voltage of single half wave and full wave rectifier are same.

* 1-Q Uncontrolled & controlled
rectifier (D & S):

→ Uncontrolled are naturally turn on whenever positive voltage is applied b/w its terminal and when you stop by applying it voltages become negative.

→ Uncontrolled rectifier is a diode
→ It has two terminals and will only allow flow in one direction only. While a controlled rectifier has a third connection, that controls at which point the rectifier will work.

→ Controlled rectifier does not become conducting immediately after its voltage has become positive.

→ It requires triggering by means of gate pulse signal.

Question No: 02

Solution:

$$V_m = 53 \text{ V}$$

$$R = 50 \Omega$$

we know that

For half wave

1) V_{dc}

$$\Rightarrow \frac{V_m}{\pi} \quad \text{--- (1)}$$

where $V_m = 53 \text{ V}$

$$\pi = 3.14$$

Putting values in (1), we get

$$\frac{53}{3.14} = 16.87 \text{ V}$$

For Full wave

$$\Rightarrow \frac{2 V_m}{\pi} \quad \text{--- (2)}$$

where $V_m = 53 \text{ V}$

$$\pi = 3.14$$

Putting values in (2), we get.

$$\frac{2(53)}{3.14} = 33.7 \text{ V}$$

2) I_{dc}

For half wave

$$I_{dc} = \frac{V_m}{\pi R}$$

PAGE: 05

Putting values, we get

$$\frac{53}{(3.14)(50)} = 0.33 \text{ A}$$

For Full wave

$$I_{dc} = \frac{I_m}{\pi} \quad \text{where } I_m = \frac{V_m}{R}$$

$$I_m = \frac{53}{50} = 1.06$$

Putting value of I_m in above eq,
we get

$$\frac{1.06}{3.14} = 0.3 \text{ A}$$

3) V_{rms}

$$\text{For half wave } V_{rms} = \frac{V_m}{2}$$

$$= \frac{53}{2} = 26.5 \text{ V}$$

For Full wave

$$V_{rms} = \frac{V_s}{\sqrt{2}}$$

Now put values

$$V_{rms} = \frac{37.4}{\sqrt{2}}$$

$$V_{rms} = 26.5 \text{ V}$$

$$\text{where } V_s = \frac{V_m}{\sqrt{2}}$$

$$V_s = \frac{53}{\sqrt{2}}$$

$$V_s = 37.4 \text{ V}$$

4) I_{rms}

For half wave

$$I_{rms} = \frac{V_m}{2R}$$

$$I_{rms} = \frac{53}{2(50)}$$

$$I_{rms} = 0.53A$$

For Full wave

$$I_{rms} = \frac{I_m}{2}$$

$$I_{rms} = \frac{1.06}{2}$$

$$I_{rms} = 0.53A$$

$$\text{Where } I_m = \frac{V_m}{R}$$

$$I_m = \frac{53}{50}$$

$$I_m = 1.06$$

5) The uncontrol Full wave bridge rectifier because the efficiency of it, is better than in half wave bridge rectifier and output frequency is also greater than half wave rectifier.


Question No: 03

Solution:

Principals And Working OF
Buck converter:

PAGE: 07

The main working principle of buck converter is that the inductor in the input circuit resists sudden variations in input current. When switch is ON the inductor store energy in the form of magnetic energy and discharges it when switch is CLOSED. The capacitor in the output circuit is assumed larger enough that the time constant of RC circuit in the output stage is high. The large time constant compared to switching period ensures a constant output voltage.

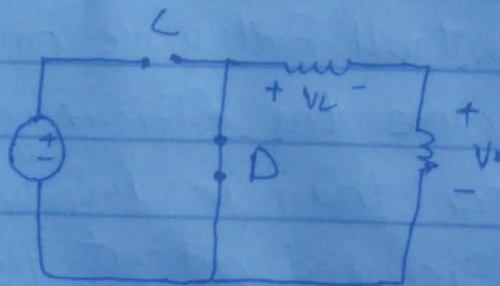

Data:

$$V_{in} = 50V$$

$$V_{out} = 53\%$$

$$R = 50\Omega$$

$$\text{Frequency} = 20\text{kHz}$$

1) V_{out}

we know that

$$V_{out} = D \times V_s$$

which is $53\% = 0.53$

putting values, we get

$$(0.53)(50)$$

$$= 26.5V$$

2) I_{out}

$$I_{out} = \frac{V_o}{R}$$

$$= \frac{50}{50}$$

$$I_{out} = 1A$$

3) I_{in}

we know that

$$I_o = \frac{I_i}{D}$$

$$I_i = I_o \times D$$

$$I_i = 1 \times 0.53$$

$$I_i = 0.53A$$

4) Inductor (L)

$$L = \frac{RT_{off}}{2} \times R \quad \text{let suppose } T_{off} = 0.004$$

$$L = \frac{0.004}{2} \times 50$$

$$L = 0.1H$$

Question No: 04

Solution:

Working Principle of Boost Converter:

A boost converter is one of the simplest types of switch mode converter. It takes an input voltage and boosts or increases it. It is less cumbersome than an AC transformer or inductor. It has high efficiency up to 99%. It means output voltage is greater than input voltage.

The main working principle of a boost converter is that the inductor in the input circuit resists sudden variation in input current. When the switch is OFF, the inductor stores energy in the form of magnetic energy and discharges when the switch is CLOSED.

Data:

$$V_{in} = 50V$$

$$D = 53\%$$

$$R = 50$$

$$\text{Frequency} = 20 \text{ kHz}$$

1). V_{out}

we know that

$$V_{out} = D \times V_s$$

$$V_{out} = (0.53)(50) = 26.5V$$

2). I_{out}

$$I_o = I_i(1-d)$$

$$I_o = 1.2649(1-0.53)$$

$$I_o = (1.2649 \times 0.47)$$

$$I = 0.594 A$$

3). I_{in}

$$I_i = \frac{V_i}{(1-d)^2} \times \frac{1}{R}$$

$$I_i = \frac{50}{(1-0.53)^2} \times \frac{1}{50}$$

$$I_i = 1.2649 A$$

4). Inductor L

$$L = \frac{R T_{on} (1-d)^2}{2}$$

$$d = \frac{T_{on}}{T}$$

$$T_{on} = 0.53 \times 0.0104$$

$$T_{on} = 0.005$$

$$L = \frac{R T_{on} (1-d)^2}{2} \Rightarrow L = \frac{50 (0.005) (1-0.53)^2}{2}$$

$$L = 0.224H$$

Question No: 05

Solution:

Working Principle of Buck Converter:

The main working principle of Buck converter is that the inductor in the input circuit resists sudden variations in input current. When switch is ON the inductor stores energy in form of magnetic energy and discharges it when switch is CLOSED.

Data:

$$V_{in} = 50V$$

$$V_{out} = 53\%$$

$$R = 50\Omega$$

$$\text{Frequency} = 20\text{KHz}$$

1) Duty cycle (D)

we know that

$$\frac{V_o}{V_i} = \frac{D}{1-D}$$

$$V_o = + V_i \frac{D}{1-D} \quad \text{put values}$$

$$0.53 = + 50 \frac{D}{1-D}$$

$$(0.53)(1-d) = 50d$$

$$0.53 - 0.53d = 50d$$

$$0.53 = 50d + 0.53d$$

$$0.53 = 50.53d$$

$$\frac{0.53}{50.53} = \frac{50.53d}{50.53}$$

$$d = 0.0104$$

2). I_{out}

we know that

$$I_{max} + I_{min} = \frac{2dV}{R(1-d)^2}$$

$$I_{max} + I_{min} = \frac{2(0.0104)(50)}{50(1-0.0104)^2}$$

$$= 0.0212$$

we know that

$$I_{out} = \frac{I_{max} + I_{min}}{2}$$

$$= \frac{0.0212}{2}$$

$$I_{out} = 0.0106 A$$

3). Inductor:

$$L = \frac{R T d}{2} (2-d)^2$$

Putting values where $T = 1/R$

$$T = \frac{1}{20 \times 1000} = T = 0.0005$$

PAGE: 13

$$L = \frac{50(0.00005)}{2} (1 - 0.0104)^2$$

$$L = 0.124 \text{ H}$$

The END