

Name :- MIR - Muhammad

ID # :- 15062



Sess. Assign : E.N. A

Instructor :- Shaharyar Sir.

Q1: For the circuit in Fig 1,
if $v = 10e^{-4t}$ ξ $0.2e^{-4t}$ $t > 0$

(a) Find R ξ C (b) ... (c) ... (d) ...

50% of the initial energy.

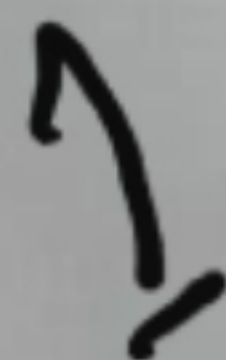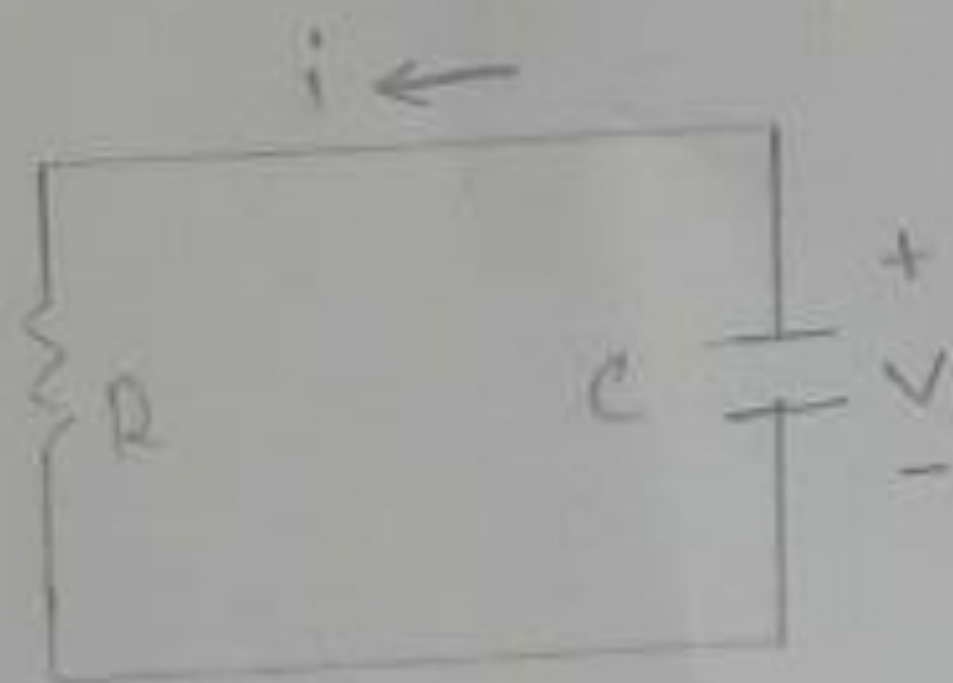

Step 1

(A) $\tau = RC = \frac{1}{4}$

$\Rightarrow -1 = C \frac{dv}{dt}$

$\Rightarrow -0.2e^{-4t} = C(10)(-4)e^{-4t}$

$\Rightarrow C = 5 \text{ mF}$

$R = \frac{1}{4C} = 50 \Omega$

Step 2

(B) $\tau = RC = \frac{1}{4} = 0.250$

Step 3

(C) $W_C(0) = \frac{1}{2} C v^2$

$\Rightarrow \frac{1}{2} (5 \times 10^{-3}) (100)$

$\Rightarrow 250 \text{ mJ}$

Step 4

2

$$(D) \quad W_R = \frac{1}{2} \times \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{1}{2} C V_0^2 (1 - e^{-\frac{2t_0}{\tau}})$$

$$0.5 = 1 - e^{-8t_0} \Rightarrow e^{-8t_0} = \frac{1}{2}$$


OR

$$e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2)$$

$$\Rightarrow 88.6 \text{ ms}$$

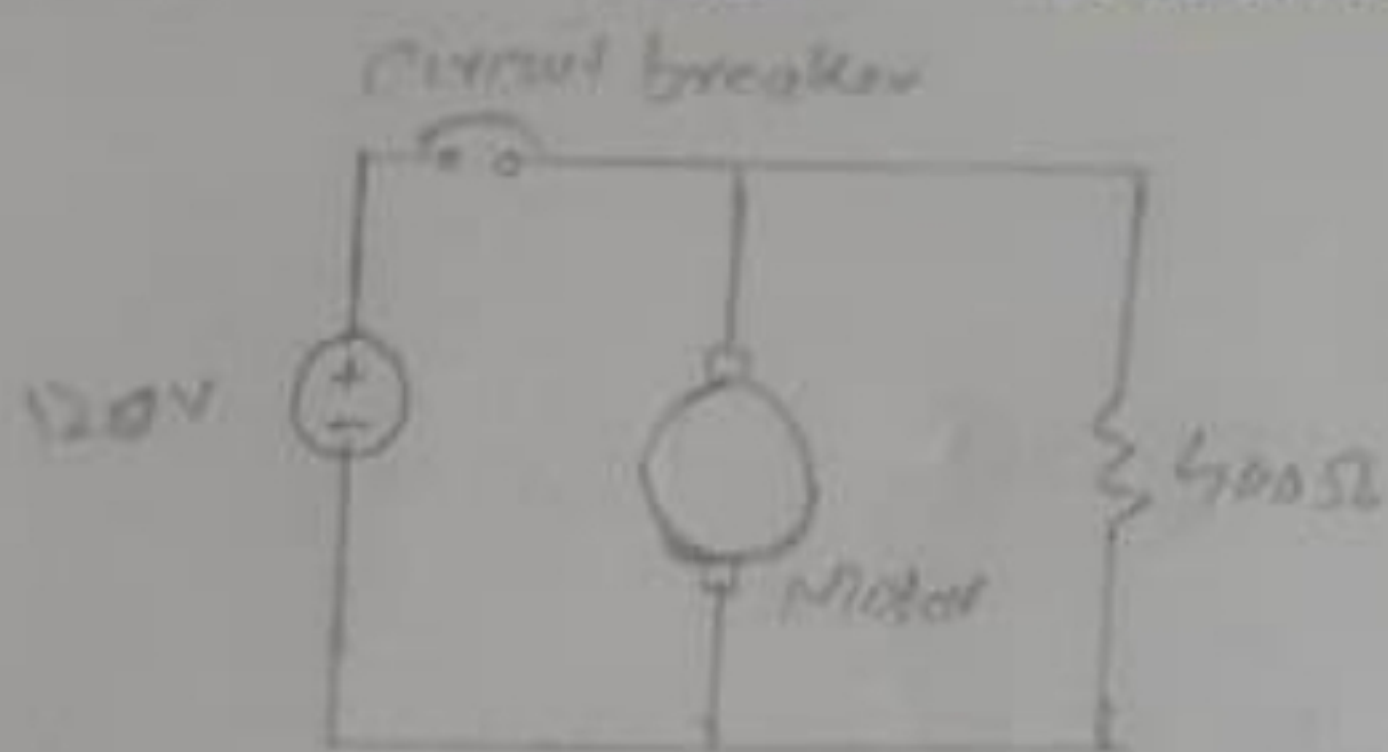A 120-V dc generator energize a motor whose coil the breaker is tripped.



Let the inductor current.

For $t < 0$

$$i(0) = \frac{120}{100} = \frac{12}{10}$$

$$\Rightarrow \frac{6}{5} = 1.2 \text{ A}$$

For $t > 0$ We have an RL circuit

$$\tau = \frac{L}{R} = \frac{50}{100+400}$$

$$\Rightarrow \frac{50}{500} \Rightarrow \frac{5}{50}$$

$$\Rightarrow \frac{1}{10} = 0.1$$

$$i(\infty) = 0$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$i(t) = 1.2 e^{-10t}$$

$$\text{At } t = 100 \text{ ms} = 0.1 \text{ s}$$

$$i(0.1) = 1.2 e^{-1} = 0.441 \text{ A}$$

The Response of RLC series RLC circuit
 Determine the value of R, L, C

Series RLC Circuit

$$v_c(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$V(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0]$$

$$40e^{-20t} - 60e^{-30t} \text{ mA}$$

$$\Leftrightarrow i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0]$$

Comparing these equ... we get

$$V_s = 30$$

$$A_1 = -10 ; A_2 = 30 ;$$

$$s_1 = -20 ; s_2 = -10 \rightarrow (a)$$

$$A_1' = 40 ; A_2' = -60 ;$$

$$s_1' = -20 ; s_2' = -10 \rightarrow (b)$$

Step 2

NOIN

Equ (a) & (b)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{And} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 + s_2 = -2\alpha \quad \& \quad s_1 s_2 = \omega_0^2$$

$$\left[\text{where } \alpha = \frac{R}{2L} ; \omega_0 = \frac{1}{\sqrt{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$\Rightarrow \alpha = 15$$

$$\Rightarrow \frac{R}{2L} = 15 \rightarrow (c)$$

$$200 = \frac{1}{Lc} \Rightarrow \frac{1}{Lc} = 200 \rightarrow (d)$$

Step 3

$$i(t) = c \frac{dv(t)}{dt} = c [200e^{-20t} - 300e^{-30t}]$$

$$(A_1 e^{s_1 t} + A_2 e^{s_2 t}) \times 10^{-3} \text{ A} = c [200e^{-20t} - 300e^{-30t}] \text{ V}$$

or

$$[s_1 = s_1' \quad s_2 = s_2']$$

$$\Rightarrow 200c = A_1 = 40 \times 10^{-3}$$

$$\Rightarrow C = 200 \times 10^{-6} \text{ F} \Rightarrow C = 200 \mu\text{F}$$

Using Equ (c) & (d)


$$L = \frac{1}{200c} \text{ F} = \frac{1}{200 \times 200 \times 10^{-6}} \Rightarrow L = 25 \text{ H}$$

$$\text{or } R = 30L = 30 \times 25 = 750 \Omega$$

Qu


The circuit in Fig. 3 is the electrical analog of body Function

6

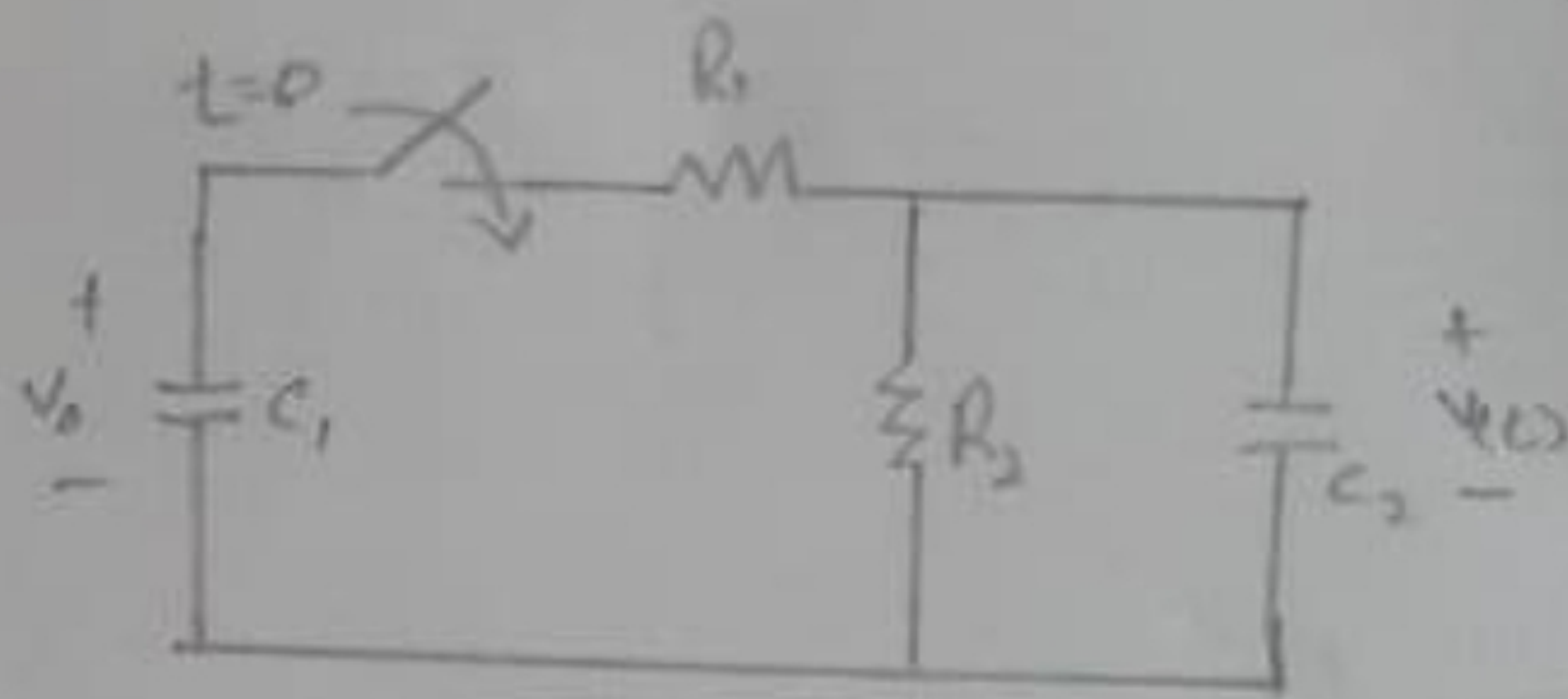

For $t = 0^-$, $V(t) = 0$

For $t > 0$ the circuit is shown below.

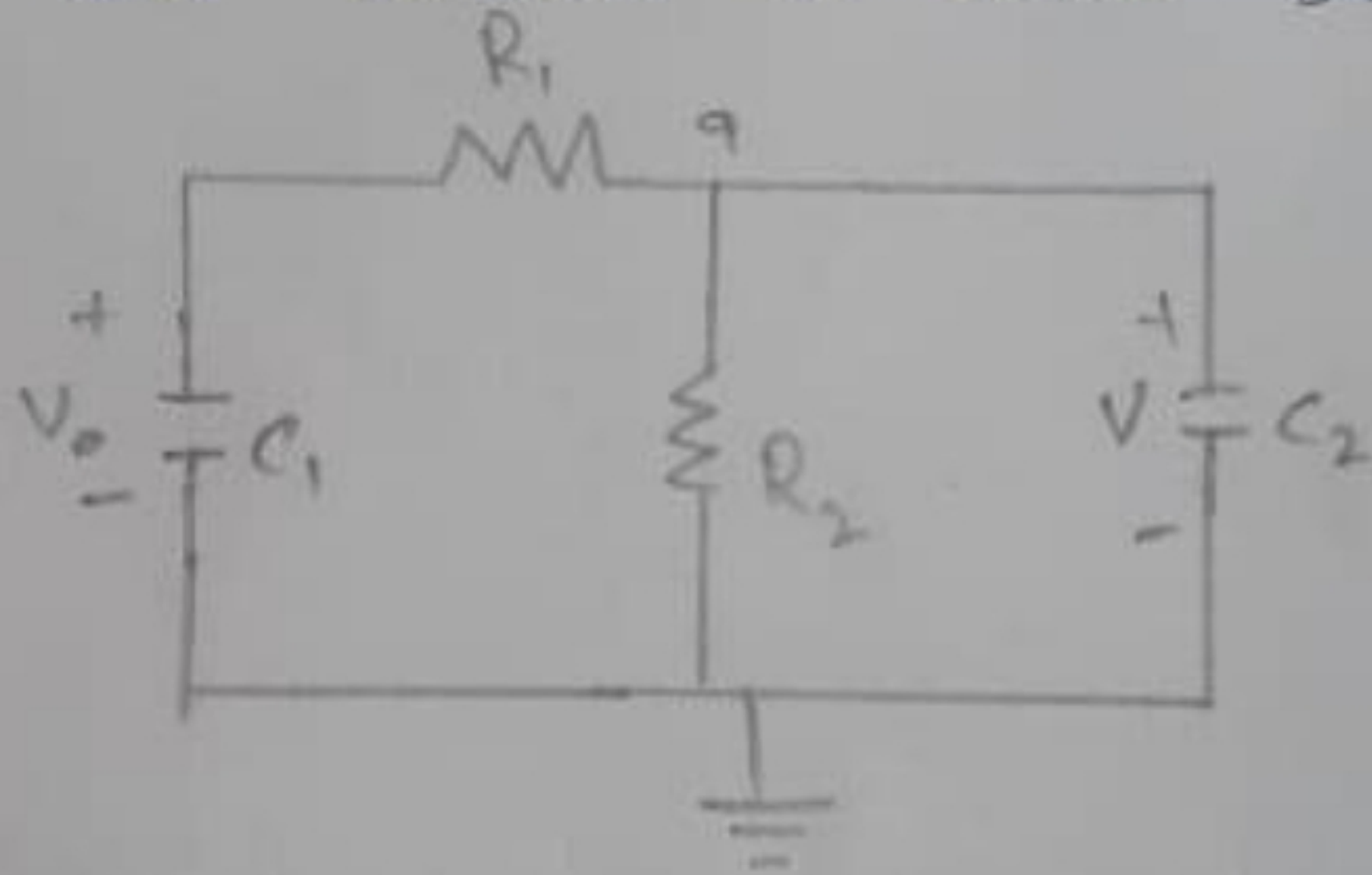

$$V_0 - V/R_1 = (V/R_2) + C_2 dv/dt$$

$$V_0 = V(1 + R_1/R_2) + R_1 C_2 dv/dt$$

$$60 = (1 + 5/2.5) + (5 \times 10^6 \times 5 \times 10^6) dv/dt$$

$$60 = 3V + 25 dv/dt$$

$$V(t) = V_s + [Ae^{-3t/25}]$$

1/where


$$3V_s = 60 \text{ yields } V_s = 20$$

$$V(0) = 0 = 20 + A \text{ or } A = -20$$

$$V(t) = 20(1 - e^{-3t/25}) \text{ V}$$

7

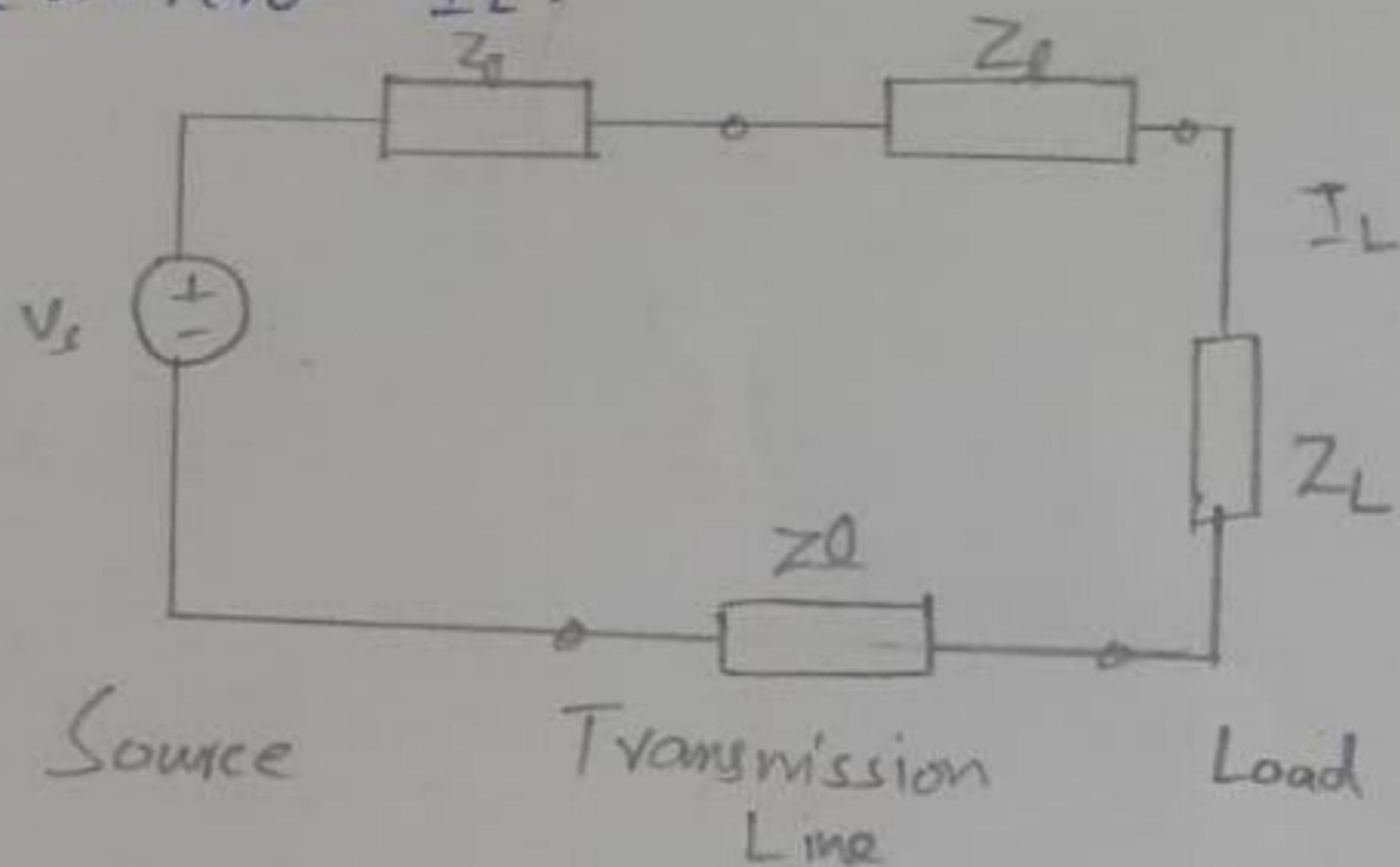A ^{Q5} power transmission system is modeled as shown. Find the load current I_L .



$$Z = Z_a + 2Z + Z_e$$

$$= (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9)$$

$$Z = 25 + j20$$

$$I_L = \frac{V_s}{Z} = \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ}$$

$$I_L = 3.592 \angle -38.66^\circ \text{ A}$$