

Haroon Rashid

Reg# 16549

Semester: 6th

Major Assignment: DLD Final Term

Submitted to: Sir Muhammad Amin



Q.10 Draw Circuit for adding or subtracting two 4 bits number

Control Input (M)
 For Adding we input 0 in Control Input

Adder

For Adding $M=0$ ($A+B$) add

 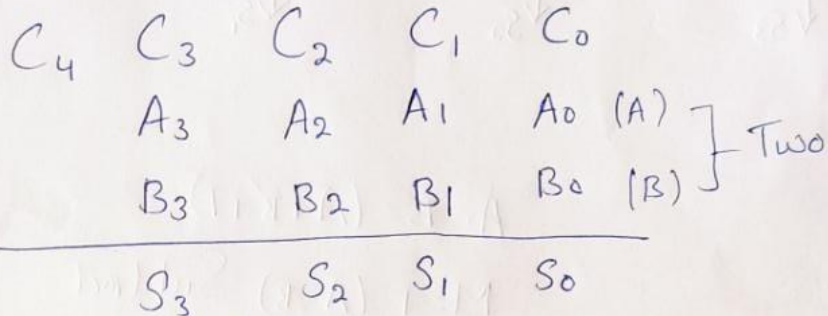$A \oplus 0 = B$
$A \oplus 1 = B'$
$A - B = (A+B')$




Initial Carry = 0 because for adder we input 0

Final Output is equal to C_4

For Subtractor input will be 1

$$A \oplus 0 = A$$

$$S_0 = M = 1$$

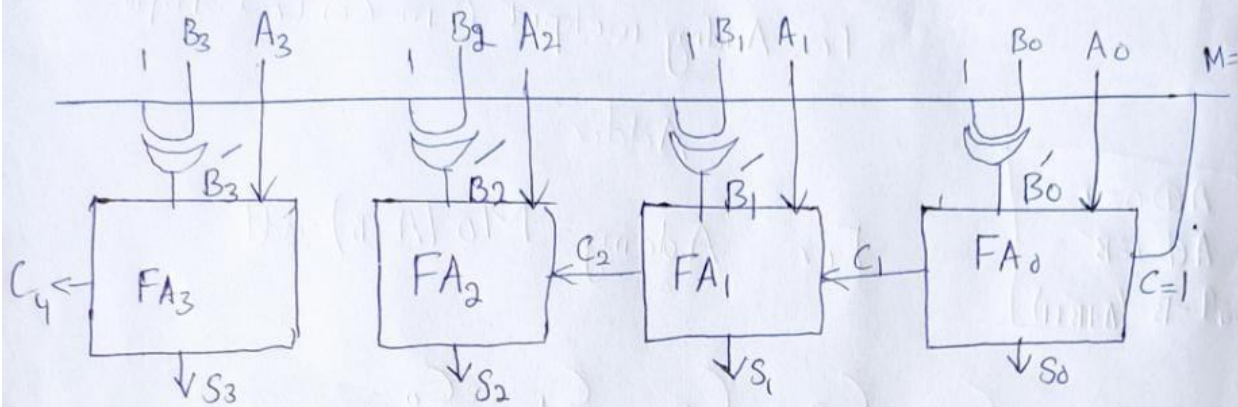

$$A - B = (A + B' + 1)$$

M=1 (A-B) Subtract

C ₄	C ₃	C ₂	C ₁	C ₀
	A ₃	A ₂	A ₁	A ₀
	B ₃	B ₂	B ₁	B ₀
	S ₃	S ₂	S ₁	S ₀


$$\begin{array}{r} \text{if we } 1001 (9) \\ - 0111 (7) \\ \hline 0010 (2) \end{array}$$

it will be subtractor if input is 1

b) Draw a circuit of 4-bit active low decoder


4-bit Decoder for Active low

Binary Inputs A_0, A_1, A_2, A_3

 


In an active-low output is required for each decoded number, the entire decoder can be implemented with NAND gates & inverters.

(b) Circuit of 4-bit active low

 

 
(c) Logic Diagram of ~~BCD~~ decimal to BCD encoder



Truth Table

Decimal Digit	BCD CODE			
	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

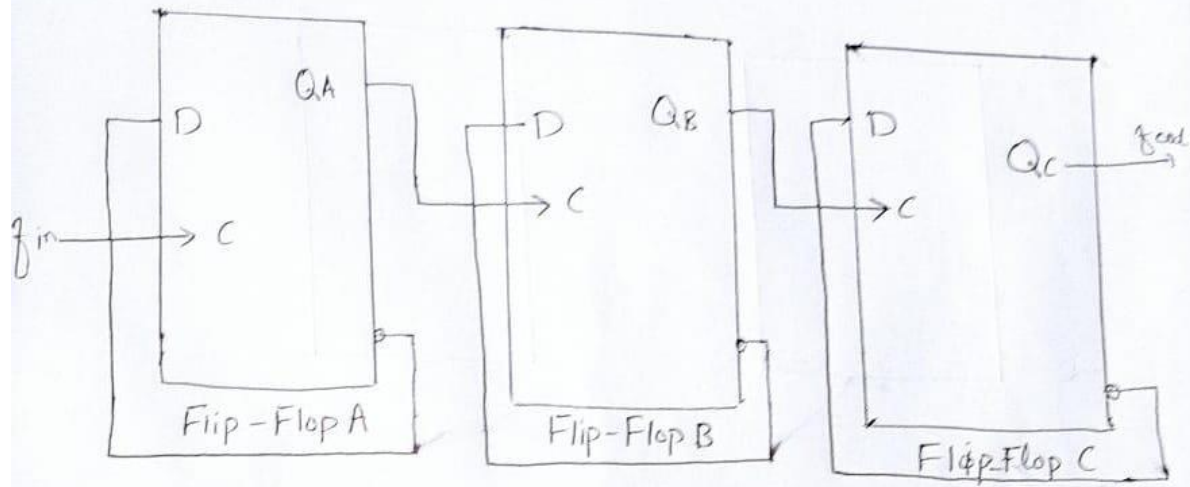(d) Frequency divider (Use 3-JK Flip Flop & assume 16 KHZ frequency of the initial wave form)



Q2: For the 4-Input multiplexer, data inputs are given as

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

Find the Output Y if the select inputs are given as


a) $S_0 = 1, S_1 = 0$

$$S_0 = 0, S_1 = 1$$

$$S_0 = 1, S_1 = 1$$

$$S_0 = 0, S_1 = 0$$

Answer:-

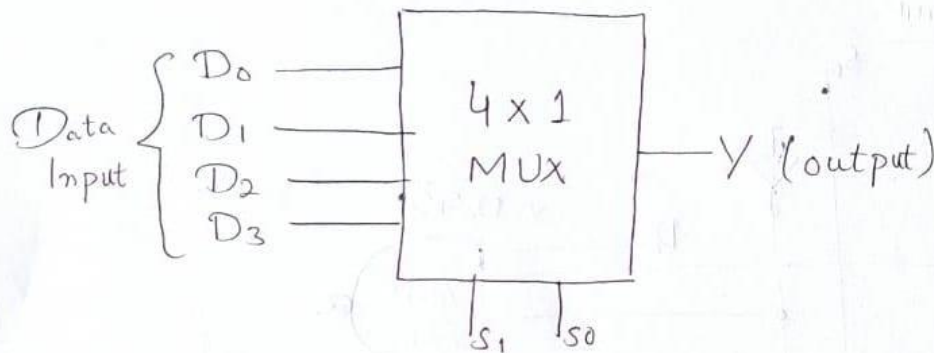

Find Select lines:-

$$n = 4$$

$$m = \log_2 n$$

$$m = \log_2 4$$

$$= \log_2 2^2 \quad \because \log_a a = 1$$


$$m = 2 \log_2 2 = 2 \cdot 1 = 2 \rightarrow \text{Select lines}$$

S_0	S_1	Data
1	0	D_0
0	1	D_1
1	1	D_2
0	0	D_3

Output (Y)


$$Y = D_0 S_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 S_0 + D_3 \bar{S}_1 \bar{S}_0$$

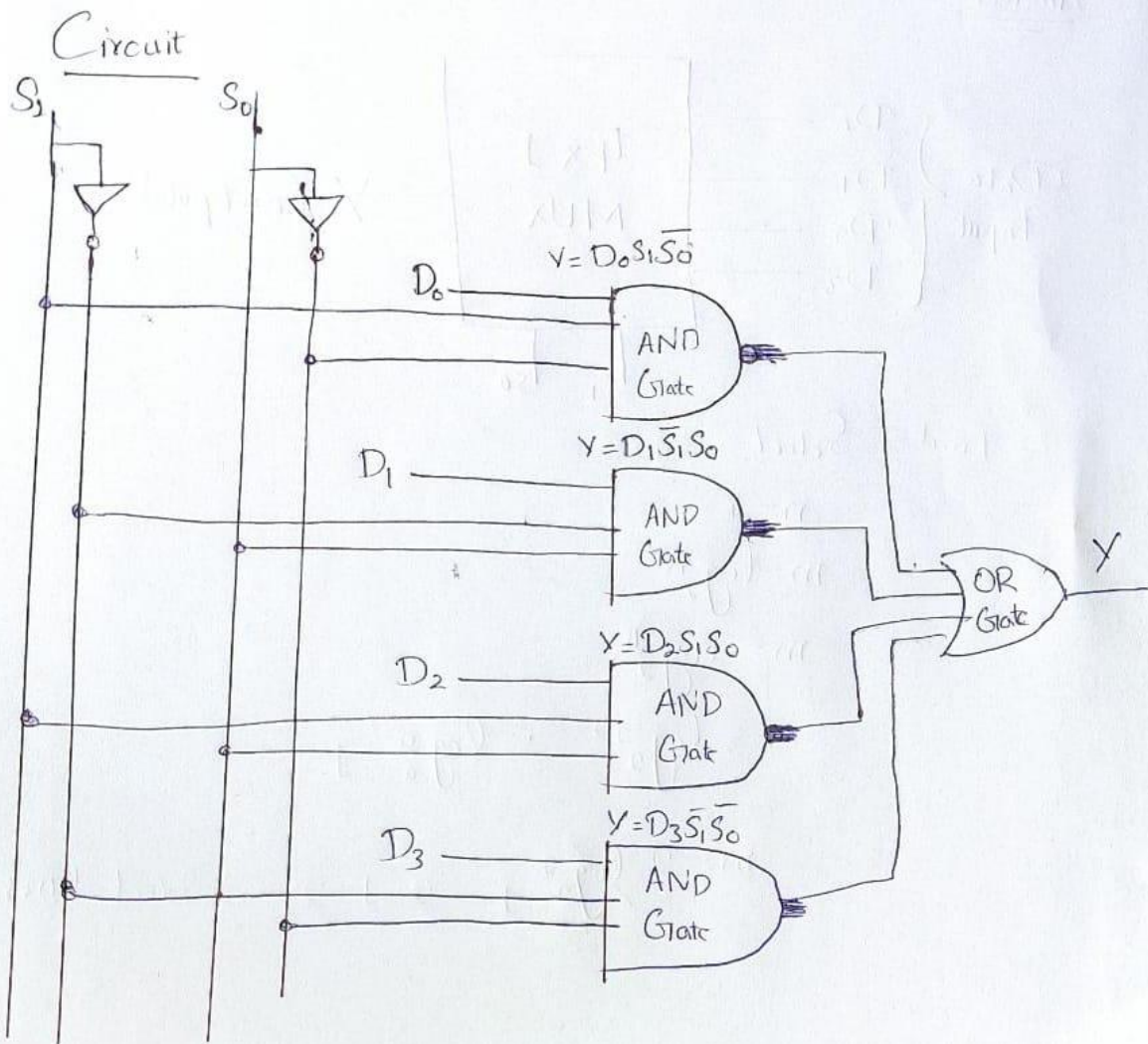Output = $Y = D_0 S_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 S_0 + D_3 \bar{S}_1 \bar{S}_0$



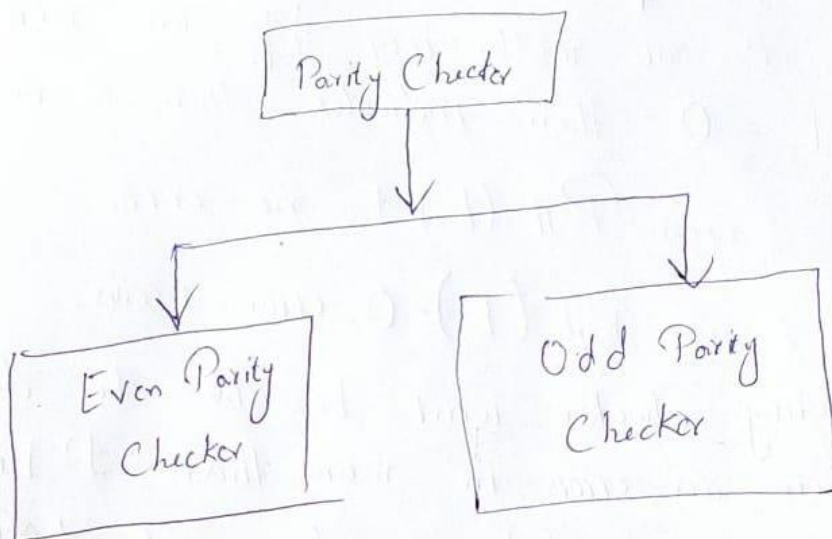Q3:- Timing diagram in Figure 01 Shows input to a 9-bit parity checker. Draw the Σ Even & Σ Odd output for the even parity checker

Answer- Parity Check: The combinational circuit at the receiver is the parity checker. This checker takes the received message including the parity bit as input. It gives output '1' if there is some error found & gives output '0' if no error is found in the message including the Parity bit.



Even Parity Checker:- In ^{even} Parity checker if the error bit (E) is equal to '1', then we have an error bit $E=0$ then indicates there is no error.

Error Bit (E) = 1, error occurs

Error Bit (E) = 0, no error

Odd Parity Checker:-

In odd parity checker if an error bit (E) is equal to '1', then it indicates there is no ~~matter~~ error. If an error bit $E=0$ then indicates there is an error

Error Bit (E) = 1, no error

Error Bit (E) = 0, error occurs.


The parity checker won't be able to detect if there are errors in more than '1' bit & the correct of data is also not possible, these are the main disadvantages of the parity checker.

The below table Shows the truth table for the even parity checker in which $PEC=1$ if the error occurs, i.e, if odd number of 1s
 $\& PEC=0$ if no error.

A	B	C	P	Parity error check C_p
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Q4- The waveforms in Figure 02 are applied to the $J, K, \overline{PRE},$ & \overline{CLR} inputs as indicated. Determine the Q output, if the flip-flop is initially Reset.


Answer:

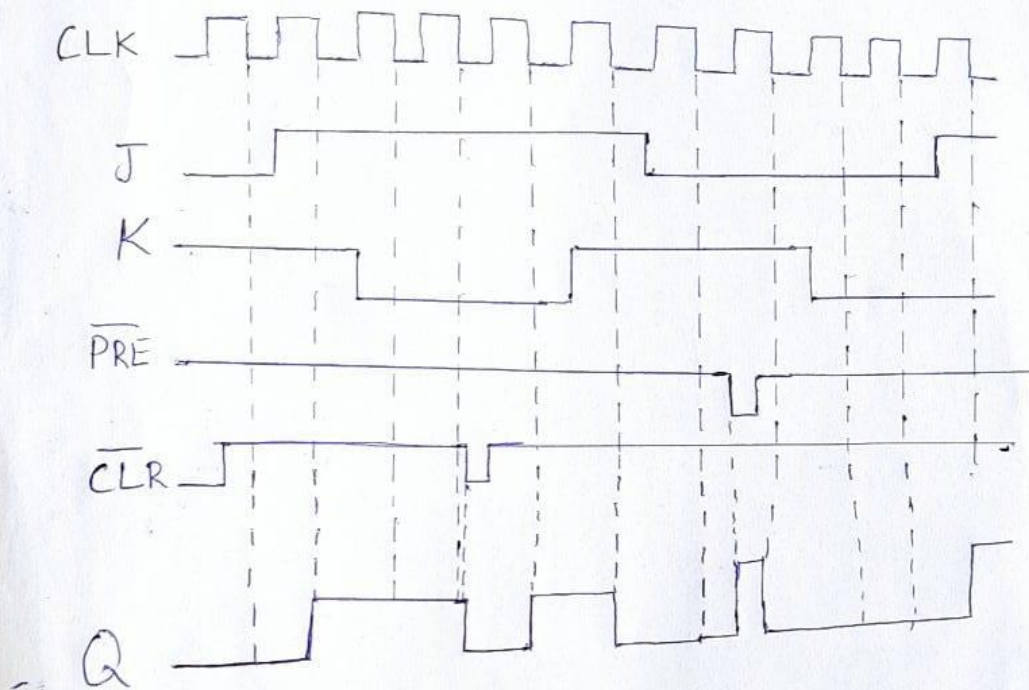

Q5: Use the waveforms in Figure 03 to draw the timing diagram for the parallel outputs (Q_1, Q_2, Q_3, Q_4) for the Shift register. Assume that register is initially cleared.


Ans: Diagram:-

is Below:-

 


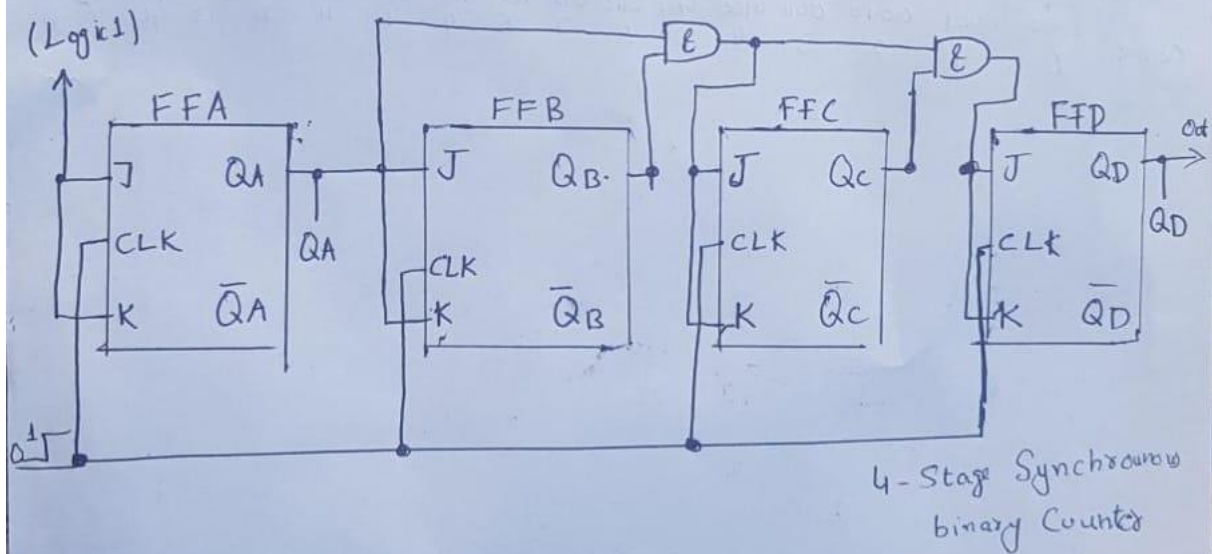Q6:- Draw the logic diagram & timing diagram for the 4-stage Synchronous binary Counter. Verify that the waveforms of the Q outputs represent the Proper binary number after each clock pulse.

Ans:- Logic Diagram of 4 Stage Synchronous



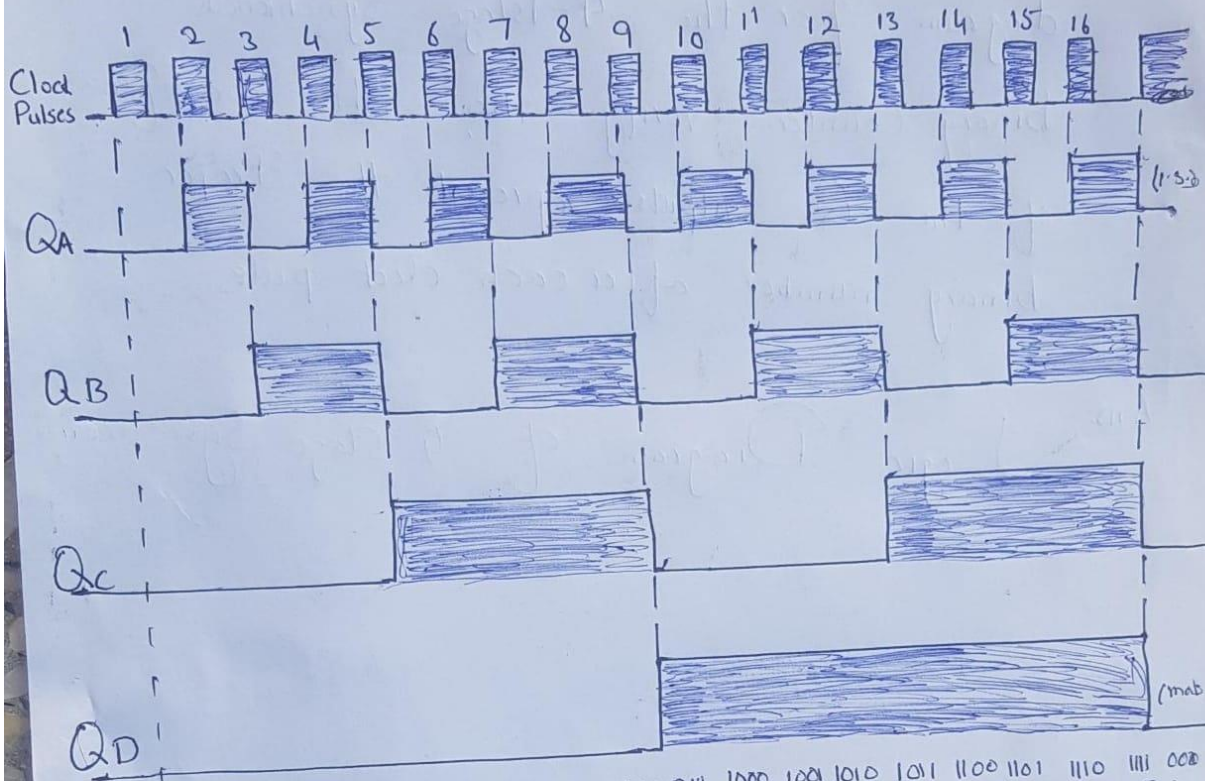4-Stage Synchronous Counter Waveform Timing Diagram



Count	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	0
	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111	000

