

NAME :

Daniyal Alam

I.D :

15385

Subject :

DKD


Final Exam Paper

Teachers :

Sir Amin


Q1: Draw and explain the logic diagram for each of the following:

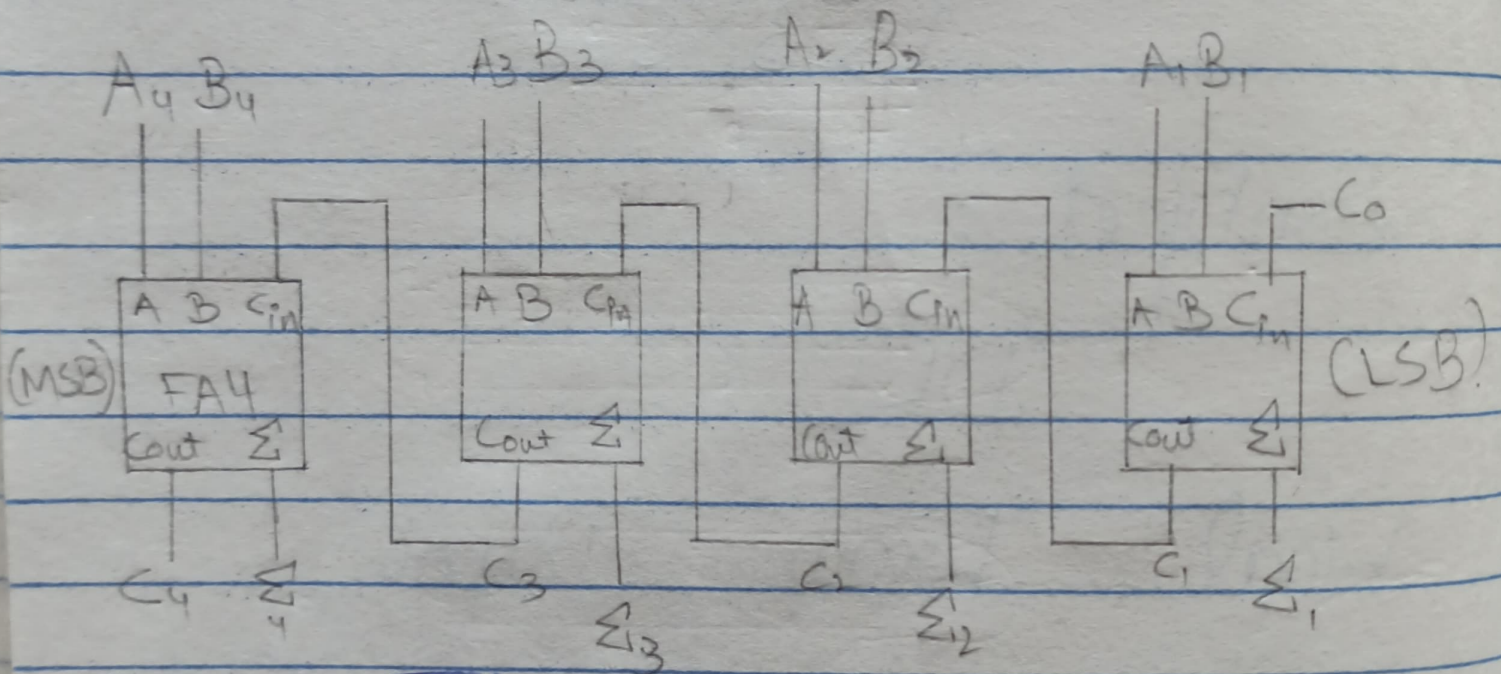a) A circuit for adding or subtracting two 4-bit numbers.




Explanation: Following diagram is the 4 bit parallel adder. 4 bits are entered and the result outcome is the sum of all the 4 bits.

Q1: part: D : 4 bit active low decoder.

 



The following diagram is a 4-bit decoder. Bits are decoded and output is given in $D_3 D_2 D_1 D_0$.

Q1: Part c: Decimal to BCD Encoder.

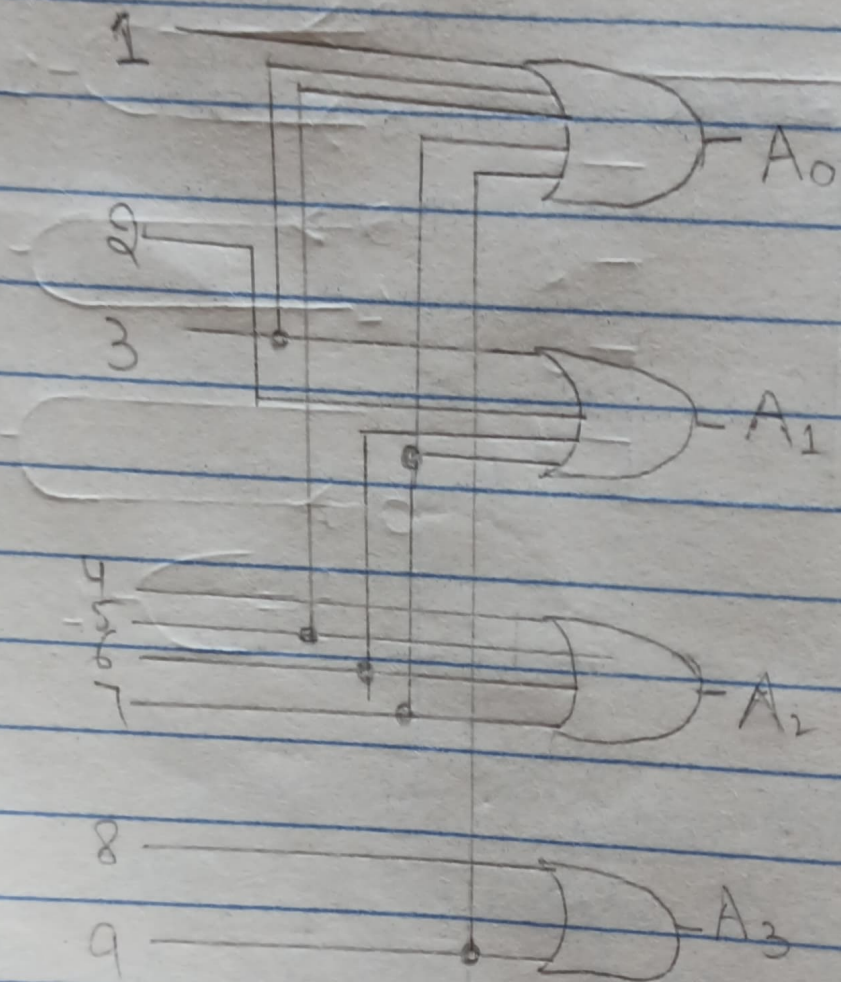

Explanation: The basic operation of the circuit is as follows. When a HIGH appears on one of the decimal digit input lines, the appropriate levels occur on the four BCD output lines.

Q: 1 : part : D :

 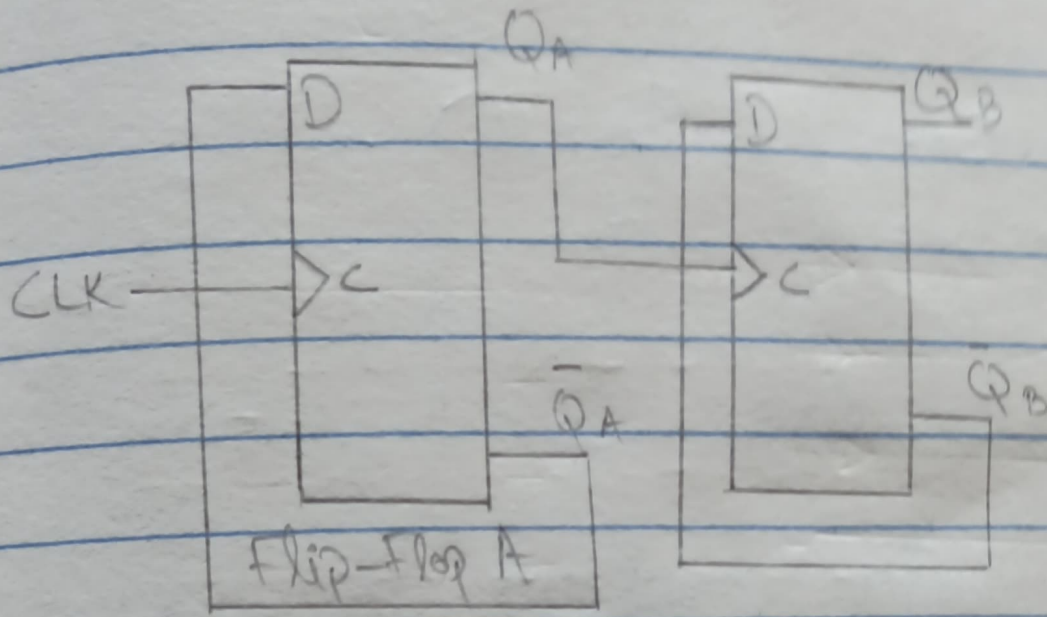

Explanation:

These two D-flip flops are used to divide the clock frequency by 4. Q_A is one-half the frequency and Q_B is one-fourth the frequency of CLK.

Q: 2 : Past : a :

a) $S_0 = 1, S_1 = 0$

b) $S_0 = 0, S_1 = 1$

c) $S_0 = 1, S_1 = 1$

d) $S_0 = 0, S_1 = 1$

\Rightarrow The data output is equal to D_0 only if $S_1 = 0$ and $S_0 = 0 : Y = D_0 \bar{S}_1 \bar{S}_0$

\Rightarrow The data output is equal to D_1 only if $S_1 = 0$ and $S_0 = 1 : Y = D_1 \bar{S}_1 S_0$

\Rightarrow The data output is equal to D_2 only if $S_1 = 1$ and $S_0 = 0 : Y = D_2 S_1 \bar{S}_0$

\Rightarrow The data output is equal to D_3 only if $S_1 = 1$ and $S_0 = 1 : Y = D_3 S_1 S_0$


The total expression for data output is:

$$Y = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$

The implementation of this equation requires four 3-input AND gates, a 4-input OR gate, and two inverters to generate the complements of S_1 and S_0 .


Q3:

ANSWER:-

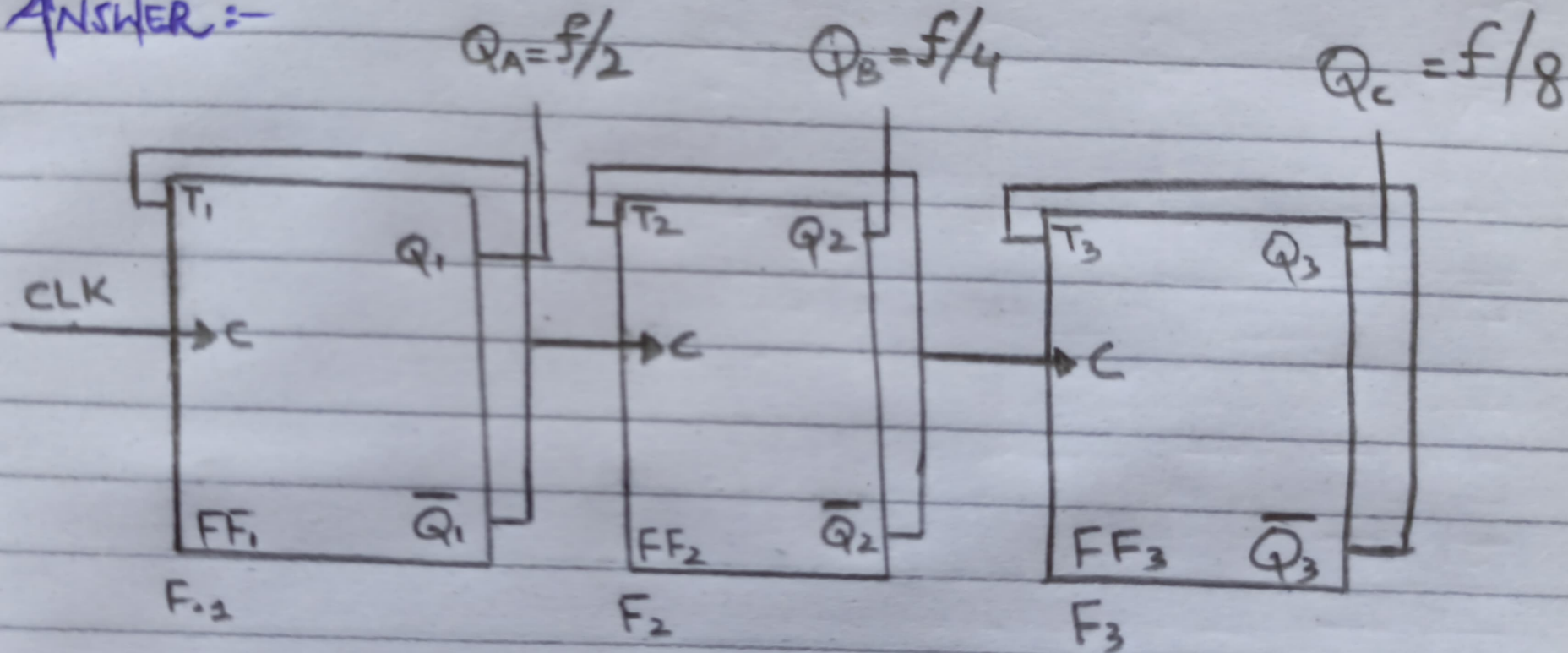

Q4:


Answer :-

 



The resulting 'Q' waveform is shown in the above figure. Each time a low is applied to the PRE or CLK, the flip flop is set or reset the Q regardless of the state of the other inputs.

Q5:


Answer:

 Data in 

 
clk 

 

Q1

 


Q2

 

Q3



Q4

 

Q:6:

ANSWER:-

CLK

