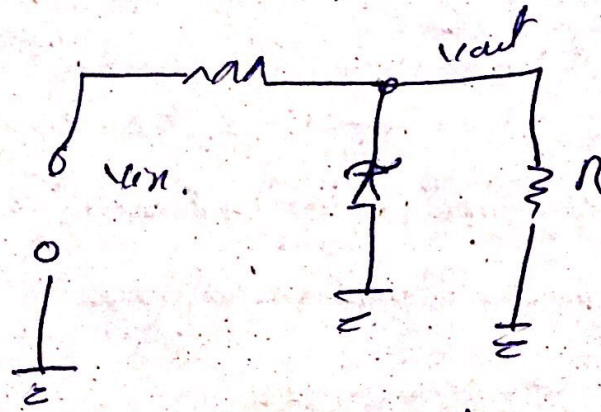




Name	Fawad Niaz
ID#	14568
Module	Summer
Subject	Electronic Devices and Circuits
Instructor	Dr.Shahyryar Shafiq
Department	BEE

Q No 1: Form Data sheet.



from the data sheet $I_{2R} = 0.25$

$$V_2 = 20 \quad I_2 = 12.5 \quad \& \quad Z_2 = 22$$

$$I_{2R} = 0.25$$

(a) = for I_{2R} :

$$\begin{aligned} V_{act} &= V_2 - \Delta I_2 I_2 \\ &= 20 - (I_2 - I_{2R}) Z_2 \\ &= 20 - (12.5 - 0.25)(22) \\ &= 20 - (0.9225)(22) \\ &= 20 - 0.2695 \\ &= 19.7305 \text{ V} \end{aligned}$$

calculating maximum

zener max current the power dissipation is

$$P_D (\text{max}) = \frac{I_{2m} V_2}{V_2} = \frac{110}{20} = 0.55$$

$$I_{2m} = 80 \text{ mA}$$

for I_{zm}

$$V_{out} = V_z + \Delta I_z Z_z$$

$$= 20V + (I_{zm} - I_z) Z_z$$

$$= 20V + (50mA - 12.5mA) 22\Omega$$

$$= 20V + (37.5mA) 22$$

$$= 20V + 0.825$$

$$V_{out} = 20.825V$$


(b) calculate the value of R for maximum zener current when there is no load as show in figure.

$$R = \frac{V_{in} - V_{out}}{I_{zm}}$$

$$= \frac{24V - 20.825V}{50mA}$$

$$R = 63.5\Omega$$

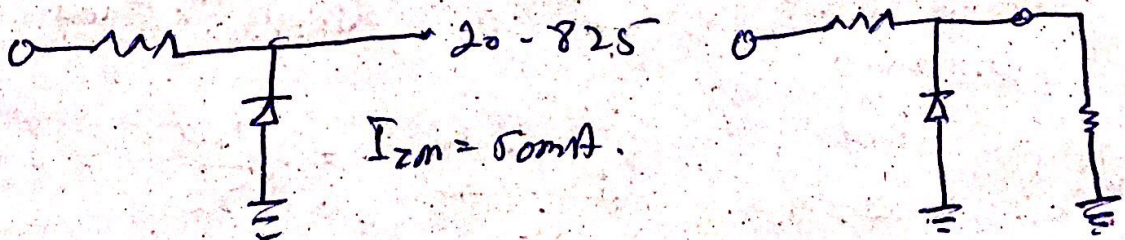$R = 70\Omega$ (Nearest largest standard)



(c) for maximum load Resistance
(maximum current) the zener diode current,
minimum ($I_{zk} = 0.25$)

$$I_T = \frac{V_{in} - V_{out}}{R}$$
$$= \frac{24V - 19.73V}{70V}$$

$$= 0.061A$$
$$= 61mA$$

$$I_T = 61mA$$

$$I_L = I_T - I_{zk}$$

$$= 61 - 0.25mA$$

$$I_L = 60.75mA$$

$$R_L = \frac{V_{out}}{I_L} = \frac{19.3}{60.75} = \frac{19.3}{60.75} mA$$

$$= \frac{19.3}{0.0671}$$

$$= 285.92 \Omega$$

$$R_L = 286 \Omega$$

Q no 2 :- Determine I_B , I_C , I_E , V_{BE} ---

Ans : $V_{BE} = 0.7 \text{ V}$

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{3.9 \text{ k}\Omega}$$

$$= 1102 \mu\text{A}$$

$$\Rightarrow I_C = \beta_{DC} \cdot I_B = (150)(1102 \mu\text{A}) = 165.3 \text{ mA}$$

$$\Rightarrow I_E = I_C + I_B = 165.3 \text{ mA} + 1102 \mu\text{A} = 166.4 \text{ mA}$$

so we find V_{CE} and V_{CB} .

$$V_{CE} = V_{CC} - I_C R_C = 15 \text{ V} - (165.3 \text{ mA})(180 \Omega)$$

$$= 15 \text{ V} - 29.7 \text{ V}$$

$$= -14.7 \text{ V}$$

$$V_{CB} = V_{CE} - V_{BE} \Rightarrow -14.7 \text{ V} - 0.7 \text{ V}$$

$$= -15.4 \text{ V}$$

since the collector is at a lower voltage than the base, the collector base junction is forward biased.

Q no 3:


Ans: For using BJT as an amplifier we need to set them in Active region because BJT working as an amplifier when use is active region.

Transistor has three basic configurations for using it in Amplifier mode.

Common Base voltage gain no current.

Common Emitter Both gain

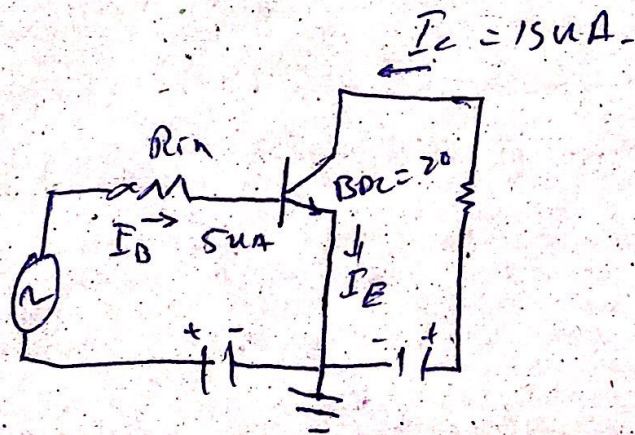Common collector current gain no voltage.



so This is common emitter configuration of transistor which has both voltage & current amplification.

$$I_C = \beta \cdot I_B$$

$$= 200 + 5 \mu A$$

$$I_C = 200 \cdot 0.0005 \mu A$$

$$I_E = I_C + I_B$$

$$I_E = 200 \cdot 0.0005 \mu A + 15 \mu A$$

$$I_E = 200 \cdot 0.0005 \mu A$$

Q No 4: For a transistor to act as a "switch" ---

Ans

ON conditions


- (i) Transistor fully on
- (ii) Maximum of saturation current I_c flows.
- (iii) BE Junction is forward bias.
- (iv) BC " " " forward bias.
- (v) $V_{CE} = 0V$

OFF conditions

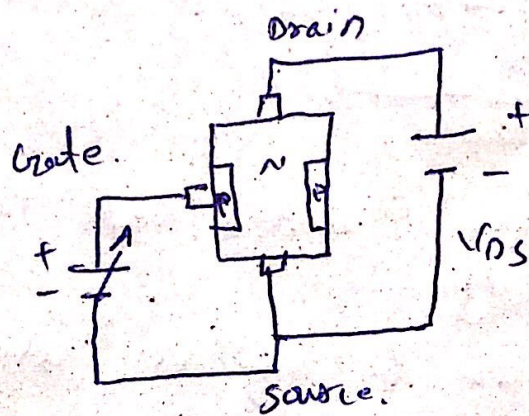
- (i) Transistor fully off.
- (ii) Input and base are at 0V
- (iii) collector current $I_c = 0$
- (iv) $V_{CE} = V_{CC}$
- (v) BE junction is reverse bias.
- (vi) BC " " " " bias.
- (vii) BE junction is less than 0.7V.

Q No 5 :-


Ans. JFET is a type of junction field effect transistor which is voltage controlled device as differ from BJT which is current controlled.



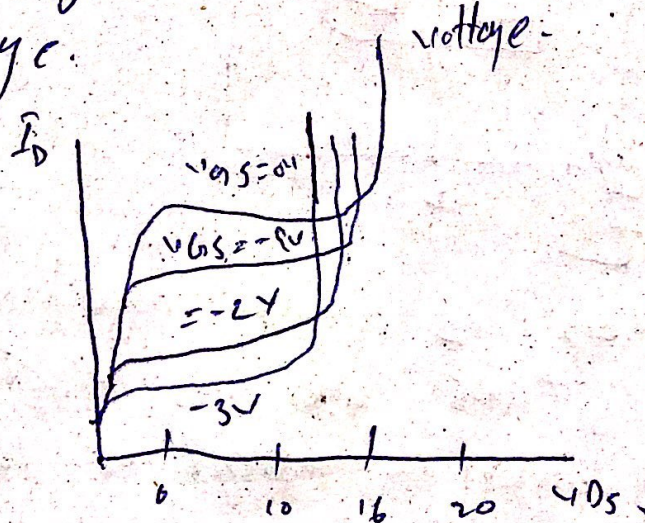
Actually in FET The drain to source current is controlled by the width of the channel the electric field is produced by the gate to source voltage.



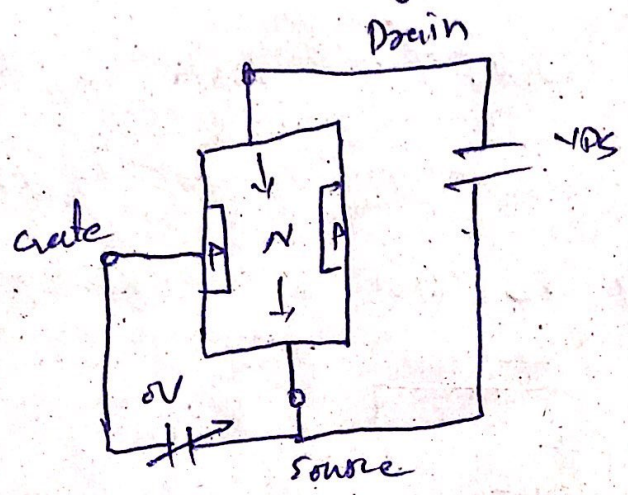so if we see to the graph which
 The no voltage applied to the gate the
 current flows freely.



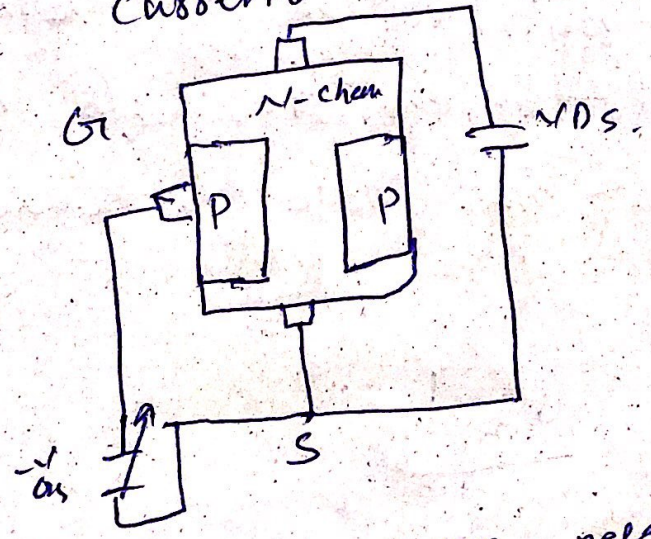
The channel are wider and Drain
 current moves freely.
 If we move V_{DS} to negative value the
 channel width start to decrease
 and current cannot move.



so V_{GS} is more negative so no
 current flows and this effect is called
 Pinch off region no current or less current
 flow.

Qno 6:-

①

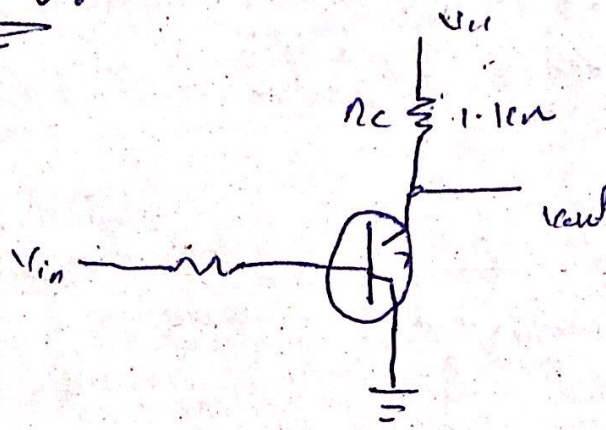

Given data:

$$P_{DC} = 125^-$$

$$V_{CE}(\text{sat}) = 0.4V$$

$$R_C = 1k\Omega$$

$$V_{CC} = 10V$$

Required:

$$V_{CE} = ? \quad I_B = ?$$

Sol:-

(a) $V_{CE} = ?$ $V_{in} = 0V$

when $V_{in} = 0V$, so transistor is in cut-off mode and

$$V_{CE} = V_{CC} = 10V$$

② $\min I_B = ?$ $P_{DC} = 125^-$ $V_{CE} = 0.4V$

$$I_C(\text{sat}) = \frac{V_{CC}}{R_C} = \frac{10V}{1k\Omega} = 10mA$$

