

**Department of Electrical Engineering**

**Sessional Assignment**

**Date: 04/05/2020**

**Course Details**

**Course Title:** Electronic Circuit Design

**Module:** 04

**Instructor:** Engineer Mujtaba Ehsan

**Total Marks:** 20


**Student Details**

**Name:** Asfandyar Awais

**Student ID:** 11461

Q1.	<p><b>Explain</b> the trans conductance curve for n-channel JFET given below</p>	Marks 04
		CLO 1
Q2.	<b>State</b> the characteristics of a practical operational amplifier.	Marks 04
		CLO 1
Q3.	<b>Calculate</b> output voltage for summing amplifier if $V_1 = 0.2V$ , $V_2 = 0.5V$ and $V_3 = 2V$ and $R_1=R_2=R_3=R_f = 6k\Omega$	Marks 05
		CLO 2
Q4.	(a) You are working on an audio circuit in the lab. Which class of power amplifier will you not consider for your work? <b>Justify</b> your answer with reason.	Marks 04
		CLO 2
	(b) <b>Outline</b> the differences between an amplifier and a rectifier.	Marks 03
		CLO 2

Q1 ANSWER:

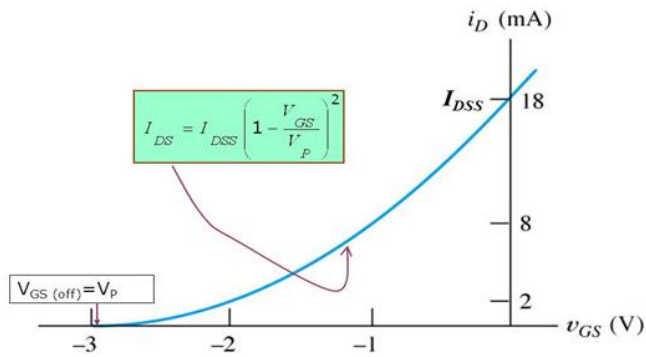

The relationship between the current  $I_D$  and  $V_{GS}$  is called transfer curve. This relation is non linear as it is evident from the graph. And mathematically the relationship can be explained by the equation shown in graph. In the equation  $I_{DSS}$  is the maximum value of the drain current where as  $V_P$  is the pinch-off voltage of this JFET. Whenever  $V_{GS}=0$  the value of drain current is maximum i.e.  $I_D=I_{DSS}$ . Similarly in the expression whenever we put  $V_{GS}=V_P$  at that time  $I_D$  will be 0. By putting these values we will get two extreme points of this curve. By the given expression we can find the value of  $I_D$  at different values of  $V_{GS}$  and  $V_D$ . If we put  $V_{GS}=-2$  V  $V_P=-3$  V and  $I_{DSS} = 18$  mA we will get  $I_D=2$  mA.

Similarly through this expression we can find the values of  $v_{GS}$  as well.

Q2 ANSWER:

Characteristics of practical operational amplifier:

- The open loop voltage gain is maximum and finite, a typical value for the practical op-amp is considered to be 200,000.
- The input impedance is maximum and is finite i.e. in the order of 100k or more.
- The output impedance is minimum, not zero, in the order of 100 or less.
- The CMRR is maximum and finite.
- Bandwidth is maximum and finite i.e. it can amplify dc to 1MHz signal.
- A slight drift of characteristics due to the change in temperature, not null.
- Two terminals may be virtually ground, not  $V_D=0$  exactly, for all conditions.
- Maximum slow rate and has the finite value.
- The output is negligible due to dc-bias when the input is zero

Q3 ANSWER:

DATA:

$$V1=0.2V$$

$$V2=0.5V$$

$$V3=2V$$

$$R1=R2=R3=Rf=6k \text{ ohms}$$

$$V_{out}=?$$

Solution:

$$V_{out}=-\left(\frac{R_f}{R}\right) \cdot (V1+V2+V3)$$

$$=-\left(\frac{6K}{6K}\right) \cdot (0.2+0.5+2)$$

$$=-2.7V.$$

#### **Q4(a) ANSWER:**

I would never consider a class C power amplifier for an audio circuit because class C amplifiers operate the output transistor in a state that results in tremendous distortion (it would be totally unsuitable for audio reproduction).

The class C amplifier is heavily biased so that the output current is zero for more than one half of an input sinusoidal signal cycle with the transistor idling at its cut-off point. In other words, the conduction angle for the transistor is significantly less than 180 degrees, and is generally around the 90 degrees area.

While this form of transistor biasing gives much improved efficiency of around 80% to the amplifier, it introduces a very heavy distortion of the output signal. Therefore, class C amplifiers are not suitable for use as audio amplifiers.

#### **Q4(b) ANSWER:**

**AMPLIFIER:** An amplifier is used to increase the amplitude of a signal waveform without changing other parameters of the waveform such as frequency or wave shape. They are one of the most commonly used circuits in electronics and perform a variety of functions in a great many electronics systems.

**RECTIFIER:** A rectifier is an electronic device that converts alternating current, which periodically reverses direction, to direct current, which flows in only one direction. The process is known as rectification, since it straightens the direction of current.

An amplifier is used to increase the strength of an electric signal whereas a rectifier allows current to pass in only one direction and is used to produce DC from AC.