

Department of Electrical Engineering

Midterm Exam

Date: 25/04/2020

Course Details

Course Title: Electronic Devices and Circuits

Module: _____

Instructor: _____

Total _____


Marks: 30

Student Details


Name: _____

Student ID: _____

Student Signature: _____

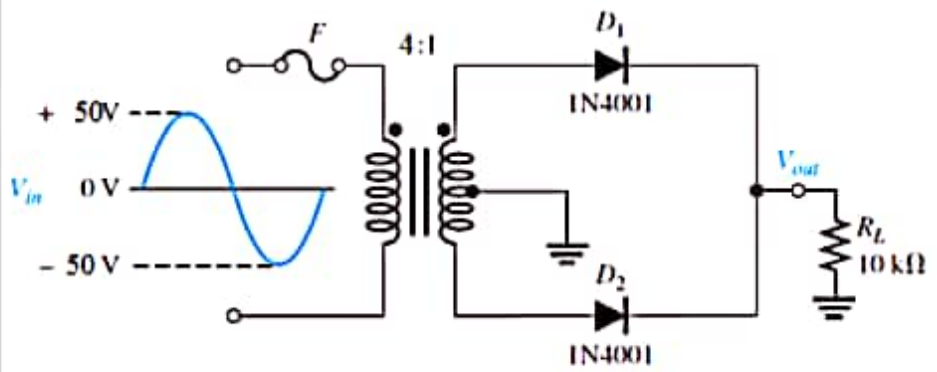Q1.	<p>For the circuit given in figure 1, answer and solve following problems.</p> <ol style="list-style-type: none"> What type of circuit is this? (1) What is the total peak secondary voltage? (1) Find the peak voltage across each half of the secondary. (1) What is the peak current through each diode? (2) What minimum PIV rating must the diodes have? (2)  <p align="center">Figure 1</p>	<p>Marks 07 CLO 02</p>
Q2.	<p>Determine the ripple factor for the filtered bridge rectifier with a load as indicated in Figure 2</p>	<p>Marks 05 CLO 02</p>

Yasir Ahmad 13788

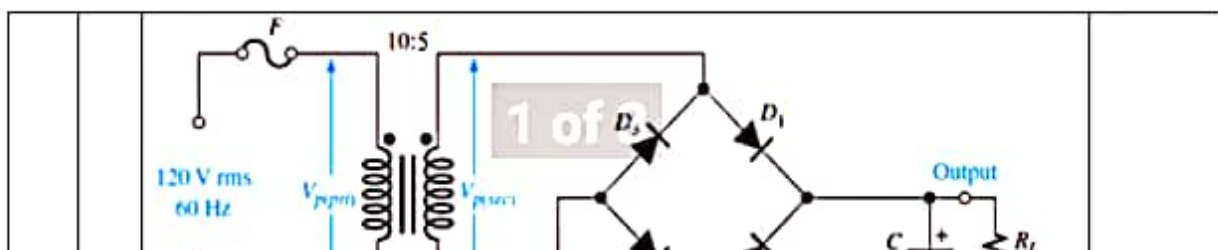

Q1



Ans) This is a Center Tapped Full wave rectifier circuit.


b) Total peak secondary voltage

$$V_p(\text{sec}) = n V_p(\text{pri}) = 0.25 (50) = 12.5 \text{ V}$$

$$V_p(\text{sec}) = 12.5 \text{ V}$$

c) Half of the secondary voltage.

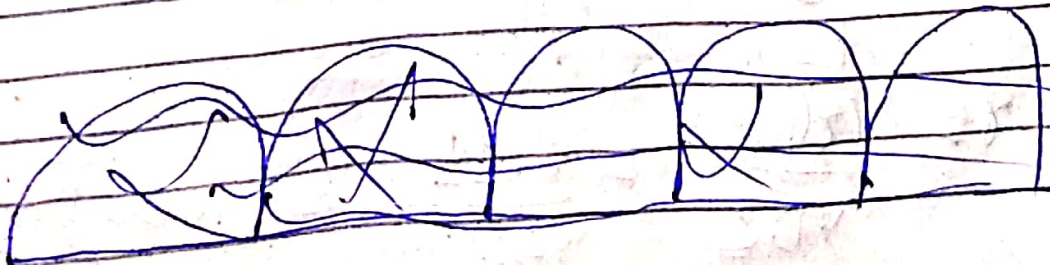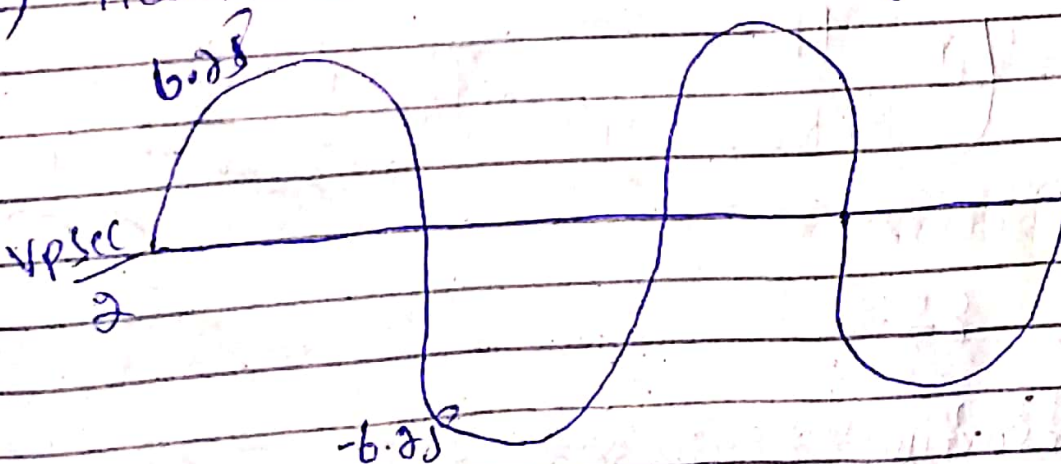

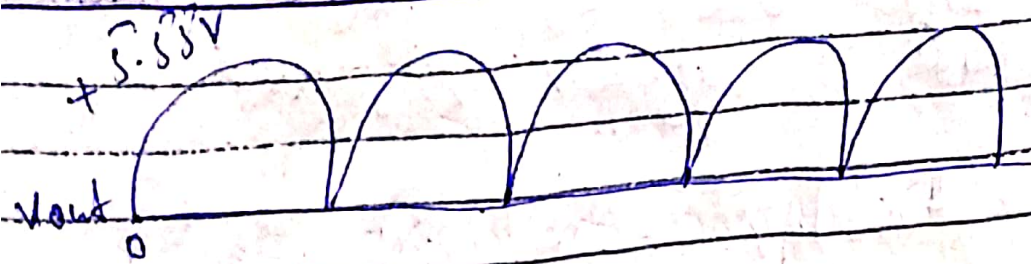

There is 6.25V peak to peak voltage
 the output voltage has a peak
 value of $6.25 - 0.7$ which is diode
 drop.

d) Peak Current through each Diode

$$I_F = \frac{V_p(\text{sec}) - 0.7}{R_L} = \frac{5.55}{10\text{k}\Omega} = 0.000555$$

$$= 0.555\text{mA}$$

e) PIV rating must diode here

$$\text{PIV} = 2V_p(\text{out}) + 0.7$$

$$= 2(5.55\text{V}) + 0.7$$

$$= 11.8\text{V}$$

Q2

sol Determine the ripple Factor

Transformer Turn ratio is $n=0.5$
Peak Primary voltage

$$V_p(Pri) =$$

$$V_{peak} = V_{RMS} \times \sqrt{2}$$

$$= 120 \times 1.414 = 170V$$

Ans The peak secondary voltage

$$V_p(sec) = (0.5)(170) = 85V$$

33.6) The unfiltered Full wave rectifier

voltage is

$$V_p(rect) = V_p(sec) - 1.4V =$$

$$85V - 1.4 = 83.6$$

The frequency of Full wave rectifier voltage is 120Hz

$$V_r(PP) = \left(\frac{1}{fR_2C} \right) V_p(\text{rect}) =$$

$$\left(\frac{1}{(120\text{Hz})(3300)(100\mu\text{F})} \right) 93.6$$

$$V_r(PP) = 2.111$$

The Approximately DC value of output voltage is determined as follows

$$V_{DC} = \left(1 - \frac{1}{2fR_2C} \right) V_p(\text{rect}) = \left(1 - \frac{1}{2(120)(3300)(100)} \right) 93.6$$


$$= 82.55$$

resulting ripple factor $\approx 2.62\%$



Percentage ripple

$$r = \frac{V_r(PP)}{V_{DC}} = \frac{2.11}{82.544} = 0.02556$$

Q3:-

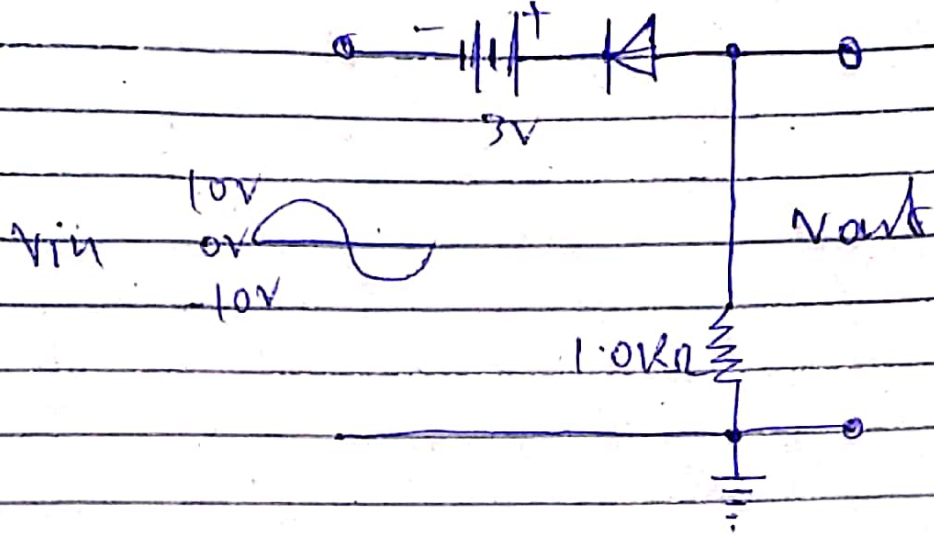

output waveform of clipper ckt.

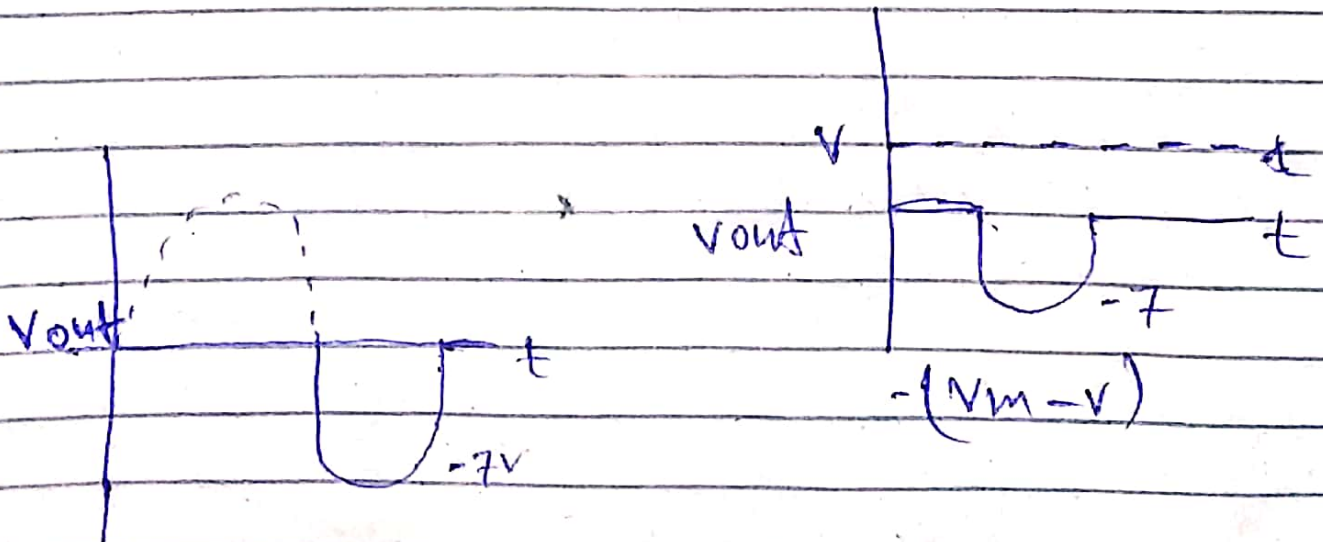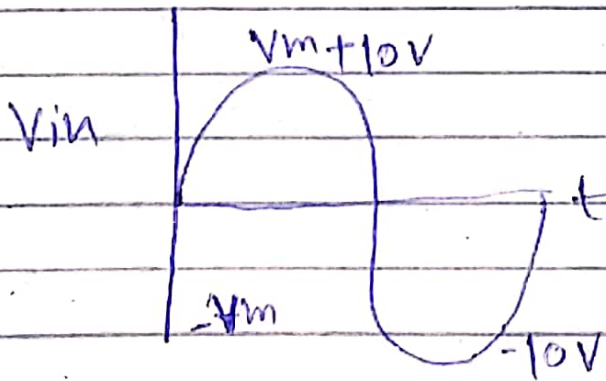

Yasir Ahmad
13788


Q1 Power Supply filter and its operation

power supplies capacitors are used to smooth filter the pulsating DC output after rectification so that a nearly constant DC voltage is supplied to the load.

filter ckt the capacitor is charged to the peak of the.

But here are certain disadvantages in using an unregulated power supply.


Circuit Diagram

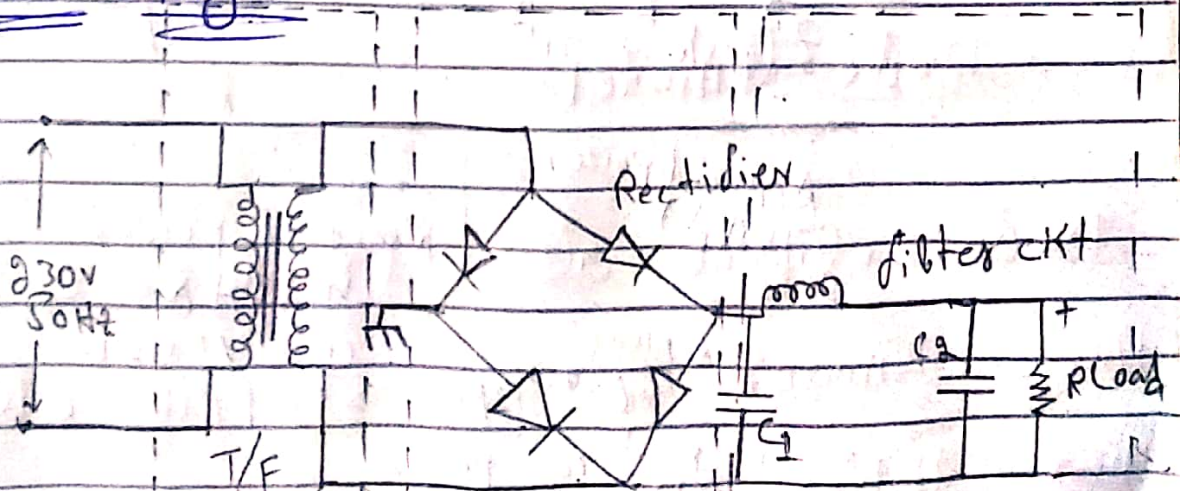

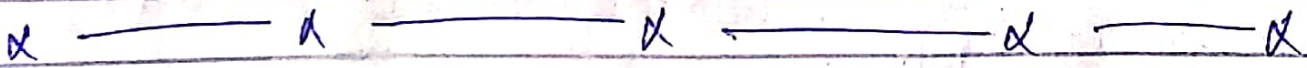Q8 b) n-Type and p-Type.

Doping of semiconductors pentavalent impurities impurity atoms with 5 valence electrons produce n-Type semiconductor by contributing extra electrons.

Trivalent impurities impurity atoms with 3 valence electrons produce p-Type semiconductor by producing a hole or electron deficiency.



Q8 Diode limiter.

Diode clipper also known as a Diode Limiter. a wave shaping ckt that takes an input waveform

and clips or cuts off its top half bottom or both halves together.

This clipping the input signal produces an output waveform.

that resembles a flattened version of the input.

Difference b/w positive and negative limiter

Series-negative limiter limits the negative portion of the input pulse.

The difference b/w a series-positive limiter is that the diode is reversed in the negative limiter.

in the parallel limiter the positive portion of the input signal is limited when the diode conducts.

(P3d)

Ans

Capacitor.

• V_{in} becomes negative the capacitor acts as a battery of the same voltage of V_{in} .

The voltage source and the capacitor counteract each other,

resulting in the net voltage of zero as seen by the load.

x — α — α — α — α —
(P3e)

Ans when a 60 Hz sinusoidal voltage is applied to the input of a half-wave rectifier the output frequency is 120 Hz. Sinusoidal voltage is twice that the half wave.

(C.S.F)

The voltage ripple is smoothed by using a capacitor it tries to hold the peak voltage across the load.

when the load is minimum then load resistance is high and draw a negligible current voltage across the load is approximately equal to source voltage ripple in voltage is depend on the load.

Also small change dv/dt due to ripple can not affect the load so much.

Q's g.

Ans

Diode limiter also called clipper as it used to limit the input voltage. A basic diode voltage limiter circuit is composed of a diode and resistor.

The clipping of input signal produces an input signal produces an output waveform that resembles version of input.

Diode clamping

A clamping Diode circuit is one consisting of a Diode capacitor and a resistor to limit the output voltage to a specified range.

The Diode is connected parallel to the load.