

Q. 1.

Part A.

Ans:

For two resistance.

$$R = \text{eq} = \frac{R_1 + R_2}{R_2 + 1}$$


For ~~(N)~~ number of Resistance

$$R = \text{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$

Q. 1.

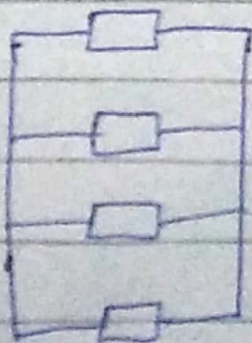Part B.

In a parallel circuit resistance decrease and conductance increase with the addition of more resistors.




Adding successive resistors in parallel.

R ↓ increase with more resistors.

G ↓ decrease with more resistor.



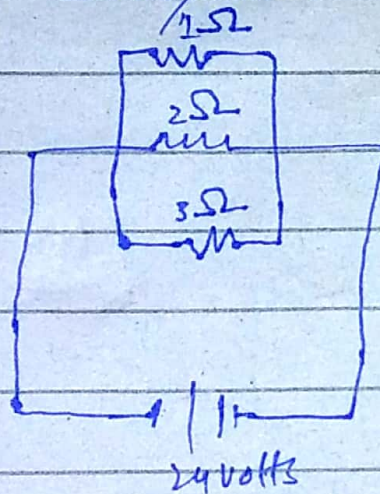Q.2. In the given circuit, Three resistors receive the same amount of voltage (24 volts) from single source. Calculate the amount of current "drawn" by each resistor, as well as the amount of power dissipated by each resistor.



Sol:

Given data:

voltage,  $V = 24$  volts.

Resistance,  $R_1 = 1 \Omega$

,  $R_2 = 2 \Omega$

$R_3 = 3 \Omega$

Required:

Current,  $I_1, I_2, I_3$

power,  $P_1, P_2, P_3$

Current:

By ohm's law.

$$I = \frac{V}{R}$$



For  $I_1$  :  $V = 24 \text{ volts}$ ,  $R_1 = 1 \Omega$

$$I_1 = \frac{V}{R_1} = \frac{24}{1}$$

$$I_1 = 24 \text{ A}$$

For  $I_2$  :  $V = 24 \text{ volts}$ ,  $R_2 = 2 \Omega$

$$I_2 = \frac{V}{R_2} = \frac{24}{2}$$

$$I_2 = 12 \text{ A}$$

For  $I_3$  :  $V = 24 \text{ volts}$ ,  $R_3 = 3 \Omega$

$$I_3 = \frac{V}{R_3} = \frac{24}{3}$$

$$I_3 = 8 \text{ A}$$

Power =  $P_1 = I \cdot V$

~~$V = 24 \text{ volts}$~~

$I = 24 \text{ A}$ ,  $V = 24 \text{ volts}$

$$P_1 = I \cdot V = 24 \cdot 24$$

$$P_1 = 576 \text{ watts}$$

$$P_2 = I_2 \cdot V$$

$$= 12 \cdot 24$$

$$P_2 = 288 \text{ watts}$$

$$P_3 = I_3 \cdot V$$

$$= 8 \cdot 24$$

$$P_3 = 192 \text{ watts}$$
 Ans



### Q.3 Differentiation b/w following:

#### 1) Current & voltage :-

##### Current

- 1) Current is the rate at which electric charge flows past a point in a circuit.
- 2) Current is the rate of flow of electric charge.

Its symbol is  $I$

unit is ampere (or) A  
Current cannot flow without voltage

$$1A = 1 \text{ coulomb/second}$$

##### voltage

- 1) voltage also called electromotive force, is the potential difference in charge b/w two points in an electrical field.
- 2) In other words, voltage is energy per unit charge.

Its symbol is  $V$

3) unit is voltage (or) volts  
4) Voltage can exist without current.

$$1V = 1 \text{ joule/coulomb}$$

#### 2) Energy

Energy is the capacity to do work. Energy is power integrated over time.  
unit is joules.

Symbol is  $w$

#### Power

1) Power is the rate at which work is done, (or) energy is transmitted.

2) unit is joules/second.

3) Symbol is  $P$ .



## b) Resistance & Conductance:

Resistor is a property of a conductor which tells us how much the resistor (or) opposes the current to pass through it.

Whereas conductance is a property of a conductor which tells us how much the resistor allow the current to pass through it.

The SI unit for electrical Resistance is  $\Omega$  Ohm ( $\Omega$ ).

The SI unit for electrical conductance is (S).

## c) Inductance & Capacitance:

Inductance is a property of a current carrying conductor which generates a magnetic field around the conductor whereas

Capacitance is a property of a device to hold and store electric charge. Inductance

is measured by Henry (H) and is symbolized as L.

Capacitance is measured in farads (F) and is symbolized as C.



E) Synchronous motor  
Construction is complicated.

Not self starting

Separate DC Source is required for rotor excitation

The speed is always synchronous irrespective of the load

Speed control is not possible.

Asynchronous motor

Construction is simpler, particular in case of cage rotor.

Self starting.

Rotor gets excited by the induced emf so separate source is not necessary.

The speed is always less than synchronous but never synchronous.

Speed control is possible through difficult.