

NAME

Asfand Yaq Safdar

ID

12982

Subject


Digital Logic design

Date

26-9-2020


Q1 Draw the logic circuit .....  
 ..... waveform Figure 01.

Answer:

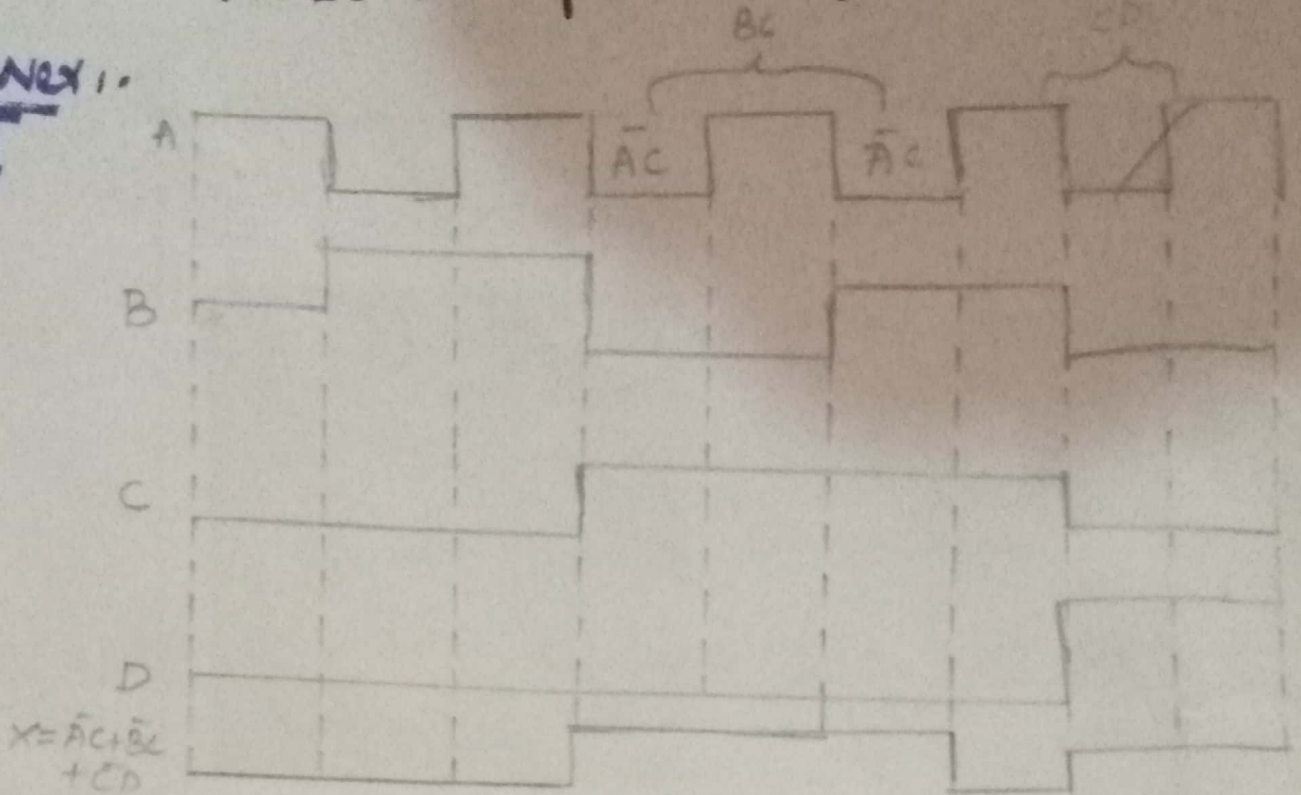

$$X = \bar{A}C + \bar{B}C + \bar{C}D$$

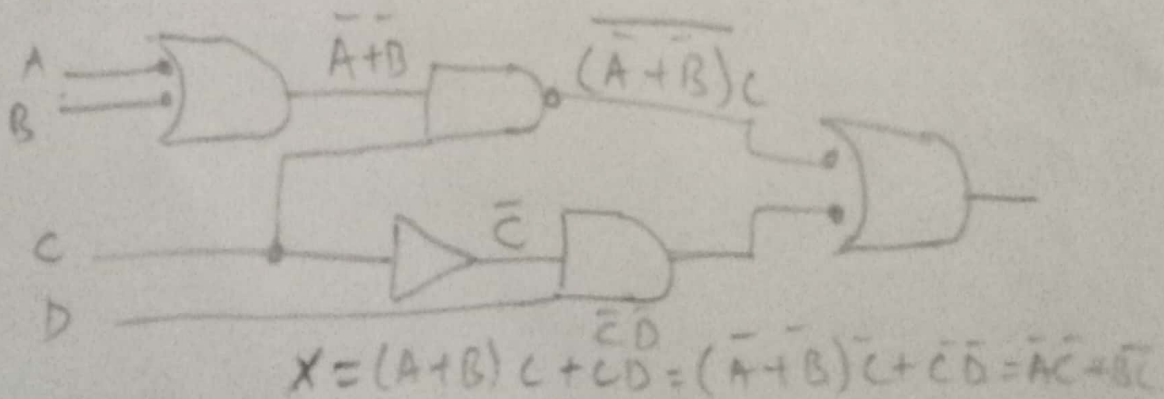Solution: The output expression for the circuit is developed in SOP form. The SOP form indicates that the output is high when A is low and C is HIGH or when B is low and C is HIGH or when C is low and D is HIGH.



Q → Q2 For the 4-input multiplexer data input are given -

Ans:- A 4x1 Multiplexer has 4 input lines ( $D_0, D_1, D_2, D_3$ ) two select input ( $S_0$  and  $S_1$ ) and one output line  $Y$ .

If  $S_1 S_0 = 00$  then  $Y = D_0$

If  $S_1 S_0 = 01$  then  $Y = D_1$


If  $S_1 S_0 = 10$  then  $Y = D_2$

If  $S_1 S_0 = 11$  then  $Y = D_3$

Data Input		output.
$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$




Question No → 05

 

The answer is 1001

 Question No  $\Rightarrow$  04 :- Determine  $A = B$ ,  $A > B$  and  $A < B$  output for the input number show on the comparator in Figure 03 :-

Ans - Determine the  $A = B$ ,  $A > B$ ,  $A < B$  outputs for the input numbers show on comparator in Figure.



Solution The number on the A inputs is 0110 and the number on the B inputs is 0011. The ~~input~~ output is HIGH and the other outputs are low.




Question No  $\Rightarrow$  05:- Show the logic required to convert code word to binary 1011:-

Solution:-

- ① The MSB is kept the same
- ② Next take the XOR of the first and the second binary bit
- ③ Next take the XOR of the second and third binary bit.
- ④ Next take the XOR of
- ⑤ Lastly take the XOR of the fourth and fifth binary bit.

 Gray code of binary conversion:-  
 $g(3) \ g(2) \ g(1) \ g(0)$




$B(3) \ (B_2) \ (B_1) \ (B_0)$

$$b(3) = g(3)$$

$$b(2) = b(3) \oplus g(2)$$


$$b(1) = b(2) \oplus g(1)$$

$$b(0) = b(1) \oplus g(0)$$

 



Question No  $\Rightarrow$  06 - Draw and explain logic diagram for 4 bit active low decoder?

Solve:-

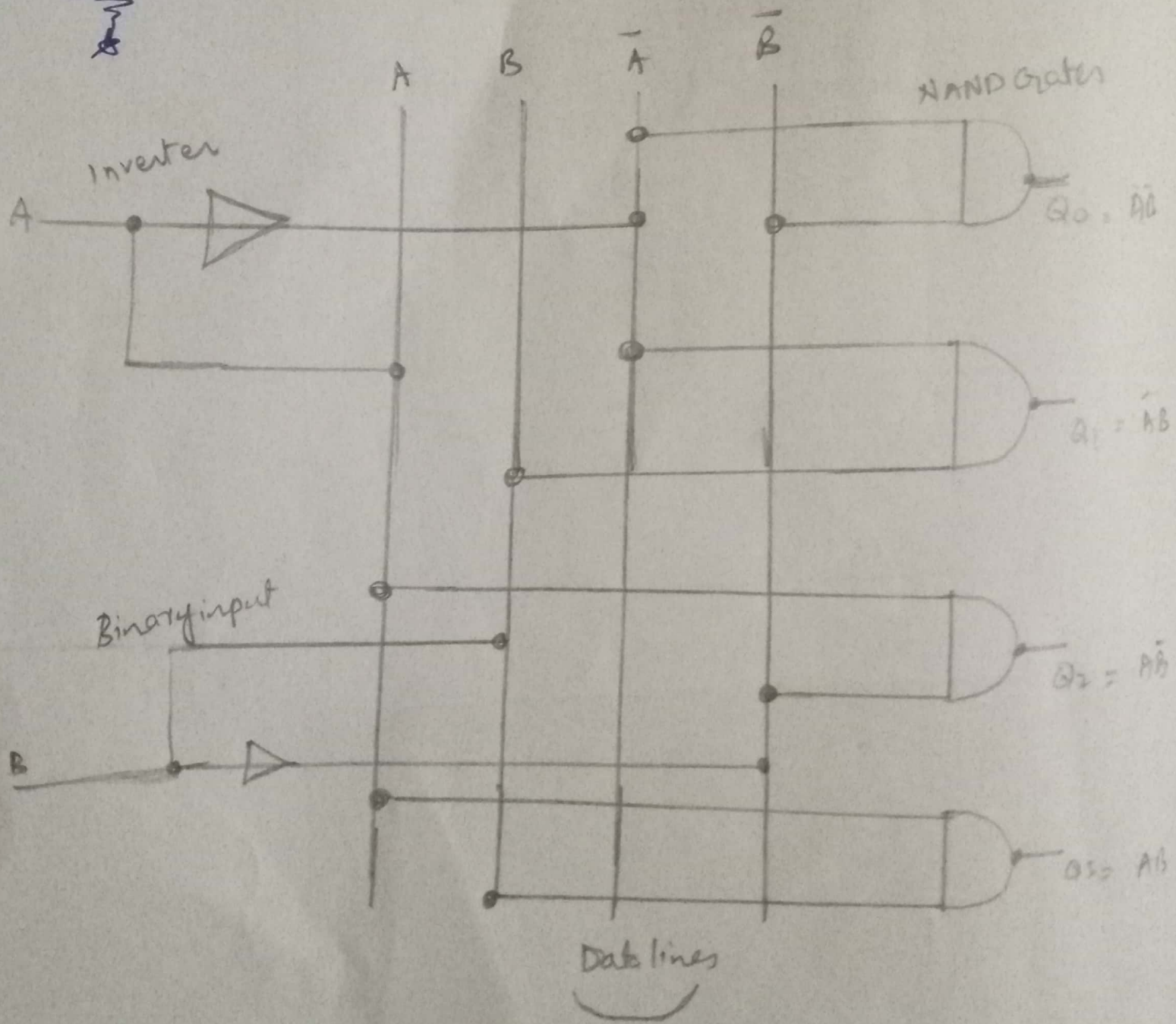



# Question 07

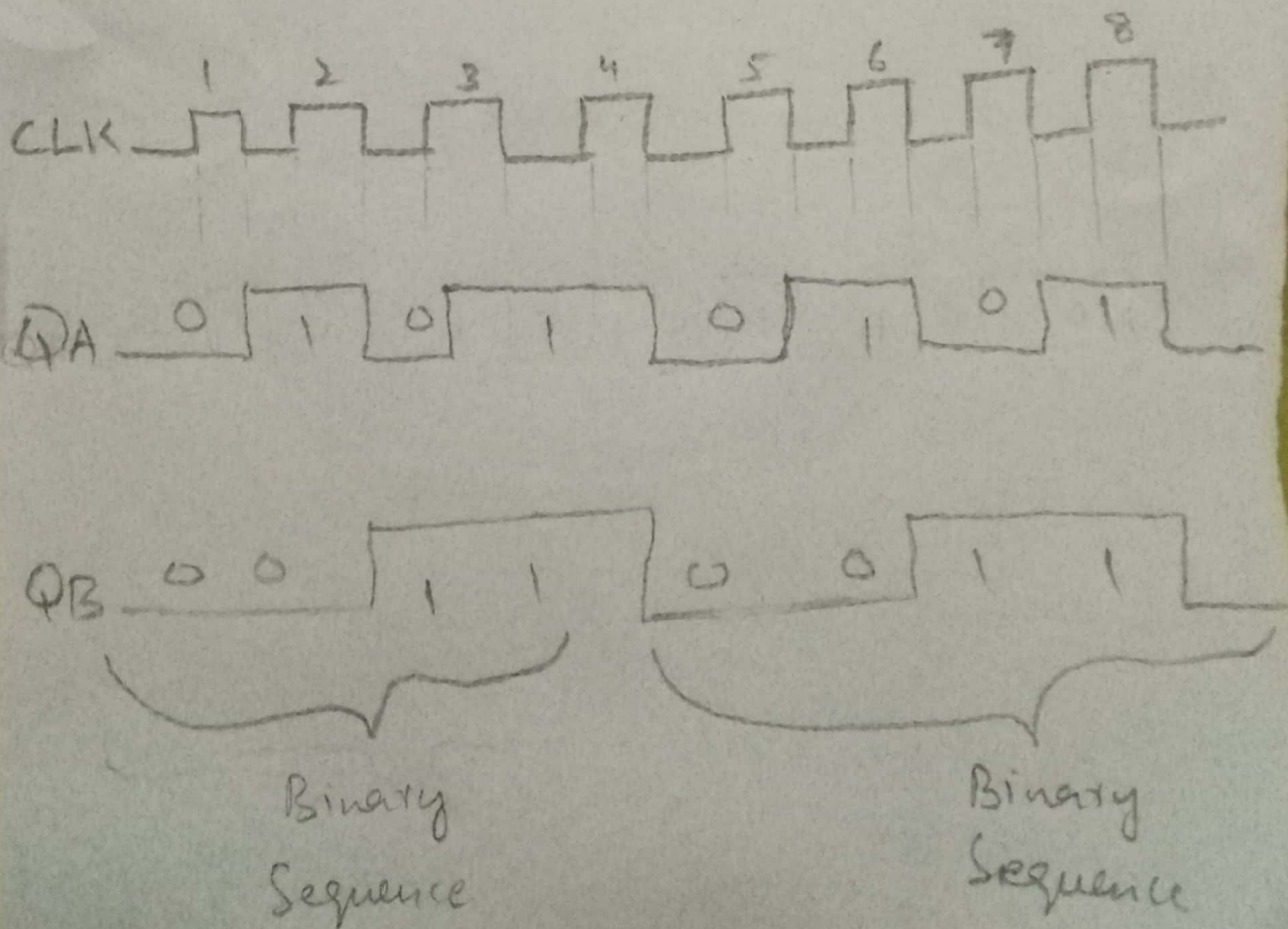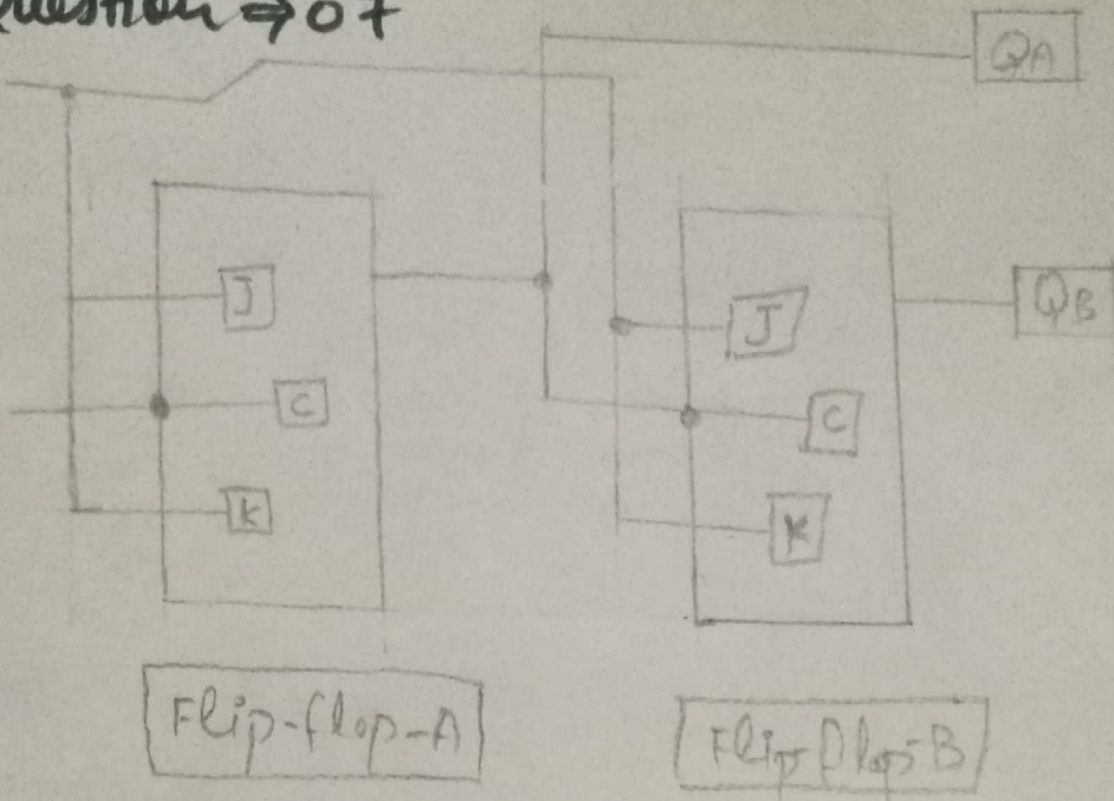





Question No  $\Rightarrow$  08:- Determine the Q waveform relative to the clock of the sigle  $\text{---}$   
 $\text{---}$  Q is initially low.

Solve


CLK

 


J

 


K

 


PRE

 


Q

 

CLR

 

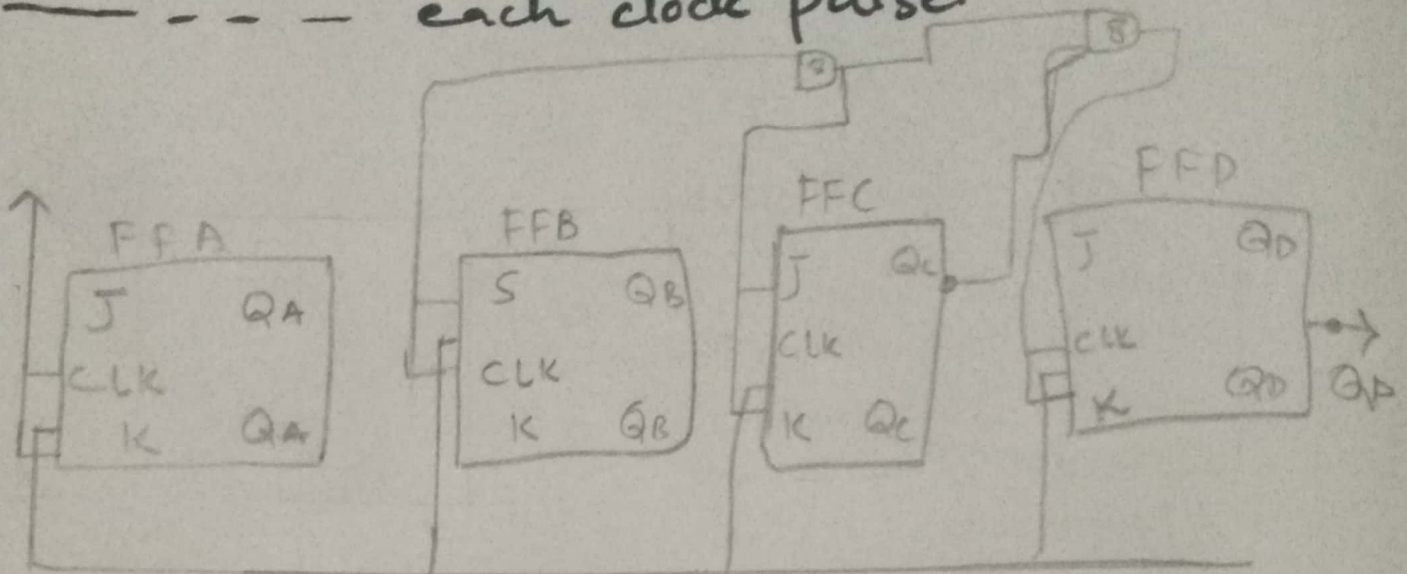Question No → 09 Draw the logic diagram and timing diagram for 4-stage synchronous  
 ----- each clock pulse.



It can be seen above that the external clock pulse are feed directly to each of the J-K flipflops in the clock chain both the J and K inputs J-K inputs of flip-flop (FFB) are connected to output QA of (FFA) but J-K input of (FFC) and (FFD) are driven from separate AND gates which also supplies with signals from input and output of the previous stage.