

Name

Amad

Afridi

ID

13119

Class

BS - SE - B

Subject

DLD


8th

Semester

26-9-2020

Q1. Draw the logic circuit using input (A, B, C, D) and the output (X) waveform is Figure 01-


Ans:-

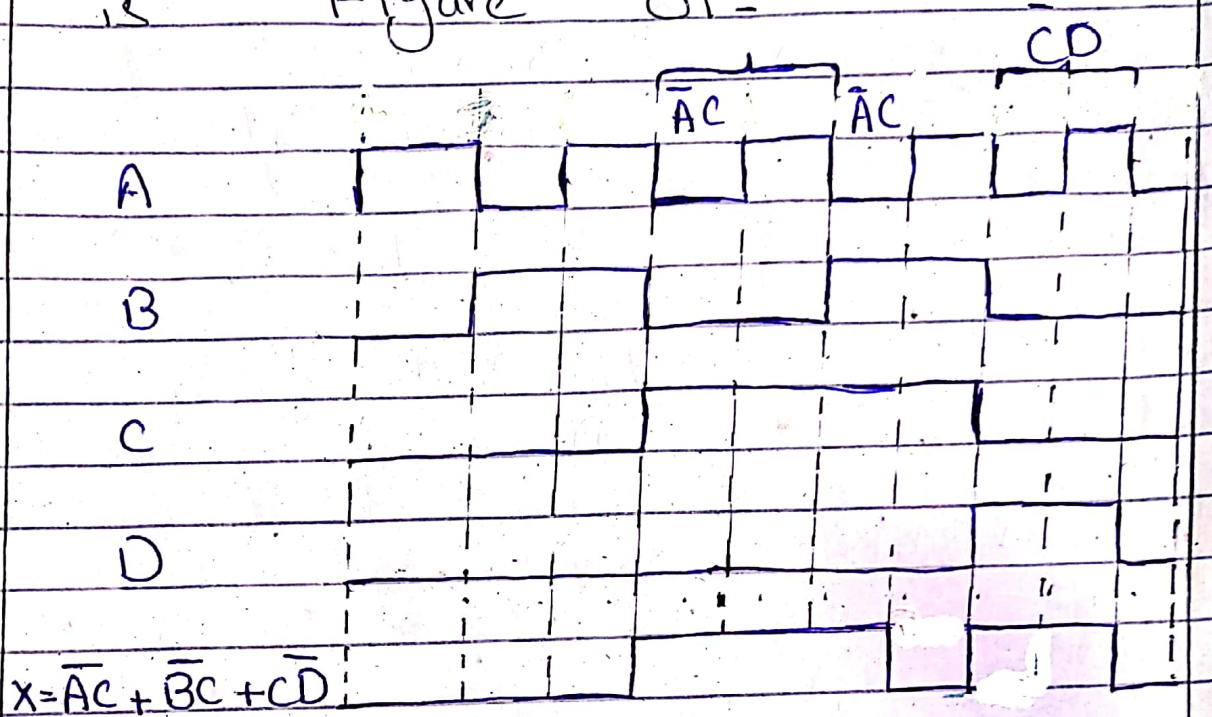

$$X = \bar{A}C + \bar{B}C + \bar{C}D$$

Sol:-

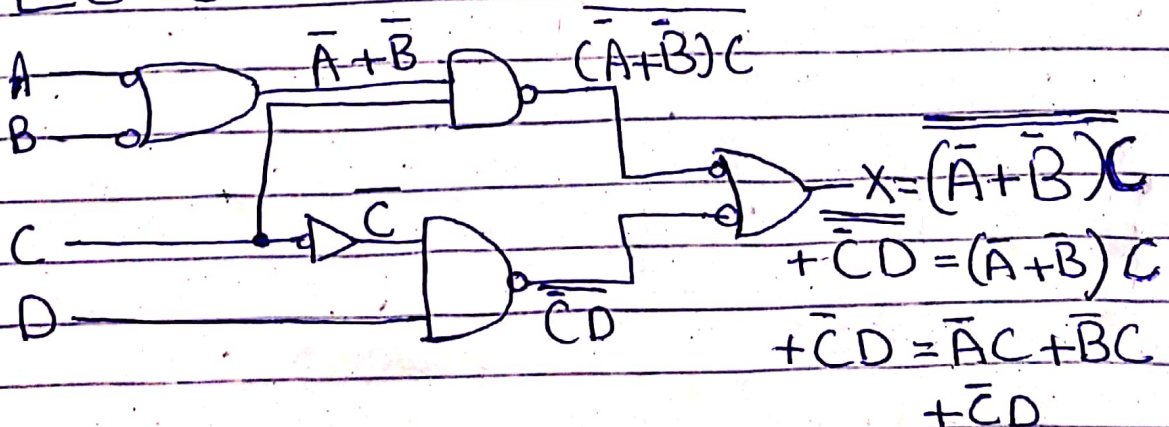The output expression for the circuit is develop in SOP form indicates that output is HIGH when A is LOW and C is HIGH or when B is LOW and C is HIGH or when C is LOW and D is HIGH.



Q2. For the 4-input multiplexer data input are given as,
 $D_0 = 0$, $D_1 = 1$, $D_2 = 0$, $D_3 = 1$

2
 Anki

Data select inputs	input selected
S_1	S_0
0	1
1	0
1	1
0	0

look at logical circuit required to perform this multiplexing operation. The data output is equal to the state of selected data input. You can therefore, derive a logic expression for output in terms of data input and the select inputs.

⇒ The data output is equal to D_0 only if $S_1 = 0$ and $S_0 = 1$: $Y = D_0 \bar{S}_1 \bar{S}_0$

⇒ The data output is equal to D_1 only if $S_1 = 1$ and $S_0 = 0$: $Y = D_1 \bar{S}_1 S_0$

⇒ The data output is equal to D_2 only if $S_1 = 1$ and $S_0 = 1$: $Y = D_2 S_1 \bar{S}_0$


⇒ The data output is equal to D_3 only if $S_1 = 0$ and $S_0 = 0$: $Y = D_3 S_1 S_0$

When these terms are ORed, the total expression for data output is

$$Y = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$

Q3. For the circuit in figure 02 assume the inputs are Add/subt = 1, $A = 1010$ and $B = 1101$ what is output?

3
Ansi

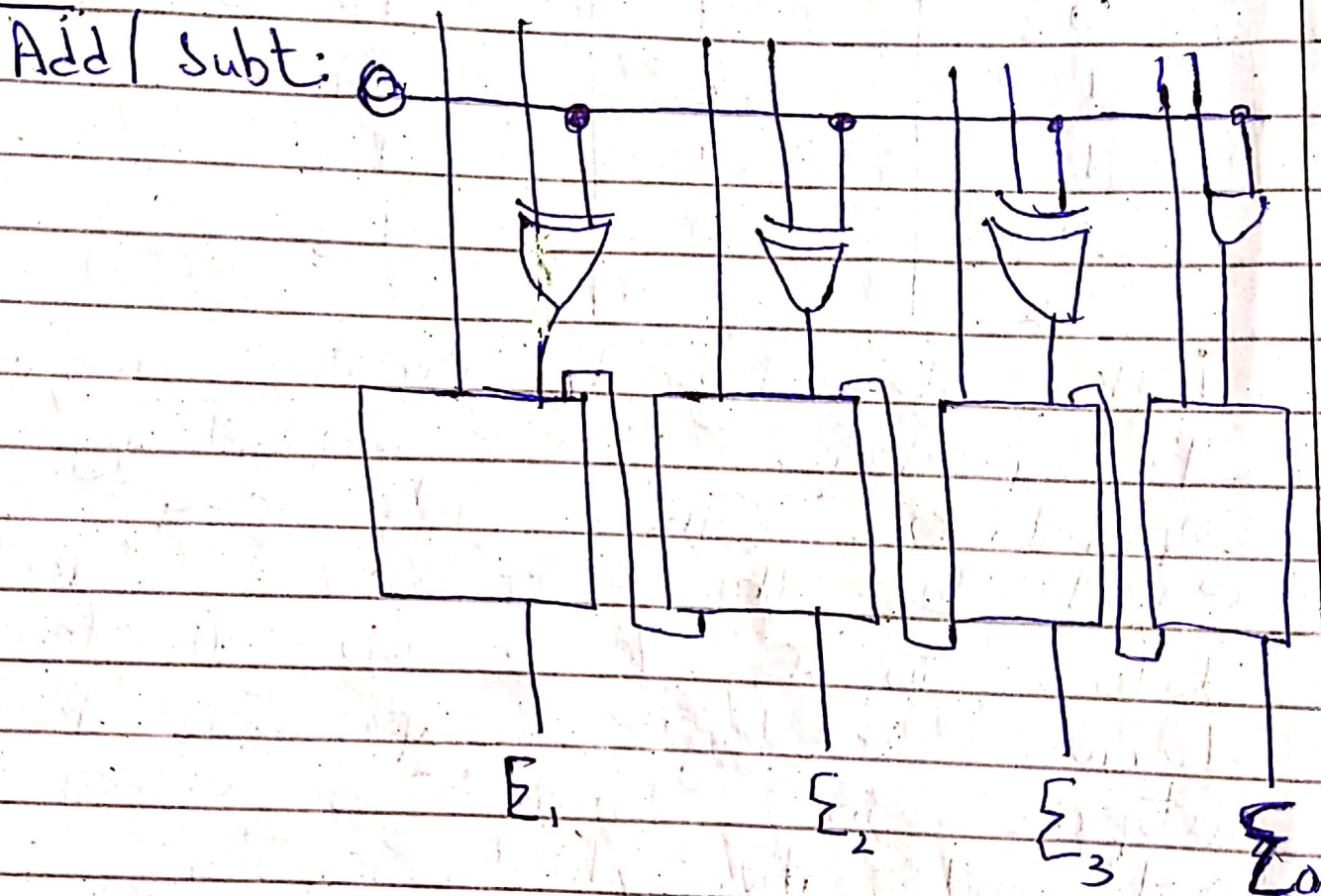


The Answer is

1001

Q4 Determine output for $A=B$, $A>B$, $A<B$ shown on the comparator in figure 6-22

4
Ans

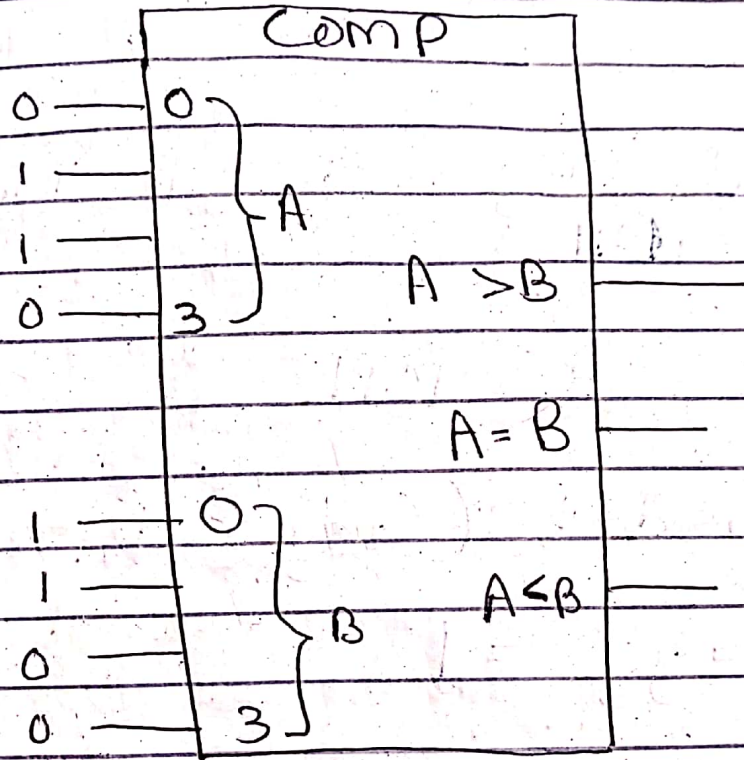

Sol

The number on the A inputs is 0110 and the number on B input is 0011. The $A > B$ output is HIGH and the other output is LOW.

Q51 - Show the logical required to convert a 4 bit Gray code to binary and use the logic to convert the follow Gray code word to binary : 1011

Ans

Sol,

Convert Gray code to binary code = 1011

Gray code 1011

Method-1 : (Gray code to Binary)

$$b_3 = g_3 = 1$$

$$b_2 = b_3 \oplus g_2 = 1 \oplus 0 = 1$$


$$b_1 = b_2 \oplus g_1 = 1 \oplus 1 = 0$$

$$b_0 = b_1 \oplus g_0 = 0 \oplus 1 = 1$$

Binary Code : 1101

Q61. Draw and explain the logic diagram 4 bit active low decoder.

Ans. 4 Bit Active decoder

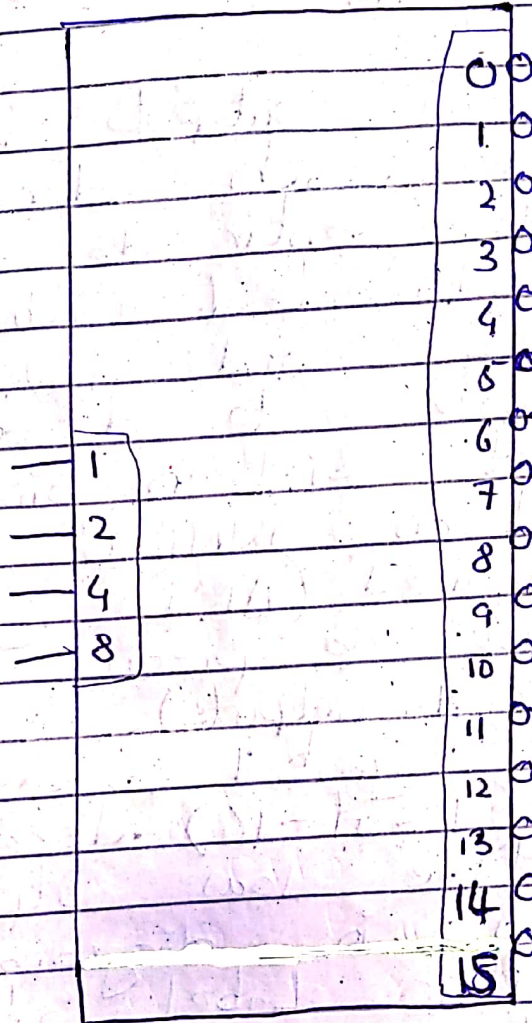

The 4 Bit decoder to decode all positive combination of four bits (sixteen decoding gates are = 16). This type of decoder is commonly called either a 4-line-to-16-line decoder because there are four inputs and sixteen outputs or a 1-of-16 decoder because for any given code on the inputs, one of the sixteen outputs is activated.


A list of sixteen binary code and their corresponding decoding functions is given in diagram.

If an low output is required for each decoded number, the entire decoder can be implemented with NAND gates and inverters. In order to decode each of sixteen binary code, sixteen NAND gates are required (AND gates can be used to produce active - HIGH outputs).

A logic symbol for a 4-line to 16-lines (1-of-16) decoder with active low output is shown in diagram.

The BIN/DEC Label indicates that a binary input makes the corresponding decimal output active.



Logic Diagram 4 bit active decoder

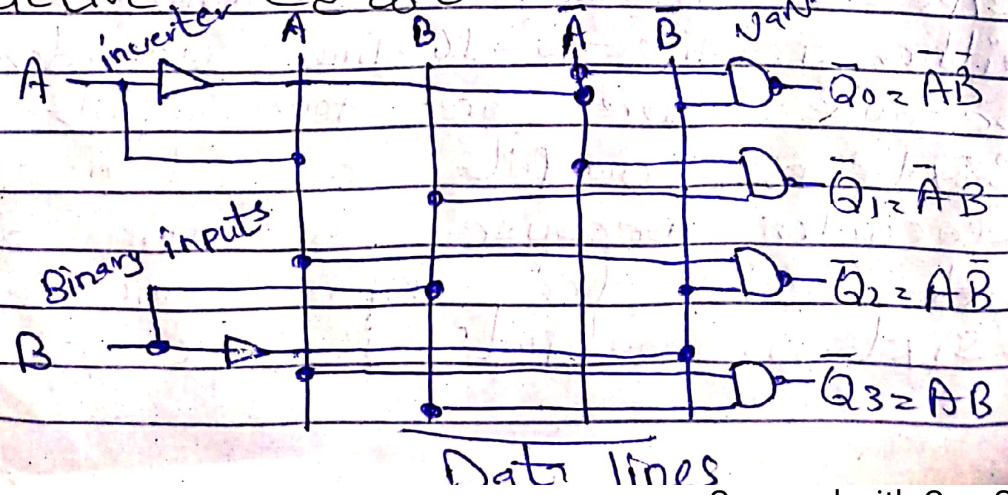

Q7. Draw and explain the logic daigram for frequency divider (use 3 J-k flip-flops and assum 16 KHZ frequency -

Ans.

HIGH

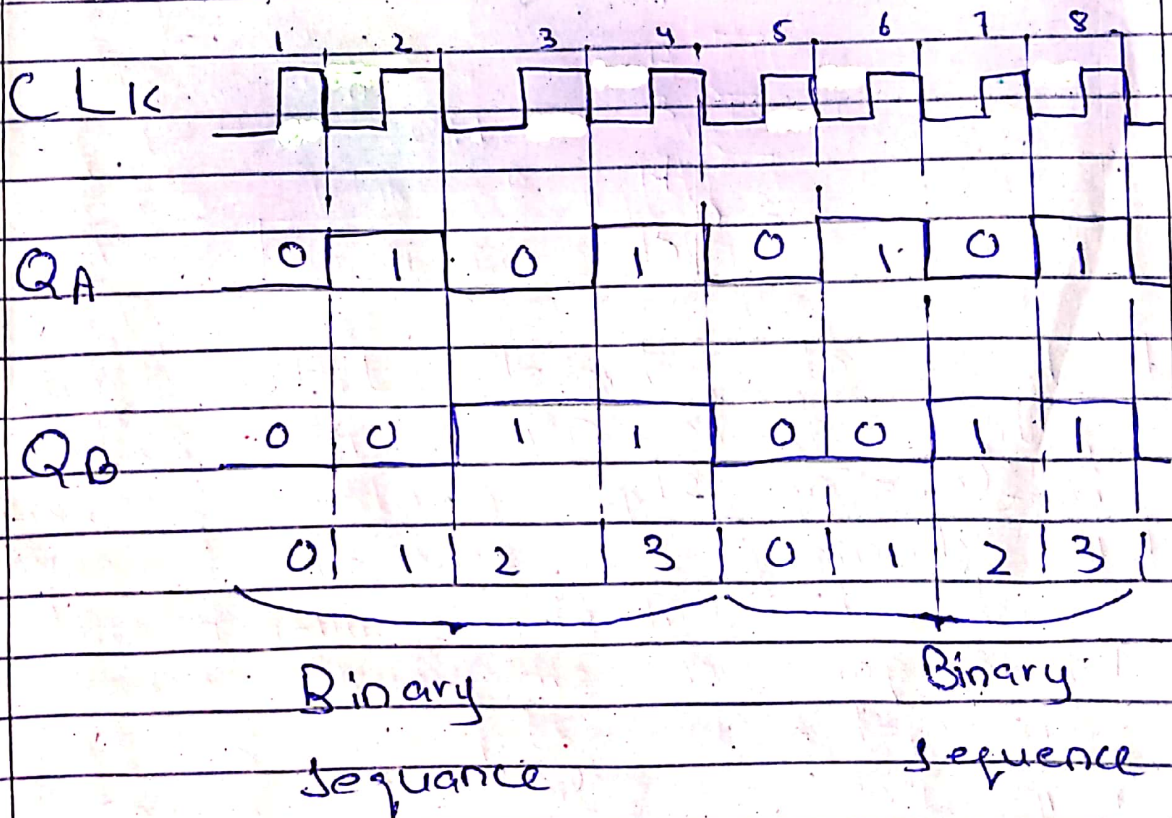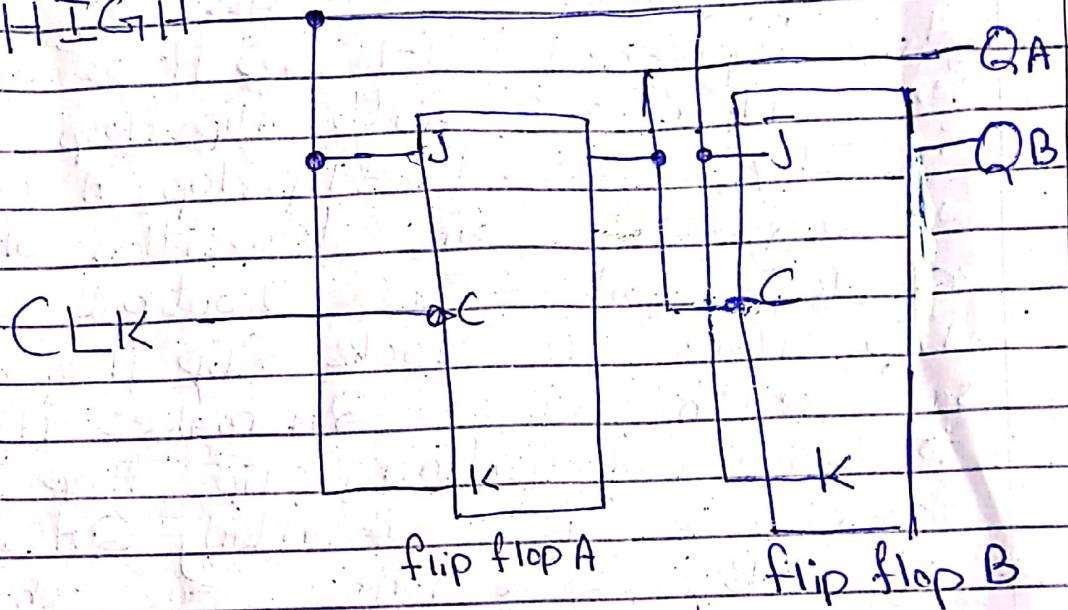


The logic diagram for frequency divider using 3 J-K flip flops and assume 16 kHz frequency of the initial wave form - the negative edge triggered J-K flip flops are used for illustrate - Both flip flop are initially RESET - flip flop A toggles on negative going transition of each clock pulse - The Q output the flip flop A clocks flip flop B, so each time QA makes High to Low transition, flip flop B toggles - The resulting QA and QB wave forms are shown in the diagram -

Q.81- Determine Q waveform relative to the clock --- --
--- - Assum that is Q initially Low -

Ans

Sol

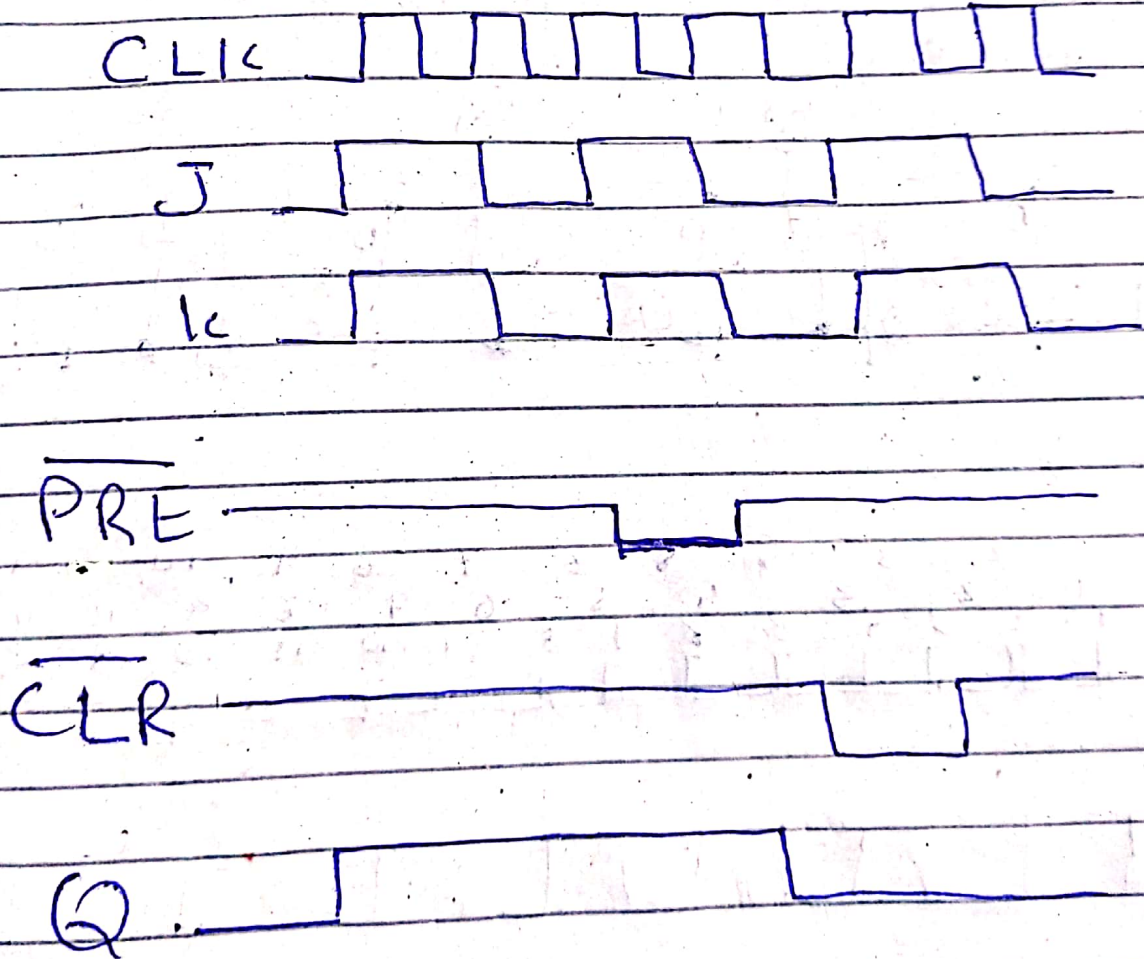

Q91 Draw the logic diagram and timing diagram for the 4 stage Synchronous counter after each clock pulse -

Ans Four bit Synchronous Counter,

