

Name Majid Mahmood
ID 13876
Subject Electronic Device
Exam Circuit
Summer

* _____ *

Question # 1

(Part a)

-Answer: It is a centre-tapped full wave rectifier operation circuit.

Question # 1

(Part b)


Total Peak secondary voltage,


$$V_{P(sec)} = n V_{P(prim)} = 0.25(50)$$

$$= 12.5 \text{ V}$$

$$V_{P(sec)} = 12.5 \text{ V}$$

Question # 1 (c)

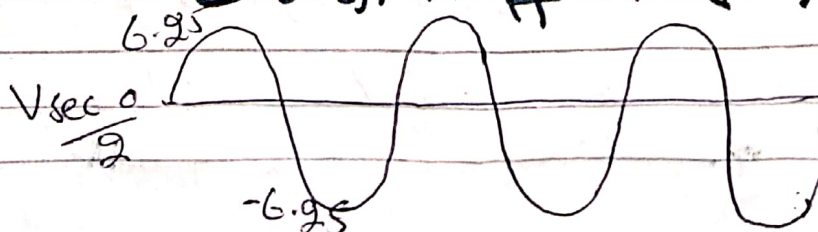

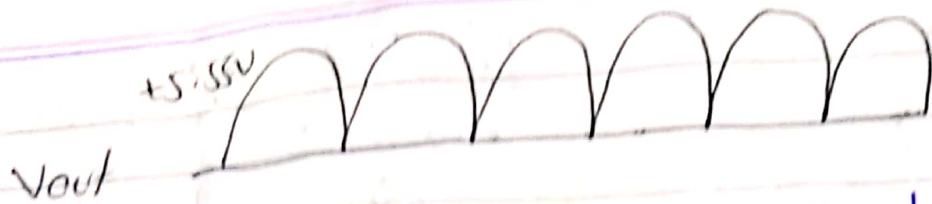

There is 6.25V peak to peak voltage the output voltage has a peak value of 6.25-0.7 which is diode drop.

Question # 1

(Part d)

Peak current through each Diode

$$I_P = \frac{V_{P(sec)} - 0.7}{2 R_L} = \frac{5.55V - 0.7}{10K\Omega} = 0.000555$$

$$\approx 0.555 \text{ mA}$$

Question # 1

(Part e)

PIV rating must a have diode


$$PIV = 2V_{P(owl)} + 0.7$$

$$= 2(5.55V) + 0.7$$

$$= 11.8V$$

Question # 2

Answer ::

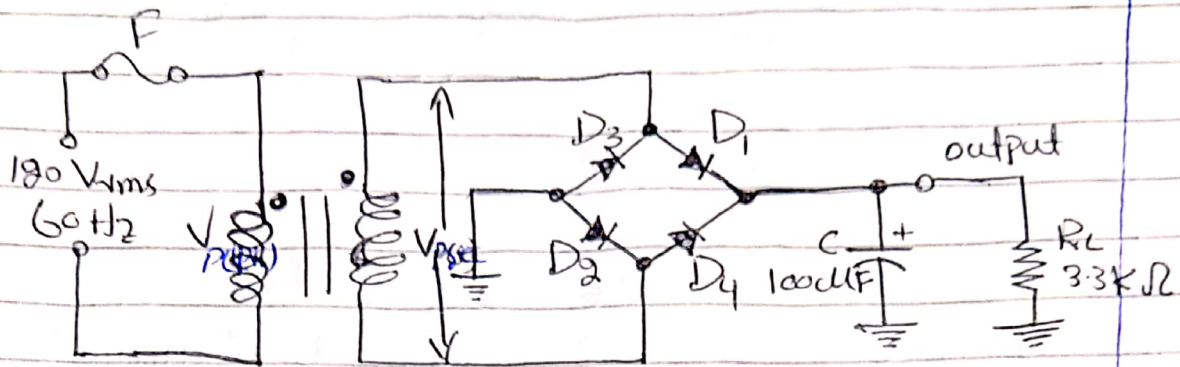

Sol :: The transformer turns ratio is

$$n = 0.1$$

The peak primary voltage is

$$V_{p(\text{pri})} = 1.414 V_{\text{rms}} = 1.414(120) = 170 \text{ V}$$

The peak secondary voltage is =

$$V_{p(\text{sec})} = n V_{p(\text{pri})} = 0.1(170 \text{ V}) = 17 \text{ V}$$

The unfiltered peak full wave rectified voltage is :

$$V_p(\text{rec}) = V_{p(\text{sec})} - 1.4 \text{ V} = 17 \text{ V} - 1.4 \text{ V} = 15.6 \text{ V}$$

The frequency of full wave rectifier voltage is 120 Hz.

The approximate peak to peak ripple voltage at the output is =

$$V_r(PP) = \left(\frac{1}{f R_{LC}} \right) V_{P(1\text{ed})}$$

$$= \left(\frac{1}{(120\text{Hz})(3300\Omega)(100\mu\text{F})} \right) 15.6\text{V}$$

$$= 0.393\text{V}$$

The approximate DC value of the output voltage is determined as follows:

$$V_{DC} = \left(1 - \frac{1}{2f R_{LC}} \right) V_{P(1\text{ed})}$$

$$= \left(1 - \frac{1}{(240\text{Hz})(3300\Omega)(100\mu\text{F})} \right) 15.6$$

$$\Rightarrow 15.4\text{V}$$

The resulting ripple factor is


$$\gamma = \frac{V_r(PP)}{V_{DC}} = \frac{0.393\text{V}}{15.4\text{V}} \Rightarrow 0.025$$

The present ripple factor is 2.5%


*

Question # 3

Answer

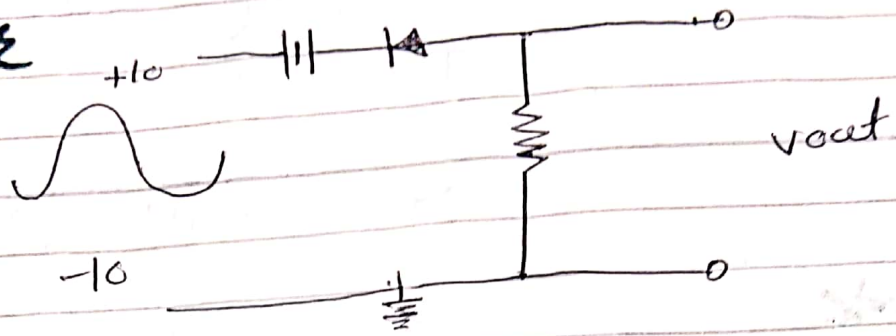


Solution

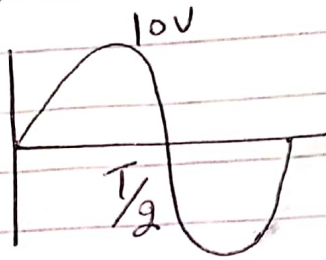

$$V_i + 3V = 0V$$

$$V_i = -3V$$

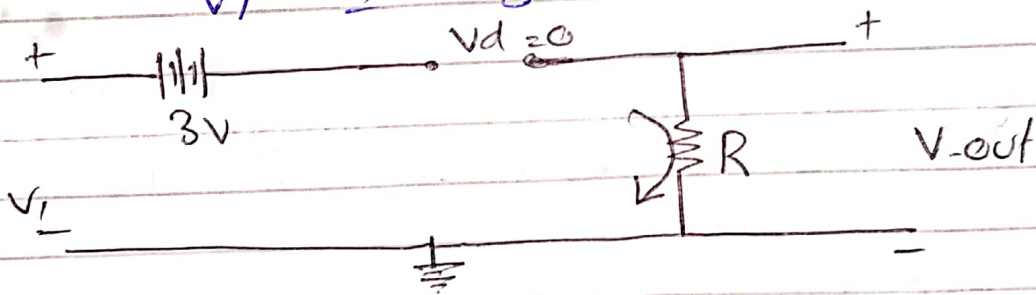

$$V_o = V_R = I R (R) = 0 (R) = 0$$

$$V_o = V_i + 3V$$


Transition voltage

$$V_i + 3V = 10V + 3V = 13V. \text{ If}$$

$$V_o = 0V + 3V = 3V$$

$$V_o = -3V + 3V = 0$$

out put.

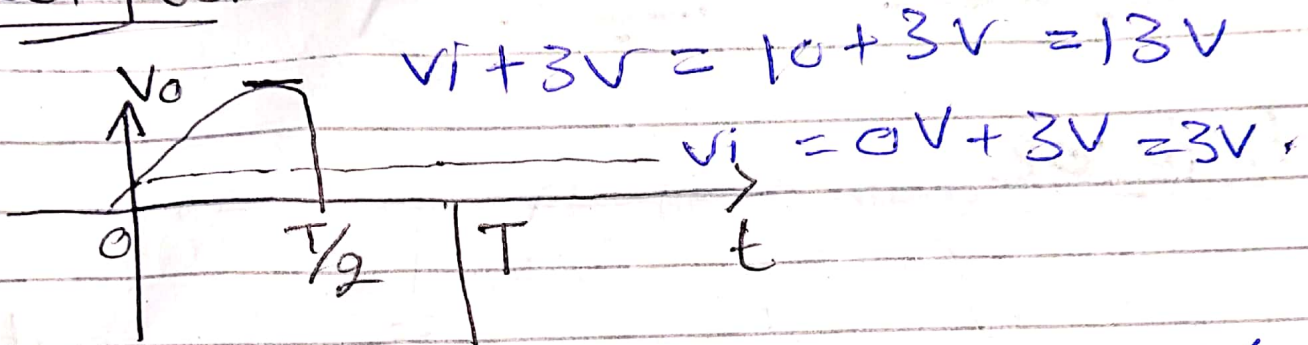


$$V_o = -3V + 3V = 0V$$



Question # 4

Answer:

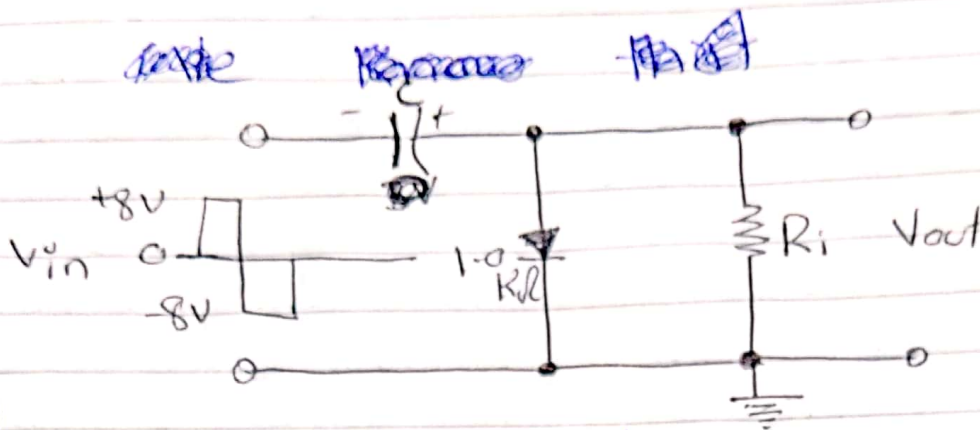

We know that


$$\Rightarrow V_{DC} \cong -(V_{p(in)} - 0.7V) =$$

$$\rightarrow -(8V - 0.7V) = -7.3V$$

\Rightarrow The output wave form goes upto $+0.7V$ approximately

\Rightarrow The output voltage will have an average value of slightly less than calculated

So the wave form will be

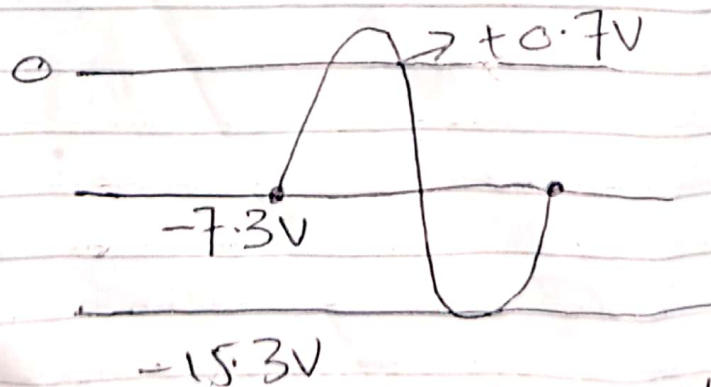

The output voltage wave form.

Question # 5 (a)

Power supply filters:

The ripple components of output voltage is removed by placing a filter circuit. The output voltage of rectifier is pulsating in nature.

It consists of two parts.

- ① Desire DC components of voltage
- ② unwanted ripple component.

The unwanted comp are removed by power supply filters.

In power supplies capacitors are used to filter the pulsating DC output, so that constant DC voltage is supplied to the load.

Filter capacitors reduces the ripple voltage to acceptable level.

In filter circuit capacitor is charged to peak of rectified input voltage during positive portion of voltage.

Q# 5(a)

When input become negative, the capacitor begins to discharge to load. The rate of discharge is determined by RC times constant.

The capacitance value for output current (I) and ripple current (V_{rms}) is

$$C = \frac{I}{V_{rms} \times 4f}$$

$$V_{rms} = \frac{V(P-P)}{2} \text{ for } f=60\text{Hz}$$


$$\Rightarrow C = \frac{2 \cdot 4I}{V_{rms}}$$

I = DC load current

$$C = \frac{I \times V_{dc}}{V_{rms} V_m} = V_{dc} = \frac{V_m + V_{P-P}}{2}$$

V_m = maximum voltage

V_{P-P} = peak to peak ripple voltage

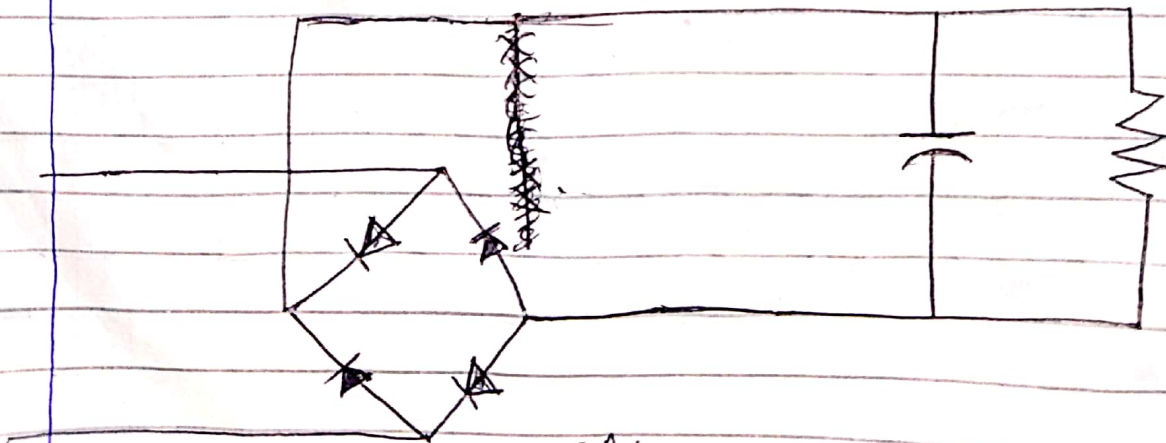

Filtering

Question No 5(b)

Ans: Formation of P-type and N-type Semi conductors:

Semi conductors are of two types.

- * Intrinsic Semi-conductors &
- * extrinsic Semi-conductors.

The Semi-conductors which are doped with impurity atoms are called extrinsic Semi-conductor.

⇒ There are two/2 types based upon the type of impurity added.

- ① N-type Semi-conductor &
- ② P-type Semi-conductor.

N-type Semi-conductor: It is a type of extrinsic Semi-conductor which is doped with a penta valent impurity element, which has 5 / five electrons in its valence shell.

Formation of N-type semi-conductor.

N-type Semi-conductor is doped with the Pentavalent impurity like phosphorus, antimony and arsenic.

The impurity is added in very minute amount

The penta-valent impurity makes covalent bond with four/4 Silicon atoms & one electron is not bonded with any Si atoms.

Each penta-valent elements impurity donates one/1 e^- to the N-type semi-conductor. So it is called Donor impurity. So in N-type semi-conductor electrons are main conductor of current.

P-type semi-conductors:

The extrinsic P-type is formed when a tri-valent impurity is added to a pure semi-conductor. As a result large no. of holes created & these holes acts as a carrier. These impurities are called acceptor impurities. Such as gallium and indium.

For example:

In tri-valent impurity like gallium and is added into germanium crystal in such a way that its three/3 valence e^- forms a covalent bond with the ~~three/3~~ germanium.

In the four/4 covalent bond only germanium atoms

contributes one valence e^-
so there is a missing e^-
is hole.

Q # 5 (c)

Diode Limiters:

Diode clippers or diode limiters is a wave shaping circuit that takes an input wave form & cuts-off its top-half, bottom half or both halves together and produces wave forms that resembles flattened version of the input. There are two types of clippers.

(1) Positive Diode limiters/clippers:
In this diode limiting circuit, the diode is forward biased. For the diode to become forward biased, it must have the input voltage magnitude greater than +0.7 volts.

A voltage bias is added in series with the diode.
For example:


If voltage bias is set 4 volts than the sinusoidal voltage, then the diode anode terminal must be greater than

$4 + 0.7 = 4.7 \text{ V}$ to become forward bias.

Any voltage level above this

Q #5 (c)

point is cut-off

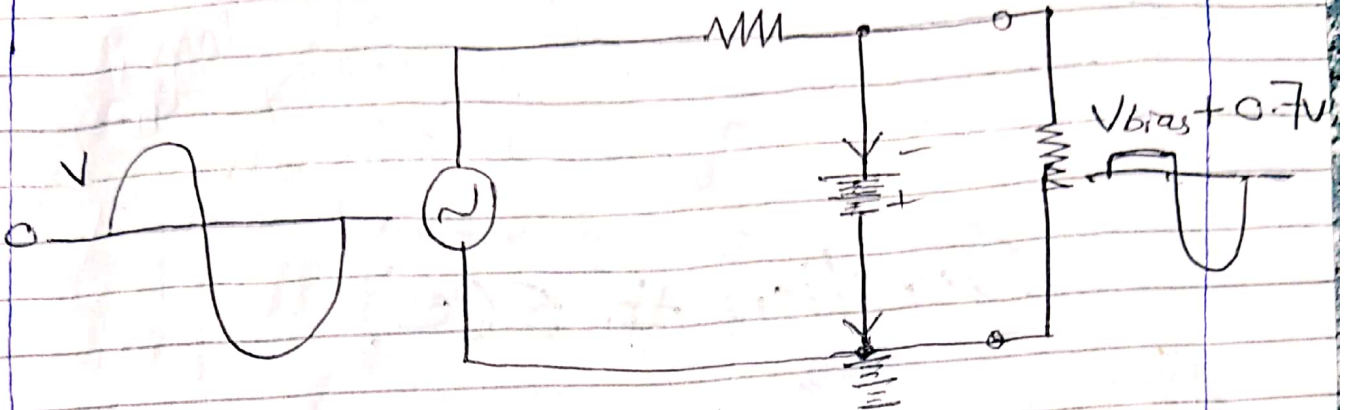


Positive diode limiter.

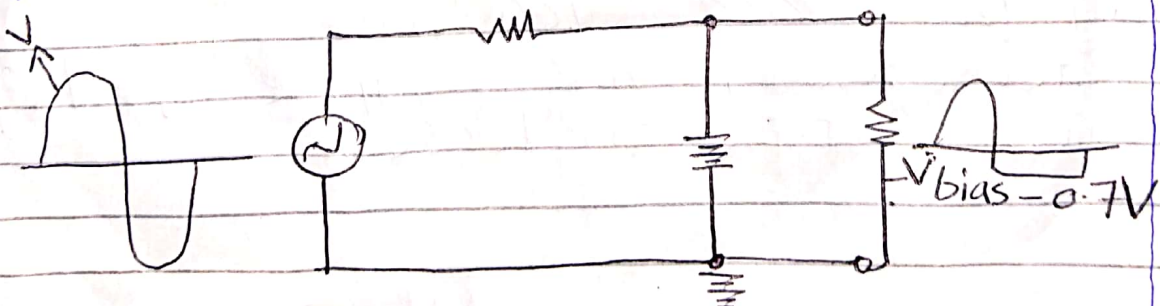(2) Negative Diode Limiters:

When the diode is forward biased during a negative half of the cycle and limits it $0.7V$, while allowing the positive half of the cycle is called negative limiters of the circuit.

The output wave form is held to a level $- \text{Bias} - 0.7V$



Negative Diode limiter.

Question # 5 (d)

Answer: The capacitor effectively acts as a battery in a clamping circuit.

Question # 5 (e)

Answer: The output frequency of half wave rectifier is same to input frequency. So if 60 Hz sinusoidal voltage is applied, then the output frequency will also be 60 Hz.

Question 5 (f)

Answer: The ripple voltage and load resistance are inversely related to each other.

Ripple voltage $\propto \frac{1}{\text{load resistance}}$.

If the load resistance is decreased, the ripple voltage will be increase.

Question # 5(g)

Difference between diode limiter and diode clamper.

Diode limiter

① It limits the amplitude of output voltage

② output voltage less than the input voltage

③ the shape of voltage changes

④ Its DC level remain same

Diode clamper

① It shifts the DC level of output voltage

② Its output voltage is multiple of input voltage.

③ shape remain same.

④ DC level gets shifted.