

NAME

FANAI ANNAI

ID

14231

DEPARTMENT

BE (E)

SUBJECT

ELECTRICAL MACHINE


Q1(a) Discuss two methods of speed control each for series and shunt wound DC motors. (1)

Answer: Speed Control of DC Shunt Motor:

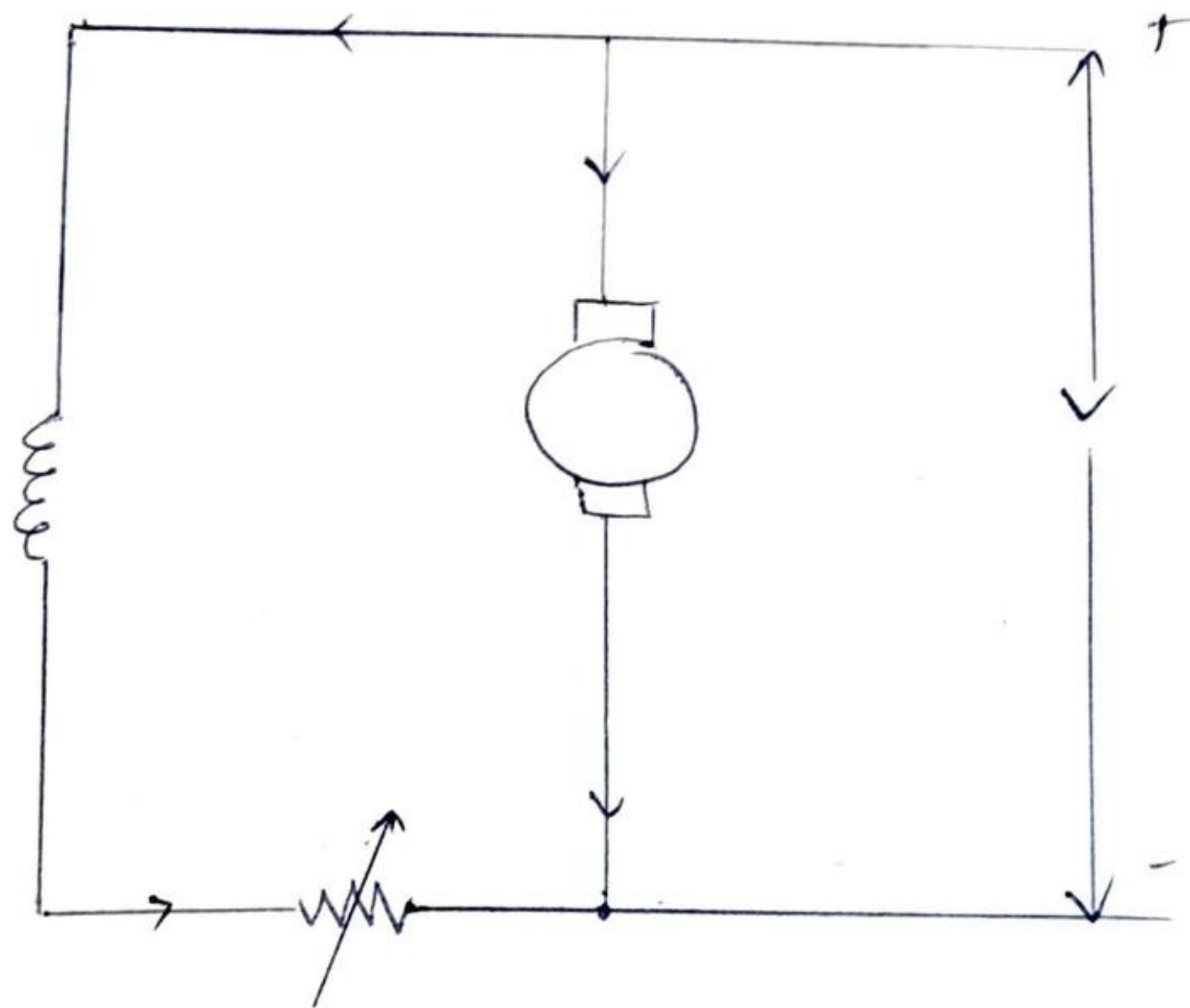(i) Flux Control Method:-

In this method, a variable resistance is placed in series with shunt field winding.


An increase in controlling resistance reduces the field current with a reduction in flux and an increase in speed.



Field
Rheostat

② ARMATURE CONTROL METHOD:- ②

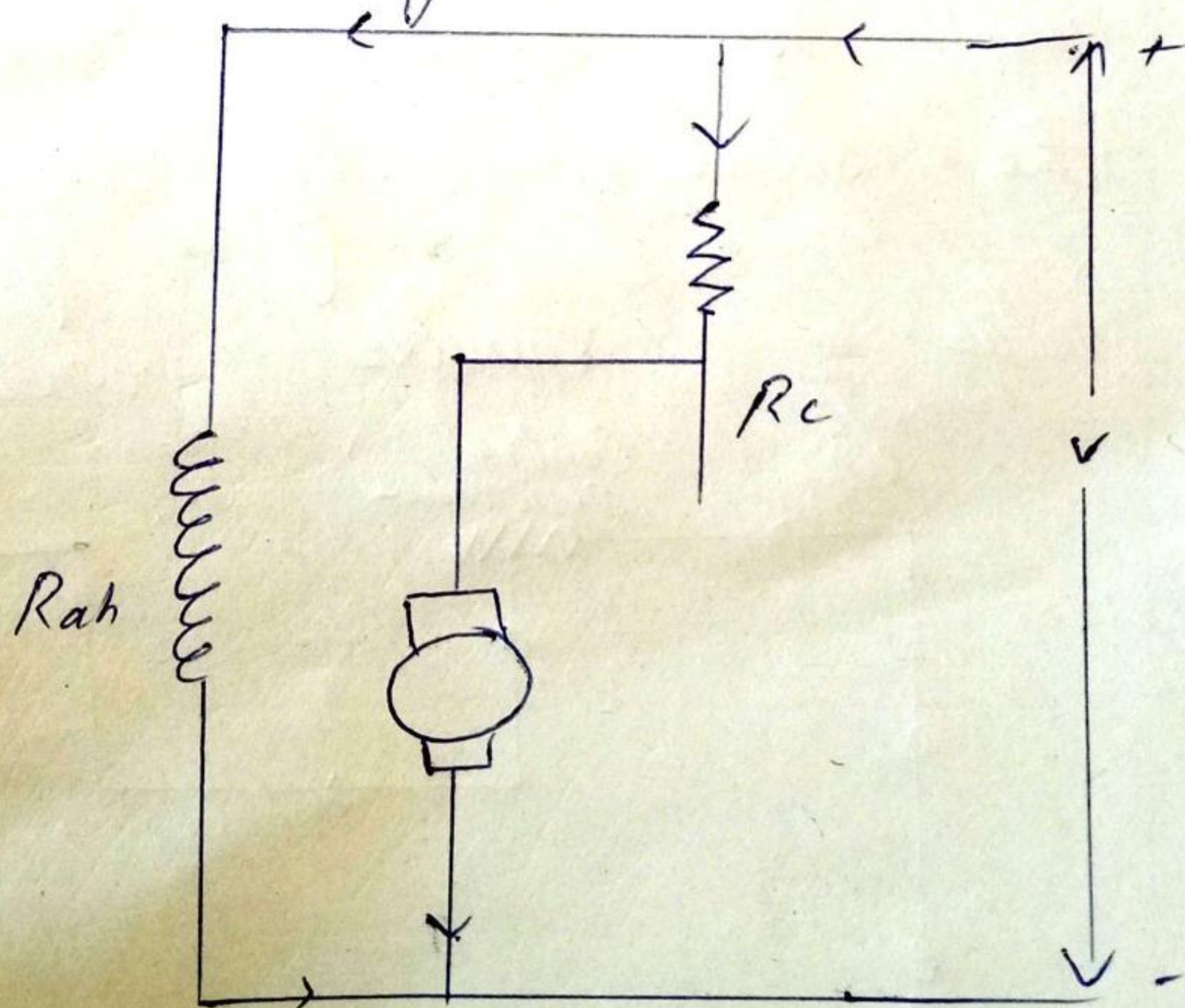- * This is done by inserting a variable resistance R_c (known as controller resistance) in series with the armature as shown.
- * The Φ_{an} remains constant while armature current is changed produces change in speed.




Speed Control of DC Series Motor: (3)

* ARMATURE RESISTANCE CONTROL

METHOD:-

Here the controlling resistance is connected directly in series with the supply of the motor

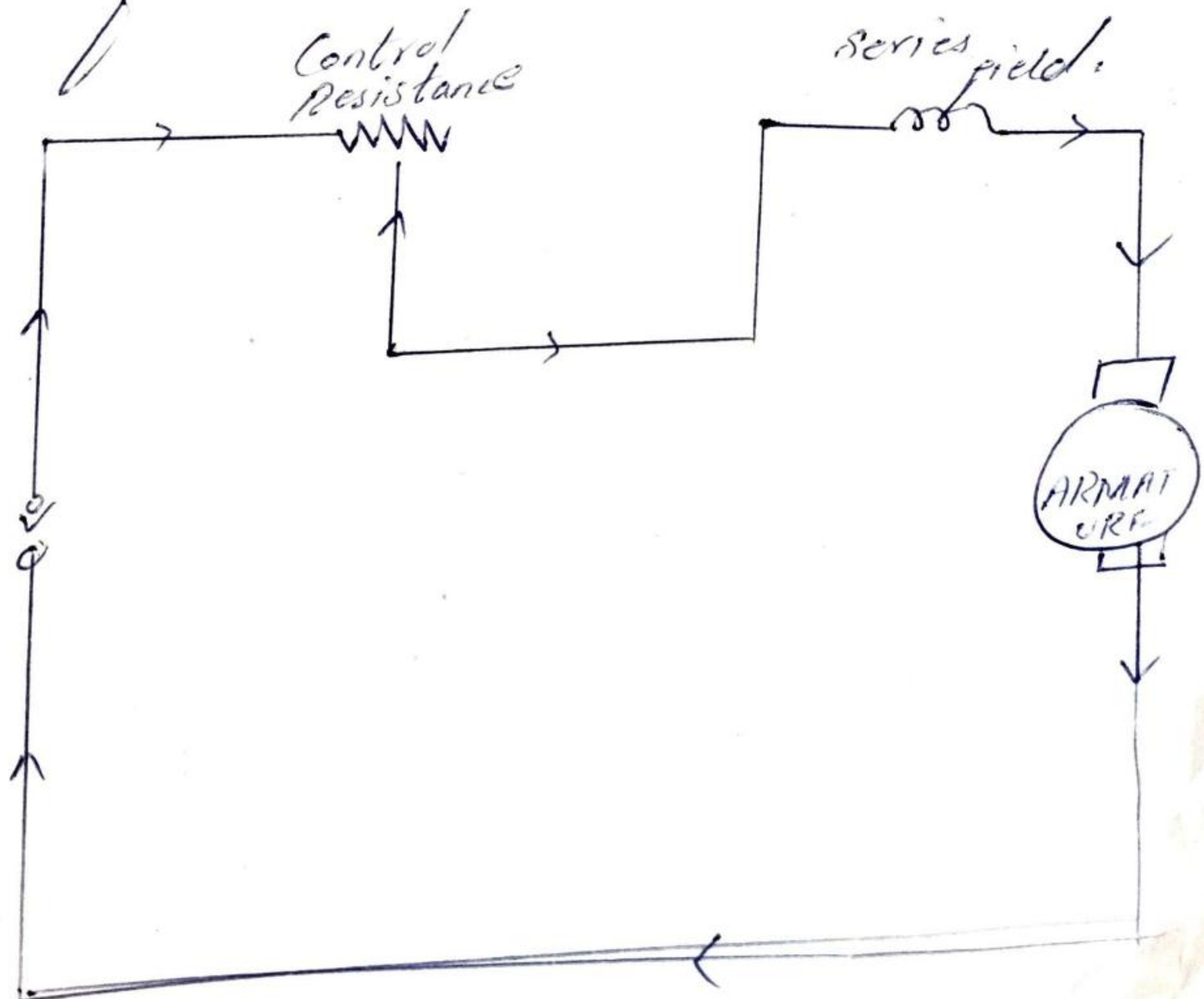
This reduces the voltage available across the armature and hence the speed falls. By changing the value of variable resistance.



(FIELD) DIVERTER METHOD:-

* This method uses a diverter.

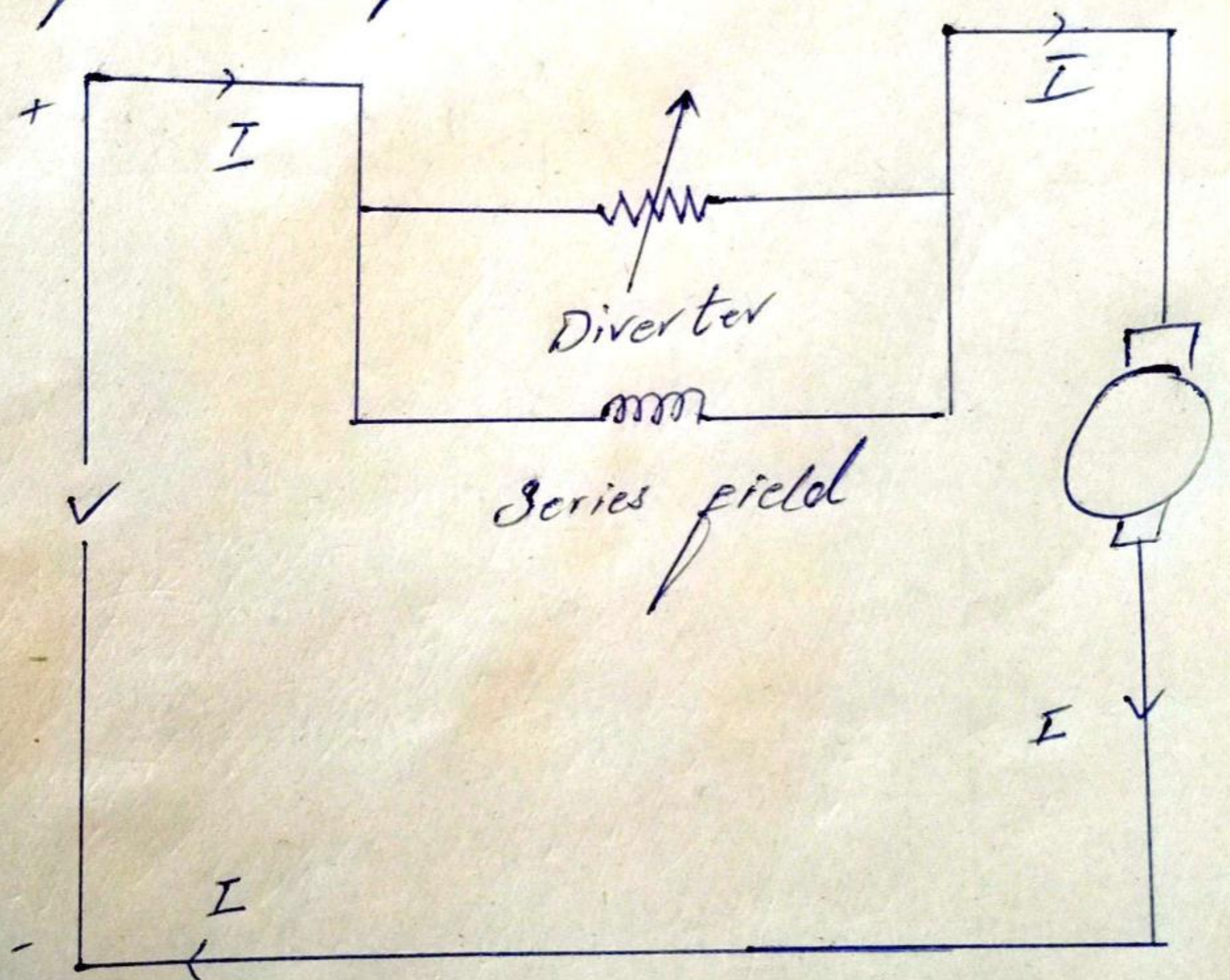Here the field flux can be reduced by shunting a portion of motor current around the series field. Lesser the diverter resistance less is the field current, less flux therefore more speed.



(b)
Q1

Consider 8 poles DC --- (5)
--- --- --- Wave Winding.

Sol:-

$$Z = 480$$

$$P = 8$$

$$\text{emf} = 2.2 \text{ V}$$

$$\text{current} = 100 \text{ A}$$

total voltage = ?

opp current = ?

$$P = ?$$

For Lap $A = 8$

$$\text{Emf} = 2.2 \times \frac{480}{8} = 132$$

$$\text{current} = 100 \times 8 = 800$$

$$P = VI = 800 \times 132 \\ = 105 \text{ kW}$$

For Wave

$$A = 2$$

$$\text{emf} = 2.2 \times \frac{480}{2} = 528$$

$$\text{Current} = 100 \times 2 = 200$$

$$P = 105 \text{ kW}$$

Q2(a)

Determine Relationship between torque and armature current? (b)

Ans:-

$$P_e = P_m$$

P_e = Electrical power

P_m = Mechanical power

$$P_e = E_a I_a \text{ as } (E_a = E_b + I_a R_a) \text{ KVL}$$

$$P_e = (E_b + I_a R_a) I_a$$

$$P_e = E_b I_a + I_a^2 R_a \text{ (as dissipate in form of heat)}$$

$$P_e = E_b I_a$$

Now

$$P_m = T \omega \quad \therefore T \text{ (Torque in N.M) and } \omega \text{ (angular speed in rad/sec)}$$

$$1 \text{ radian} = \frac{1}{2\pi} \therefore \text{In RPM} = N \cdot \frac{2\pi}{60} = \text{rad/sec}$$

$$P_m = T \cdot N \cdot \frac{2\pi}{60}$$

$$P_m = P_e$$

$$E_b = \frac{P \cdot \phi \cdot Z \cdot N}{60 \cdot A}$$

$$T \cdot N \cdot \frac{2\pi}{60} = E_b I_a$$

$$T = \frac{P \cdot Z \cdot \phi \cdot I_a}{2 \cdot \pi \cdot A}$$

Q2(b)

Differentiate between lap winding (7) and wave winding?

Ans:-

LAP WINDING

WAVE WINDING

Definition	The coil is lap back to the succeeding coil.	The coil of the winding form the wave shape
Connection	The end of the armature coil is connected to an adjacent segment on the commutator.	The end of the the armature coil is connected to two commutator segments some distance apart.
Parallel Path	The number of parallel path are equal to the total of number poles.	The number of parallel paths is equal to two
EMF	Less	More
Number of Brushes	Equal to the Number of parallel paths	Two
Types	Simplex and Duplex lap winding	Progressive and Retrogressive wave winding
Efficiency	Less	High
Additional Coil	Equalizer Ring	Dummy coil
Winding Coil	High (because more conductor is required).	Low
Uses	In low voltage, high current machines.	In high voltage, low current machines.