

Syed Daniyal Shah

14127

26-09-2020

DLD

Q1 Answers


a) In digital circuits, A binary Adder-subtractor is one which is capable for both addition and subtraction of binary numbers in one circuit itself.

lets consider two 4-bit binary numbers A and B as inputs to the Digital Circuit for the operation with digits

A0 A1 A2 A3 for A
B0 B1 B2 B3 for B

It continues and full adder performing on 4-bit numbers, There is control line K that holds a binary value 0 or 1, which determines operation carried out in addition or subtraction.

Diagram:-

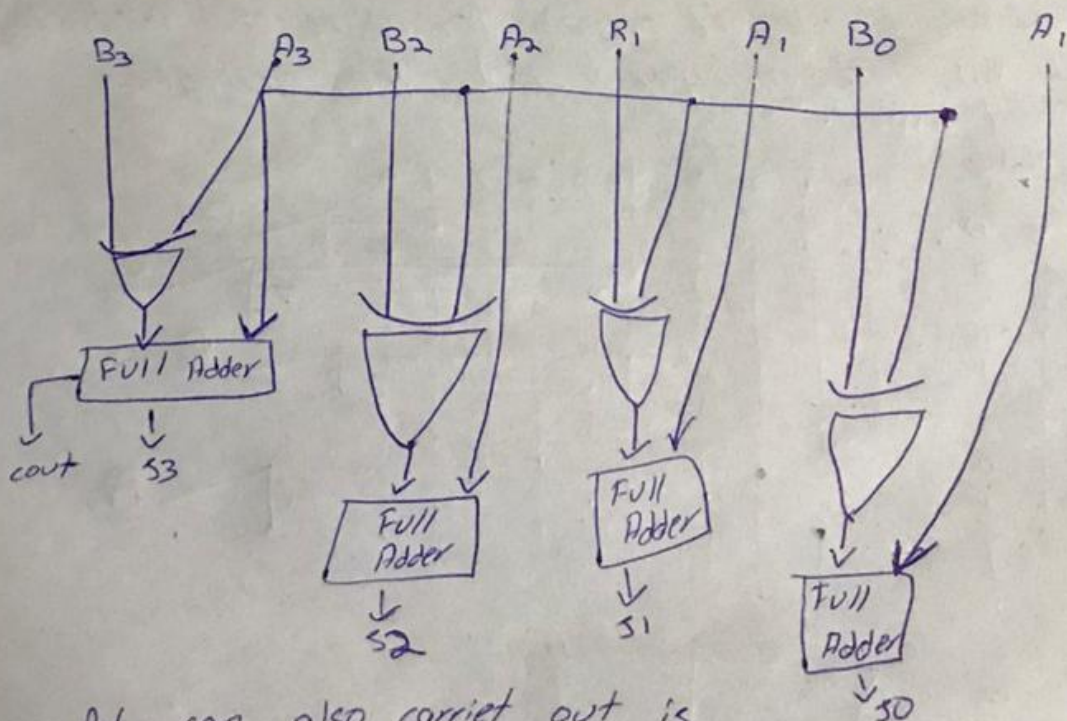


It can also carry out is addition or subtraction.

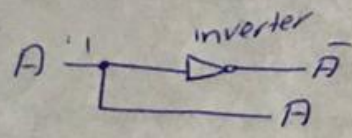Q1 b Answer:-

In digital circuits when a signal is 'active low' means that the signal will performing its function when its logic level is 0, if it is an active-low pin, you must pull that pin low by connecting it to ground. For an active high pin you connect it to your High voltage (usually 3.3V/5V)

4 bit depends upon the number of data inputs, lines, so decoder that has a set of two or more bits will be defined as n-bit code. by ~~and~~ 2^n possible values into a non binary one by setting exactly one of its n outputs to logic 1. If a binary decoder receives n inputs it activates one and only one of its 2^n outputs based on that input with all ~~imp~~ outputs deactivated.





Q1 c Answer 1- Decimal to BCD encoder

A decimal to BCD encoder is also known as 10-line to 4-line encoder. It accepts 10-inputs and produces a 4-bit out corresponding to the activated decimal input.

Truth Table

	0	1	2	3	4	5	6	7	8	9
D	0	0	0	0	1	1	1	1	0	0
C	0	0	0	1	0	0	0	0	1	1
B	0	0	1	0	0	1	0	1	0	0
A	0	1	0	0	0	0	1	1	1	0

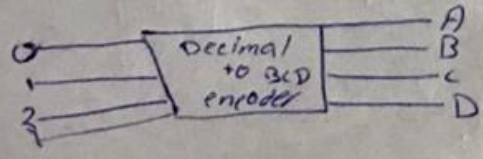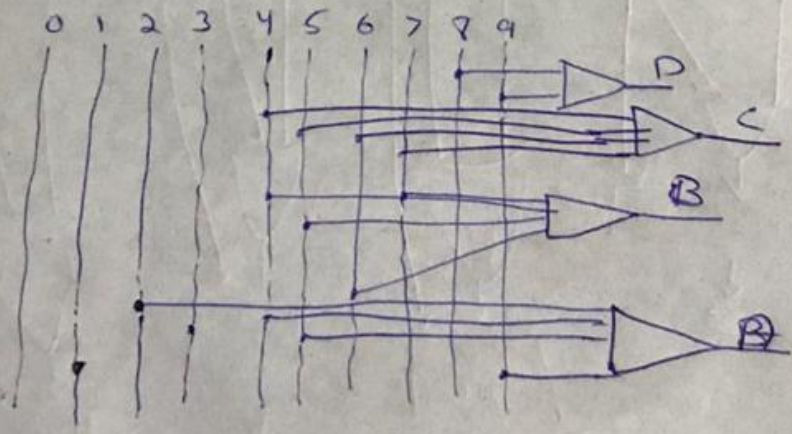

Q1 D Answer

3


14127
Daniyal

Frequency Divider

$$\text{Mod} = 2^n$$

$$= 2^{16}$$

$$= 65536$$

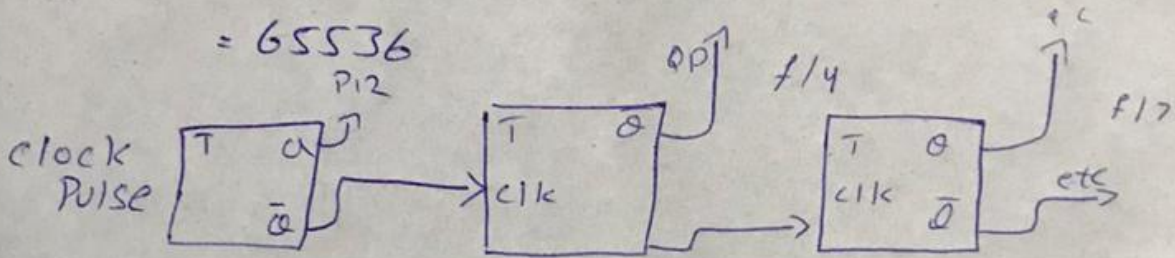


(4)

14127
Danial**Q2 Answer**

Soln Given inputs:-

$$D_0 = 0, D_1 = 1, D_2 = 0, D_3 = 1$$

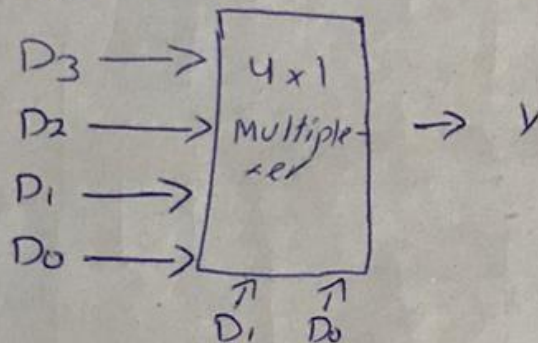4x1 Multiplexer has four data inputs D_0, D_1, D_2, D_3 two selection lines S_1 and S_0 and one output Y . The Block diagram.




One of these 4 inputs will be connected to the output based on the combination of inputs present, at these two selection lines.

selection	Lines	Output
D_0	D_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$Y = S_1 S_0 D_0 + S_1 \bar{S}_0 D_1 + \bar{S}_1 S_0 D_2 + \bar{S}_1 \bar{S}_0 D_3 \text{ Ans.}$$

Q3 Answer

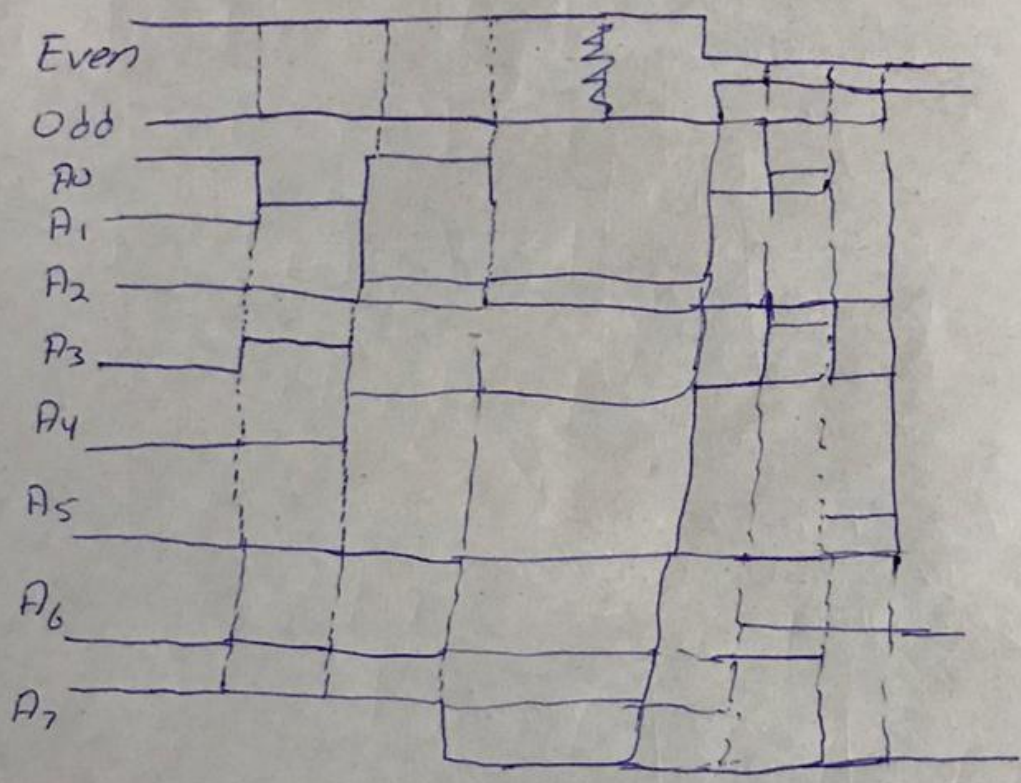

~~(a) Even parity: 110100~~

~~(b) Even parity: 00110001~~ generators/checkers.

~~(c)~~

(a) Even parity: 110100

(b) Even parity: 00110001

(a) Odd parity: 11010101

(b) Odd parity: 11000001


(a) Code is correct, four 1s

(b) Code is error, seven 1s.

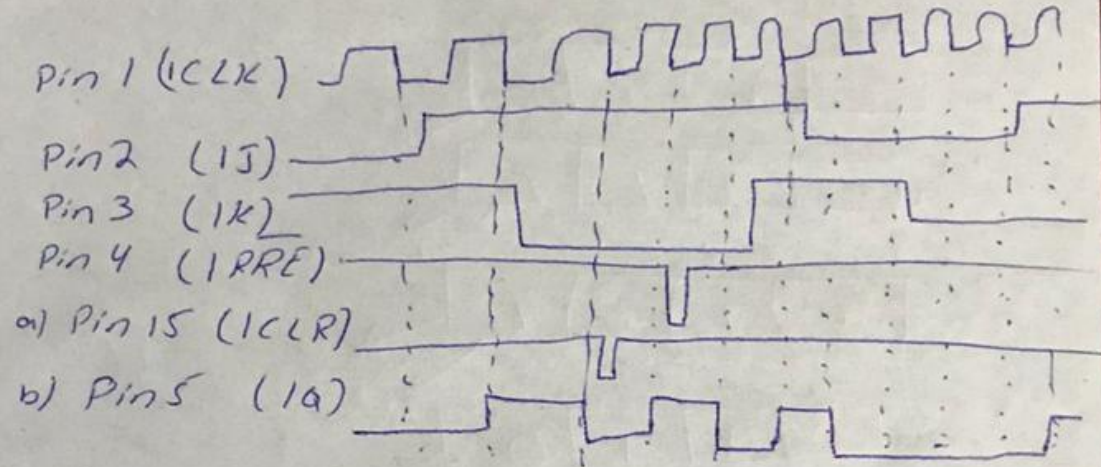Q4 Answer.

6

Soln The $I\bar{J}$, $I\bar{K}$, $I\bar{CLK}$, $I\bar{PRE}$ and $I\bar{CLR}$ waveforms are applied to one of the negative edge-triggered flip-flops in a 74HC112 package. Determine the $I\bar{Q}$ output waveform.




Solution:- The resulting $I\bar{Q}$ waveform each time a low is applied to the $I\bar{PRE}$ or $I\bar{CLR}$, the flip-flop is reset or preset regardless of the states of the 3 other inputs.

Q5 Answer 1.

Use the wave form.

Soln.

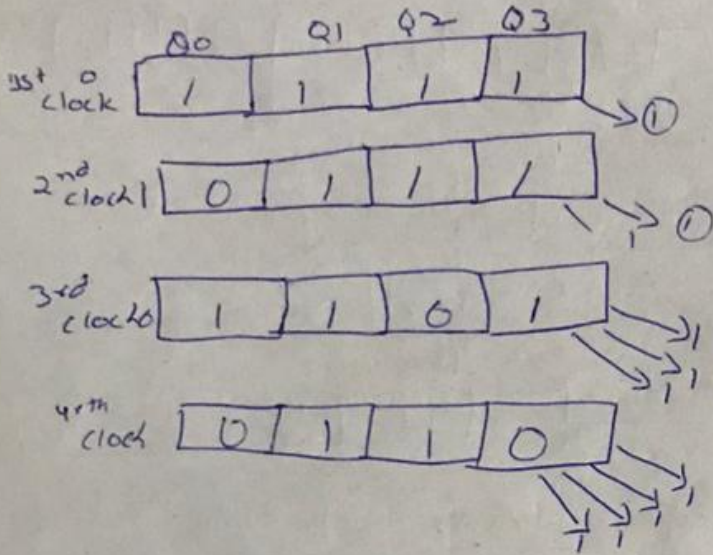

Data in 0 1 1 0

