

Department of Electrical Engineering

Assignment

Date: 13/04/2020

Course Details

Course Title:	Linear Circuit Analysis	Module:	_____2_____
Instructor:	SIR SOHAIL IMRAN	Total Marks:	_____30_____


Student Details

Name: MUHAMMAD BILAL KHAN


Student ID: 16434

Q1	(a)	<p>For each of the circuits in figure, find the current I and compute the power absorbed by the resistor</p> <div style="text-align: center;"> </div>	Marks 3
			PLO1
	(b)	<p>Determine the power supplied by the leftmost element in the circuit of following figure</p> <div style="text-align: center;"> </div>	Marks 4
			PLO1

(c)	Following figure depicts the current-voltage characteristic of three different resistive elements. Determine the resistance of each, assuming the voltage and current are defined in accordance with the passive sign convention.	Marks 3
		PLO1

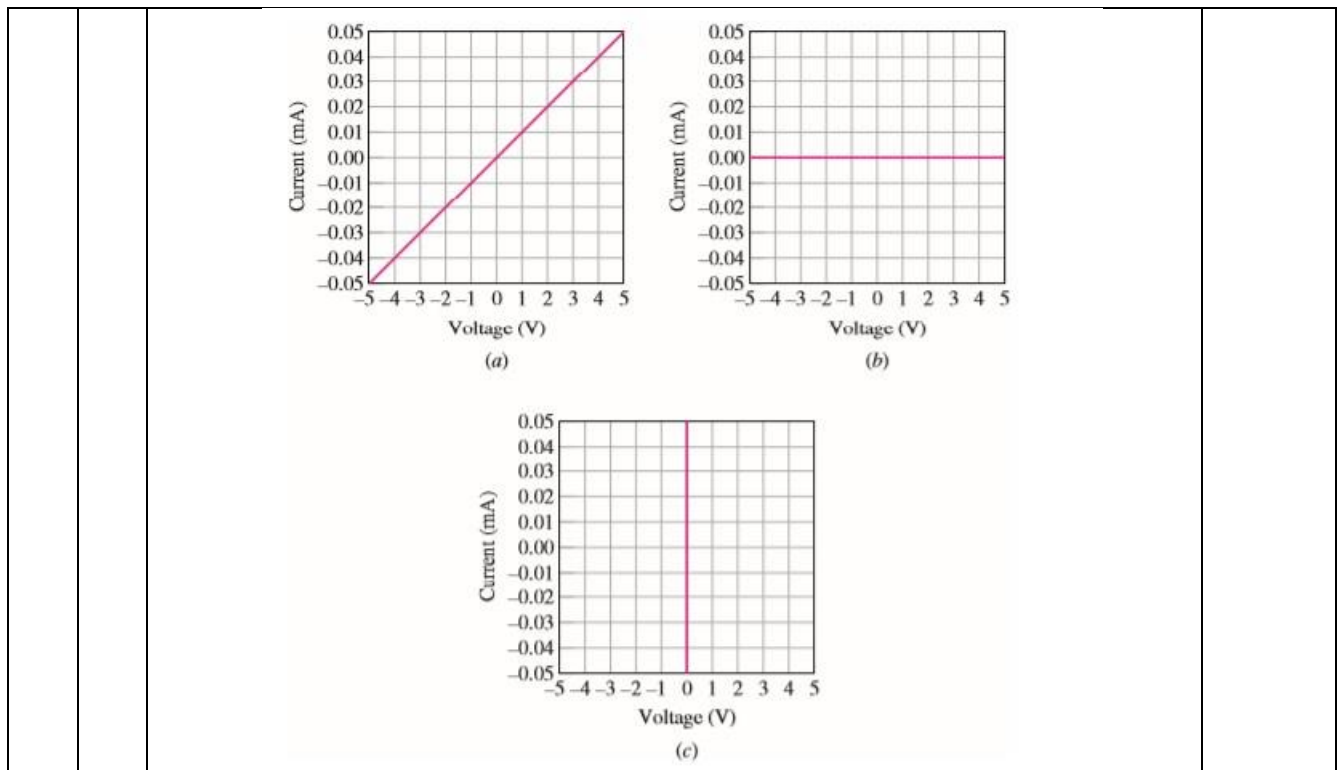

Q2	(a)	<p>Refer to the circuits of following figures, and answer the following:</p> <ol style="list-style-type: none"> How many distinct nodes are contained in the circuit? How many elements are contained in the circuit? How many branches does the circuit have? Determine if each of the following represents a path, a loop, both, or neither: <ol style="list-style-type: none"> A to B B to D to C to E C to E to D to B to A to C C to D to B to A to C to E 	Marks 4
			PLO2
(b)		<p>For the circuit of following figure (which is a model for the dc operation of a bipolar junction transistor biased in forward active region), I_B is measured to be $100 \mu\text{A}$. Determine I_C and I_E</p>	Marks 6
			PLO2

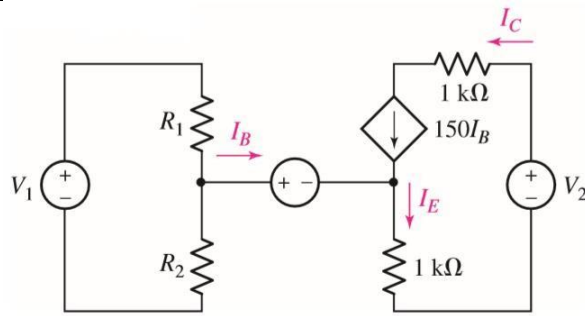


Q3

(a)


Although drawn so that it may not appear obvious at first glance, the circuit of following figure is in fact a single-node-pair circuit.

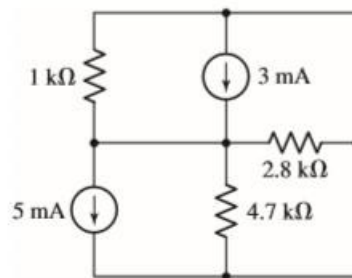- Determine the power absorbed by each resistor.
- Determine the power supplied by each current source.
- Show that the sum of the absorbed power calculated in (a) is equal to the sum of the supplied power calculated in (b).



(b)

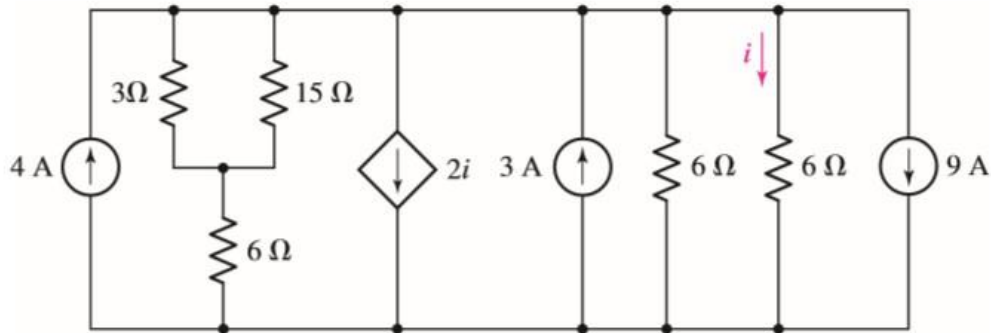Determine the power absorbed by the $15\ \Omega$ resistor in the circuit of following figure



Marks
5

PLO1

Marks
5

PLO1

Name : Muhammad Bilal Khan.

ID :- 16434.

Subject :- LCA (Linear circuit Analysis)

Exam :- Mid


Teacher :- Sohail Imran.

Page # 1

Question Number 1

Ans

Ans:-

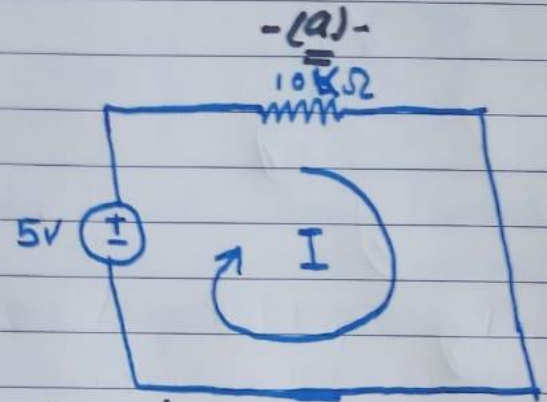

Find Current and power absorbed by the resistor.

To find current and power we have KVL rule.

$$(-5) + V_x = 0$$

$$V_x = 5V$$

$$I = \frac{V}{R} = \frac{5}{10 \times 1000}$$

$$I = 0.5 \text{ mA}$$


We know

$$P = VI$$
$$(5)(0.5 \times 10^{-3})$$

$$P = 2.5 \times 10^{-3} \text{ W}$$

-(b)-

Ans:-

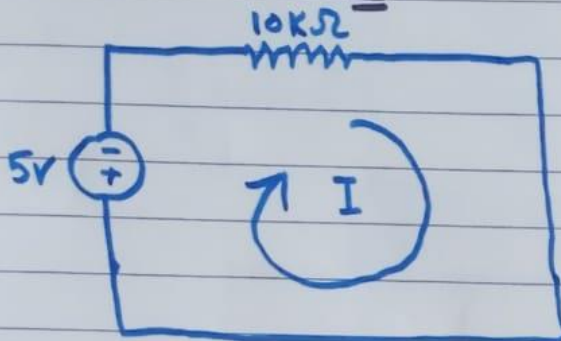

Find Current and power absorbed by resistor.

To find Current and power we use KVL rule.

$$(5) + V_x = 0$$

$$V_x = -5$$

To find Current:-

$$I = \frac{V}{R}$$

$$= \frac{-5}{10 \times 1000}$$

$$I = -0.5 \text{ mA}$$

To find power:-


$$P = VI$$

$$P = (-5) (-0.5 \times 10^{-3})$$

$$P = 2.5 \times 10^{-3} \text{ W}$$

-(C)-

Ans: - Circuit: -

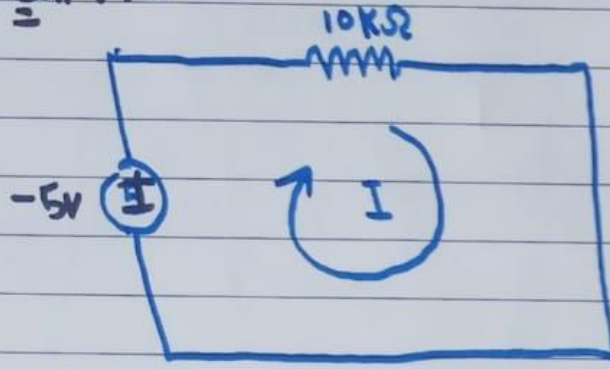

To find current and power absorbed by the resistor we have KVL rule.

We know we have KVL rule.

$$-(-5V) + V_x = 0$$

$$5V + V_x = 0$$

$$V_x = -5V$$

To find current: -

$$I = \frac{V}{R}$$

$$= \frac{-5}{10 \times 1000}$$

$$I = -0.5 \text{ mA}$$


To find power: -

$$P = VI$$

$$P = (-5) (-0.5 \times 10^{-3})$$

$$P = 2.5 \times 10^{-3} \text{ W}$$

Ans:- Circuit:-

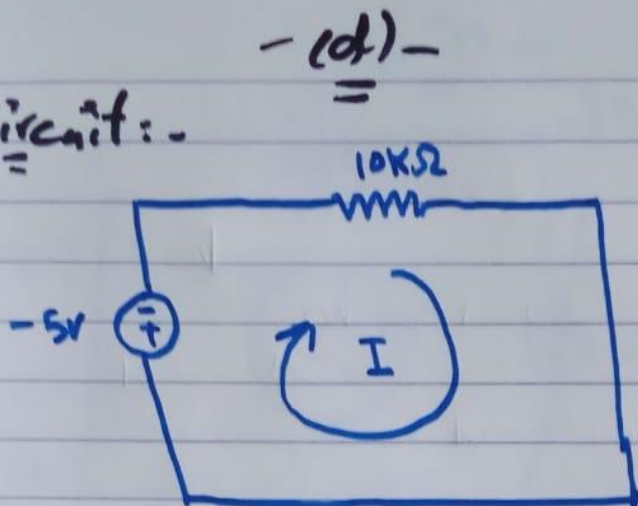

Find current and power:-

Ans:- To find current and power we use KVL rule.

$$(-5V) + V_x = 0$$

$$V_x = 5V$$

To find current:-

$$I = \frac{V}{R}$$

$$I = \frac{5}{10 \times 1000}$$

$$I = 0.5 \text{ mA}$$

To find power:-

$$P = VI$$

$$P = (5)(0.5 \times 10^{-3})$$

$$P = 2.5 \times 10^{-3} \text{ W}$$

Question Number 1

Part (c)

Ans:- 1st Graph :-

By using graph :-

$$\Delta I = 0.05 + 0.05$$

$$\Delta I = 0.1 \text{ A}$$

$$\Delta V = 5 + 5$$


$$\Delta V = 10 \text{ V}$$

$$R = ?$$

$$R = \frac{\Delta V}{\Delta I}$$

$$= \frac{10}{0.1} = 100$$

$$R = 100 \Omega$$

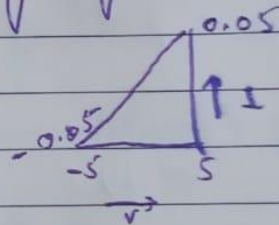

Page #6

2nd Graph

that

By using graph, we see

$$\Delta I = 0$$

$$\Delta V = 10 \text{ V}$$

$$R = \frac{10}{0}$$

$R = \text{undefined}$



3rd Graph

see that

By using graph we

$$\Delta V = 0$$

$$\Delta I = 0.1$$

$$R = \frac{\Delta V}{\Delta I}$$


$$= \frac{0}{0.1}$$

$R = 0 \Omega$

constant



Question Number 2

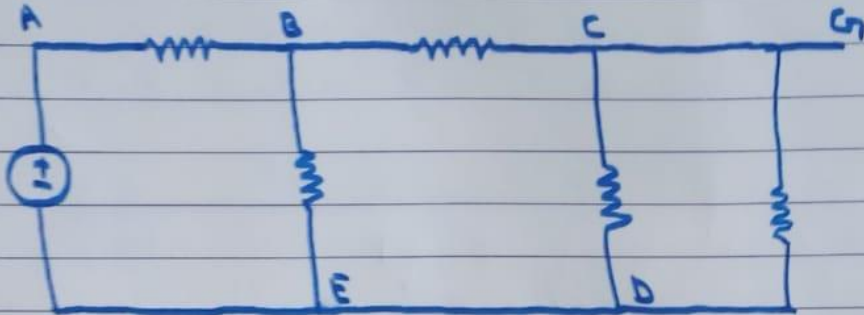


In this circuit:-

- (i) Nodes 4 nodes
- (ii) Elements 6 elements
- (iii) Branches 10 branches
- (iv) - (i) A to b = path

B to D to C to E = path

C to E to D to B to A to C = Loop and path

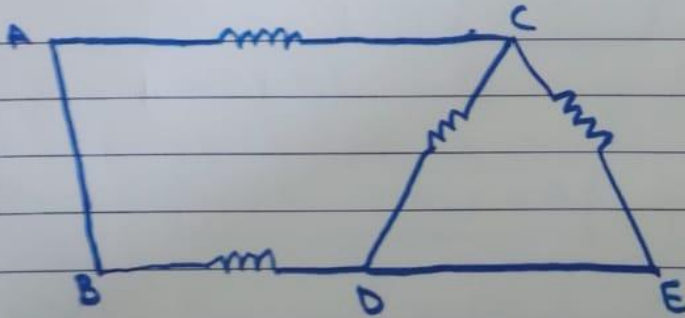C to D to B to A to C to E = Loop and path



In this circuit:-

- (i) nodes :- 4 nodes
- (ii) elements :- 5 elements
- (iii) Branches :- 9 branches

Page # 8

(i) A to b = Path

(ii) B to D to C to E = Path Loop

(iii) C to E to D to B to A to C = ~~Path~~ Loop

(iv) C to D to B to A to C to E = Loop Path



Question Number 2


(b)



Q. No. 2

Question Number 2

(b)

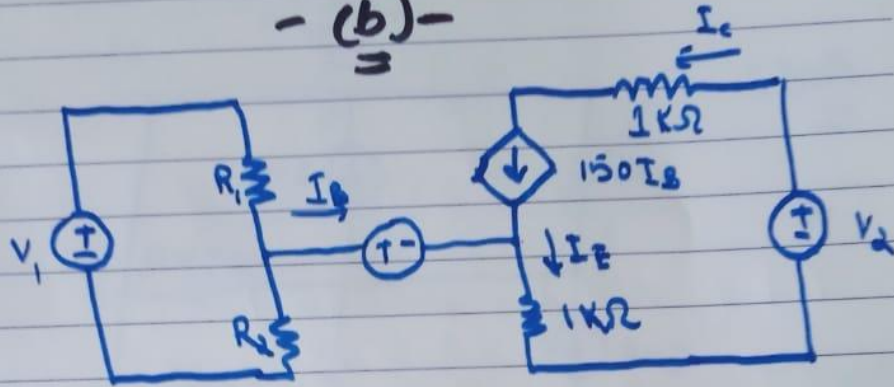

Ans:- I_c is a collector current and I_B is a base current.
So,

$$I_B = 100 \mu A, \quad I_c = ?$$
$$I_c = 150 I_B, \quad I_E = ?$$

$$I_c = I_E + I_B$$

$$150 I_B = I_E + I_B$$

$$149 I_B = I_E$$

$$149 \times 100 \mu = I_E$$

$$I_E = 14900 \mu A$$

$$I_c = 150 I_B$$

$$I_c = 150 \times 100 \mu$$


$$I_c = 15000 \mu A$$



Question Number 3

-(a)-

Ans:-

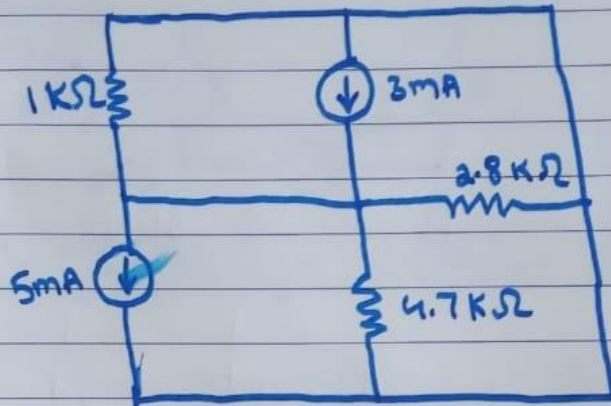

In this circuit diagram we find power.

$$P_1 = I^2 R$$

$$P_1 = (5)^2 (1000)$$

$$P_1 = 25 \times 10^3 \text{ W}$$

$$P_2 = (5)^2 (4.7 \text{ K})$$

$$P_2 = (25) (4.7 \times 1000)$$

$$P_2 = 117.5 \text{ Kw}$$

Total power $P_1 = P_1 + P_2 + P_3$

$$P_3 = (3)^2 \times 2.8 \times 1000$$

$$P_3 = 25.2 \text{ Kw}$$

Total power $P_T = P_1 + P_2 + P_3$

$$P_T = 25 \text{ Kw} + 117.5 \text{ Kw} + 25.2 \text{ Kw}$$

$$P_T = 167.7 \text{ Kw}$$

-(b)-

$$V_1 = I_1 R_1$$

$$V_1 = 5 \text{ KV}$$

$$V_2 = I_2 R_2$$

$$V_2 = 4.7 \text{ K} \times 5$$

$$V_2 = 23.5 \text{ KV}$$

$$V_3 = 3 \times 2.8 \text{ K}$$

$$V_3 = 8.4 \text{ KV}$$

$$P_1 = V_1 I_1$$

$$P_1 = (5 \text{ K})(5)$$

$$P_1 = 25 \text{ KW}$$

$$P_2 = V_2 I_2$$

$$P_2 = 23.5 \text{ K} \times 5$$

$$P_2 = 117.5 \text{ KW}$$

$$P_3 = V_3 I_3$$

$$P_3 = 8.4 \text{ K} \times 3$$

$$P_3 = 25.2 \times 10^3 \text{ W}$$

Question Number 3

-(b)-

Ans:- Find power = $P = ?$
By using circuit diagram.

Let R_1 and R_2 are in parallel.

So,

$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_e} = \frac{1}{3} + \frac{1}{15} = \frac{5+1}{15}$$

$$= \frac{26}{185}$$

$$R_e = \frac{5}{2} \Omega$$

$$R_2 = 6 \Omega$$

Let $R_e = R_1$

Now?

$$R_e = R_1 + R_2$$

$$R_e = \frac{5}{2} + \frac{6}{1}$$

$$\frac{5+12}{2} = \frac{17}{2}$$

$$R_e = \frac{17}{2} \Omega$$

$$V = IR_e$$

$$V = \frac{2}{4} \times \frac{17}{2}$$

$$V = 34V$$

for 15 ohm resistor.

$$V_1 = I_1 R_1$$

$$34 = I_1 \times 15$$

$$\frac{34}{15} = I_1$$

$$I_1 = 2.26A$$

$$P = I^2 R$$

$$P = (2.26)(15)$$

$$P = 76.6W$$