

Power Electronic

Final paper.

Manic Khan

13169 .


Scanned with CamScanner

Question # 1:


Answers:-

Difference b/w Half & full wave Rectifier:-

A half wave Rectifier & full wave Rectifier have significant difference. A rectifier convert AC voltage into Pulsating DC voltage. A half wave rectifier is an electronic circuit which converts only one-half of the AC cycle into pulsating DC. It utilizes only half of AC cycle for the conversion process. On the other hand full wave rectifier is an electronic circuit which converts entire cycle of AC into Pulsating DC. The half wave Rectifier is unidirectional; it means it will allow the conduction in one direction only. That's why it can convert positive half only or negative half only into DC voltage. This is the Reason that it is called Half wave Rectifier. While full wave Rectifier is bi-directional, it conducts for positive half as well as negative half of the cycle. Thus, it is termed as full wave rectifier.

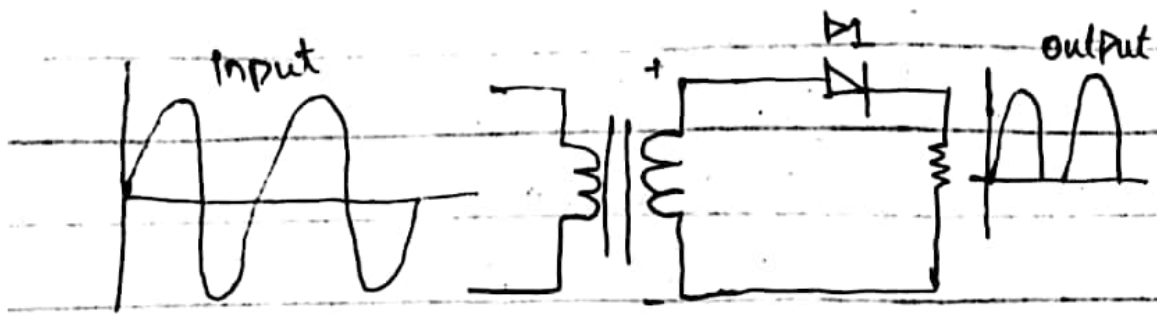

Half wave rectifier.

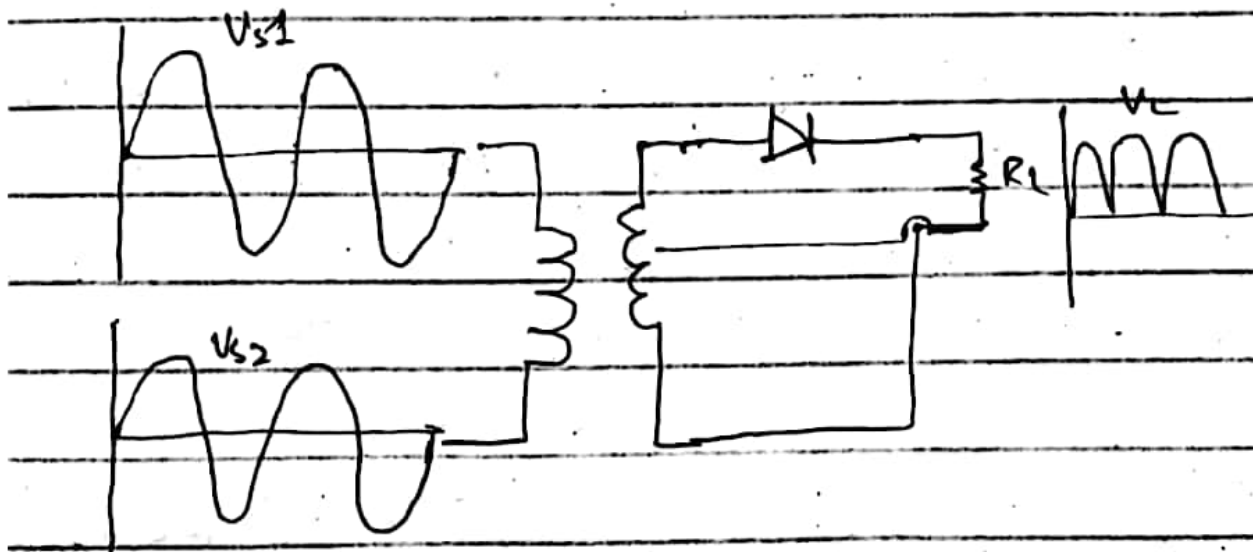

Full wave Rectifier.

Part (2).

Basic rectifier circuits several type of rectifier are available: Single Phase & three phase, half wave & full wave, controll & uncontrolled etc. for a given application, the type used is determined by the requirements of that application. In general the types of rectifiers are

(1) Uncontrolled Rectifier:- Provide a fixed dc output voltage for a given AC supply where diodes are used only.

(2) Controlled Rectifier:- Provides an adjustable dc output voltage by controlling the phase at which the devices are turned ON. Where thyristors & diodes are used.

Q710

Answer:

Given data :-

ID: 13169

$$V_m = 69 \text{ V.}$$



$$R_L = 13 \Omega$$

$$I_m = V_m / R_L = \cancel{69} \cdot 69 / 13$$

$$I_m = 5.30 \text{ A}$$

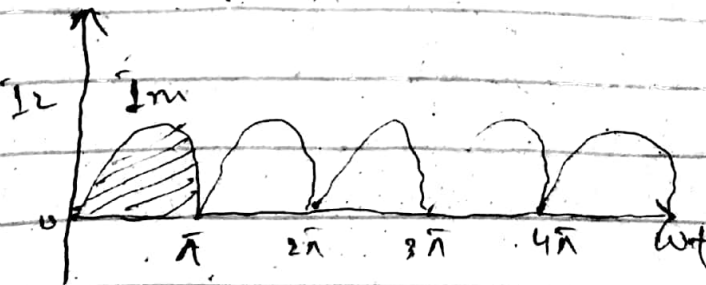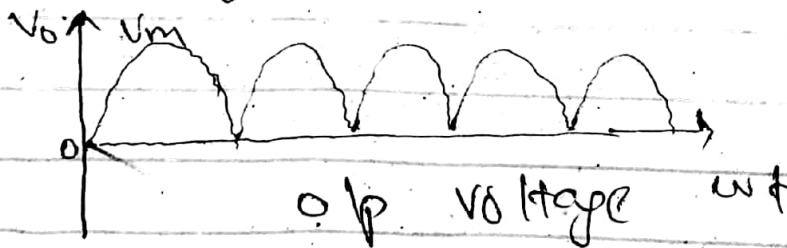(i) $I_{dc} = ?$

first we find I_{dc} in full wave rectification.



\bar{I}_{dc} = area under the load current
over full cycle
Period of cycle.

$$\bar{I}_{dc} = \int_0^{\pi} \frac{I_m \sin \omega t}{\pi} d(\omega t)$$

$$\bar{I}_{dc} = \frac{I_m}{\pi} \int_0^{\pi} \sin \omega t d(\omega t)$$

$$\bar{I}_{dc} = \frac{I_m}{\pi} \left[-\cos \omega t \right]_0^{\pi}$$



$$\bar{I}_{dc} = \frac{I_m}{\pi} [-\cos \pi - (-\cos 0)]$$

$$\bar{I}_{dc} = \frac{I_m}{\pi} [1 + 1]$$

$$\bar{I}_{dc} = \frac{2I_m}{\pi}$$

$$\bar{I}_{dc} = \frac{2I_m}{\pi}$$

$$(3) \quad I_{rms} = ?$$

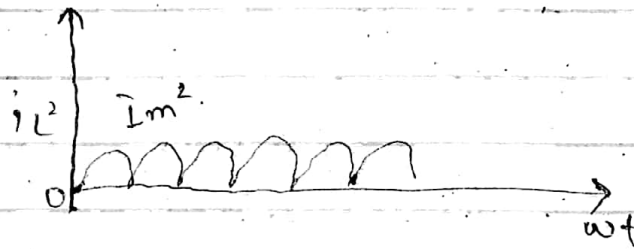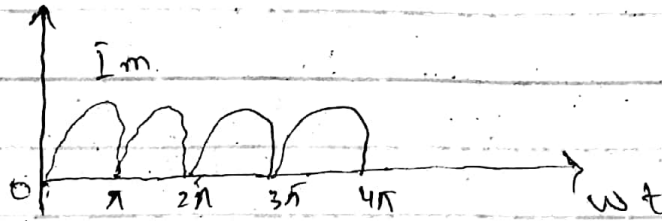

Now

$I_{rms} = \sqrt{\frac{A \cdot \text{sq. of } i \text{ current over full cycle}}{\text{period of the sq. waveform}}}$

$$I_{rms} = \sqrt{\frac{\int_0^{2\pi} I_m^2 \sin^2 \omega t \, d(\omega t)}{2\pi}}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} 2 \sin^2 \omega t \, d(\omega t)}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} 2 \sin (1 - \cos 2\omega t) \, d(\omega t)}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{2\pi}}$$

$$I_{rms} = \frac{I_m^2}{2\pi} \left[\pi - \frac{\sin 2\pi}{2} - 0 + \frac{\sin 2(0)}{2} \right]^{1/2}$$

$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \times \pi}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

Putt the values.

$$I_{rms} = \frac{5.30}{\sqrt{2}} \Rightarrow \boxed{3.74 \text{ A} = I_{rms}}$$

And:

$$V_{rms} = I_{rms} \times R_L$$

$$= \frac{I_m}{\sqrt{2}} \times R_L$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad \text{Putt values}$$

$$V_{rms} = \frac{69}{\sqrt{2}}$$


$$\boxed{V_{rms} = 48.79 \text{ V}}$$

Q.#3 ANSWER


Buck Choppers:-

- 1, \Rightarrow Output voltage is less than i/p voltage.
- 2, \Rightarrow The thyristor in the circuit acts as a switch.
- 3, When thyristor is ON, supply voltage appears across the load.
- 4, When thyristor is OFF, the voltage across the load will be zero.
- 5, Practical arrangement includes an inductor L and diode which are used to eliminate current pulsation providing a smooth DC current.
- 6, With S closed, D is OFF and it remains OFF as long as S is ON.
- 7, The i/p current builds up expanding exponentially and flows through L & Load.
- 8, V_o equal to V_i .
- 9, With S OFF or open, the current through L decays to zero.
- 10, This causes inductive voltage with opposite polarity across inductor (L).

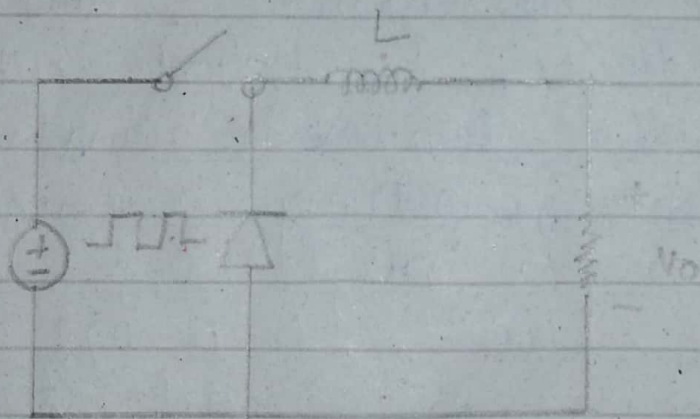- 11) V_2 forward bias diode D.
- 12) Current flows through L & Load & diode D.
- 13) This arrangement permit the use of simple filter Inductance L to provide a satisfactory smooth DC Load Current.
- 14) With high switch frequency, smaller inductance is sufficient to get desired output.



Circuit of Buck Converter.

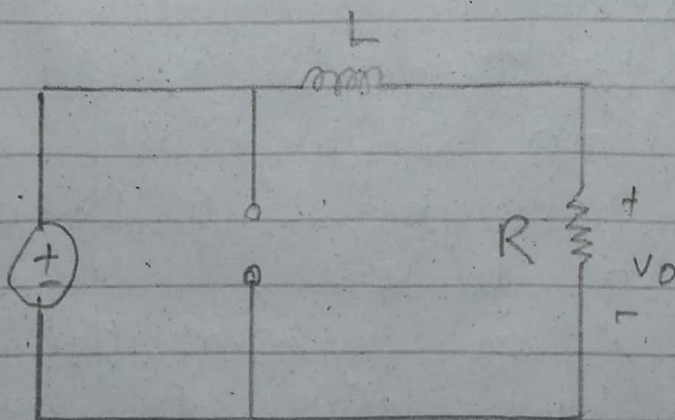

Circuit when closed.

Exam example :

ID : 13169

Given data :

DC source $V_{in} = 50V$

Duty cycle $D = 69\%$

Load of $R = 13 \Omega$
Switching frequency $f = 20 \text{ kHz}$

To find :

1) V_{out} , 2) I_{out} , 3) I_{in} , 4) L ^{incl.}

Solution :

1) V_{out}

We know that

$$V_{out} = L \times V_s \quad \text{OR} \quad D \times V_s \rightarrow (1)$$

Here L is duty cycle,

which $69\% = 0.69$

Putting by (1),

$$(1) \Rightarrow V_{out} = (0.69)(50)$$

$$V_{out} = 34.5 \text{ V}$$

$$2) \bar{I}_{out} = V_o/R \Rightarrow 34.5/13$$

$$\bar{I}_{out} = 2.65 \text{ A}$$

$$3) \bar{I}_{in} = ?$$

∵ we know that.

$$\bar{I}_o = \frac{\bar{I}_i}{2 \cdot D}$$

$$\bar{I}_i = \bar{I}_o \times D = (2.65) (0.69)$$

$$\bar{I}_i = 1.828$$

4) Inductor:

$$L = \frac{\bar{I}_{OFF} \times R}{2}$$

Suppose $\bar{I}_{OFF} = 0.009$

$$L = \frac{0.009 \times 13}{2}$$

$$L = 0.0595 \text{ H}$$

Q4

Boost Chopper:-

=> The output voltage is more than the input voltage by several times.

=> L is used to provide smooth input current.

=> with S ON, the L is connected to the supply.

=> The SCR (S) acts as the switch which works in PWM mode.

=> when S is open, the current passes and energy stored in L is transferred to C through D.

=> The current that was flowing through S now flows through L, D & C to load.

=> Energy stored in inductor is released to load.

$$V_o = V_i + V_L$$

$\Rightarrow V_o$ is always higher than V_i as polarity of inductor voltage V_L is same as V_s .

$$W_{OFF} = (V_o - V_i) * I_i * T_{OFF}$$

\Rightarrow Since losses are neglected, the energy stored transferred during T_{OFF} by L_{min} be equal to energy gained during T_{ON} .

$$W_{ON} = W_{OFF} = V_i I_i T_{ON}$$

$$= (V_o - V_i) * I_i * T_{OFF}$$

$$V_o = V_i \left(1 + \frac{T_{ON}}{T_{OFF}} \right) = V_i \left(\frac{1}{1-d} \right)$$

$$V_i = V_t \left(\frac{1}{1-d} \right)$$

Thus V_i is always greater than V_t .

$$\Rightarrow P_1 = P_0 \rightarrow V_1 \hat{I}_1 = \frac{V_0^2}{R} \Rightarrow \hat{I}_1 = \frac{V_0^2}{V_L} * \frac{1}{R}$$

$$\Rightarrow \hat{I}_0 = \hat{I}_1 * \frac{T_{off}}{T} \Rightarrow \hat{I}_0 = \hat{I}_1 (1-d)$$

$$\Rightarrow P_0 = P_1 \Rightarrow V_1 \hat{I}_1 = \frac{V_0^2}{R} \Rightarrow \frac{V_0^2}{R} = \frac{V_1^2}{(1-d)^2} * \frac{1}{R}$$

$$\Rightarrow \hat{I}_1 = \frac{V_1}{(1-d)^2} * \frac{1}{R}$$

$$\Rightarrow \hat{I}_L = \frac{V_L}{(1-d)^2} * \frac{1}{R}$$

$$\Rightarrow \hat{I}_L = \frac{\hat{I}_{max} + \hat{I}_{min}}{2} = \hat{I}_1$$

$$\Rightarrow \hat{I}_{max} + \hat{I}_{min} = 2 * \hat{I}_1$$

\Rightarrow Voltage across L is;

$$V_L = V_1 = L * \frac{di}{dt}$$

$$\Delta \hat{I}_1 = \frac{V_1}{L} * T_{on}$$

Example:

Given data:

$$ID = 13169$$

$$V_{in} = 50 \text{ V.}$$

$$D \cdot \text{cycle} = D = 0.69 \quad \left. \begin{array}{l} 69\% \\ \downarrow \end{array} \right\}$$

$$\text{Resistor} = R = 13$$

$$\text{frequency} = f = 20 \text{ kHz.}$$

Soln:

1)

$$V_{out} = V_i \left(\frac{1}{1-d} \right)$$

$$= 50 \left(\frac{1}{1-0.69} \right) \Rightarrow \frac{50}{0.31}$$

$$V_{out} = 161.29 \text{ V}$$

2)

$$I_{out} = ?$$

$$I_o = I_i (1-d) \quad \text{--- (1)}$$

$$I_i = \frac{V_i}{(1-d)^2} \times \frac{1}{R} \Rightarrow \frac{50}{(1-0.69)^2} \times \frac{1}{13}$$

$$I_i = \frac{50}{0.0961} \times \frac{1}{13}$$

$$I_i = 40.022 \text{ A}$$

Put in (1).

$$I_{out} = I_1 (1 - d)$$

$$I_{out} = 40.022 (1 - 0.69)$$

$$I_{out} = (40.022) (0.31)$$

$$I_{out} = 12.406 \text{ A.}$$

Q45

Answer:

Buck-Boost Chopper:

=> It combines the concept of both step-up & step down.

=> The output voltage is either higher or lower than input voltage.

=> The output voltage polarity also be reversal.

=> The switch is either an SCR or GTO or IGBT.

=> when S is OFF, the source is disconnected.

=> with S = ON (T_{ON}), $I_{NOV} = V_1 * I_1 * T_{OFF}$

=> with S = OFF (T_{OFF});

$$I_{NOFF} = V_1 * I_1 * T_{OFF}$$

⇒ Ignoring Losses:

$$P_{ON} = P_{OFF} = V_g * \bar{I}_1 * T_{ON}$$

$$\Rightarrow V_g * \bar{I}_1 * T_{OFF}$$

$$\Rightarrow V_o = V_g \frac{dt}{(1-d)T} \Rightarrow V_o \frac{d}{(1-d)}$$

$$\bar{I}_L = \frac{I_{max} + I_{min}}{2}$$

$$I_1 = I_L d = \left(\frac{I_{max} + I_{min}}{2} \right) * d$$

The average input power

$$P_1 = V_g \bar{I}_1$$

$$= \left(\frac{I_{max} + I_{min}}{2} \right)$$

$$* d \Rightarrow P_o = \frac{V_o^2}{R}$$

$$I_{max} - I_{min} \Rightarrow \frac{V_i}{L} T_{ON}$$

Again $I_{max} + I_{min} = 2 * \bar{I}_1$

Now

$$I_{max} = V_g \left[\frac{1}{R(1-d)^2} + \frac{T_{ON}}{2L} \right]$$

$$I_{\min} = V_g \left[\frac{1}{R(1-d)^2} - \frac{T_{ON}}{2L} \right]$$

$$I_{P-D} = I_{\max} - I_{\min} = \frac{V_i T_{ON}}{L}$$

For continuous current mode.

$$I_{\min} = V_g \left[\frac{1}{R(1-d)^2} - \frac{T_{ON}}{2L} \right]$$

$$\Rightarrow \frac{1}{R(1-d)^2} = \frac{T_{ON}}{2L}$$

$$L = \frac{RT_{ON}}{2} (1-d)^2$$