

**NAME**                      **RAFI UD DIN**  
**ID**                            **12401**

**Department of Electrical Engineering**

**Assignment**

**Date: 24/06/2020**

---

**Course Details**

**Course Title:**    Electronic Circuit Design                      **Module:**                      04  
**Instructor:**     Sir Mujataba ihsan                                      **Total Marks:**            50

---

**Student Details**

**Name:**                      RAFI UD DIN    **Student ID:**            12401

---

Q1.	(a)	<b>Discuss</b> the darlington connection for multistage amplifiers.	Marks 05+10
	(b)	The input of a certain regulator increases by 4.5 V. As a result, the output voltage increases by 0.062 V. The nominal output is 40 V. <b>Evaluate</b> the line regulation in both % and in %/V	CLO 2
Q2.		<b>Explain</b> Colpitts and Hartley oscillators.	Marks 10
			CLO 2
Q3.	(a)	<b>Describe</b> the idea behind class B amplifiers.	Marks 06+06
	(b)	<b>Explain the</b> types of voltage regulators and their purposes.	CLO 2
Q4.		<b>Explain</b> the working of Flash ADC.	Marks 05
			CLO 2
Q5.	(a)	<b>Differentiate</b> between the following: Low pass & high pass filters	Marks 04+04
	(b)	Active and passive filters	CLO 2

QNo1

a) Discuss the darlington connection for multistages amplifiers.

Ans: Multistage Amplifiers:-

Two or more amplifiers can be connected to increase the gain of an AC signal. The overall gain can be calculated by simply multiplying each gain together.

$$A_v = A_{v1} A_{v2} A_{v3} \dots$$

### DARLINGTON CONNECTION:-

The main feature is that the composite transistor act as a single unit with a circuit gain that is the product of the current gains of the individual transistors.

- It provide high current gain than a single BJT
- The connection is made by using two separate transistor having current gain of  $\beta_1$  and  $\beta_2$


So the current gain

$$\beta_D = \beta_1 \beta_2$$

$$\text{If } \beta_1 = \beta_2 = \beta$$

The Darlington connection provides a current gain of

$$\beta_D = \beta^2$$

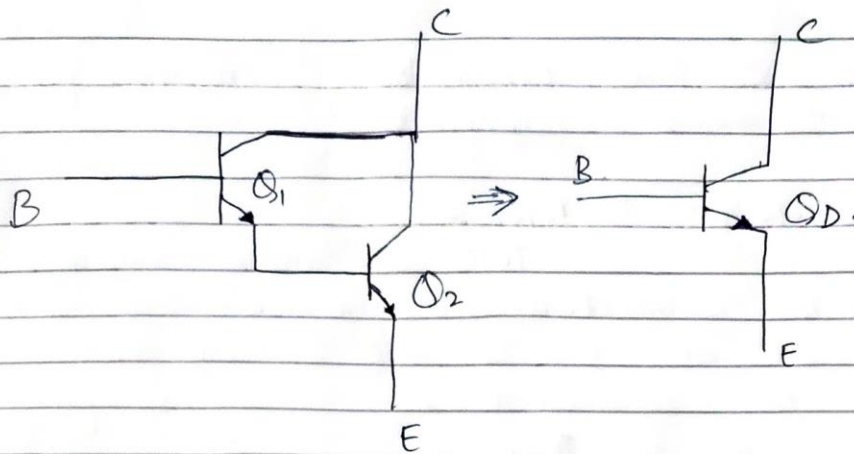

Darlington transistor

Part (b) The input of the certain voltage regulator increase by 4.5 V as a result the output voltage increased by 0.062 V the nominal output is 40 V evaluate line regulation in both % and in %/V

Sol:-

$$\text{Line Regulation} = \frac{0.062 \times 100\%}{4.5}$$

$$= 1.377\%$$

and

$$\text{Line Reg} = \frac{0.062}{40} \times 100$$


$$\frac{4.5}{4.5}$$

$$= 0.034\% / V$$

Q.No2:- Explain Colpitts and Hartley Oscillator.

Ans:- Hartly Oscillators:-

It is an electronic oscillator circuit in which the oscillation frequency is determined by a tuned circuit consisting of capacitors and inductors that is an LC oscillator. The distinguishing feature of the Hartley oscillator is that the tuned circuit consists of a single capacitor in parallel with two inductors in series (or a single tapped inductor) and the feedback signal needed for oscillation is taken from the center connection of the two inductors.

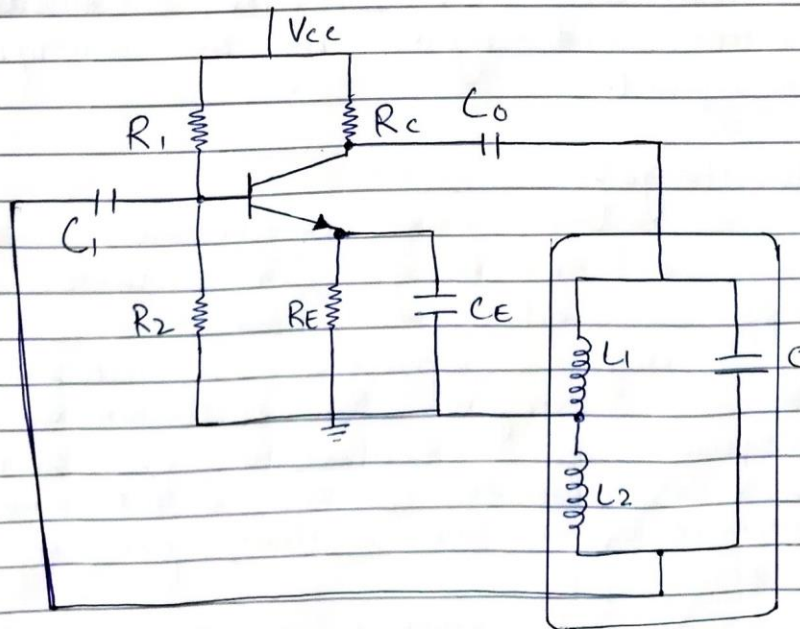

The circuit diagram of a Hartley Oscillator consist of single stage inverting amplifier and LC phase shift network. The phase shift network consist of two series inductors  $L_1$  and  $L_2$  connected in parallel to a capacitor  $C$ . The output of the amplifier is applied across inductor  $L_1$  and the voltage across the inductor  $L_2$  from the feedback voltage the coil  $L_1$  is inductively coupled to coil  $L_2$  the combination functions as an auto-transformer.

Resistor  $R_1$  and  $R_2$  gives a potential divider bias for the transistor  $Q$  and parallel combination of  $R_e$  and  $C_e$  provide terminal stability and bypass by the amplified AC signal.

### Advantages:-

- Very few components are needed including two inductors or tapped coil.
- By using a variable capacitor or by varying the inductance frequency of oscillation can be varied.
- The amplitude of the output remain constant over the working frequency range.

### Disadvantage:-


The output is rich in harmonics and therefore not suitable where a pure sin wave is required.

Applications:-

- Used a local oscillation in radio receiver.
- It is suitable for Oscillations in RF range upto 30MHz

COLPITTS Oscillator:-

The electronic circuit that produces periodically oscillating electronic signal such as sine wave square wave or any other wave is termed as electronic oscillator. Oscillator can be classified into different types generally based on their output frequencies. Electronic oscillator can be termed as voltage controlled oscillators as their frequency of oscillation can be controlled by their input voltage.

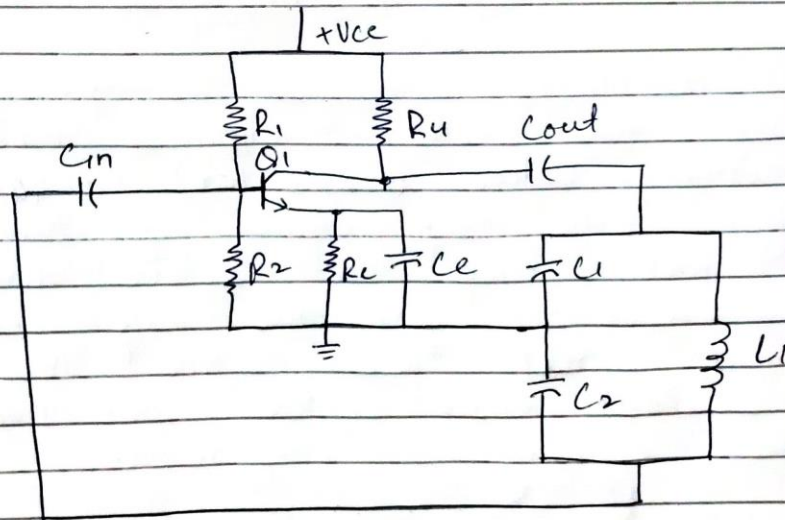

## Applications of Colpitts Oscillator

- It is ~~used~~ used for generation of sinusoidal output signal with very high frequency.
- It frequently used for the application in which very wide range of frequencies are involved.
  - Used for applications in which undamped and continuous oscillation are desired for a function.
  - It used for ~~mobile~~ the development and radio communication.

QNo3

a) Describe the idea behind the class B amplifiers.

Class B amplifier is the type of the power amplifier where the active device (transistor) conduct only for one half cycle of the input signal since the active device is switched off for the half for the input signal the active device dissipates less power and hence the efficiency is improved.

page 7

## Advantages and disadvantages of class B.

### Advantages:

- Very low standing bias current. Negligible power consumption with out signal.
- Can be used for much more powerful outputs than class A
- More efficient than class A.

### Disadvantages:

- It creates crossover distortion.
- Supply current changes with signal stabilised supply may be needed
- More distortion than class A.

QNo3 b) Explain the type of voltage regulator and their purpose.

Ans Voltage regulator:-

It is used to regulate a voltage levels. When a steady reliable voltage is needed then the voltage regulator is the preferred device it generates a fixed output voltage that remain constant for any changes in an input voltage or load condation. It acts as a buffer for protecting components for damage.



The main two types:

Linear voltage regulator  
Switched voltage regulator

The purpose of the voltage regulator is to keep the voltage in a circuit relatively closed to desired value. Voltage regulator is one of the most common electronic component since a power supply frequently produces raw current that would otherwise damage one of the component in the circuit.

Q No 4:

Explain the working of ~~Flash~~ Flash ADC.

Ans. Analog voltage is applied to non inverting terminals for all comparators using a single line. Reference voltage is applied to inverting terminals of comparator using ~~direct~~ divider circuit.

Each comparator produces digital output in the form of 0 or 1. If unknown analog voltage is greater than reference voltage comparator produces high logic. If analog voltage is less than reference voltage then comparator produces low logic i.e.

Thus all the parallel comparator produces digital representation of analog voltage in the form of zeros and ones. The encoder converts these zeros and ones into binary number and produces digital binary output.

e.g. when unknown voltage is 5 that is lies between 4.375 & 5.625 is applied to the flash ADC first four encoder produces output 1 and the last three encoder produces output 0 encoder convert this 1111000 comparator output into 100 binary number as digital output.

Q No 5:- Differentiate between the following.

a) Low pass and high pass filter.

Ans:- Low pass

It is the circuit which allows the frequency below the cut off frequency to pass through it.

→ It consist of resistor followed by capacitor

→ It is significant in removing aliasing effect.

high pass.

It is a circuit which allows the frequencies above cut off frequency to pass through it.

It consist of capacitor followed by resistor.

It's significant when the distortion due to low frequency signal such as noise is to be removed.

→ operating frequency is lower than the cut off frequency.

operating frequency is higher than cut off frequency.

→ It used in communication circuit as anti aliasing filter.

It used in audio amplifiers low noise amplifiers etc.

Q No 5

b) Active and passive filter.

Ans: Active:-

Active filter are those filter circuit that are designed using transistor and op-amp as their basic components along those element circuit of active filters also contain resistor and capacitor but not inductor. The active filter circuit use transistor and op-amp to pass only the selective band of frequency while attenuating rest of the frequency.

PASSIVE FILTER:-

Passive filter are the filter that are formed using only resistor inductor and capacitor as their major components. As no amplifying element is present in it thus passive filter offer low signal gain.