

Name : ~~#~~ Syed Daniyal Shah

ID # 15863

Paper # LCA

Date 24/09/2020

Q NO :-> 01


~~Part~~

Required $V_{AB} = ?$

Sol :->

Using Superposition theorem

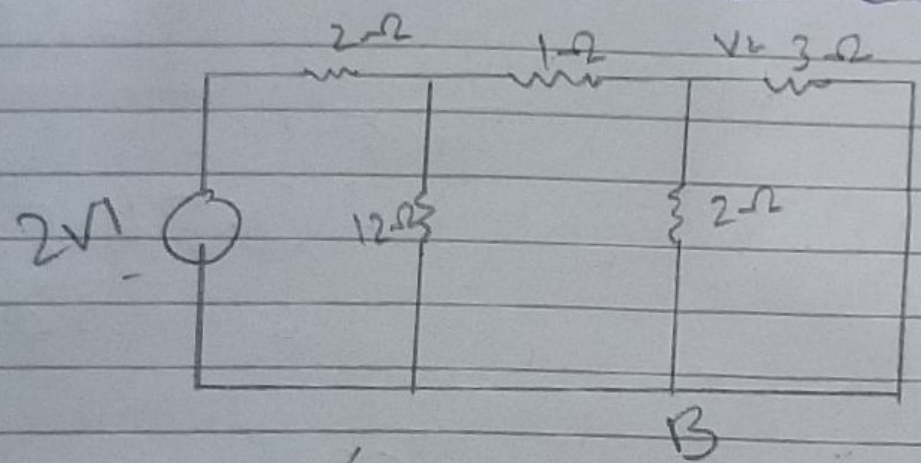Suppose downe 2v Source &
4v is short ckt.



$V'_{AB} = ?$

Using Nodal Analysis.

$$V_1 = \frac{V_1 - 2}{2} + \frac{V_1}{12} + \frac{V_1 - V_2}{1} = 0$$

$$19V_1 - 12 + V_1 + 12V_1 - 12V_2 = 6$$

$$19V_1 - 12V_2 = 12 \rightarrow \text{✓}$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2}{3} = 0$$

$$6V_2 - 6V_1 + 3V_2 + 2V_2 = 0$$

$$-6V_1 + 11V_2 = 0$$

$$V_2 = \frac{6V_1}{11} \rightarrow \text{put in } \textcircled{1}$$


$$19V_1 - 12 \left(\frac{6V_1}{11} \right) = 12$$

$$V = 0.9635V$$

$$V_2 = 0.525547V$$

$$V'_{AB} = V_2 - 0 = 0.5225V$$

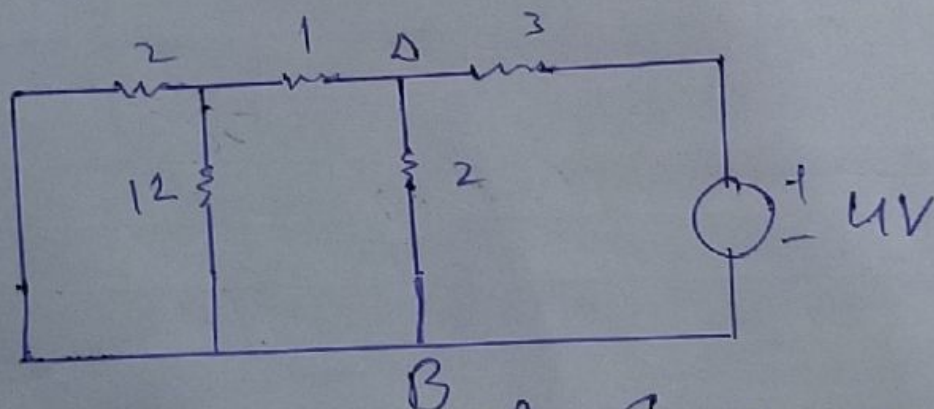Now 2V is short circuit
 and 4V is emf as source




After parallel & source
 Simplification

$$R_{12} = 2 \parallel 12$$

$$R_{123} = 2 \parallel 12 + 1$$
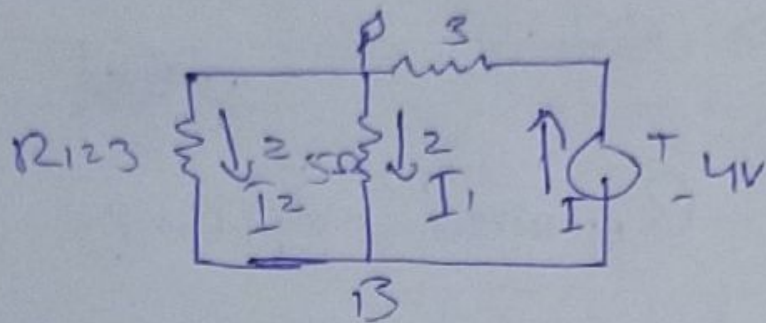
$$R_{123} = 1.5 + 1 = 2.5 \Omega \quad \text{Page no 3}$$



$$V'_{AB} = I_1 (2) \rightarrow \text{A}$$

$$I = \frac{4}{2.5 + 2 + 3} = \frac{4}{4.111} = 0.9725 \text{ A}$$

Using current division Rules.

$$I_1 = \left(\frac{2.5}{2 + 2.5} \right) I = 0.5405 \text{ A}$$

$$V'_{AB} = I_1 (2) = (0.5405) (2) = 1.081 \text{ V}$$

So



Net voltage

$$V_{AB} = V_{AB} + V'_{AB} = 0.5225 + 1.081 \text{ V}$$

$$V_{AB} = 1.6035 \text{ V}$$

Page No 04

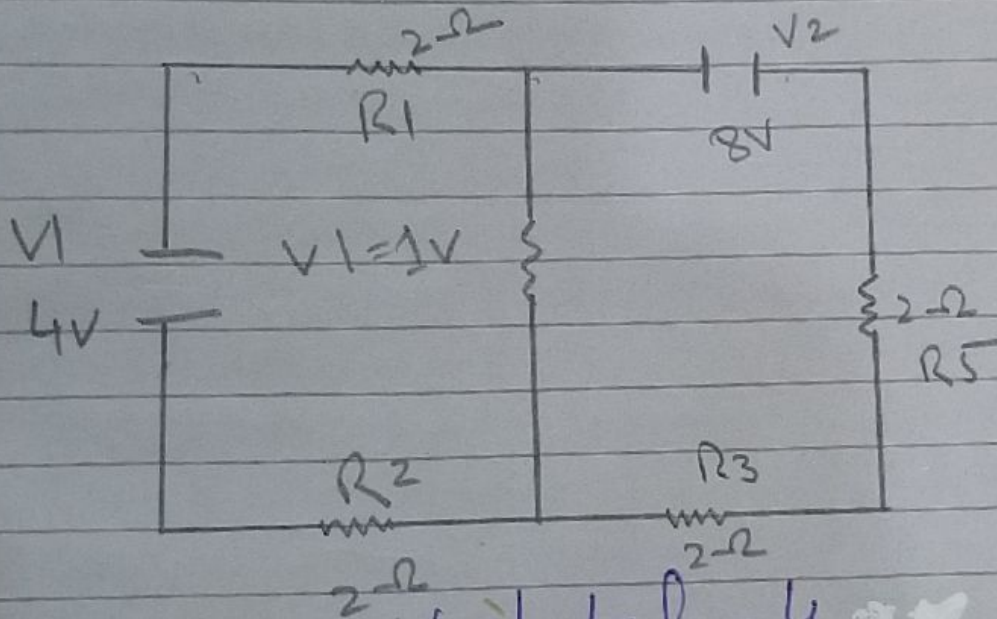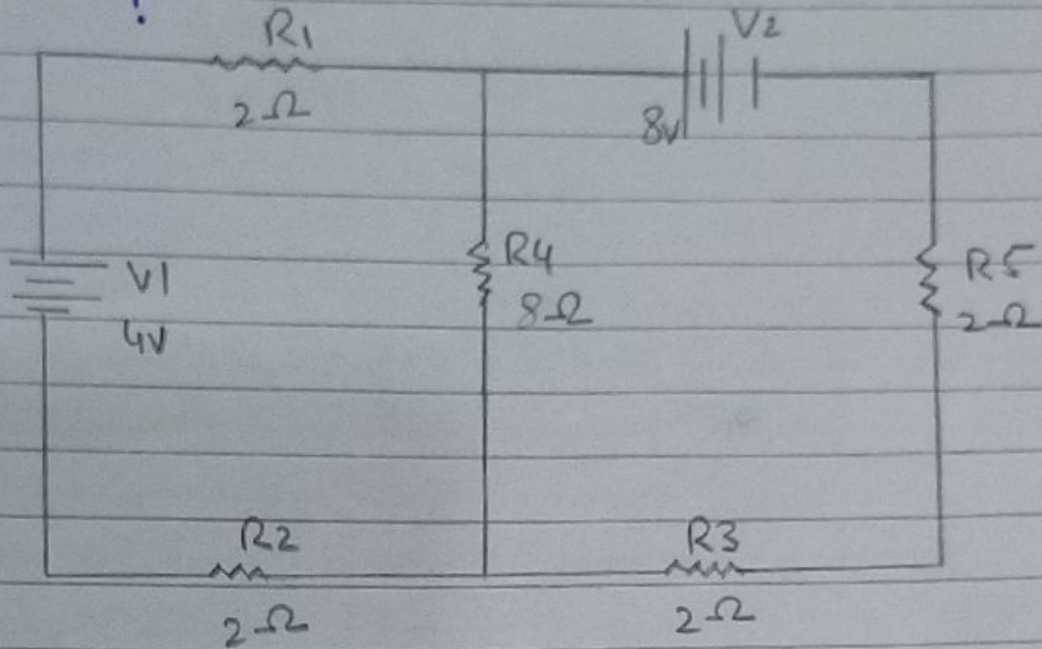Q NO \rightarrow 2 Find the current in 8Ω Resistor using Thevenin's theorem?



$$V_{\text{total}} = 4$$

$$R_{\text{total}} = 8$$

$$I = \frac{V}{R} \quad (= V = IR)$$

$$I = \frac{4}{8} = 0.5A$$

$$V_1 = 1 \text{ V}$$

$$V_2 = 1 \text{ V}$$

$$V_3 = 1 \text{ V}$$

$$V_4 = 1 \text{ V}$$

$$\frac{1}{R} = \frac{1}{1} + \frac{1}{4}$$

$$\frac{4+1}{4} = \frac{5}{4}$$

$$= \frac{4}{5}$$

$$V_{TH} = 6 \text{ V}$$


$$R_{TH} = 2 \Omega$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{1+1}{4} = \frac{2}{4}$$

$$\frac{1}{R} = \frac{1}{2}$$

$$R = 2 \Omega$$

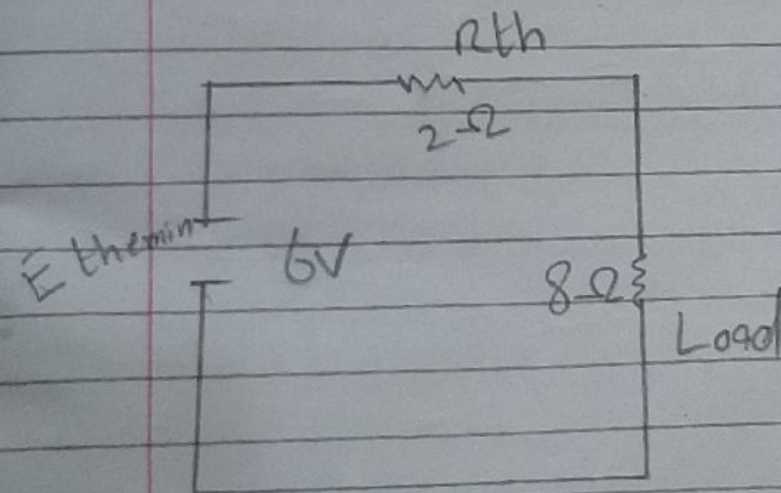


$$V = IR$$


$$I = \frac{V}{R} = \frac{6 \text{ V}}{10} = 0.6 \text{ A}$$

$$I = 0.6 \text{ A}$$

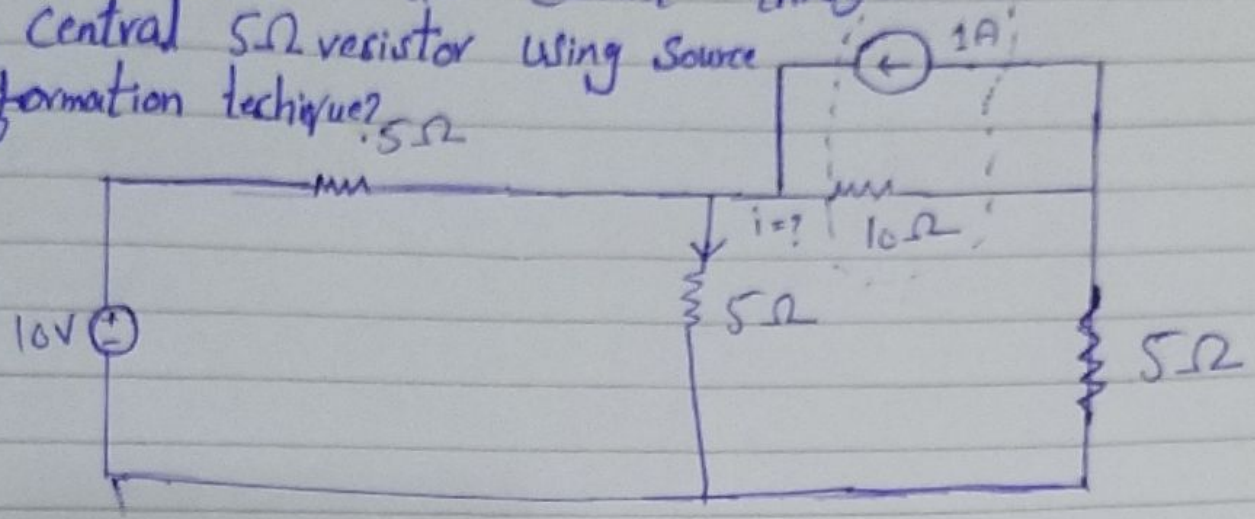
Q No: \rightarrow 3 Find the current through the central 5Ω resistor using source transformation technique?




Sol: \rightarrow

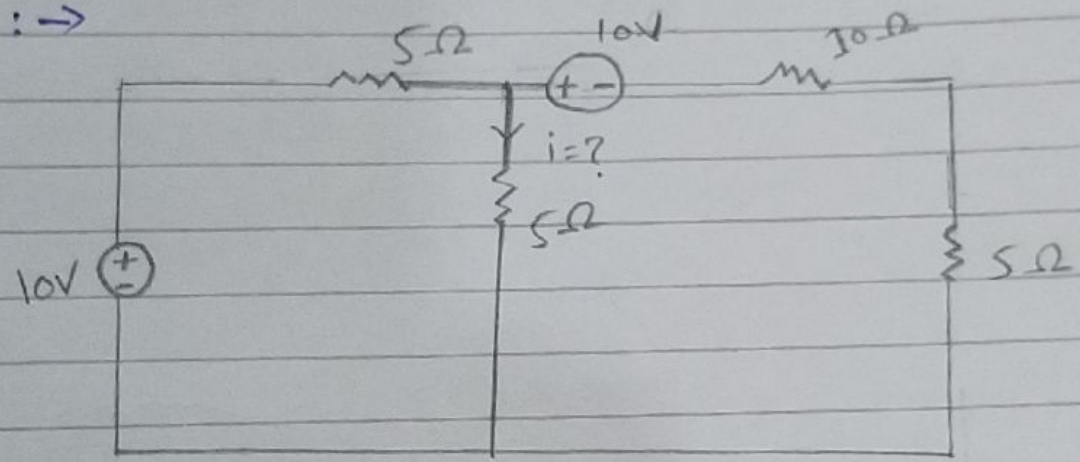

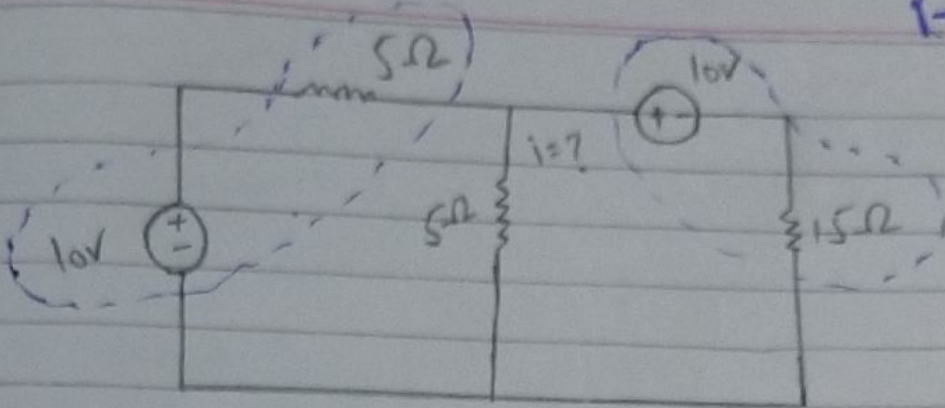Note that the +ve terminal of the 10V source is placed to the left because the current source arrow was pointing to the left.




$I = 10/5 = 2A$

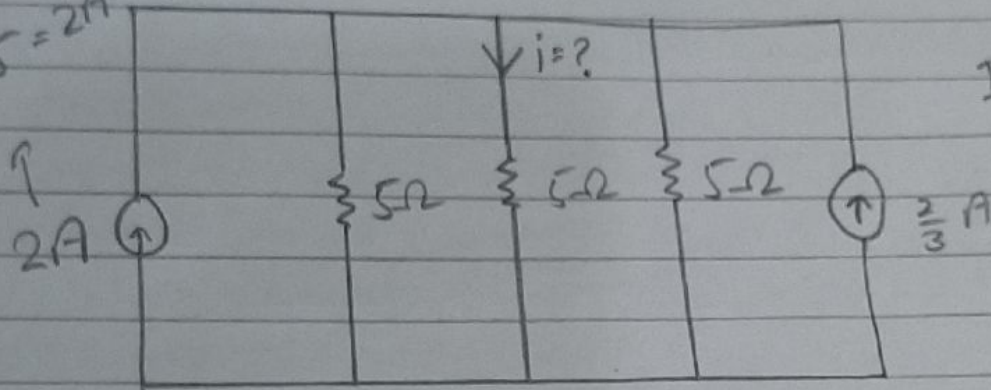

$I = 10/15 = 2/3 A$

$2 \times 2/3$

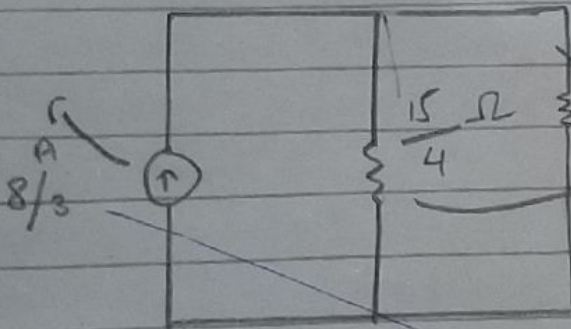


$\frac{3+1}{15} = \frac{4}{15}$

$\frac{1}{R_{eq}} = \frac{1}{15} + \frac{1}{5}$

$R_{eq} = \frac{15}{4} \Omega$

$8/3 \times 15/4 = 10V$

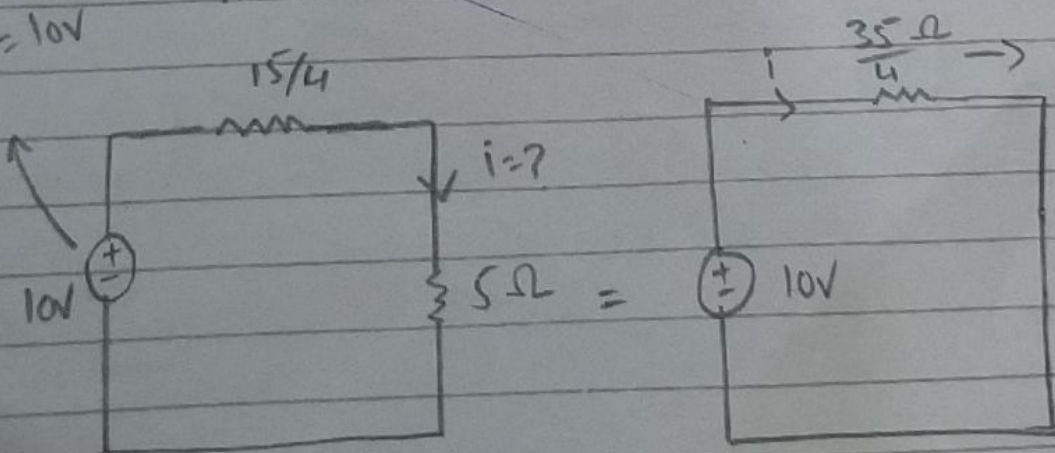

$15/4 + 5 = \frac{15+20}{4}$

$\frac{15+20}{4}$



Page NO 08

$$i = \frac{10}{\frac{35}{4}} = \frac{10 \times 4}{35} = \frac{8A}{7}$$

Q NO: \rightarrow 4

(Part A)

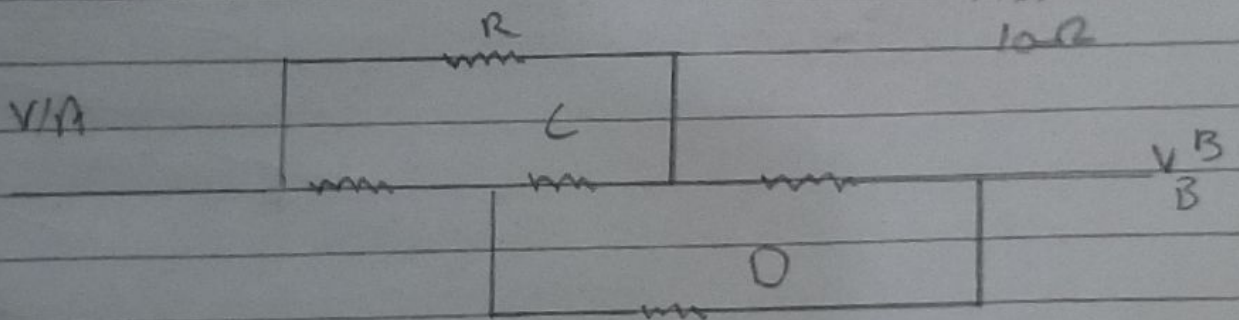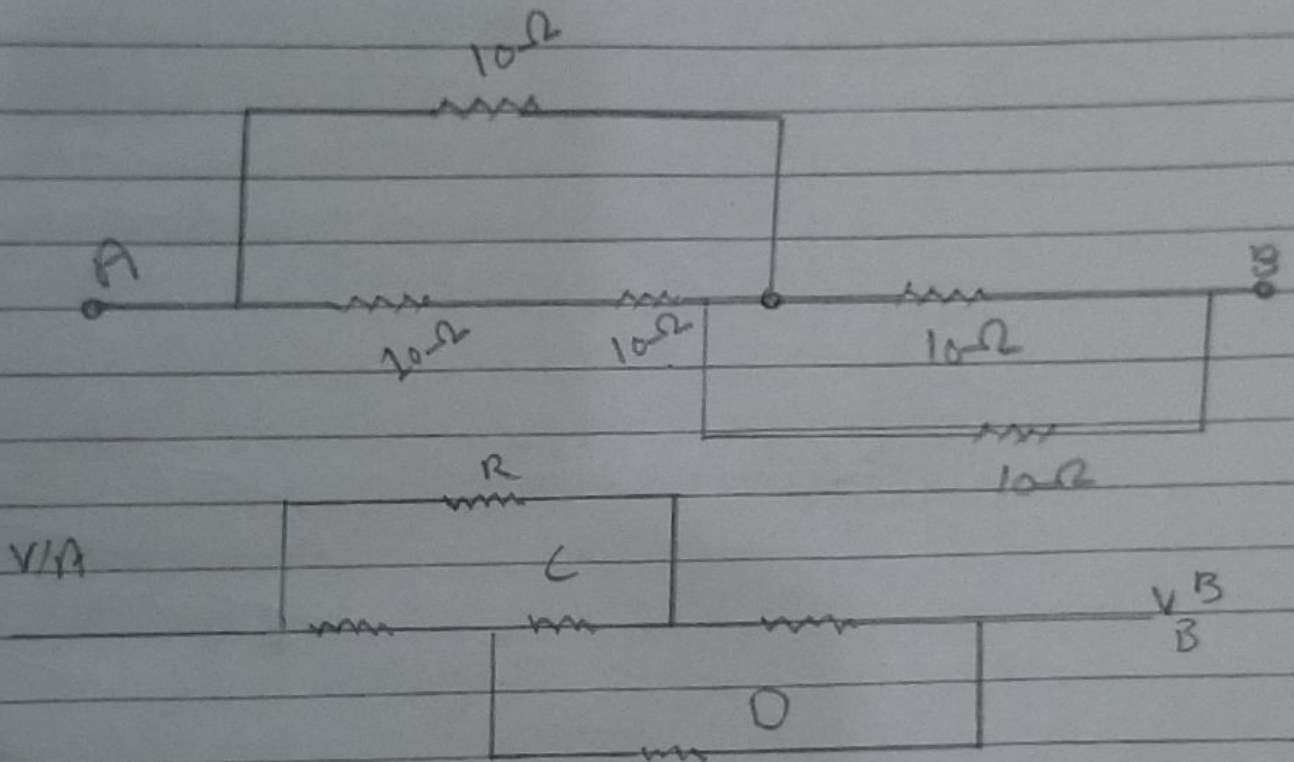
(a) Calculate the resistance between terminal A and B for the circuit shown below:




$A = V_A$

$B = V_B$

all have same values R

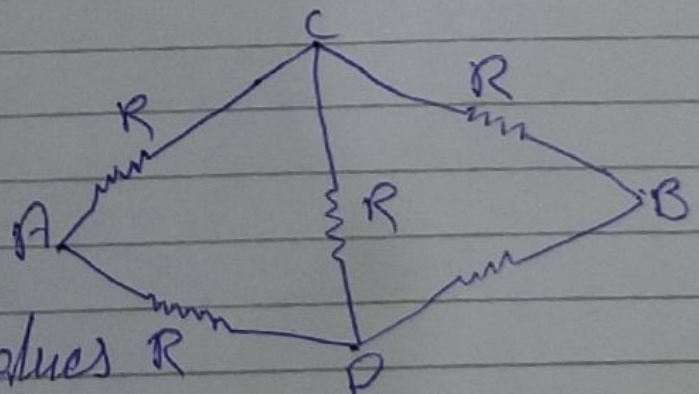

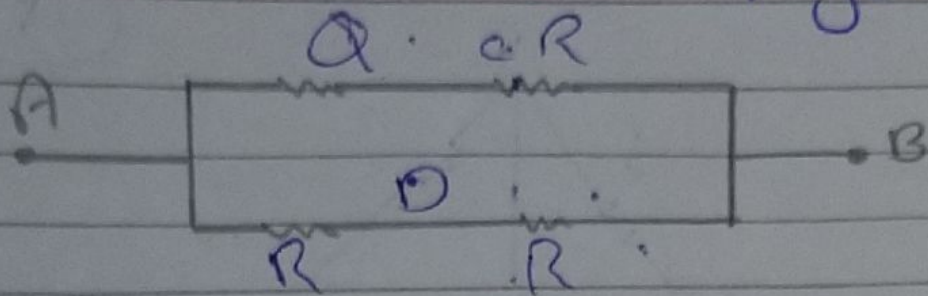


$$R_{eq} = \frac{2R \times 2R}{2R + 2R} \Rightarrow \frac{2(10) \times (2(10))}{2(10) + 2(10)}$$

$$R_{eq} = R$$

Q No 4 \rightarrow part B



Ray = ?

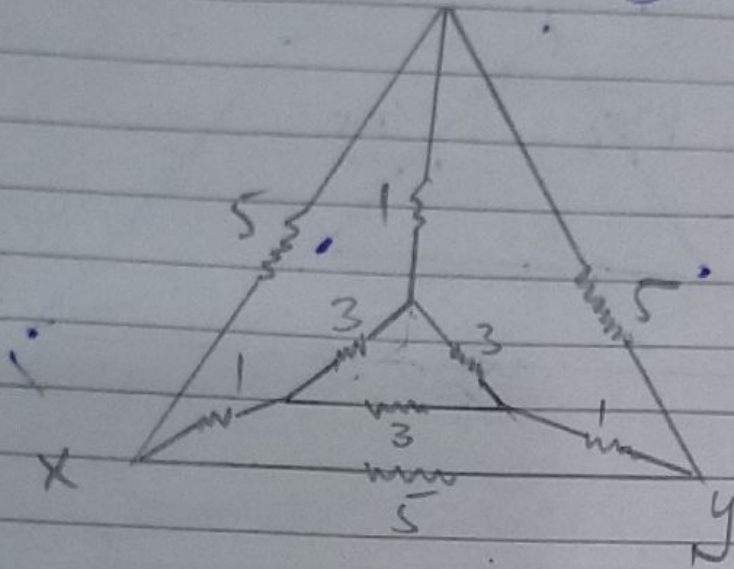


$$R_1 = \frac{3 \times 3}{3 \times 3 \times 3} = \frac{9}{9} = 1$$


$$R_2 = 1$$

$$R_3 = 1$$

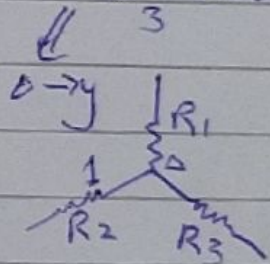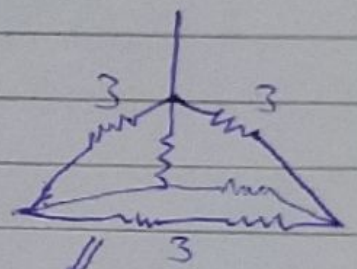

Put in cut (A)

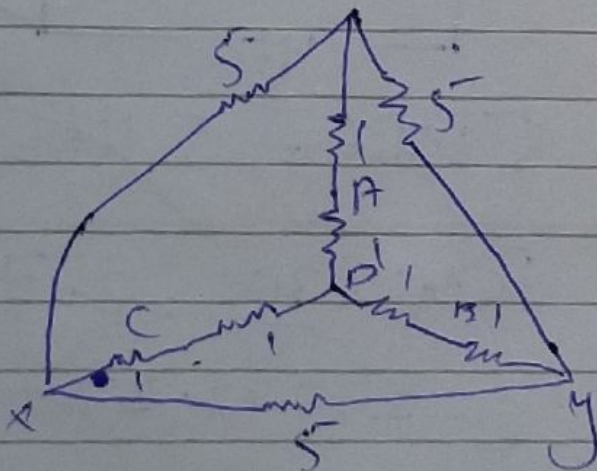

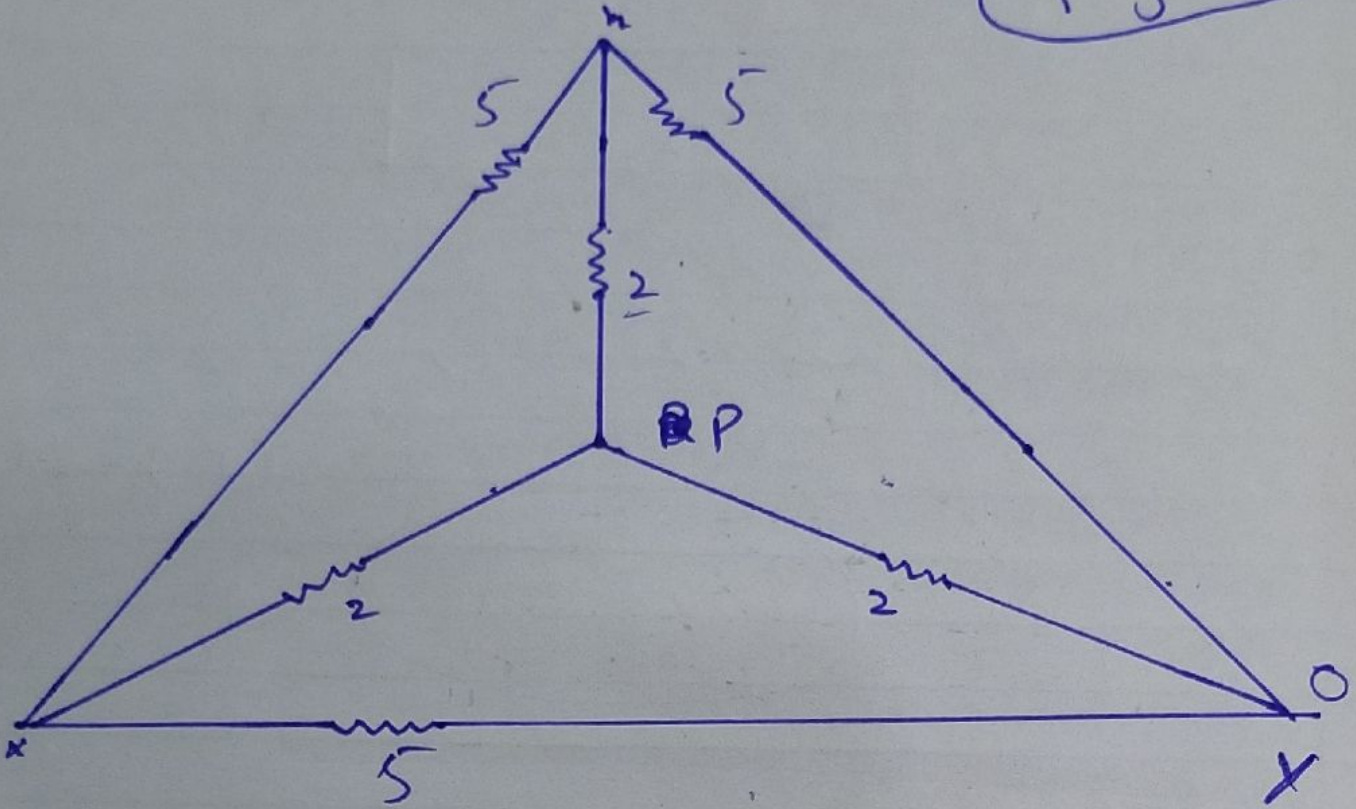


$$R_4 = 2 + 2 + \frac{2 \times 2}{2}$$



$$R_4 = 4 + 2 = 6x$$

$$R_5 = 4 + 2 = 6x$$

$$R_6 = 6n$$

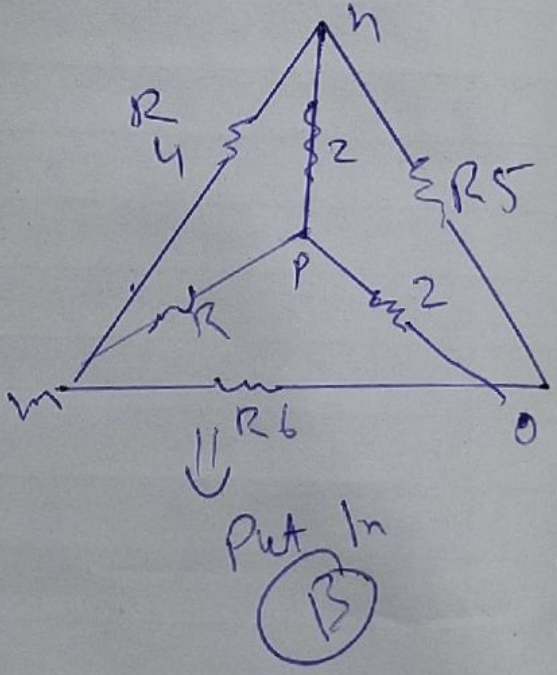


Page No 13

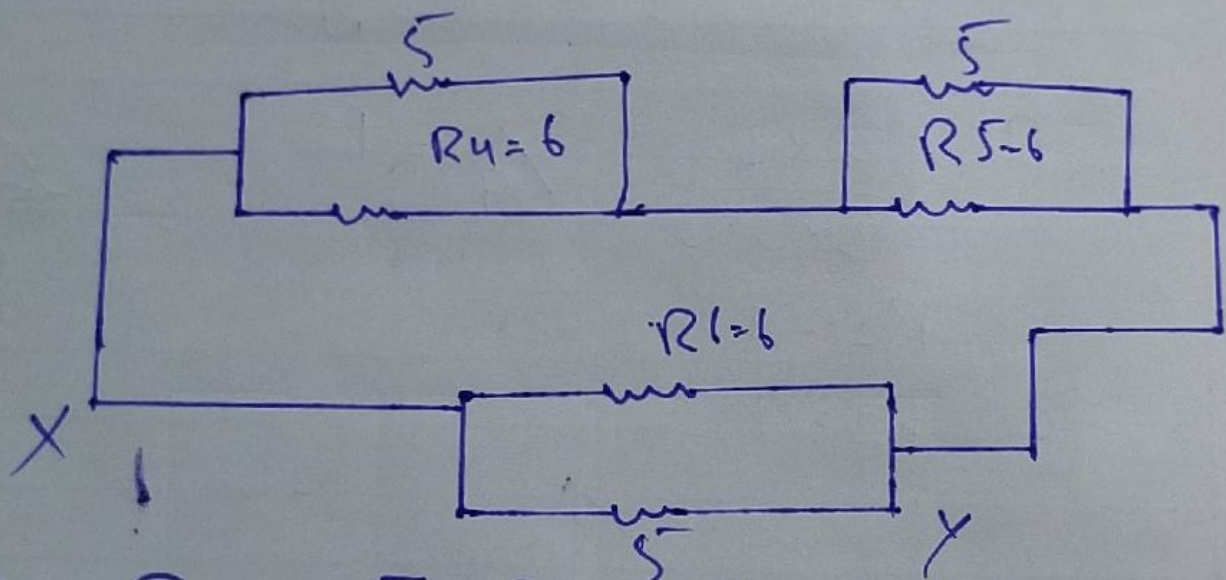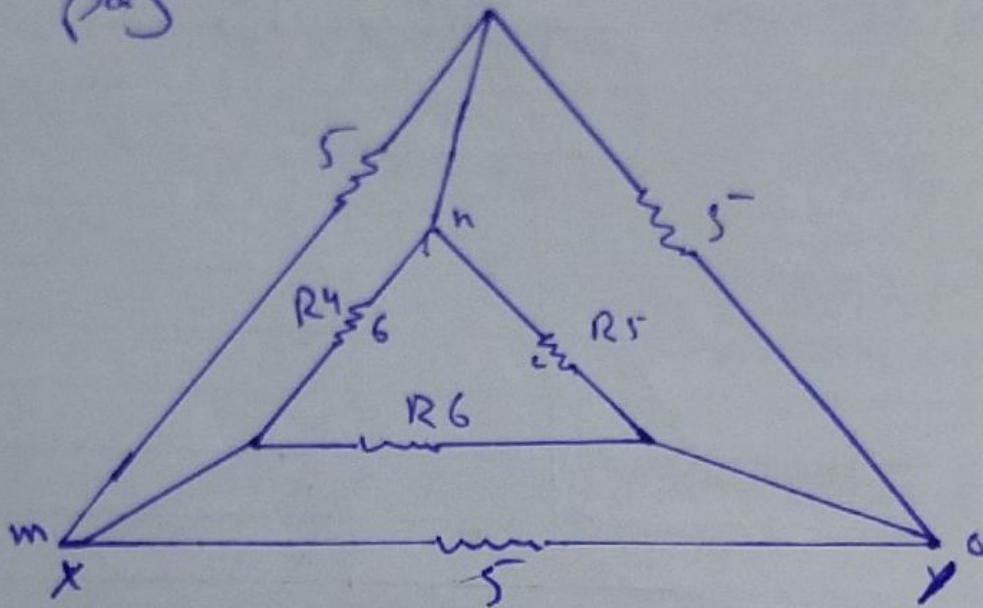


So $R_{eq} = 5 \parallel R6 = 5 \parallel 6 = \frac{5 \times 6}{5 + 6} = \frac{30}{11}$

$R_{eq} = \frac{30}{11} = 2.727 \Omega$

$2.727 + 2.727$

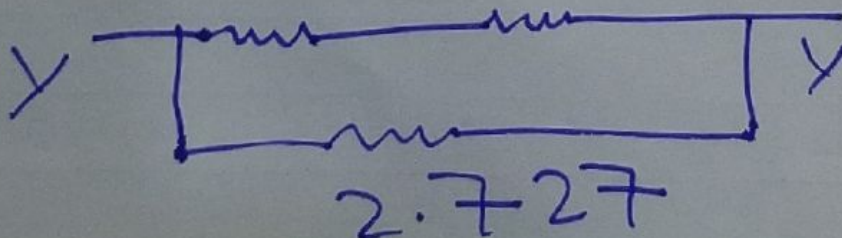

$$5.45\Omega$$

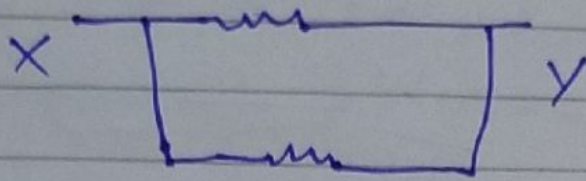

$$2.725\Omega$$

$$\frac{1.81717\Omega}{\text{resistor symbol}} = \frac{5.45 \times 2.725}{5.45 + 2.725}$$

$$R_{\text{eq}} = Z_{\text{ny}} = 1.81717\Omega$$