



NAME: AMIT SINGH
ID: 15478

SUBJECT: DIGITAL LOGIC DESIGN

SEMESTER: 3RD

PROGRAMME: BS (SOFTWARE ENGINEERING)

HALF ADDER

AIM: Design and verify the logic circuit of Half adder using logic gates.





OBJECTIVES: • To understand the principle of binary addition. • To understand half adder concept. • Use truth table and Boolean Algebra theorems in simplifying a circuit design. • To implement half adder circuit using logic gates

PROCEDURE: 1. collect the components necessary to accomplish this experiment. 2. Plug the IC chip into the breadboard. 3. Connect the supply voltage and ground lines to the chips. PIN7 = Ground and PIN14 = +5V. 4. According to the pin diagram of each IC mentioned above, make the connections according to circuit diagram. 5. Connect the inputs of the gate to the input switches of the LED. 6. Connect the output of the gate to the output LEDs. 7. Once all connections have been done, turn on the power switch of the bread-board 8. Operate the switches and fill in the truth table (Write "1" if LED is ON and "0" if LED is OFF Apply the various combination of inputs according to the truth table and observe the condition of Output LEDs.

HALF ADDER: Half Adder: A half adder is a logical circuit that performs an addition operation on two binary digits. The half adder produces a sum and a carry value which are both binary digits.

OBSERVATION TABLE:

A	B	SUM (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

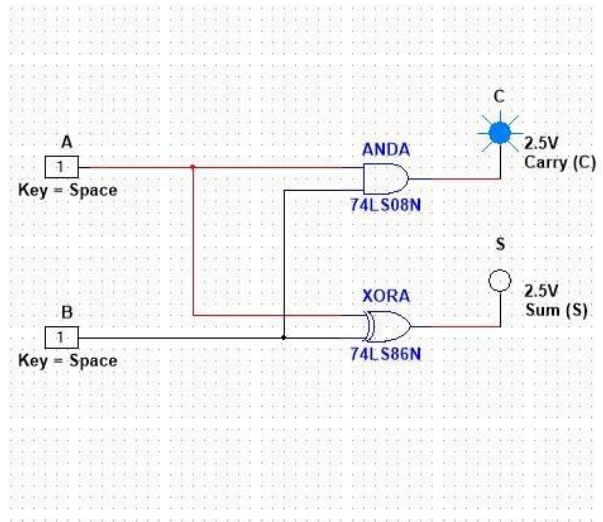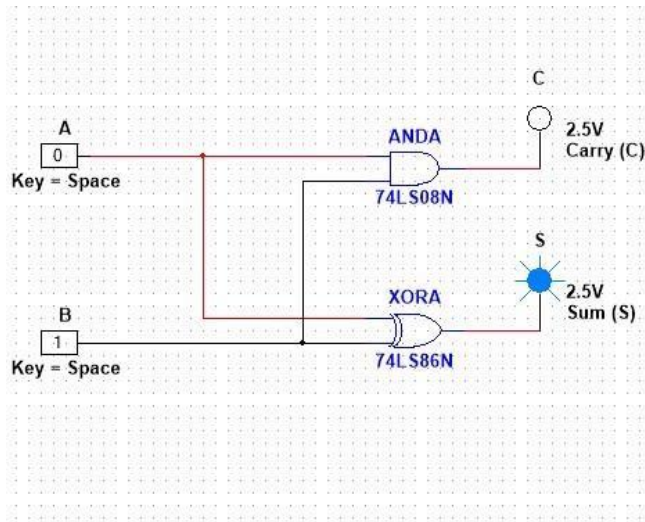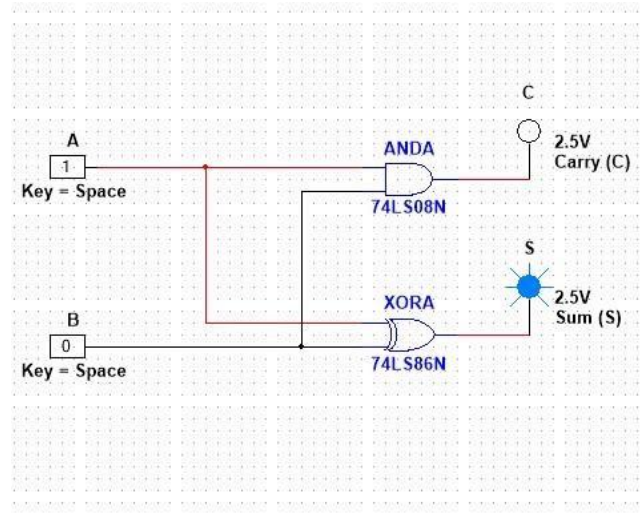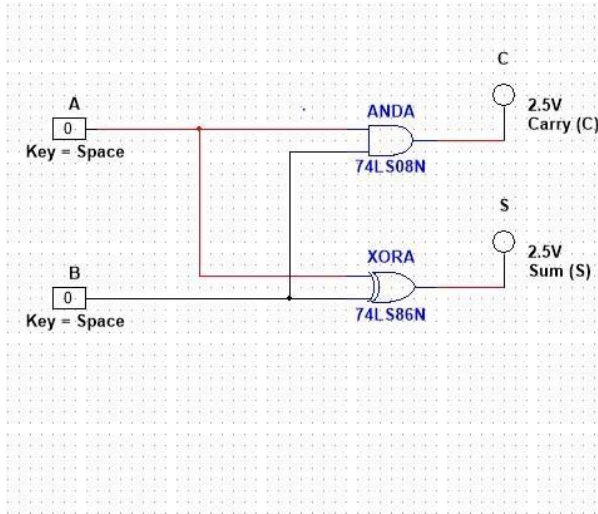

RESULTS AND ANALYSIS: Half Adder: Verified the truth table of Half Adder as $S = 1$ i.e. LED which is connected to S terminal glows when inputs are A, B. Verified the truth table of Half-Adder as $C = 1$ i.e. LED which is connected to C terminal glows when inputs are A, B.

CONCLUSION: • To add two bits we require one XOR gate (IC 7486) to generate Sum and one AND (IC 7408) to generate carry. • To add three bits we require two half adders.



HALF SUBTRACTOR

AIM: Design and verify the logic circuit of Half-subtractor using logic gate.

OBJECTIVES: • To understand the principle of binary subtraction. • To understand half-subtractor concept. • Use truth table and Boolean Algebra theorems in simplifying a circuit design. • To implement half-subtractor circuit using logic gates

PROCEDURE: • Collect the components necessary to accomplish this experiment. • Plug the IC chip into the breadboard. • Connect the supply voltage and ground lines to the chips. PIN7 = Ground and PIN14 = +5V. • According to the pin diagram of each IC mentioned above, make the connections according to circuit diagram. • Connect the inputs of the gate to the input switches of the LED. • Connect the output of the gate to the output LEDs. • Once all connections have been done, turn on the power switch of the bread-board • Operate the switches and fill in the truth table (Write "1" if LED is ON and "0" if LED is OFF Apply the various combination of inputs according to the truth table and observe the condition of Output LEDs.

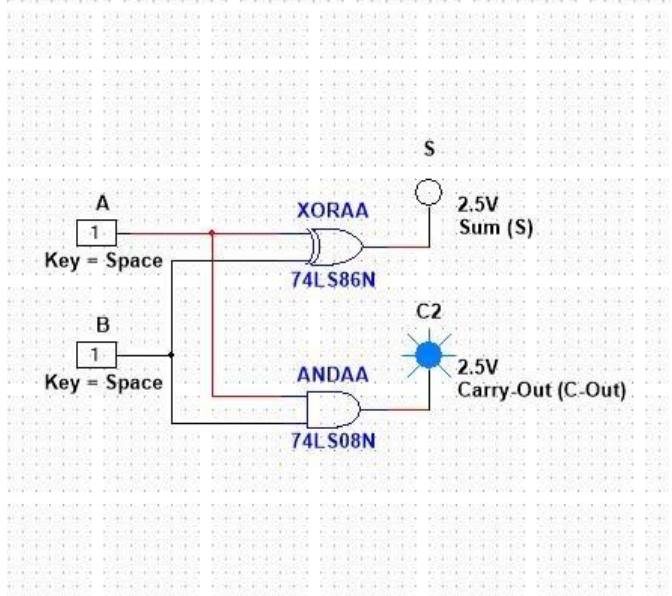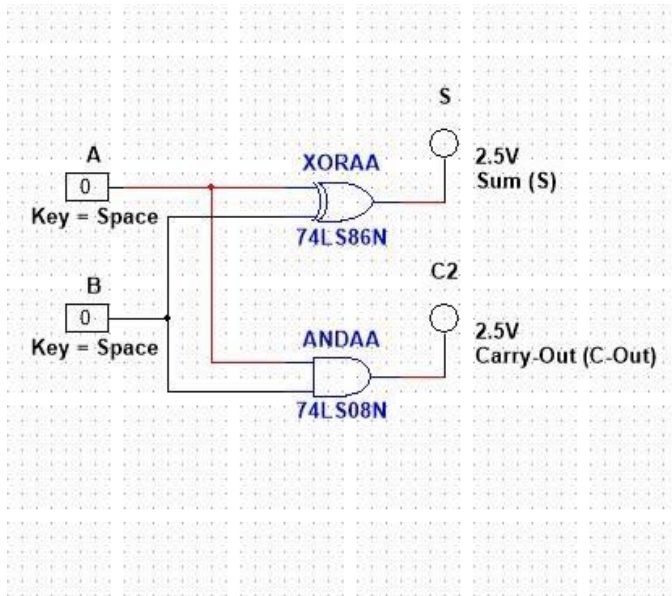HALF SUBTRACTOR: The half-subtractor is a combinational circuit which is used to perform subtraction of two bits. It has two inputs, X (minuend) and Y (subtrahend) and two outputs D (difference) and B (borrow).



OBSERVATION TABLE:

A		B	D
0		0	0
0		1	1
1		0	1
1		1	0

RESULTS AND ANALYSIS: Verified the truth table as follows. Verified the truth table of Full Subtractor as $D = 1$ i.e. LED which is connected to D terminal glows when inputs are, Y, BIN Verified the truth table of Full Subtractor as $BOUT = 1$ i.e. LED which is connected to BOUT terminal glows when inputs are X, Y, BIN

CONCLUSION: • To add two bits, we require one XOR gate (IC 7486) to generate Difference and one AND (IC 7408) and NOT Gate (IC 7432) to generate Borrow. • To add three bits, we require two half subtractor.

JK FLIP FLOP

AIM:

To Design and verify the truth table of J K Flip flop using IC 7473

OBJECTIVES:

- To understand the principle of operation of sequential circuit
- To differentiate between combinational circuit and sequential circuit.
- To get familiar with basic Flip flops
- Determine the logic operation of JK flip flops.

Connect and observe the state transition of JK as connected to the clock generator circuit.

PROCEDURE:

- Collect the components necessary to accomplish this experiment.
- Plug the IC chip into the breadboard.
- Connect the supply voltage and ground lines to the chips. PIN7 = Ground and PIN14 = +5V.
- According to the pin diagram of each IC mentioned above, make the connections according to circuit diagram.
- Connect the inputs of the gate to the input switches of the LED.
- Connect the output of the gate to the output LEDs.
- Once all connections have been done, turn on the power switch of the breadboard

Operate the switches and fill in the truth table (Write "1" if LED is ON and "0" if LED is OFF Apply the various combination of inputs according to the truth table and observe the condition of Output LEDs.

OBSERVATION TABLE:

CK	J	K	Q	<u>Q</u>
1	0	0	-	-
1	0	1	0	1
1	1	0	1	0

1	1	1	0	1
---	---	---	---	---

The function table of JK flip flop using IC 7473 has been verified.

