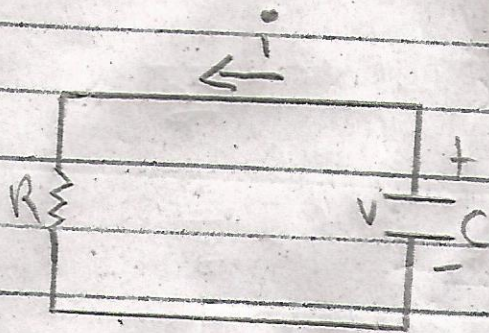


$$-40e^{-4t}$$

Sol:-



a) Find R & C

The time constant

$$\tau = \frac{1}{e} = RC = \frac{1}{4}$$

Now we know that

$$i = C \frac{dv}{dt}$$

$$0.2e^{-4t} = C \frac{(10)e^{-4t}}{4} = 10(-4)e^{-4t}$$

$$\frac{0.2e^{-4t}}{-40e^{-4t}} = C = \frac{40e^{-4t}}{-40e^{-4t}}$$

$$C = -0.005$$

we write it as
 $C = 5 \text{ m.F}$

Now

$$R = \frac{V(t)}{i_R(t)} = \frac{10e^{-4t}}{0.2e^{-4t}}$$

$$R = 50 \Omega$$

b) for the time constant

we know that
time constant

$$\tau = R \times C$$


$$= 50 \Omega \times 0.005 \text{ C}$$

$$= 0.25 \text{ s}$$

c) Now to find initial energy in the capacitor

we know that

$$W(0) = \frac{1}{2} C V_0^2$$

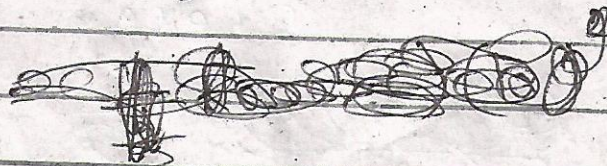

$$c) \Rightarrow \frac{1}{2} (5 \times 10^{-3}) (10)^2$$

$$= \frac{1}{2} (5 \times 10^{-3}) (100)$$

$$= \frac{1}{2} (500 \times 10^{-3})$$

$$= 250 \times 10^{-3} \text{ J}$$

$$\therefore 10^{-3} = \text{m}$$

$$W_c(0) = 250 \text{ m J}$$

d) Now to find the time to obtain of initial energy to dissipate 50% we use.

$$W_c(t) = \frac{1}{2} C v^2(t)$$

To dissipate 50%

$$W_c(t) = \frac{W_c(0)}{2}$$

from (c) the initial energy of capacitor

~~250 m J~~

✓

$$\frac{w_c(t)}{2} = \frac{1}{2} (v^2(t))$$

$$\frac{250 \times 10^{-3} \text{ J}}{2} = \frac{1}{2} 5 \times 10^{-3} (10 e^{-4t})^2$$

$$125 \times 10^{-3} \text{ J} = \frac{1}{2} \times 5 \times 10^{-3} \times 100 e^{-8t}$$

$$\frac{125 \times 10^{-3}}{500 \times 10^{-3}} = \frac{500 \times 10^{-3} \times e^{-8t}}{500 \times 10^{-3}}$$

$$0.5 = e^{-8t}$$

$$\therefore \tau = \frac{1}{e}$$


$$\ln 0.5 = -8t \ln e$$

$$\therefore -0.6931 = -8t$$

$$t = 86.643 \text{ ms}$$

Q21

Sol:

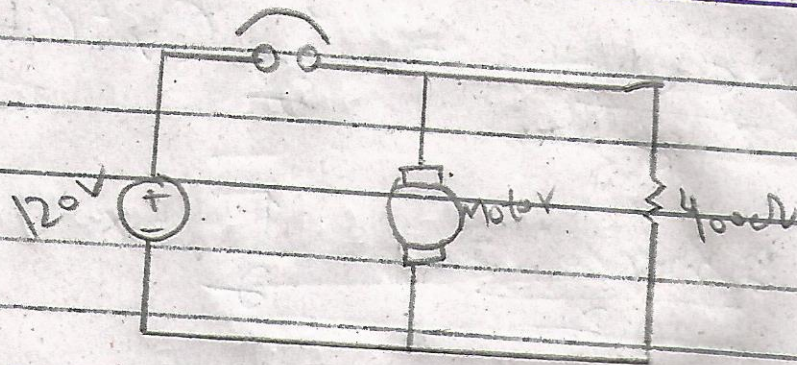

Given:-

$$V_s = 120V$$

$$L = 50mH$$

$$R = 100\Omega$$


$$t = 100ms$$

when the circuit is closed:-

Steady state condition apply
& the inductor act as
short circuit


The current that flows through
the 100Ω resistor at $t=0$
(Before the circuit opens) given by
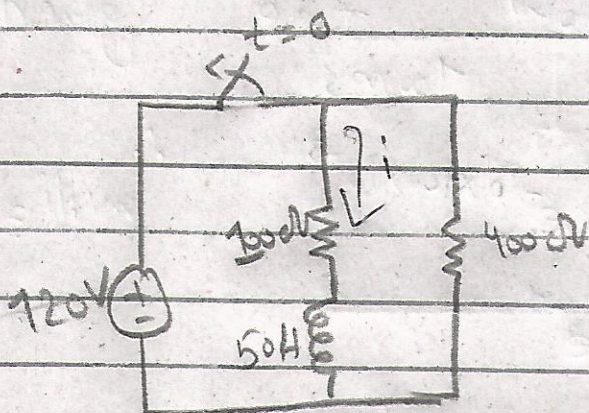
$$V = iR$$
$$i = \frac{120}{100} = 1.2A$$



$$i = \frac{V}{R} = \frac{120}{100} = 1.2 \text{ A}$$

After the switch is open

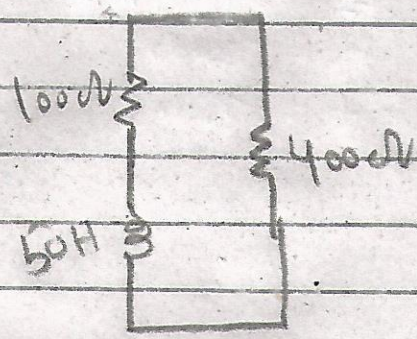

we know that transient response is always decaying

$$\tau = \frac{L}{R} = \frac{50}{100+400} = 0.115$$

Now the inductor will discharge & the circuit has no source

$$i(t) = i(0)e^{-t/\tau} = 1.2e^{-\frac{t}{0.115}}$$

$$i(t) = 1.2e^{-10t}$$

So now the given
time is 100ms

$$i(100\text{ms}) = 1.2 e^{-10 \times 100 \times 10^{-3}} \quad \therefore \text{milli} = 10^{-3}$$

$$= 1.2 e^{-1}$$

$$= 0.4474$$

$$= 447.4 \text{ mA}$$

Q31-

Sol:

Given that:

$$V_c(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA}$$

aim that response of this circuit is (overdamp) we So now Given that

$$s_1 = -10$$

$$s_2 = -20$$

we

know

that

$$s_1 + s_2 = -2\alpha$$

$$-10 - 20 = -2\alpha$$

$$\frac{-30}{-2} = \frac{-2\alpha}{-2}$$

$$\alpha = \frac{15}{1} = 15$$

$$\alpha = 15$$

now

$$s_1 - s_2 = 2\sqrt{(15)^2 - \omega_0^2}$$

$$-10 + 20 = 2\sqrt{(15)^2 - \omega_0^2}$$

$$10 = 2\sqrt{15^2 - \omega_0^2} \rightarrow$$

S₀

$$S_1 = -15 + \int 15^2 - \omega_0^2$$

$$-10 = -15 + \int 15^2 - \omega_0^2$$

$$15^2 - \omega_0^2 = 25$$

$$\omega_0 = \sqrt{225 - 25} = \sqrt{200}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$LC = \frac{1}{200}$$

Since we have a series

RLC

$$i_L = i_C = C \frac{dv_C}{dt}$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA}$$

$$i_L(t) = 40 \times 10^{-3} e^{-20t} - 60 \times 10^{-3} e^{-10t} \text{ A}$$

$$= 0.04e^{-20t} - 0.06e^{-10t}$$

$$i_L = C \frac{dv_C}{dt}$$

$$= 0.04e^{-20t} - 0.06e^{-10t} = C \frac{d}{dt} (30 - 10e^{-20t} + 30e^{-10t})$$

The derivative of this give us.

$$0.04e^{-20t} - 0.06e^{-10t} = C (200e^{-20t} - 300e^{-10t})$$

$$C = \frac{0.04e^{-20t} - 0.06e^{-10t}}{200e^{-20t} - 300e^{-10t}}$$

$$C = 2 \times 10^{-4} \text{ F} \quad \text{(i)}$$

Now for "L"

Previous

$$LC = \frac{1}{200} \quad \frac{1}{LC} = 200$$

$$\frac{1}{L(2 \times 10^{-4})} = 200$$

$$L = 25 \text{ H} \quad \text{(ii)}$$

Previous


$$\alpha = \frac{R}{2L} = 15 \quad \text{eq}$$

$$\frac{R}{2(25)} = 15$$

$$\frac{R}{50} = 15$$

$$R = 750 \Omega \quad \text{(iii)}$$

Q41-

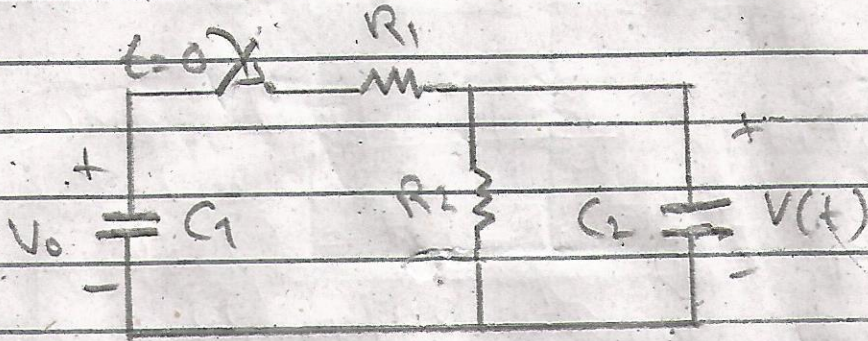

Given data-

$$C_1 = 0.5 \mu\text{f}$$

$$C_2 = 5 \mu\text{f}$$

$$R_1 = 5 \text{ M}\Omega$$

$$R_2 = 2.5 \text{ M}\Omega$$

$$V_0 = 600(t) \text{ V}$$

for $t < 0$ the switch is open
therefore C_1 is detached from
network.

$$V(0) = 0 \text{ V}$$

for $t > 0$ the switch is closed
at $t = 0$ C_1 is connected
to the circuit as shown



Applying KCL at node b/w
 R_1 & R_2

$$-iR_1 + iR_2 + iC_2 = 0$$

thus $iR_1 = iR_2 + iC_2$

$$\frac{V_0 - v}{R_1} = \frac{v}{R_2} + C_2 \frac{dv}{dt}$$

multiply by R_1 , thus

$$V_0 - v = \frac{R_1 v}{R_2} + R_1 C_2 \frac{dv}{dt}$$

Rearrange

$$V_0 = v \left(1 + \frac{R_1}{R_2} \right) + R_1 C_2 \frac{dv}{dt}$$

Substitute

$$V_0 = v \left(1 + \frac{5}{2.5} \right) + \left(5 \times 10^6 \times 5 \times 10^{-6} \frac{dv}{dt} \right)$$

thus
$$V_0 = 3V + 25 \frac{dv}{dt} \dots 2$$

when the steady state condition apply, the capacitor act as an open circuit and no current will flow through it

thus
$$i_c = C \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} = 0$$

Substitute in (2)

$$V_0 = 3V \dots 3$$

where V_s is the steady state voltage across the capacitor but the unit step function for $t > 0$ is given by

$$u(t) = 1 \quad t > 0$$

thus

$$V_0 = 60u(t) = 60V \quad t > 0$$

Substitute

$$60 = 3V_s$$

thus

$$V_s = 20V$$

The voltage across the capacitor $v(t)$ is given

$$v(t) = V_s + A e^{-t/\tau}$$

the equivalent resistance of the circuit $R_1 // R_2$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{5 \times 2.5}{5 + 2.5} = \frac{5}{3} \text{ M}\Omega$$

the time constant of capacitor C_2

$$\tau = R_{eq} C_2 = \frac{5 \times 10^6}{3} \times 5 \times 10^{-8} = \frac{25}{3}$$

Now

$$v(t) = 20 + A e^{-3t/25}$$

$$v(0) = 20 + A$$

$$A = -20$$

$$v(t) = 20 - 20 e^{-3t/25}$$


$$v(t) = 20 - 20 e^{-3t/25}$$

$$v(t) = 20 (1 - e^{-3t/25}) \text{ V}$$

$$t > 0$$

$$v(t) = 20 (1 - e^{-3t/25}) \text{ V } t > 0$$

Q5

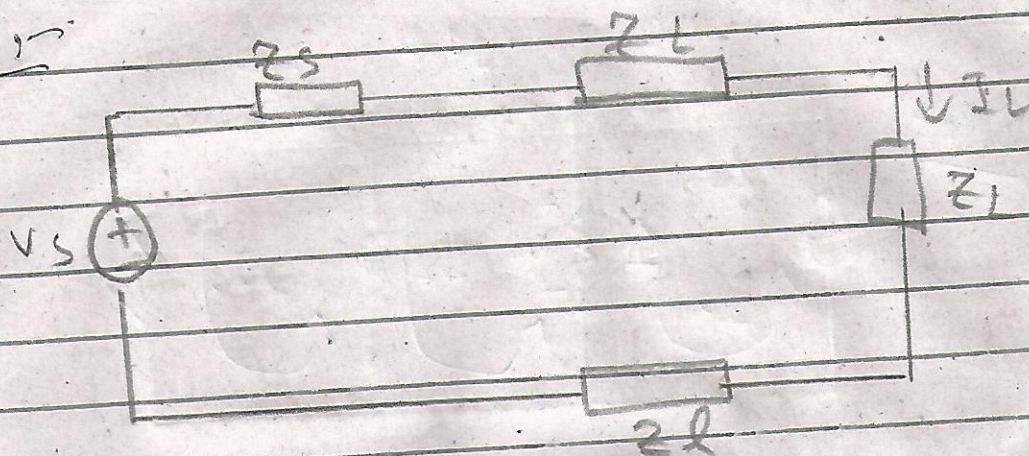

using

$$I_L = \frac{V_s}{Z}$$

So this in series so

$$I_L = \frac{V_s}{Z_s + Z_L + Z_L} = \frac{115 \angle 0}{(1 + j0.5) + 2(0.4 + j0.3) + (23.9 + j18.9)}$$


$$= \frac{115 \angle 0}{39.02 \angle 38.66} = 3.592 \angle -38.66$$

thus load current is

$$3.592 \angle -38.66$$

Q6:-

Sol:-

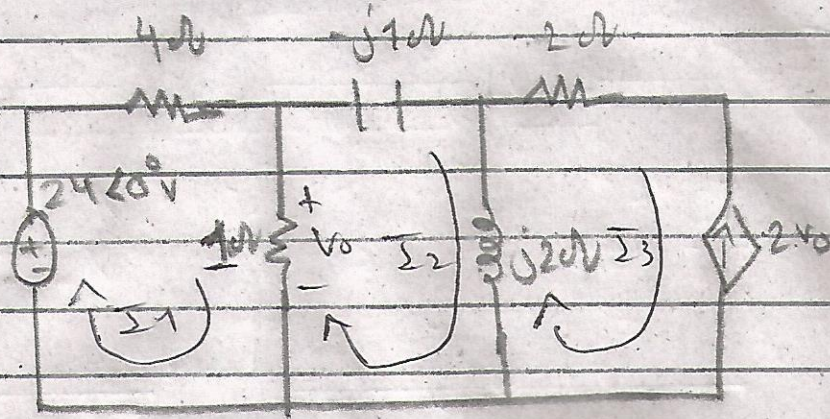

KVL at mesh 1

$$24\angle 0^\circ + 4I_1 + I_1 - I_2 = 0$$

$$\| 5I_1 - I_2 = 24\angle 0^\circ \|$$

KVL at mesh 2

$$I_2 - I_1 - j5I_2 + j2(I_2 - I_3) = 0$$
$$-I_1 + (1 - j + j2)I_2 - j2I_3 = 0$$

$$\| -I_1 + (1 + j)I_2 - j2I_3 = 0 \|$$

KVL at mesh 3

$$I_3 = -2V_o$$

$$V_o = I_1 - I_2$$

$$I_3 = -2(I_1 - I_2) = -2I_1 + 2I_2$$

$$\| 2I_1 - 2I_2 + I_3 = 0 \|$$

B Y Solving the m

$$I_1 = 6.48 \angle -1.55^\circ \text{ A}$$

$$I_2 = 8.45 \angle -5.95^\circ \text{ A}$$

$$I_3 = 4.1 \angle -19.98^\circ \text{ A}$$

Now to find voltage
across dependent source

$$j2 (4.1 \angle -19.98^\circ - 8.45 \angle -5.95^\circ + 2 (4.1 \angle -19.98^\circ) + V_s) = 0$$

$$V_s = 14.78 \angle 126.34^\circ \text{ V}$$

Now

$$I = 2V_s$$

$$= 2 (6.48 \angle -1.55^\circ - 8.45 \angle -5.95^\circ) \\ = 4.1 \angle 160.02^\circ \text{ A}$$

$$S = VI = (14.78 \angle 126.34^\circ) \times (4.1 \angle -16.02^\circ) \\ = 60.6 \angle -33.68^\circ \text{ VA}$$

$$S = 50.43 - j33.61 \text{ VA}$$

the average
reactive & so
complex power
Delivered

$$P = 50.43 \text{ W}$$

$$Q = 33.61 \text{ VAR}$$