

ID# 12595


Date: 29/09/2020

Q1 The 1N4747A Zener used in the regulator of figure is a 15V diode determine the following.

(a) Determine  $V_{out}$  at  $I_{zk}$  and at  $I_{zm}$ .

(b) Calculate the value of  $R$  that should be used.

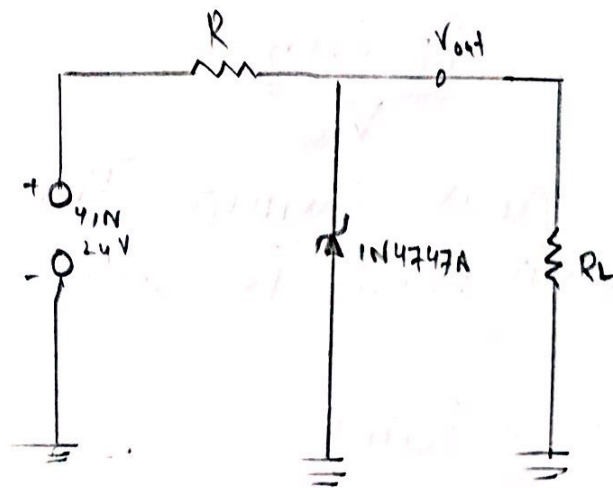(c) Determine the min value of  $R_L$  that can be used. The electrical characteristics and value of  $V_Z$ ,  $I_Z$ ,  $I_{zk}$ ,  $Z_Z$  can be found in diode datasheet:-



Solution From the data sheet we can write of 1N4747A

$$V_Z = 20$$

$$Z_Z = 22$$

$$I_Z = 20$$

$$I_{zk} = 0.25 \text{ mA}$$

$$I_Z = 12.5 \text{ mA}$$

→ (2)

Q)  $V_{out} = ?$  at  $I_{zk}$  and  $I_{zm}$

$$V_{out} = V_Z - \Delta V_Z \quad (\text{for } I_{zk})$$
$$= V_Z - (I_Z - I_{zk}) Z_Z$$

$$V_{out} = V_Z - (I_Z - I_{zk}) Z_Z$$

$$V_{out} = 20 - (12.5 - 0.25) 22$$

$$V_{out} = 20 - (12.25) 22$$

$$V_{out} = 20 - 0.2495$$

$$V_{out} = 19.7305 \text{ V for } I_{zk}$$

Now  $V_{out}$  for  $I_{zm}$  first to

$I_{zm}$

$$I_{zm} = \frac{P_D (\text{Max})}{V_Z}$$

for Zener max current The max power dissipated is 1W

$$I_{zm} = 50 \text{ mA}$$

Now  $V_{out}$  for  $I_{zm}$

$$V_{out} = V_Z + \Delta V_Z$$

$$V_{out} = V_Z + (I_{zm} - I_Z) Z_Z$$

③

$$V_{out} = 20 + (50 \text{ mA} - 12 \cdot 5 \text{ mA}) 22 \Omega$$

$$V_{out} = 20 + (37 \cdot 5 \text{ mA}) 22 \Omega$$

$$V_{out} = 20.825 \text{ V for } I_{ZM}$$

④

$$R = ?$$

As we know that

$$V_{in(\text{max})} = I_{ZM} R + V_{out}$$

$$\Rightarrow R = \frac{V_{in} - V_{out}}{I_{ZM}}$$

$$= \frac{24 - 20.825 \text{ V}}{50 \text{ mA}}$$

$$R = 63.5 \Omega$$

⑤

minimum load resistance  $R_L = ?$

$$\text{So } I_T = \frac{V_{in} - V_Z}{R}$$

$$= \frac{24 - 20}{63.5 \Omega} = \frac{4}{63.5}$$

$$I_T = 63 \text{ mA}$$

(4)

Now to find  $I_L(\text{max})$

$$I_L(\text{max}) = I_T - I_{ZK}$$
$$= 63.75 \text{mA}$$

So


$$R_L(\text{min}) = \frac{V_Z}{I_L(\text{max})}$$
$$= \frac{20}{63.75 \text{mA}}$$

$$R_L(\text{min}) = 318.72 \Omega$$



(5)

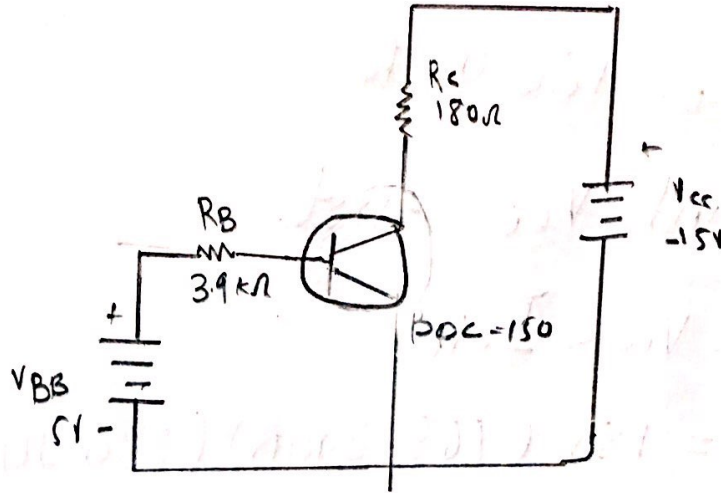Q2) Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{BE}$ ,  $V_{CE}$  and  $V_{CB}$  in the circuit.



Solution

from the given figure we can write

$$V_{BB} = 5\text{V}, R_B = 3.9\text{ k}\Omega, R_C = 180\ \Omega$$

$$V_{CC} = 15\text{V}$$

As  $I_B$  is given by  $\beta_{DC} = 150$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$= \frac{5\text{V} - 0.7\text{V}}{3.9\text{ k}\Omega} = 1102\ \mu\text{A}$$

As we know

$$I_C = \beta_{DC} I_B$$

$$(150)(1102\ \mu\text{A}) = 165.3\text{ mA}$$

(6)

$$I_E = I_C + I_B$$

$$= 165.3 \text{ mA} + 1102 \mu\text{A}$$

$$I_E = 166.4 \text{ mA}$$

Now Find  $V_{CE}$  first

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 15\text{V} - (165.3 \text{ mA})(180 \Omega)$$

$$= 15\text{V} - 29.7\text{V}$$

$$= -14.7\text{V}$$

Now

$$V_{CB} = V_{CE} - V_{BE}$$

$$= -14.7\text{V} - 0.7\text{V}$$

$$= -15.4\text{V}$$

Since collector is at a lower voltage than the base the collector-base junction is forward biased.



(3)

Solution

BJTs can be used as amplifiers by using its "Active" region of operation by achieving forward biased mode of Junction<sub>1</sub> (J<sub>1</sub>) and by reverse biasing the Junction<sub>2</sub> (J<sub>2</sub>)


SNO	J <sub>1</sub>	J <sub>2</sub>	Region of operation	works as Amplifier
1	F.B	R.B	Active	
2	F.B	F.B	Saturation	ON switch
3	R.B	R.B	Cut off	off/open circuit
4	R.B	F.B	Inverted	rarely used

The 4 modes the BJT can be used BJT to be used as an amplifier

Schematic Diagram.

next page see

Diagram

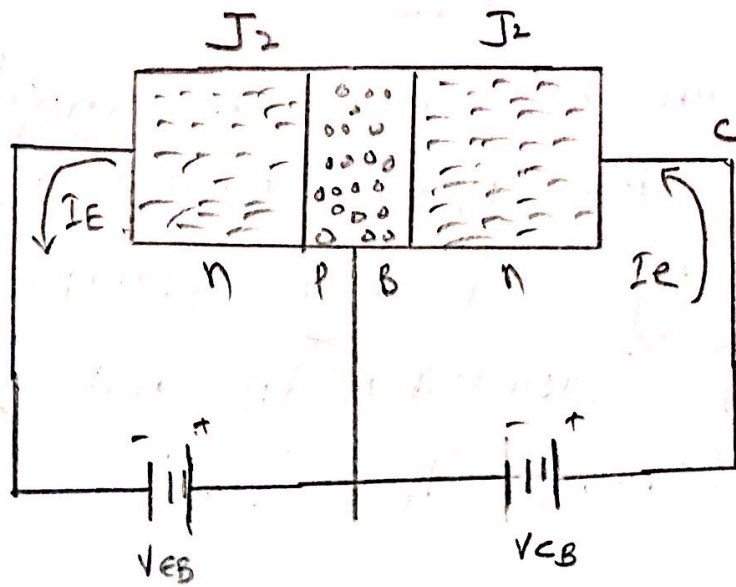

Above Diagram shows the basic configuration for using a BJT in active region. This active as an amplifier.





(9)

Q4) For a transistor to act as a switch you need to join each of the following condition on the left to ON or OFF state.

### Solution

Transistor fully ON (ON)

Transistor fully off (OFF)

Input and base are at 0V (OFF)

Collector current  $I_c = 0$  (OFF)

$V_{CE} = V_{CC}$  (OFF)

BC Junction is reverse bias (OFF)

BC Junction is reverse bias (OFF)

Max of Saturation current  $I_c$  flows (ON)

BE Junction is forward bias (ON)

BC Junction is forward bias (ON)


$V_{CE} = 0V$  (ON)

BE Junction is less than 0.7V (OFF)

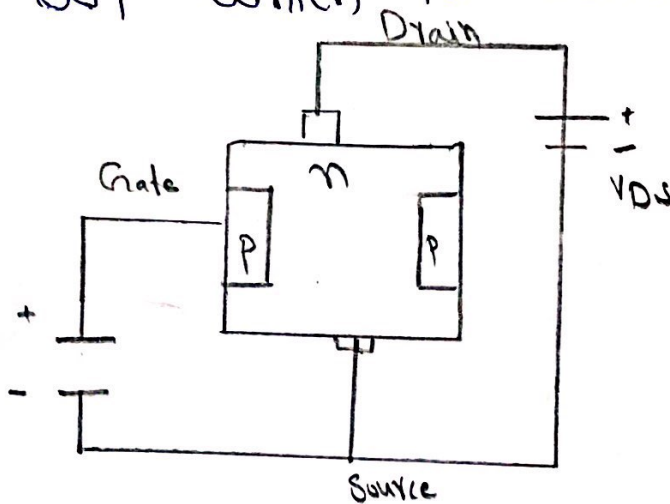
Q3

Solutions

JFET is a type of Junction field effect transistor which is a voltage controlled device as opposed to BJT which is current controlled.




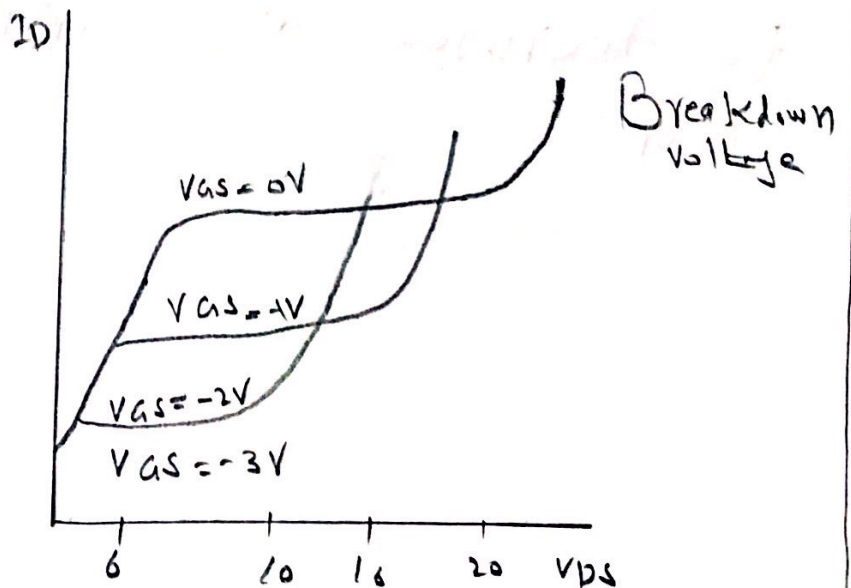Actually in FET the drain to source current is controlled by the width of the channel. The electric field is produced by the gate to source voltage.



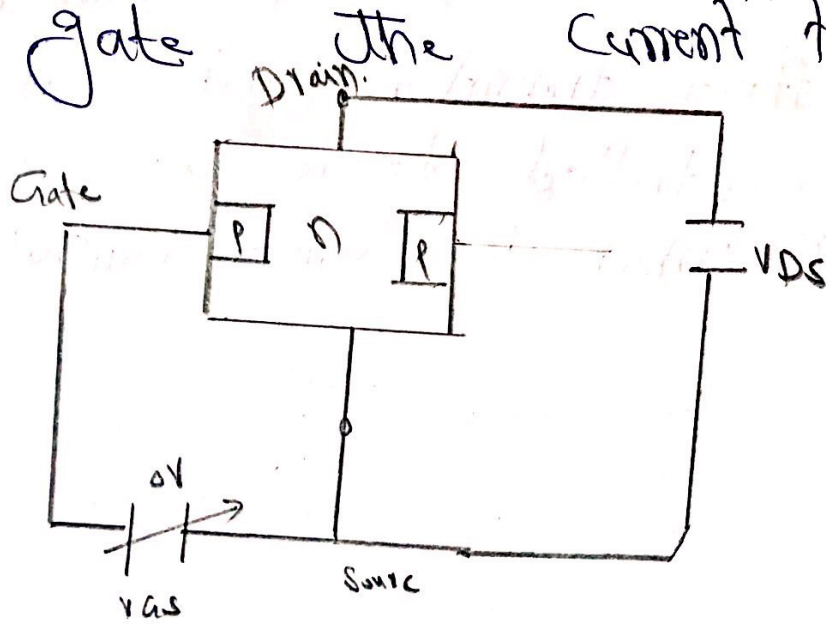(11)

So if we see to the graph which the no voltage applied to the gate the current flows freely




The channel are wider and drain current moves freely.

if we move  $V_{GS}$  to negative value the channel width start to decrease at current cannot move.



(12)

8  
6

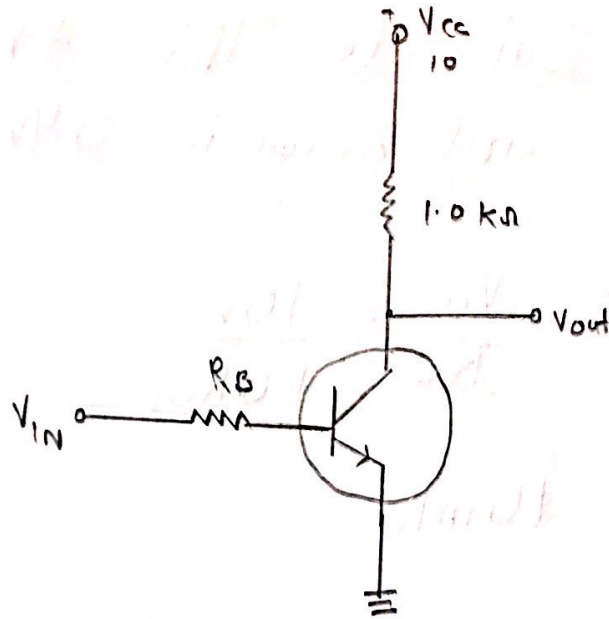

Solution

① What is  $V_{CE}$  when  $V_{IN} = 0V$ ?

② ~~Determine  $V_{CE}$~~

As we know that for  $V_{IN} = 0V$   
The transistor will be in cut off mode

$V_{CE} =$  will be the same as  $V_{CC}$

$$\Rightarrow V_{CE} = V_{CC} = 10V$$

So

$$V_{CE} = 10V$$

(13)

③ Determine The min value of  $I_B$  is required to saturate This transistor if  $\beta_{DC}$  is 125 and  $V_{CE(sat)}$  is 0.4V.

$$I_C(sat) = \frac{V_{CC}}{R_C} = \frac{10V}{1.0k\Omega}$$

$$= 10mA$$

So

$$I_B(min) = \frac{I_C(sat)}{\beta_{DC}}$$

$$= \frac{10mA}{125} = 0.08mA$$

The required min  $I_B$  to saturate the transistor.

