

Iqar national university Peshawar

Department of electrical engineering

Open ended lab

Name

Amjad ali

Id

16012

Semester

2nd

Submitted To

Waleed jan sab

Date

27/06/2020




IQRA NATIONAL UNIVERSITY
DEPARTMENT OF ELECTRICAL ENGINEERING
Linear Circuit Analysis (LAB)

Open Ended Lab

Consider a DC circuit in which two lamps, one DC motor and one DC fan are connected in series-parallel combination to a 12V DC power supply as shown in the figure below. Resistances of two lamps are denoted by R_1 and R_2 respectively. Resistance of the coil of DC motor is denoted R_3 and resistance of the coil of DC fan is denoted by R_4 . Using any of the circuit analysis techniques, compute the below given parameters:

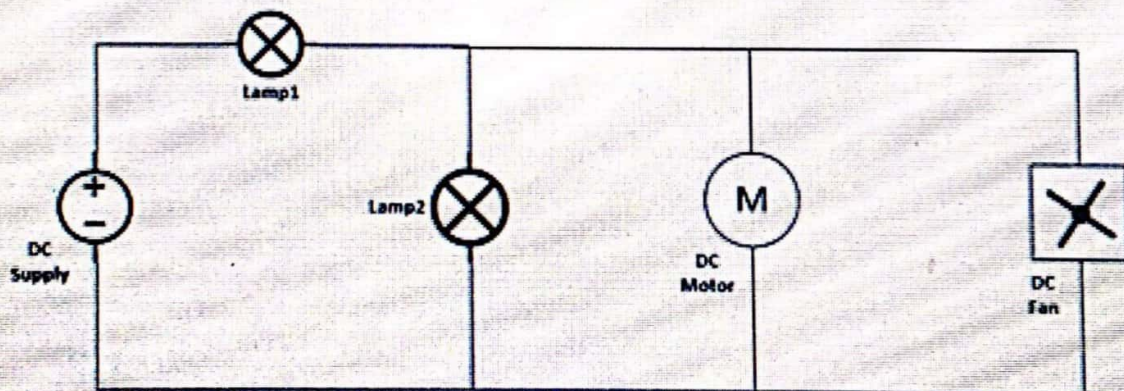- 1) Current flowing through each lamp, DC motor and DC fan.
- 2) Voltage across each lamp, DC motor and DC fan.
- 3) Power loss in each lamp, DC motor and DC fan




Note:

- a) Each student should take different value of R_1 , R_2 , R_3 , and R_4 .
- b) Verify the result practically through a circuit simulation software.

(1)

Question:.

Ans: Figure:

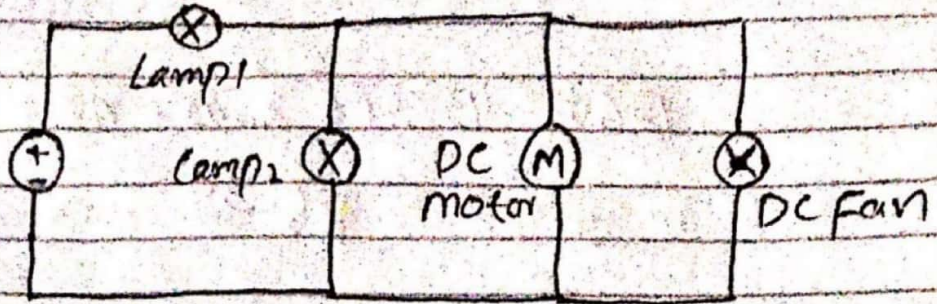

Solution:

Solving through nodals


Let

$$R_1 = 5$$

$$R_2 = 7$$

$$R_3 = 10$$

$$R_4 = 9$$

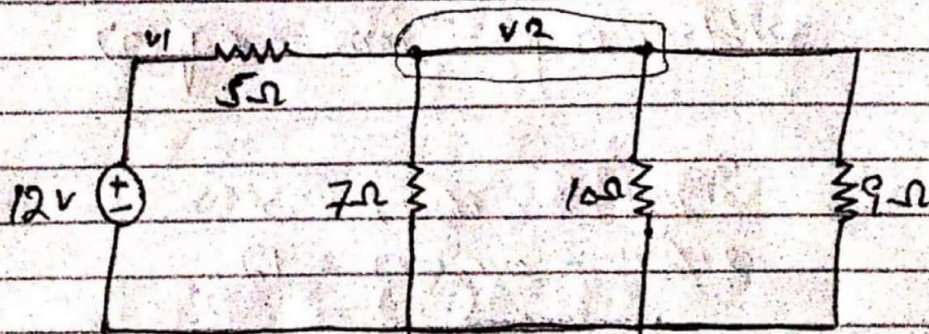

Applying KCL on v_1

$$\frac{v_2 - v_1}{5} = 12$$

$$v_1 - v_2 = 60$$

(2)
Applying KCL on node 2

$$\frac{v_2 - v_1}{5} + \frac{v_2}{7} + \frac{v_2}{10} + \frac{v_2}{9} = 0$$

$$\frac{126v_2 - 126v_1 + 90v_2 + 63v_2 + 70v_2}{630} = 0$$

$$\frac{-126v_1 + 349v_2}{630} = 0$$

$$-0.2v_1 + 0.6v_2 = 0$$

ming 0.1 with eq (1)

$$0.2v_1 - 0.6v_2 = 12 \quad \text{--- (2)}$$

Subtracting from eq (2)

$$-0.2v_1 + 0.6v_2 = 0$$

$$0.2v_1 - 0.2v_2 = 12$$

$$= 0.4v_2 = 12$$

$$\boxed{v_2 = 30V}$$

putting in eq (a)

$$0.2v_1 = 18$$

(3)

$$V_1 = 90V$$

(1) Find current

current across R_1

$$I = V/R$$

$$I = 90/5 = 18A$$

current across R_2

$$I_2 = V/R$$

$$= 30/7 = 4.3A$$

current across R_3

$$I = V/R$$

$$= 30/10 = 3A$$

current across R_4

$$I = V/R$$

$$I = 30/9 = 3.3A$$

$$\text{Result} = I_1 = 18A$$

$$I_2 = 4.3A$$

$$I_3 = 3A$$

$$I_4 = 3.3A$$

(ii) Find voltage

voltage across R_1

$$V = IR$$

$$V = (18)(5) = 90V$$

V across R_2

$$V = IR$$

$$V = (4.3)(7) = 30.1V$$

V across R_3

$$V = IR$$

$$V = (3)(10) = 30V$$

V across R_4

$$V = IR$$

$$V = (3.3)(9) = 29.7$$

Result:

$$V_1 = 90V$$

$$V_2 = 30.1V$$

$$V_3 = 30V$$

$$V_4 = 29.7V$$

(5)

(iii) Finding power across each resistor

$$\begin{aligned}P(R_1) &= (I_1)(V_1) \\ &= (18)(90) \\ &= 1620 \text{ mW}\end{aligned}$$

$$\begin{aligned}P(R_2) &= (I_2)(V_2) \\ &= (4.3)(30.1) \\ &= 129.43 \text{ mW}\end{aligned}$$

$$\begin{aligned}P(R_3) &= (I_3)(V_3) \\ &= (3)(30) \\ &= 90 \text{ mW}\end{aligned}$$

$$\begin{aligned}P(R_4) &= (I_4)(V_4) \\ &= (3.3)(29.7) \\ &= 98.01 \text{ mW}\end{aligned}$$

Result:

$P_1 =$	1620 mW
$P_2 =$	129.43 mW
$P_3 =$	90 mW
$P_4 =$	98.01 mW