

Name: SHAFIQ

ID: 14859

Page: 1


Q1:- A 2 wire D.C Distributor AD is fed from both ends. At feeding Point A, the voltage is maintained as at A, the voltage is maintained as A 240V at B 250V. The total length of the distributor is 300 meter and loads are tapped off as under.

- 25A at 50 meters from A;
- 50A at 75 meter from A;
- 30A at 100 meter from A;
- 40A at 150 meters from A;

The resistance per kilometer of one conductor is 0.5  $\Omega$ . Calculate

- Current in various sections of the distribution
- Minimum voltage and the point at which it occurs?

Solution:-

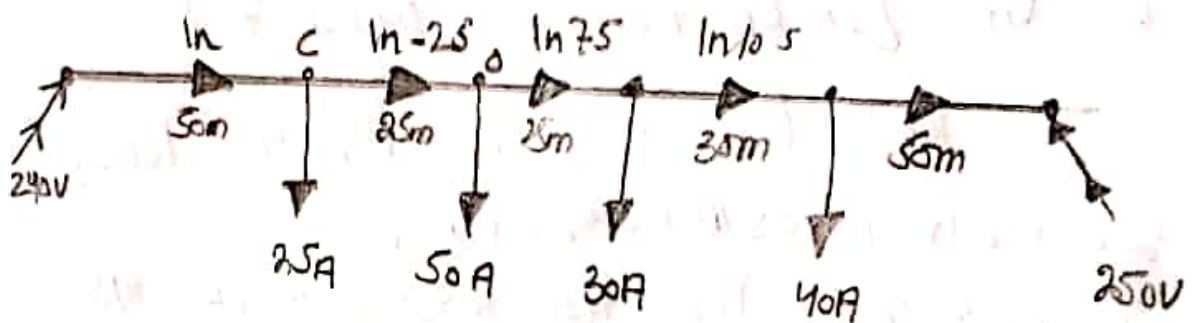

The above figure shows the distributor with its tapped current let  $I_n$  amperes be the current supplied from the feeding point of A. Then currents in the various sections of the distributors are as shown

Resistance of 1000m length of distributor  
both wires =  $2 \times 0.5 = 1$

Resistance of Section AC,  $R_{AC} =$   
 $= 1 \times 50 / 1000 = 0.05 \Omega$

Resistance of Section CD,  $R_{CD} = 1 \times 2.5 / 1000 = 0.0025 \Omega$

Resistance of Section DE,  $R_{DE} = 1 \times 2.5 / 1000 = 0.0025 \Omega$

Resistance of Section EF,  $R_{EF} = 1 \times 50 / 1000 = 0.05 \Omega$

Resistance of Section FB,  $R_{FB} = 1 \times 50 / 1000 = 0.05 \Omega$

voltage at B = voltage at A

Drop over A, B

$$V_B = V_A = [I_A R_{AC} + (I_A - 25) R_{CD} + (I_A - 75)$$

$$R_{DE} + (I_A - 105) R_{EF} + (I_A - 145) R_{FB}]$$

$$250 = 240 - [0.05 I_A + 0.0025 (I_A - 25)$$

$$\text{or } + 0.0025 (I_A - 75) + 0.05 (I_A - 105) + 0.05 (I_A - 145)]$$

$$\text{or } 250 = 240 - [0.2 I_A - 9]$$

$$\text{or } I_A = \frac{249 - 250}{0.2} = 5A$$

(i) ∴ Current in Section AC,  $I_{AC} = I_A = 5A$

$$\begin{aligned} \text{Current in Section CD, } I_{CD} &= \\ &= -2.5 = 5 - 2.5 = 2.5A \end{aligned}$$

$$\begin{aligned} \text{Current in Section DE, } I_{DE} &= I_A - 7.5 \\ &= 5 - 7.5 = -2.5A \end{aligned}$$

from D to E and from  
E to D

$$\begin{aligned} \text{Current in Section EF, } I_{EF} &= I_A - 10.5 = \\ &= 5 - 10.5 = -5.5A \text{ from E to F and } 5.5A \\ &\text{from F to E} \end{aligned}$$

$$\begin{aligned} \text{Current in Section FB, } I_{FB} &= I_A - 14.5 \\ &= 5 - 14.5 = -9.5A \text{ from F to B and } \\ &9.5A \text{ from B to F} \end{aligned}$$

(ii) The actual distribution of currents in the various sections of the distribution is the currents are coming to load point D from both sides of the distributor therefore load point D is the point of minimum potential.


$$\text{Voltage at D, } V_D = V_A - [I_{AC} R_{AC} + I_{CD} R_{CD}]$$



$$\begin{aligned}
 &= 240 - [5 \times 0.05 + 20 \times 0.025] \\
 &= 240 - 0.75 \\
 &= 239.25 \text{ V Ans}
 \end{aligned}$$

Question # 2 :- A 2-wire DC distributor cable AB is 1 km long and supplies loads of 100A, 150A, 200A and 50A situated 500m, 1000m, 1500m and 1000m from the feeding point A. Each conductor has a resistance of 0.02Ω per 1000m. Calculate the P.D. at each load point if a P.D. of 400V is maintained at point A.

Solution:-

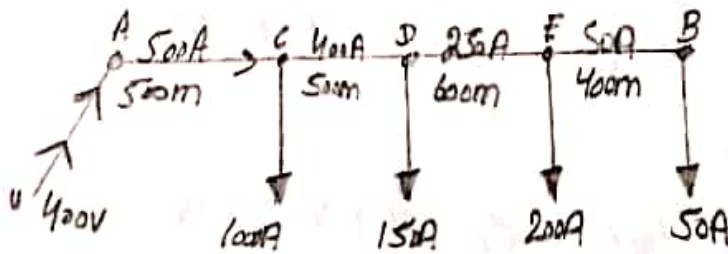

Resistance per 1000m of distributor  
 $= 2 \times 0.02 = 0.04 \Omega$

Resistance of section AC -  $R_{AC} = 0.04 \times 500 / 1000$   
 $= 0.02 \Omega$

Resistance of section CD -  $R_{CD} = 0.04 \times 500 / 1000$   
 $= 0.02 \Omega$

Resistance of Section DE,  $R_{DE} =$   
 $= 0.04 \times 600 / 1000 = 0.024 \Omega$

Resistance of Section EB,  $R_{EB} = 0.01 \times 900 / 1000$   
 $= 0.009 \Omega$

The current in the various sections of the distributors are?

$I_{EB} = 50 \text{ A}; I_{DE} = 50 + 200 = 250 \text{ A}$

$I_{CD} = 250 + 150 = 400 \text{ A}$

$I_{AC} = 400 + 100 = 500 \text{ A}$

P.D at Joad Point C,  $V_C =$  voltage at

A = voltage drop in AC

$= V_A - I_{AC} R_{AC}$

$= 400 - 500 \times 0.02$

$= 390 \text{ V}$

P.D at Joad Point D,  $V_D = V_C - I_{CD} R_{CD} =$

$= 390 - 400 \times 0.02$

$= 382 \text{ V}$

P.D at Joad Point E,

$V_E = V_D - I_{DE} R_{DE}$

$= 382 - 250 \times 0.024$

$= 376 \text{ V}$

P-D at load Point B.

$$\begin{aligned} V_B &= V_E - I_{EB} R_{EB} \\ &= 378 - 50 \times 0.016 \\ &= 375.2 \text{ V } \underline{\underline{\text{Ans}}} \end{aligned}$$

